

ECE 101 Exploring Electrical Engineering

■ ***Circuits 2***

- Resistor
- Series and parallel connection of resistors
- Voltage Dividers
- Voltage & Current Sources


Resistor

- A *resistor* is a passive electronic component that obeys Ohm's Law. It has resistance R .



- SI Unit: ohm (Ω)

- Symbol: 

- I - V relationship: $v(t) = R i(t)$

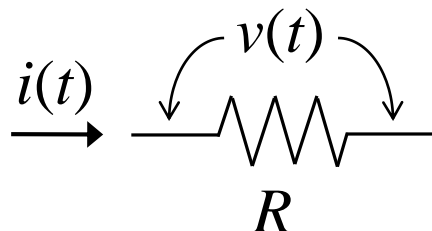

$$i(t) = \frac{1}{R} v(t)$$

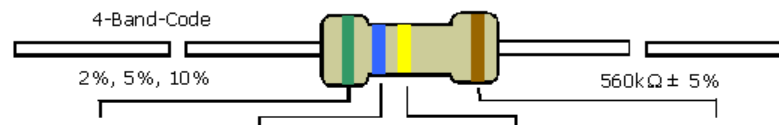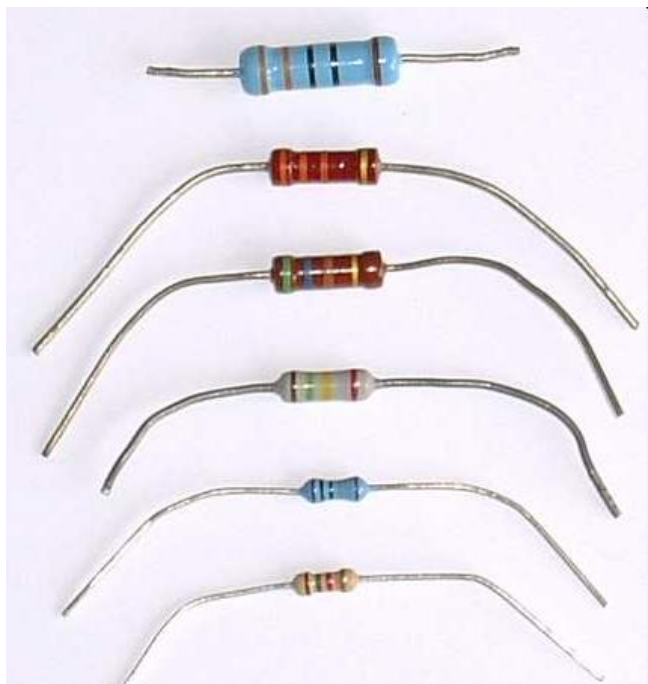

COLOR	1st BAND	2nd BAND	3rd BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8		\pm 0.05%
White	9	9	9		
Gold				0.1	\pm 5% (J)
Silver				0.01	\pm 10% (K)



Resistors Connected in Series (end-to-end)


- If N resistors are connected in series, with the i -th resistor having a resistance R_i , then the equivalent resistance R_{eq} is:

$$\begin{array}{c} R_1 \qquad R_2 \\ \text{---} \text{---} \text{---} \text{---} \end{array} \Rightarrow \begin{array}{c} R_{\text{eq}} = R_1 + R_2 \\ \text{---} \text{---} \end{array}$$

$$\begin{array}{c} R_1 \qquad R_2 \qquad R_3 \\ \text{---} \text{---} \text{---} \text{---} \end{array} \Rightarrow \begin{array}{c} R_{\text{eq}} = R_1 + R_2 + R_3 \\ \text{---} \text{---} \end{array}$$

$$R_{\text{eq}} = \sum_{i=1}^N R_i$$


Properties of Series Resistances (DC):

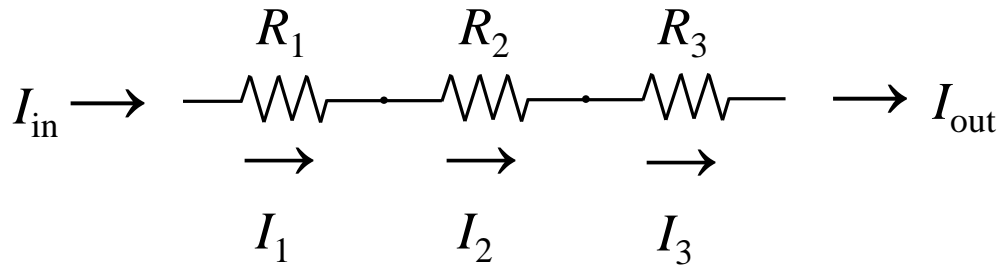

- The amount of current I_{in} entering one end of a series circuit is equal to the amount of current I_{out} leaving the other end.
- The current is the same through each resistor in the series and is equal to I_{in} .

$$I_{in} = I_{out} = I_1 = I_2 = I_3$$

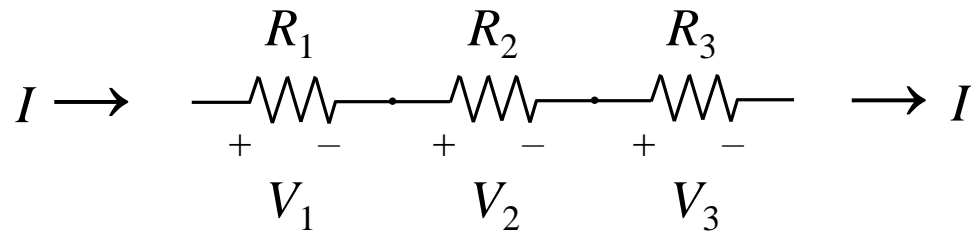
- The amount of voltage drop across each resistor in a series circuit is given by Ohm's Law.



$$V_1 = IR_1 \quad , \quad V_2 = IR_2 \quad , \quad V_3 = IR_3$$

- By convention, the resistor terminal that the current enters is labeled “+”, and the terminal the current exits is labeled “-”.
- **KVL**: total voltage drop = sum of individual drops (watch out for sign!)

Example:

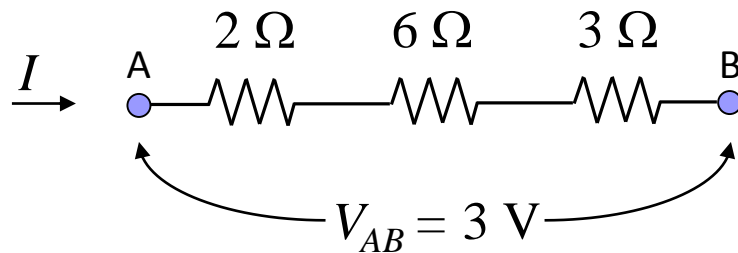

- a) Calculate the current I that flows through the resistors.
- b) Find the voltage drop across the $6\ \Omega$ resistor.

Solution:

a) Approach – Use Ohm's law:
$$I = \frac{V_{AB}}{R_{eq}}$$

Calculate the equivalent resistance:
$$R_{eq} = (2 + 6 + 3)\ \Omega = 11\ \Omega$$

Calculate the current:
$$I = \frac{3\text{ V}}{11\ \Omega} \approx \underline{\underline{0.273\text{ A}}}$$

b) Use Ohm's law again:
$$V_6 = IR_6 = (0.273\text{ A})(6\ \Omega) \approx \underline{\underline{1.64\text{ V}}}$$


Example:

- 100 V Source, 5 and 20 ohm resistors in series; find R_s, I, P, V_1, V_2
- 100 V Source, 5 and 20 ohm resistors in parallel; find R_p, I, P, I_1, I_2


Resistors Connected in Parallel (side-by-side)

- If N resistors are in parallel, with the i -th resistor having a resistance R_i , then the equivalent resistance is:
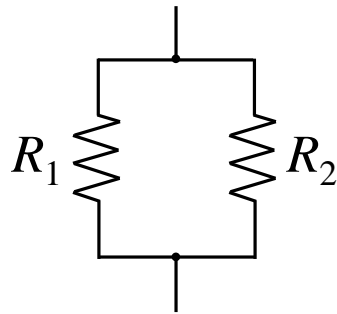
$$R_{\text{eq}} = \left(\sum_{i=1}^N \frac{1}{R_i} \right)^{-1} \leftarrow$$



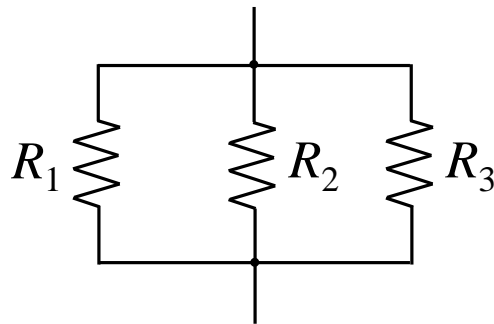
$$\Rightarrow \text{Resistor } R_{\text{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$$




$$\Rightarrow \text{Resistor } R_{\text{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

Properties of Parallel Resistances (DC):

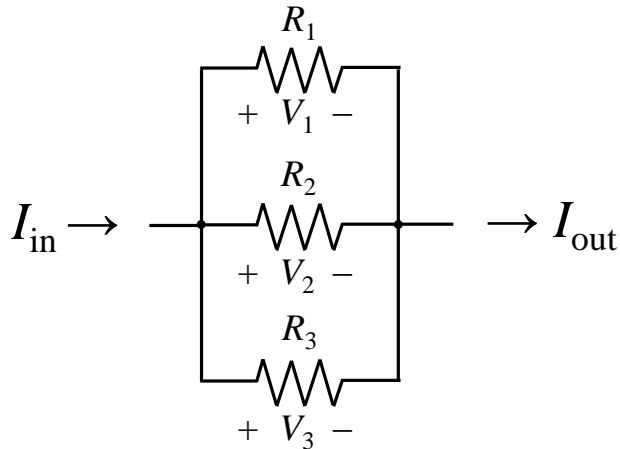

- The amount of current I_{in} entering one end of a parallel circuit is equal to the amount of current I_{out} leaving the other end: $I_{in} = I_{out}$
- For parallel resistors, the voltage drop across each resistor is the same: $V_1 = V_2 = V_3$
- KCL: Σ (sum) of currents entering a node = Σ (sum) of currents leaving a node

Example:

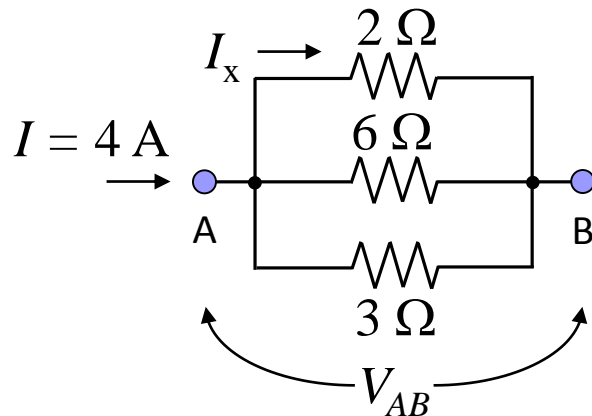

- Find the current I_x through the $2\ \Omega$ resistor.
- What is the power dissipated by the $3\ \Omega$ resistor?

Assume 3 significant figures.

Solution:

- a) Approach – Use Ohm's law: $V_{AB} = IR_{eq}$


Calculate the equivalent resistance: $R_{eq} = \left(\frac{1}{2} + \frac{1}{6} + \frac{1}{3} \right)^{-1} \Omega = 1\ \Omega$

Calculate the voltage drop: $V_{AB} = (4\text{ A})(1\ \Omega) = 4\text{ V}$

Find the current: $I_x = \frac{V_{AB}}{2\ \Omega} = \underline{\underline{2.00\text{ A}}}$

b) Use power equation: $P = \frac{V_{AB}^2}{3\ \Omega} \approx \underline{\underline{5.33\text{ W}}}$

Voltage Divider

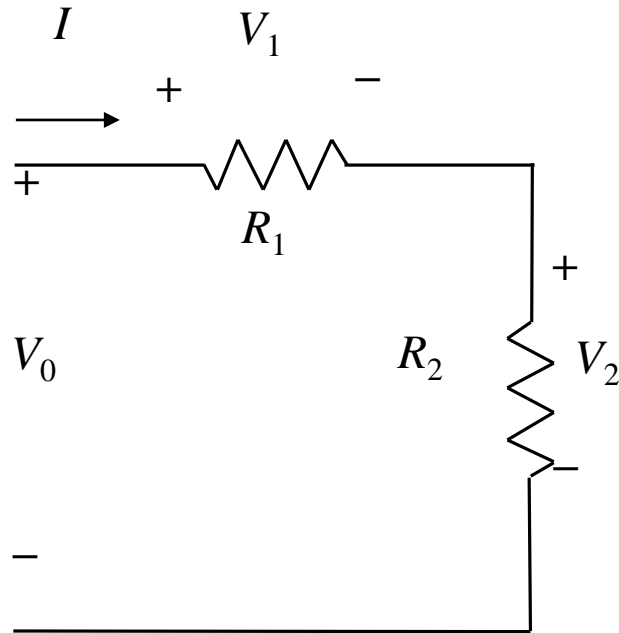


$$V_1 = \frac{R_1}{R_1 + R_2} V_0$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_0$$

Voltage Divider

Example:

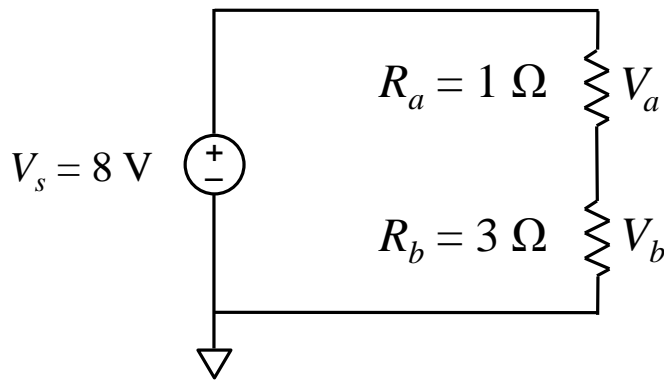

What is the voltage drop across R_a ?

$$V_a = \frac{R_a}{R_a + R_b} V_s$$

$$V_a = \frac{1\ \Omega}{1\ \Omega + 3\ \Omega} (8\text{ V}) = 2\text{ V}$$




What is the voltage drop across R_b ?

$$V_b = \frac{R_b}{R_a + R_b} V_s$$

$$V_b = \frac{3\ \Omega}{1\ \Omega + 3\ \Omega} (8\text{ V}) = 6\text{ V}$$

DC Voltage & Current Sources

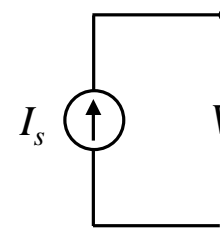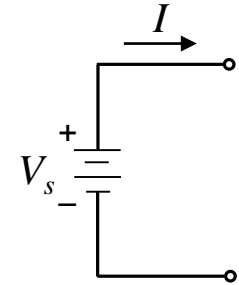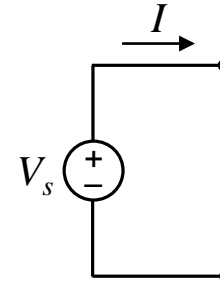
- An ideal DC voltage source outputs a constant voltage regardless of the amount of current through it.
- An ideal DC current source outputs a constant current regardless of the amount of voltage across it.




Prefixes – common engineering style

■	10^{-9}	nano	n
■	10^{-6}	micro	μ
■	10^{-3}	milli	m
■	10^3	kilo	k
■	10^6	mega	M
■	10^9	giga	G

More circuit examples

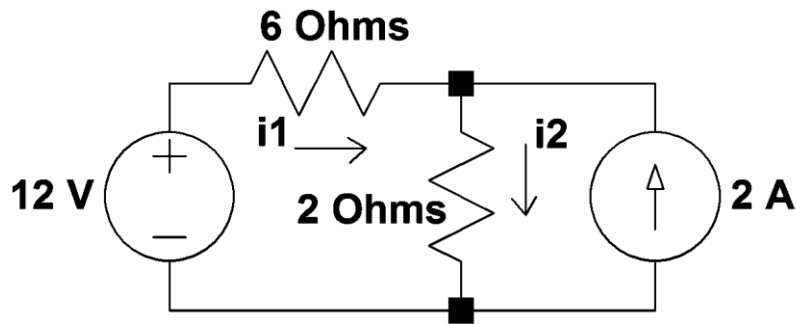

Find currents i_1 and i_2

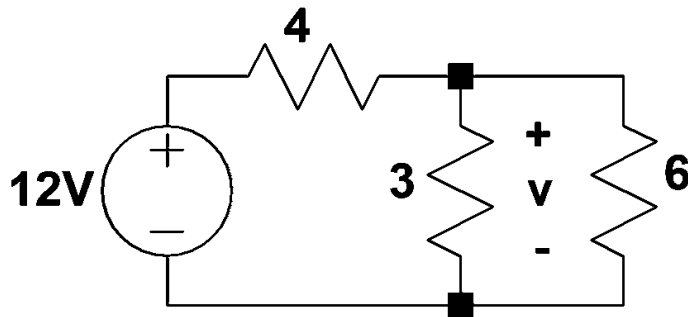

Find voltage v

Further questions:

1. Find the power in each resistor in the series and parallel examples.
2. Are household appliances connected in series or parallel? Why?