# **Introduction to Digital Logic**

- Digital systems use binary numbers
  - Decimal numbers are base 10 (digits 0, 1, ... 9)
    - Example:  $893 = 8 \times 10^2 + 9 \times 10^1 + 3 \times 10^0$
  - Binary numbers are base 2 (digits 0, 1)
  - Example: binary  $1101 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 13$
  - Example: write decimal 23 in binary

23 = 16 + 4 + 2 + 1= 1 x 2<sup>4</sup> + 0 x 2<sup>3</sup> + 1 x 2<sup>2</sup> + 1 x 2<sup>1</sup> + 1 x 2<sup>0</sup> = 10111

# Binary numbers represent information: numbers, text, colors, etc.

Numbers	
Binary	Decimal
"000"	0
"001"	1
"010"	2
"011"	3
"100"	4
"101"	5
"110"	6
"111"	7

Text	
Binary	Character
"0100 0000"	@
"0100 0001"	А
"0100 0010"	В
"0100 0011"	С
"0100 0100"	D
"0100 0101"	Е
"0100 0110"	F
"0100 0111"	G

Colors

Binary	Color
"0 0 0"	Black
"1 0 0"	Red
"0 1 0"	Green
"0 0 1"	Blue
"0 1 1"	Cyan
"1 0 1"	Magenta
"1 1 0"	Yellow
"1 1 1"	White

#### Where do we use digital logic in electronics?

- Transistors act as switches
  - Apply high voltage  $\rightarrow$  transistor conducts
  - Apply low voltage → transistor doesn't conduct
  - Can switch very fast
- Digital or *Boolean* logic describes everything in 1's and 0's
  - 1 = high voltage, say > 4 V, means "True" or "On"
  - 0 = low voltage, say < 1 V, means "False" or "Off"
- Logic operations such as NOT, OR, AND act on these logic variables and are easily implemented in transistor circuits called Logic Gates
- Logic operations are represented by Truth Tables which define every possible combination of inputs

## **Logic Operations: NOT**

- Example: A safety light is normally always on, unless you push a button to turn it off.
- Input: 1 = push button, 0 = don't push button
- Output: 1 = light on, 0 = light off
- Truth table: button light
   0
   1
   0
- Called NOT operation, output = opposite of input

## **Logic Operations: OR**

- Example: 2-door car, light goes on if either or both doors are open
- Inputs: 1 = door open, 0 = door closed
- Output: 1 = light on, 0 = light off
- Truth table: door 1 door 2 light

   0
   0
   0
   1
   1
   1
   1
   1
- Called OR operation, output = 1 if either or both inputs = 1

## **Logic Operations: AND**

- Example: passenger car window with driver master switch, window only opens if both switches on
- Inputs: 1 = switch on, 0 = switch off
- Output: 1 = window operates, 0 = doesn't operate
- Truth table: <u>switch 1 switch 2 window</u>

0	0	0
0	1	0
1	0	0
1	1	1

Called AND operation, output = 1 only if both inputs
 = 1

- Can have more inputs and more complicated logic
- Example: Joe drives instead of bikes to school if its cold and/or raining, and he has an early class
  - Inputs: A = 1 cold B = 1 raining C = 1 early class
     0 warm 0 dry 0 no early class
  - Output: 1 = drives, 0 = bikes

Truth table:	A	В	С	Out
	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	1
	1	0	0	0
	1	0	1	1
	1	1	0	0
	1	1	1	1

Out = (A OR B) AND C

#### Math Symbols and Circuit (Logic Gate) Symbols

- Math symbols:  $NOT = \overline{A}$ , OR = A + B,  $AND = A \cdot B$  (or AB)
- Circuits that perform these operations called Logic Gates
   NOT: OR: AND:







• Joe example:  $Out = (A + B) \cdot C$ 



## **Transistors behave as inverters**

V<sub>in</sub> = Low, no I flows, V<sub>out</sub> = High (= V<sub>supply</sub>)

- V<sub>in</sub> = High, large I flows, V<sub>out</sub> = Low (large voltage dropped across R)
   V<sub>supply</sub>
- V<sub>out</sub> = NOT V<sub>in</sub>



 More convenient to build circuits which use *inverse* of OR, AND – called **NOR, NAND**

## **NOR and NAND Gates**

- OR + NOT = NOR: output low if any input high
- A
   B
   A+B
   A+B

   0
   0
   0
   1

   0
   1
   1
   0

   1
   0
   1
   0

   1
   1
   1
   0

   1
   1
   1
   0



 AND + NOT = NAND: output low if all inputs high; demo on logic.ly

A	В	AB	AB	
0	0	0	1	
0	1	0	1	
1	0	0	1	
1	1	1	0	



## **Simulators**

- Logic.ly
- Examples of lab circuit do it in class

### **More circuits**

- Logic.ly
- Example of half-adder circuit use logic.ly to construct

Inputs		Outputs	
Α	В	С	S
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	0



## More circuits

