

1ST ORDER CIRCUITS


RL OR RC

GOVERNED BY 1ST ORDER D.E.



THREE ANALYSIS PHASES:

- 1) NATURAL RESPONSE (ENERGY STORED IN INDUCTOR OR CAPACITOR IS RELEASED TO A RESISTIVE NETWORK)
- 2) STEP RESPONSE (VOLTAGE OR CURRENT SOURCE SUDDENLY APPLIED TO REACTIVE NETWORK)
- 3) GENERAL METHOD

NATURAL RESPONSE
(INTRINSIC TO CIRCUIT)

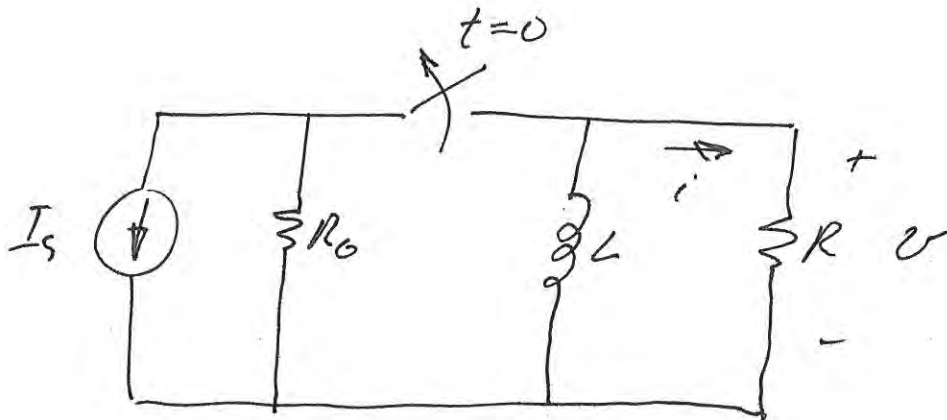

SWITCH CLOSED LONG TIME BEFORE $t=0$

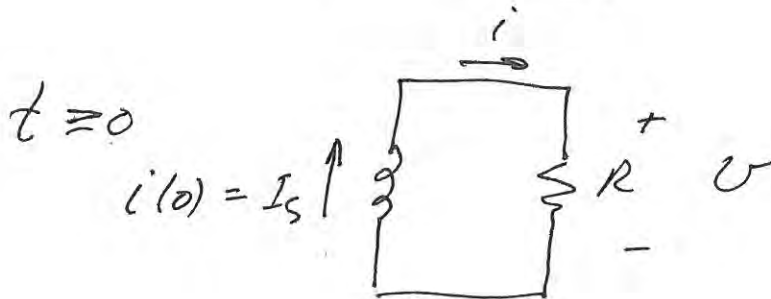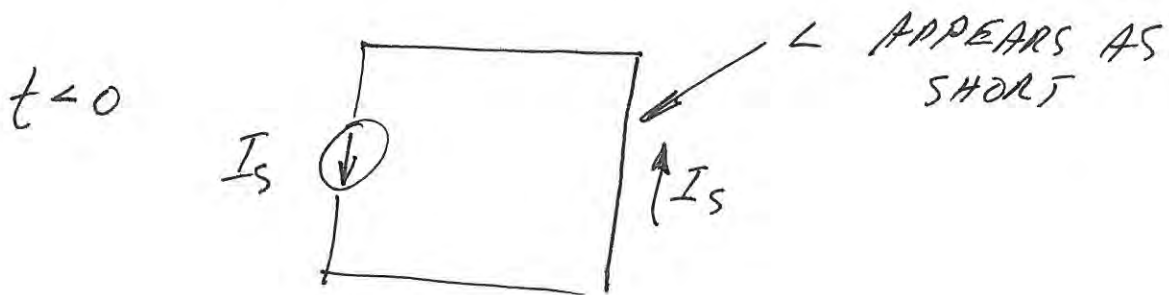

ANALYSIS BY KVL:

$$L \frac{di}{dt} + Ri = 0 \quad (\text{1ST ORDER D.E.})$$

$$\frac{di}{dt} = -\frac{R}{L} i$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\frac{dx}{x} = -\frac{R}{L} dy$$

$$\int_{i(t_0)}^{i(t)} \frac{dx}{x} = -\frac{R}{L} \int_{t_0}^t dy$$

$$\ln x \Big|_{i(t_0)}^{i(t)} = -\frac{R}{L} (t - t_0)$$


$$\ln \frac{i(t)}{i(t_0)} = -\frac{R}{L} (t - t_0)$$

$$\frac{i(t)}{i(t_0)} = e^{-\frac{R}{L} (t - t_0)}$$

$$i(t) = i(t_0) e^{-\frac{R}{L} (t - t_0)}$$

FOR THIS PROBLEM, $t_0 = 0$


$$i(t) = i(0) e^{-\frac{R}{L}t}$$

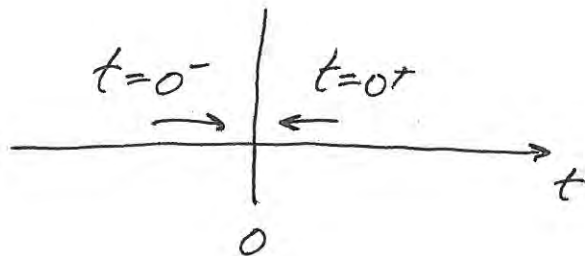

CURRENT THROUGH INDUCTOR
CANNOT CHANGE INSTANTANEOUSLY

$$\therefore i(0^-) = i(0^+) = I_s$$

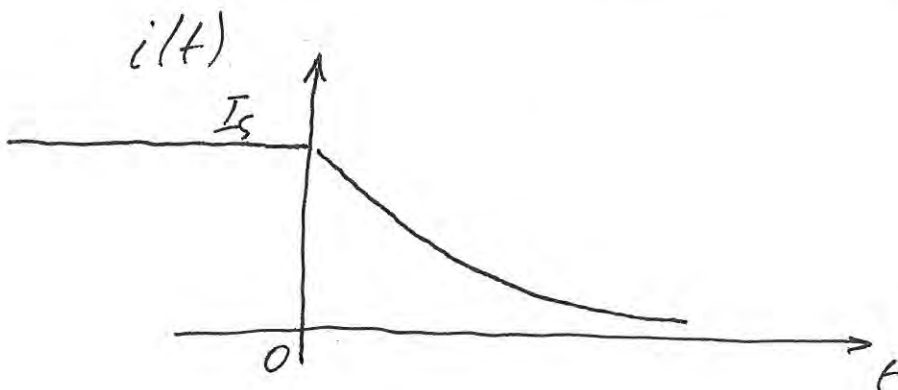FINALLY $i(t) = I_s e^{-\frac{R}{L}t}$; $t \geq 0$




WHAT ABOUT VOLTAGE, v ?

$$v(t) = i(t)R$$

$$v(t) = I_s R e^{-\frac{R}{L}t}$$

CAREFUL...


WHAT IS DOMAIN OF THIS SOLUTION?

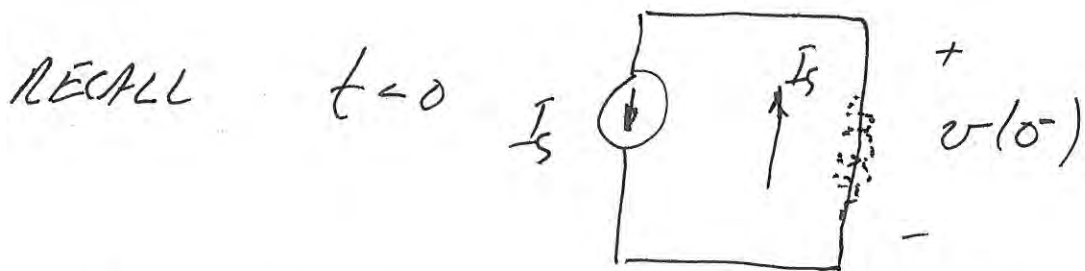

BECAUSE INDUCTOR IS SHORT, $v(0^-) = 0$

FROM SOLUTION, $v(0^+) = I_s R$

VOLTAGE CHANGES INSTANTANEOUSLY AT $t=0$

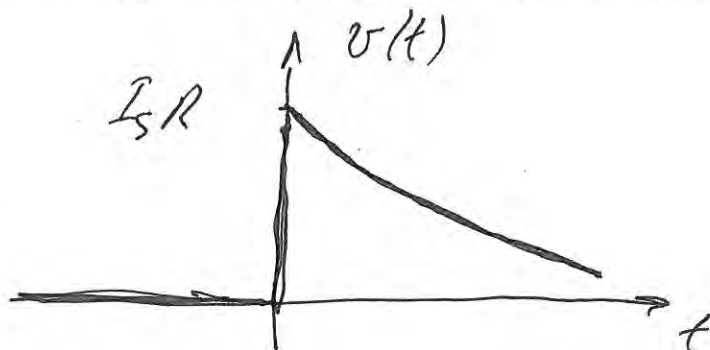

$$v(t) = I_s R e^{-\frac{R}{L}t}; t \geq 0^+$$

POWER DISSIPATED IN RESISTOR

$$p = vi = i^2 R = \frac{v^2}{R}$$

$$p = I_s^2 R e^{-2\frac{R}{L}t} ; t \geq 0$$

ENERGY DELIVERED TO RESISTOR

$$\begin{aligned} w &= \int_0^t p(x) dx = \int_0^t I_s^2 R e^{-2\frac{R}{L}x} dx \\ &= I_s^2 R \left(-\frac{1}{2\frac{R}{L}} e^{-2\frac{R}{L}x} \Big|_0^t \right) \\ &= \frac{1}{2} I_s^2 L \left(1 - e^{-2\frac{R}{L}t} \right) ; t \geq 0 \end{aligned}$$

WHAT IS ENERGY INITIALLY STORED
IN INDUCTOR?

$$i(t) = \frac{I_s}{s} e^{-\frac{R}{L}t}; \quad t \geq 0$$

↑
DIMENSIONLESS

$$\frac{[R]}{[L]} = \frac{\Omega}{H} = \frac{\Omega}{V \cdot S/A} = \frac{V/A}{V \cdot S/A} = \frac{1}{S}$$

DEFINE $\frac{L}{R} \equiv \tau$


$\tau \equiv$ TIME CONSTANT

$$[\tau] = S$$

$$i(t) = \frac{I_s}{s} e^{-t/\tau}; \quad t \geq 0$$

INSPECT $\left. \frac{d}{dt} i(t) \right|_{t=0^+}$

$$\left. -\frac{I_s}{\tau} e^{-t/\tau} \right|_{t=0^+} = -I_s/\tau$$

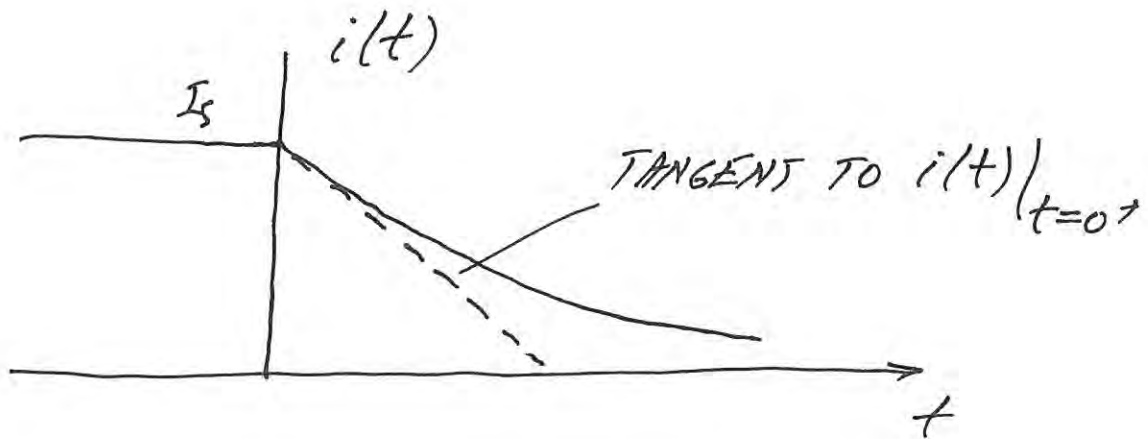

EQ OF TANGENT LINE: $mt + b = i$

$$i = I_s - \frac{I_s}{\tau} t$$

THIS TANGENT LINE = 0 WHEN $t = \tau$

$$i(t) = I_s e^{-t/\tau} ; t \geq 0$$

TRANSIENT SIGNAL EFFECTIVELY ZERO

BEYOND $t \sim 5\tau$




SOLUTION STRATEGY

- 1) DETERMINE INITIAL CURRENT
- 2) DETERMINE TIME CONSTANT
- 3) USE FORM

$$i(t) = i(0) e^{-t/\tau}$$

EX 7.1

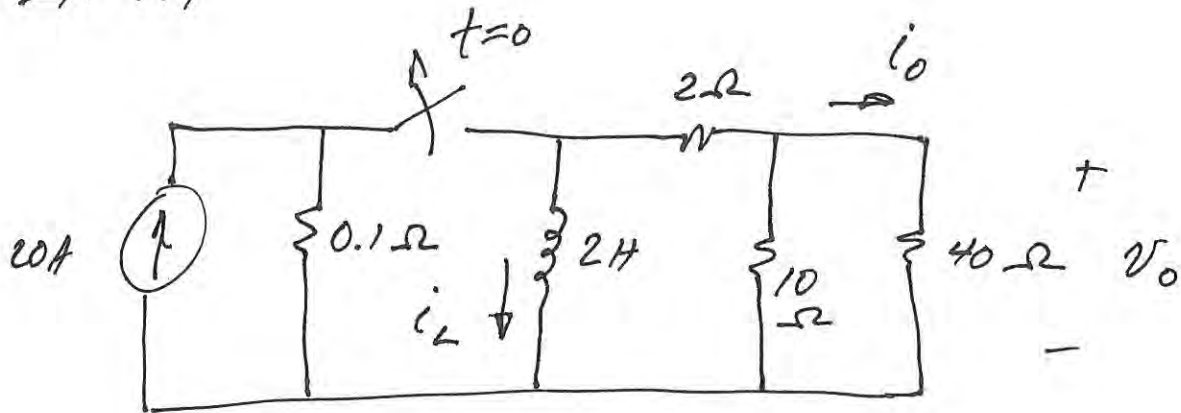


WANT $i_L(t)$; $t \geq 0$

$i_o(t)$; $t \geq 0^+$

$v_o(t)$; $t \geq 0^+$


ENERGY DISSIPATED IN 10Ω RESISTOR

1) ESTABLISH INITIAL CURRENT

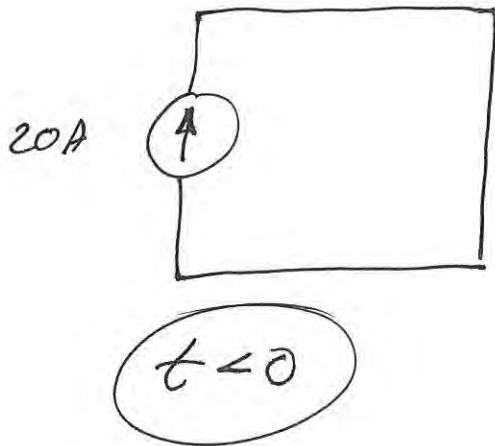


$$i_L(0^-) = 20A = i_L(0^+)$$

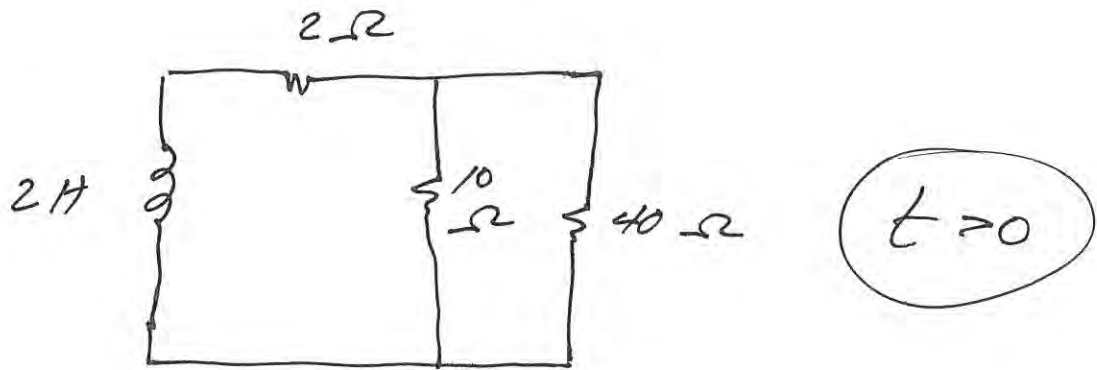(CURRENT IN INDUCTOR
CANNOT CHANGE
INSTANTANEOUSLY)



2) DETERMINE TIME CONSTANT

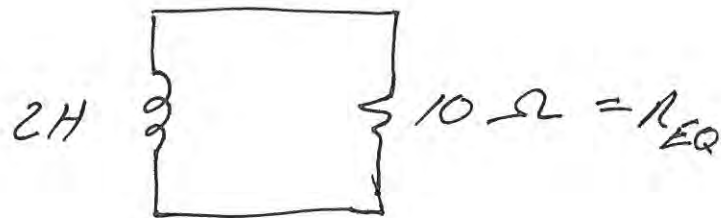


$$\tau = L/R_{EQ} = 0.2 \text{ SEC}$$

3) $i_L(t) = 20 e^{-5t} \text{ A} ; t \geq 0$

↑
NEED NOT DISTINGUISH
BETWEEN 0^- & 0^+

WHY?

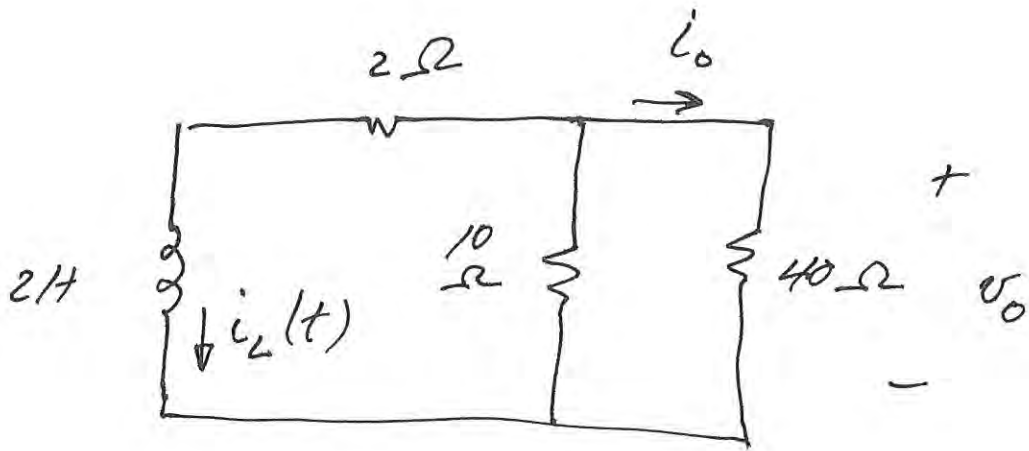

i_0 BY CURRENT DIVISION

$$i_0 = -i_L \frac{10}{10+40}$$

$$i_0(t) = -4 e^{-5t} \text{ A}; t \geq 0^+$$

↑
WHY NOT JUST
 $t \geq 0$
?

VOLTAGE, v_0 , BY OHM'S LAW:

$$v_0(t) = 40 i_0(t) = -160 e^{-5t} \text{ V}; t \geq 0^+$$

POWER DISSIPATED IN 10Ω RESISTOR:

$$P_{100\Omega}(t) = \frac{v_o^2(t)}{10\Omega} = 2560 e^{-10t} \text{ W}$$

$t \geq 0^+$

TOTAL ENERGY DISSIPATED

$$W_{100\Omega} = \int_0^{\infty} P_{100\Omega}(t) dt$$


$$= \int_0^{\infty} 2560 e^{-10t} dt$$


$$= 2560 \left(-\frac{1}{10} e^{-10t} \Big|_0^{\infty} \right)$$

$$W_{100\Omega} = 256 \text{ J}$$


INITIAL ENERGY IN INDUCTOR IS

$$W_L(0) = \frac{1}{2} L i^2(0) = \frac{1}{2} 2(20)^2 = 400 \text{ J}$$

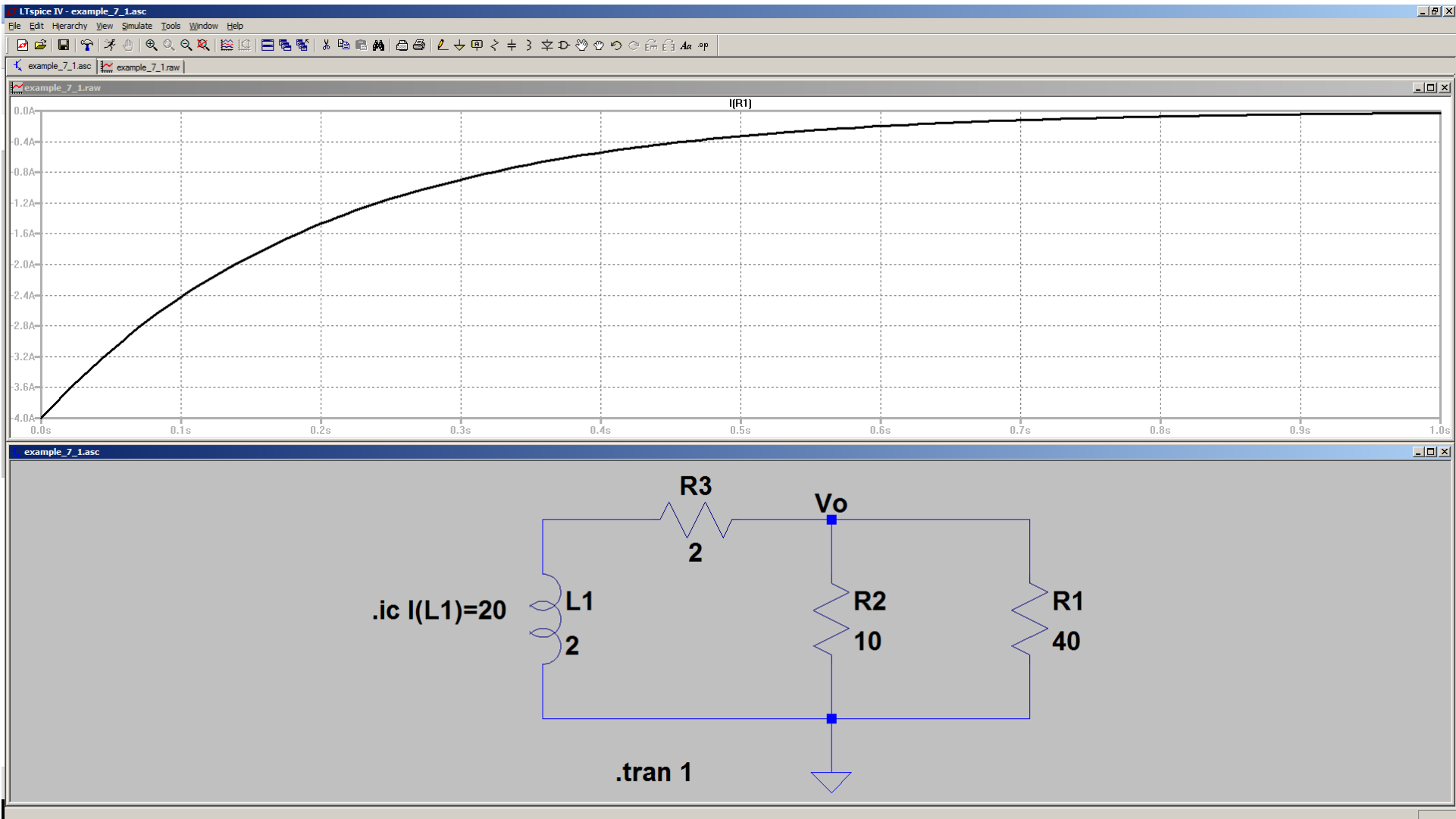

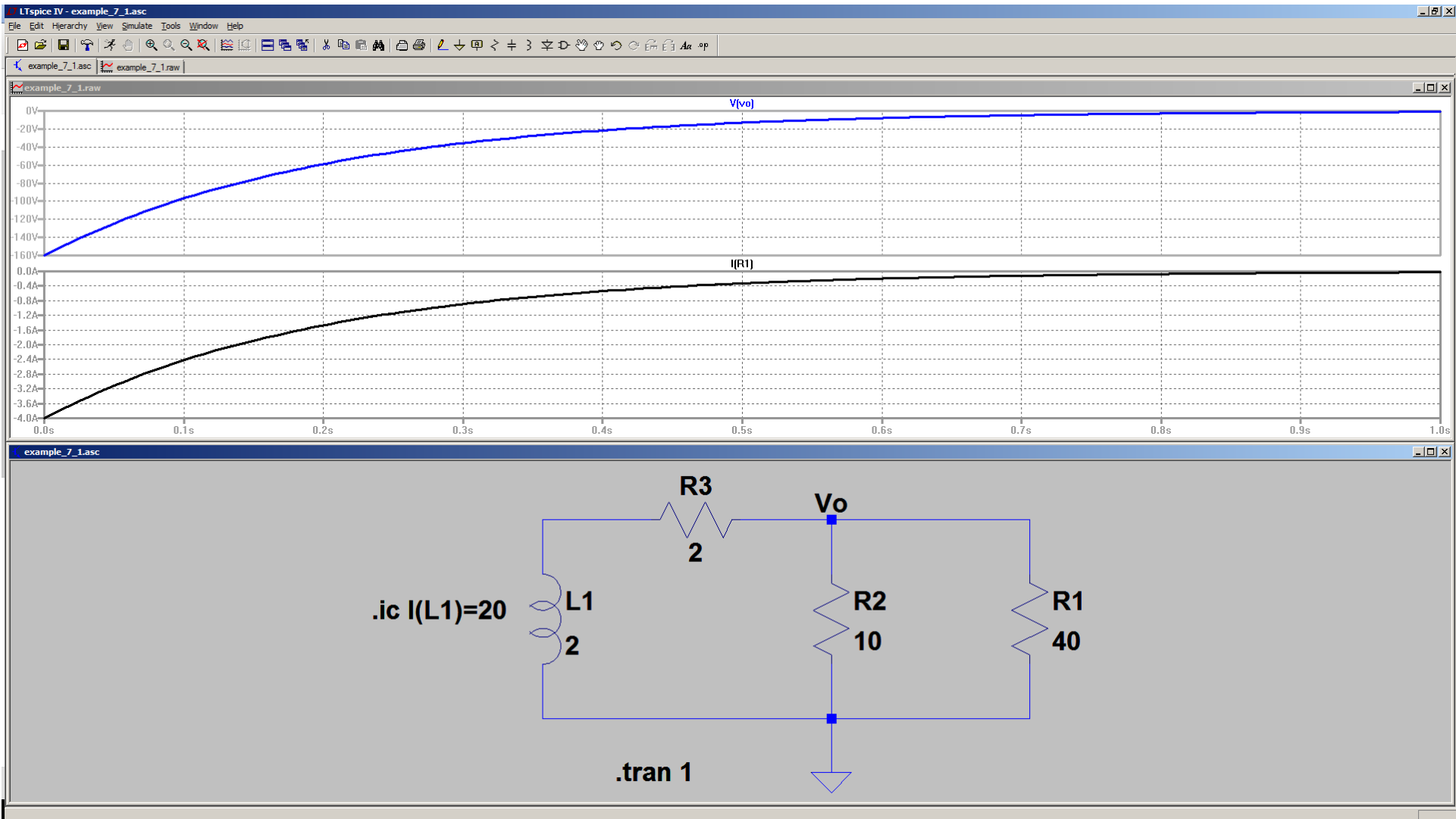

EX 7.2

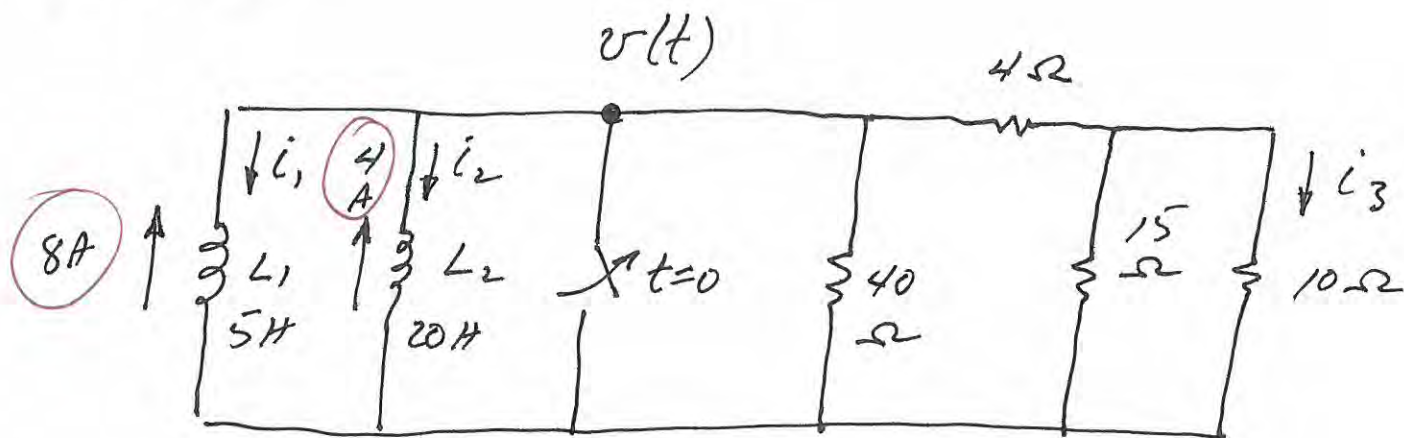


INITIAL CURRENTS

WANT: $i_1(t)$, $i_2(t)$, $i_3(t)$ FOR $t \geq 0$

INITIAL ENERGY IN INDUCTORS

ENERGY IN INDUCTORS AS $t \rightarrow \infty$

DEMONSTRATE WHERE THIS ENERGY GOES

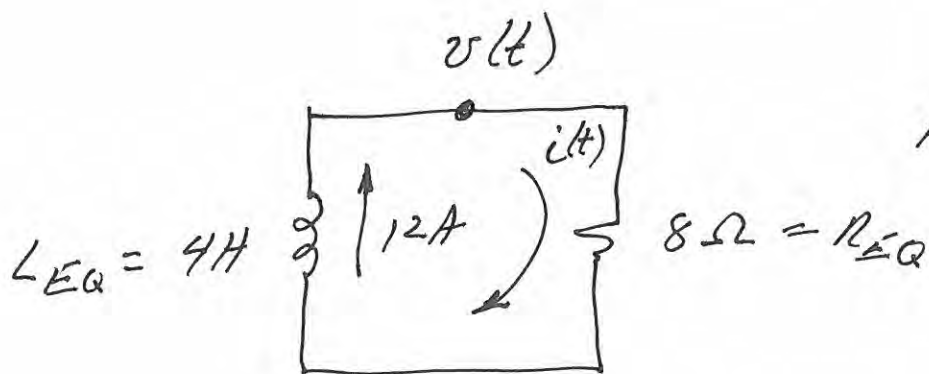


KEY IS FINDING $v(t)$

IMMEDIATELY, $i(t) = 12e^{-2t}$ A; $t \geq 0$

BY OHM'S LAW,

$$v(t) = 8i(t) = 96e^{-2t} \text{ V}; t \geq 0^+$$

WHY 0^+ ?

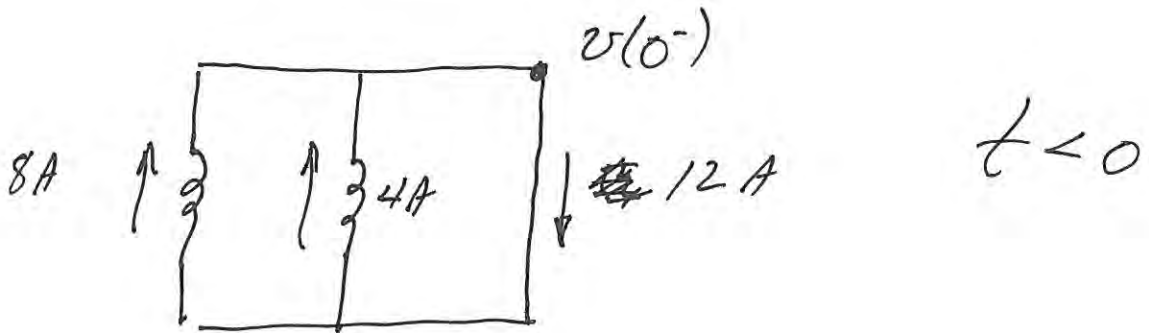

$$i_1(t) = \frac{1}{L_1} \int_0^t v(x) dx + i_1(0)$$

$$i_1(t) = \frac{1}{5} \int_0^t 96e^{-2x} dx - 8$$

$$= \frac{96}{5} \left(-\frac{1}{2} e^{-2x} \Big|_0^t \right) - 8$$

$$= \frac{48}{5} (1 - e^{-2t}) - 8 \text{ A}$$

$$i_1(t) = 1.6 - 9.6e^{-2t} \text{ A}; t \geq 0$$

SIMILARLY

$$i_2(t) = -1.6 - 2.4e^{-2t} \text{ A}; t \geq 0$$

$$i_1(t) \Big|_{t \rightarrow \infty} = 1.6 \text{ A}$$

$$i_2(t) \Big|_{t \rightarrow \infty} = -1.6 \text{ A}$$

$$W_{L_1}(0) = \frac{1}{2} L_1 i_1^2(0) = \frac{1}{2} 5 (8)^2 = 160 \text{ J}$$




$$W_{L_2}(0) = \frac{1}{2} L_2 i_2^2(0) = \frac{1}{2} 20 (4)^2 = 160 \text{ J}$$

$$W_{L_1}(\infty) = \frac{1}{2} L_1 i_1^2(\infty) = \frac{1}{2} 5 (1.6)^2 = 6.4 \text{ J}$$

$$W_{L_2}(\infty) = \frac{1}{2} L_2 i_2^2(\infty) = \frac{1}{2} 20 (-1.6)^2 = 25.6 \text{ J}$$


ENERGY TRAPPED IN INDUCTORS

EX 7.2 P219

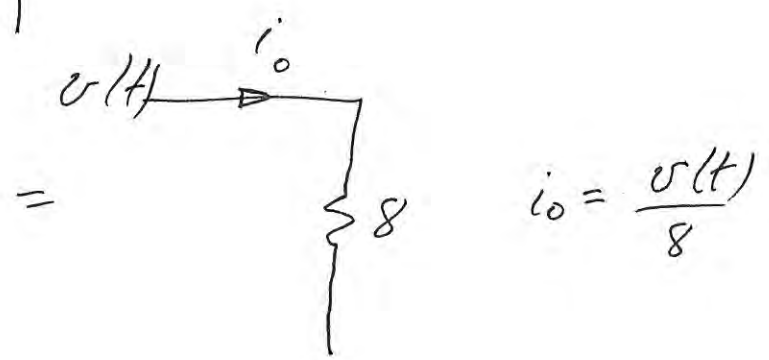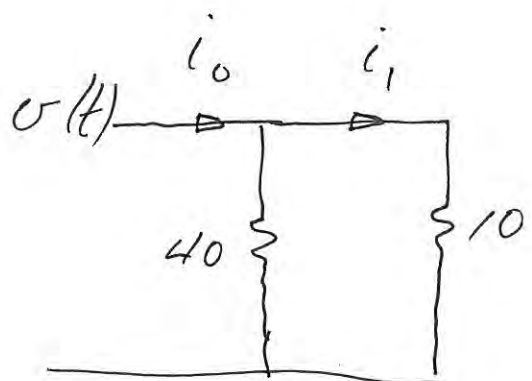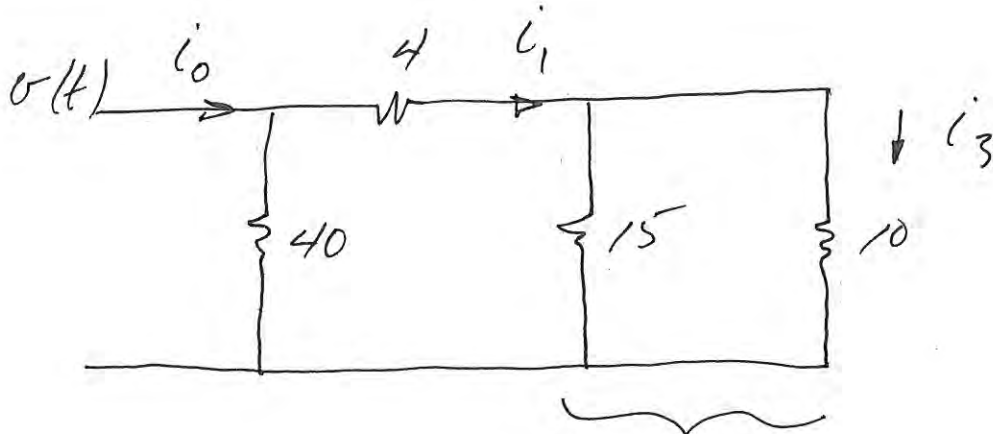

$$i_1 = i_0 \frac{40}{40+10}$$

CURRENT DIVISION

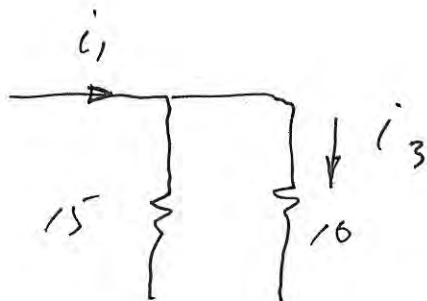

$$i_3 = i_1 \frac{15}{15+10}$$

CURRENT DIVISION


$$i_3 = \frac{15}{15+10} \frac{40}{40+10} \frac{v(t)}{8} = \frac{v(t)}{10} \frac{15}{25}$$

$$i_3(t) = \frac{15}{250} 96 e^{-2t} \text{ A}$$


$$= 5.760 e^{-2t} \text{ A}$$

$$i_3(t) \Big|_{t=15} = 5.760 e^{-2} \text{ A}$$


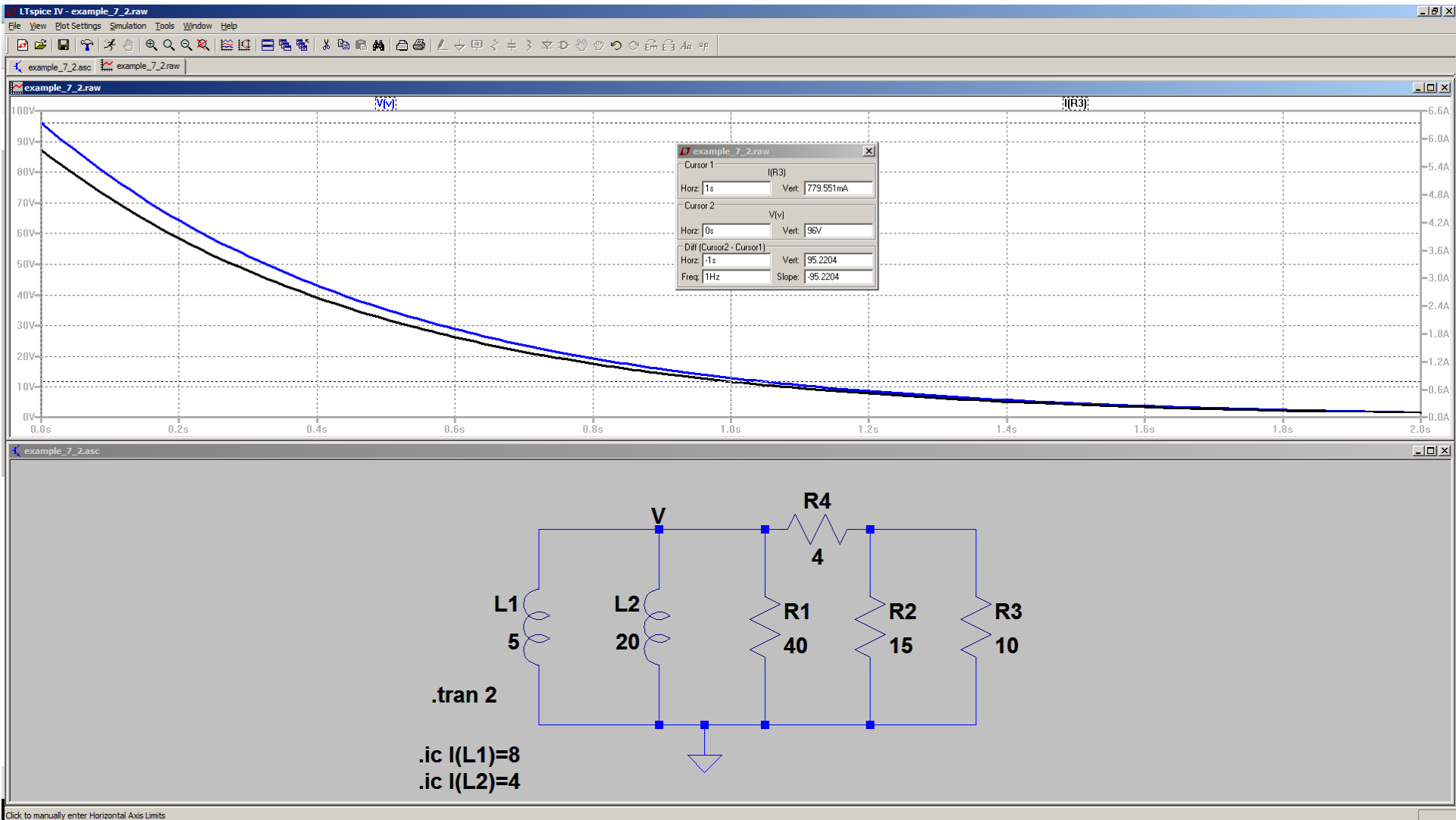
$$= \underline{\underline{779.5 \text{ mA}}}$$



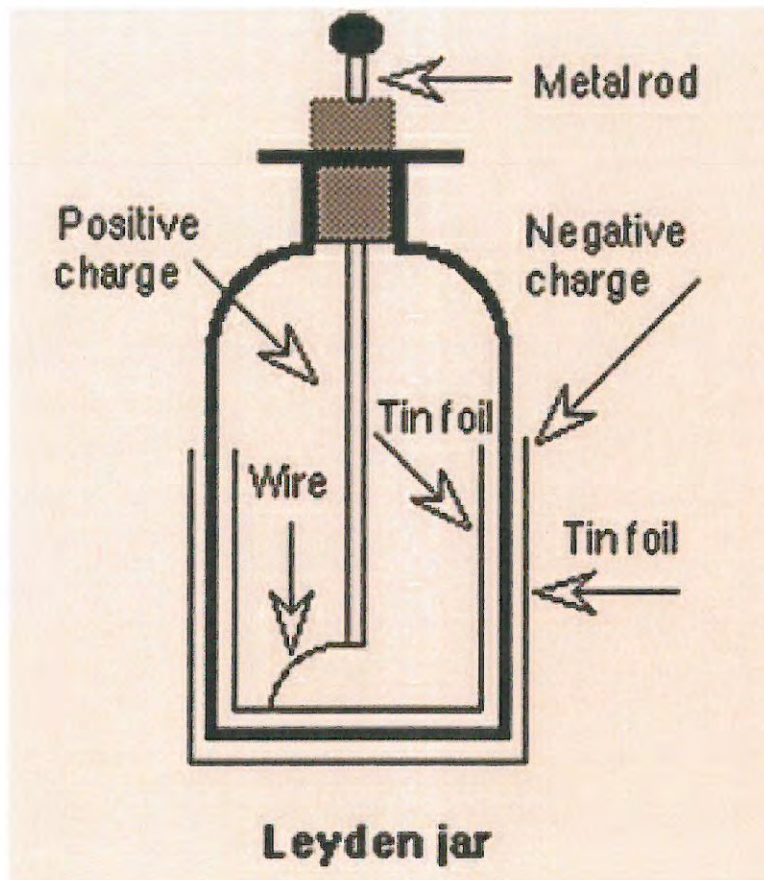
Click to manually enter Horizontal Axis Limits



CAPACITOR

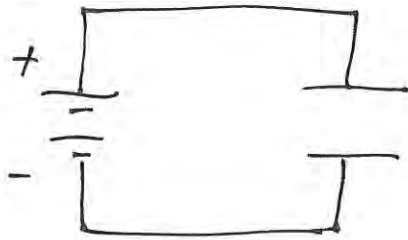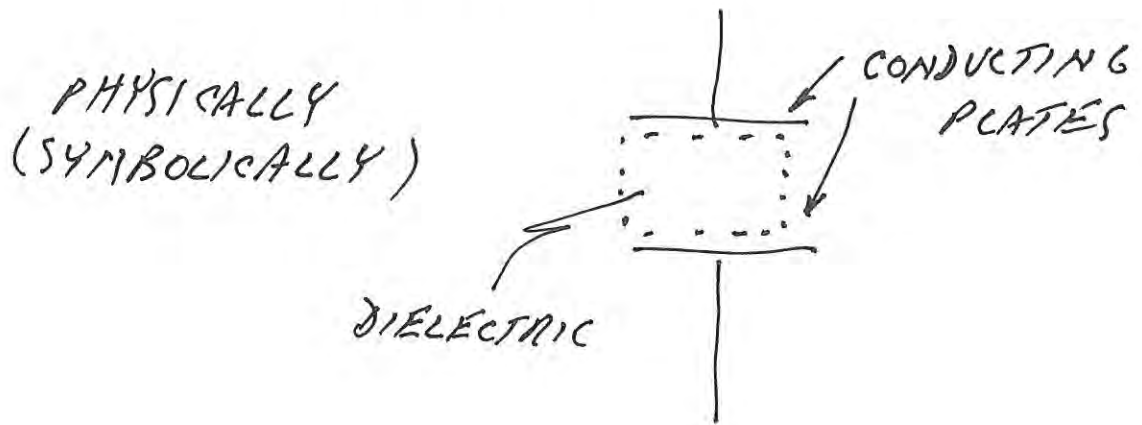

WHAT HAPPENS HERE ?

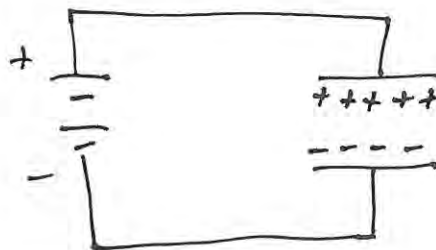

INDUCED CHARGES

NO CURRENT FLOWS

CAP IS AN OPEN CILT TO A DC SOURCE

$v-i$ RELATIONSHIP

$$i = C \frac{dv}{dt} \Rightarrow \text{IF } v = \text{CONST,}$$
$$i = 0$$

$$v = Ri$$

$$v = L \frac{di}{dt}$$

$$\frac{dv}{dt} = \frac{1}{C} i$$

HOW DO YOU THINK CAPACITORS COMBINE
IN SERIES? IN PARALLEL?

~~---~~

$$i = C \frac{dv}{dt}$$

$$\frac{1}{C} i(t) dt = dv(t)$$

$$\frac{1}{C} i(z) dz = dv(z)$$

$$\frac{1}{C} \int_{t_0}^t i(z) dz = \int_{t_0}^t dv(z)$$

$$v(t) - v(t_0) = \frac{1}{c} \int_{t_0}^t i(z) dz$$

$$v(t) = \frac{1}{c} \int_{t_0}^t i(z) dz + v(t_0)$$

IF $t_0 = 0$

$$v(t) = \frac{1}{c} \int_0^t i(z) dz + v(0)$$

\Rightarrow VOLTAGE CANNOT
CHANGE
INSTANTANEOUSLY

POWER: $p = v \cdot i$

$$p = c v \frac{dv}{dt}$$

ENERGY $w(t) = \int_{t_0}^t p(z) dz = c \int_{t_0}^t v(z) dv(z)$
 $= \frac{1}{2} c v^2(z) \Big|_{t_0}^t$

IF AT t_0 , $w(t_0) = 0$, THEN

$$w(t) = \frac{1}{2} c v^2(t)$$

PHYSICAL PROPERTY OF CAPACITOR IS

"CAPACITANCE" MEASURED IN

FARADS

$$\text{FARAD} = \text{C/V}$$


$$i = C \frac{dv}{dt}$$

↑
AMP
(C/S)

↑
FARAD
(C/V)

↑
VOLTAGE CHANGE
(V/S)

EX 6.4

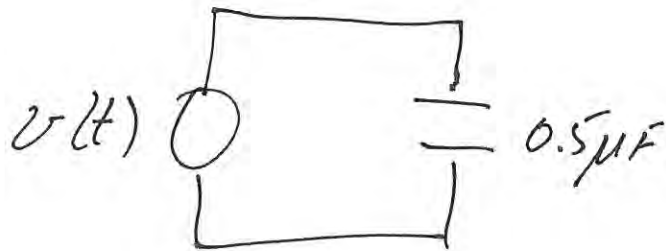

$$v(t) = \begin{cases} 0 & ; t \leq 0 \\ 4t \text{ V} & ; 0 \leq t \leq 15 \\ 4e^{-(t-1)} \text{ V} & ; t \geq 15 \end{cases}$$



WANT CAP CURRENT, POWER, ENERGY



$$i = C \frac{dv}{dt}$$

$$i = \begin{cases} (0.5 \times 10^{-6}) 0 & ; t \leq 0 \\ (0.5 \times 10^{-6}) 4 = 2 \mu\text{A} & ; 0 \leq t \leq 15 \\ (0.5 \times 10^{-6}) (-4e^{-(t-1)}) \\ = -2e^{-(t-1)} \mu\text{A} & ; t \geq 15 \end{cases}$$

$$p = \begin{cases} 0 & ; t \leq 0 \\ (4t \text{ V})(2 \mu\text{A}) = 8t \mu\text{W} & ; 0 \leq t \leq 15 \\ (4e^{-(t-1)} \text{ V})(-2e^{-(t-1)} \mu\text{A}) \\ = -8e^{-2(t-1)} \mu\text{W} & ; t \geq 15 \end{cases}$$
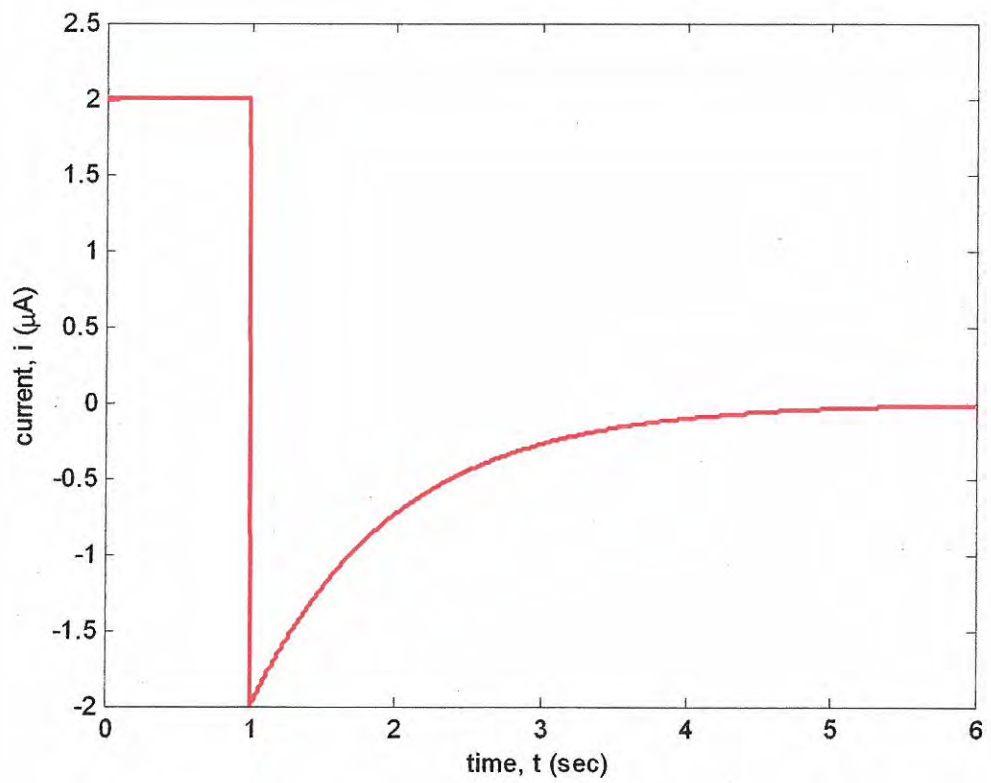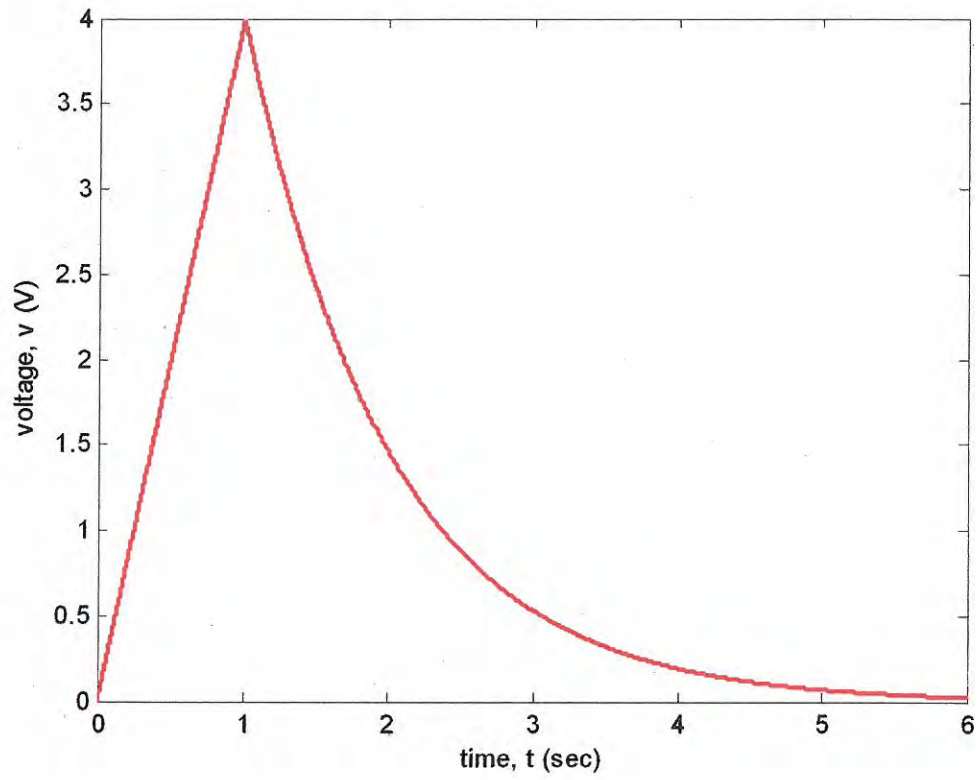
$$w = \begin{cases} 0 & ; t \leq 0 \\ 4t^2 \mu\text{J} & ; 0 \leq t \leq 15 \\ 4e^{-2(t-1)} \mu\text{J} & ; t \geq 15 \end{cases}$$



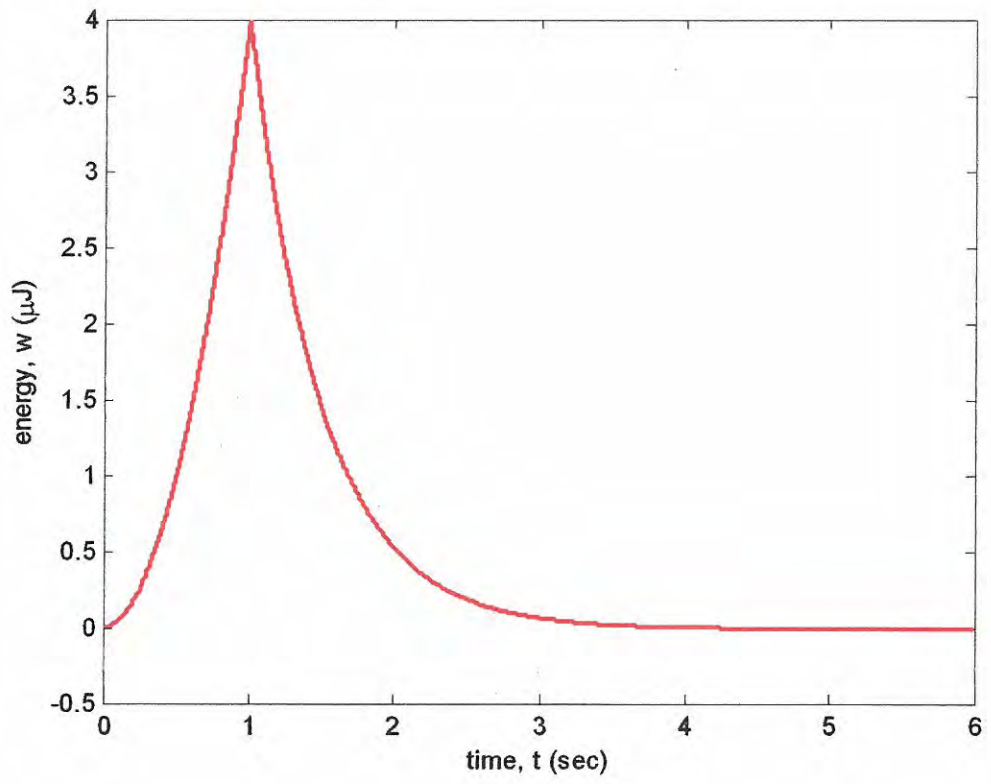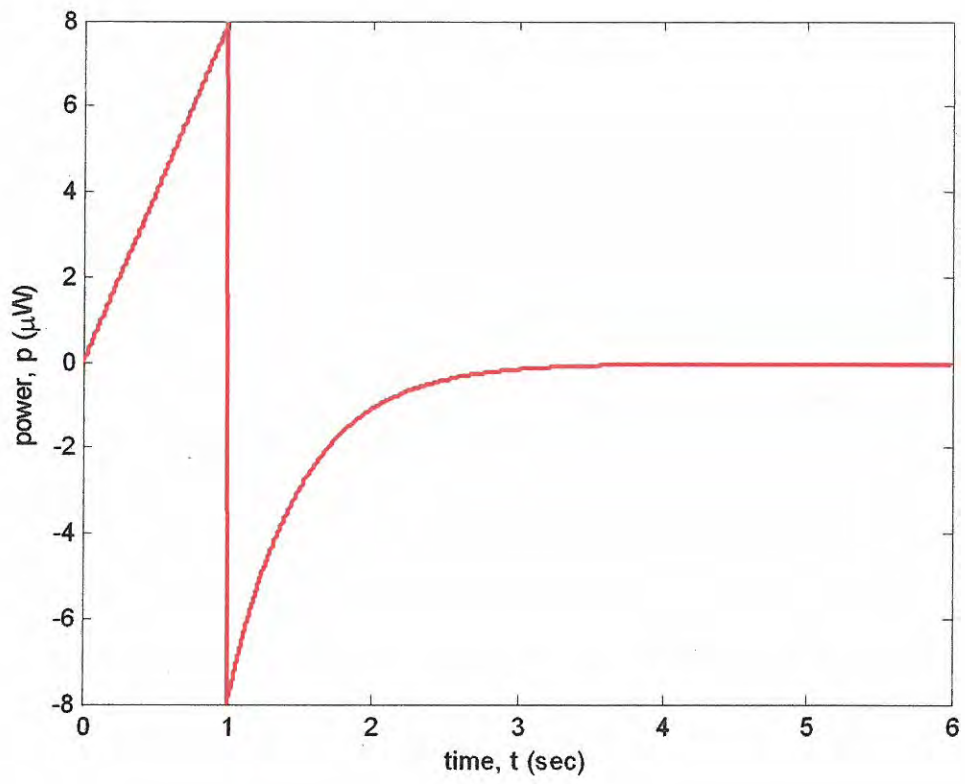


```

% example_6_4
% Nilsson & Riedel 10th ed.
% 01/05/15 D D Duncan
%
C = 0.5;% units of micro Farads
dt = 0.001;
t = 0:dt:6.0;% units of sec
v = 4*t .* (0 <= t & t <= 1) + 4*exp(-(t-1)).*(t > 1);% units of V
figure(1);plot(t,v,'r-');
xlabel('time, t (sec)');ylabel('voltage, v (V)');
i = C*diff(v)/dt;% units of microamperes
% shorten v and t by one element
t(end) = [];
v(end) = [];
figure(2);plot(t,i,'r-');
xlabel('time, t (sec)');ylabel('current, i (\muA)');
p = v.*i;
figure(3);plot(t,p,'r-');
xlabel('time, t (sec)');ylabel('power, p (\muW)');
w = cumsum(p)*dt;
figure(4);plot(t,w,'r-');
xlabel('time, t (sec)');ylabel('energy, w (\muJ)');

```

Example 6.4

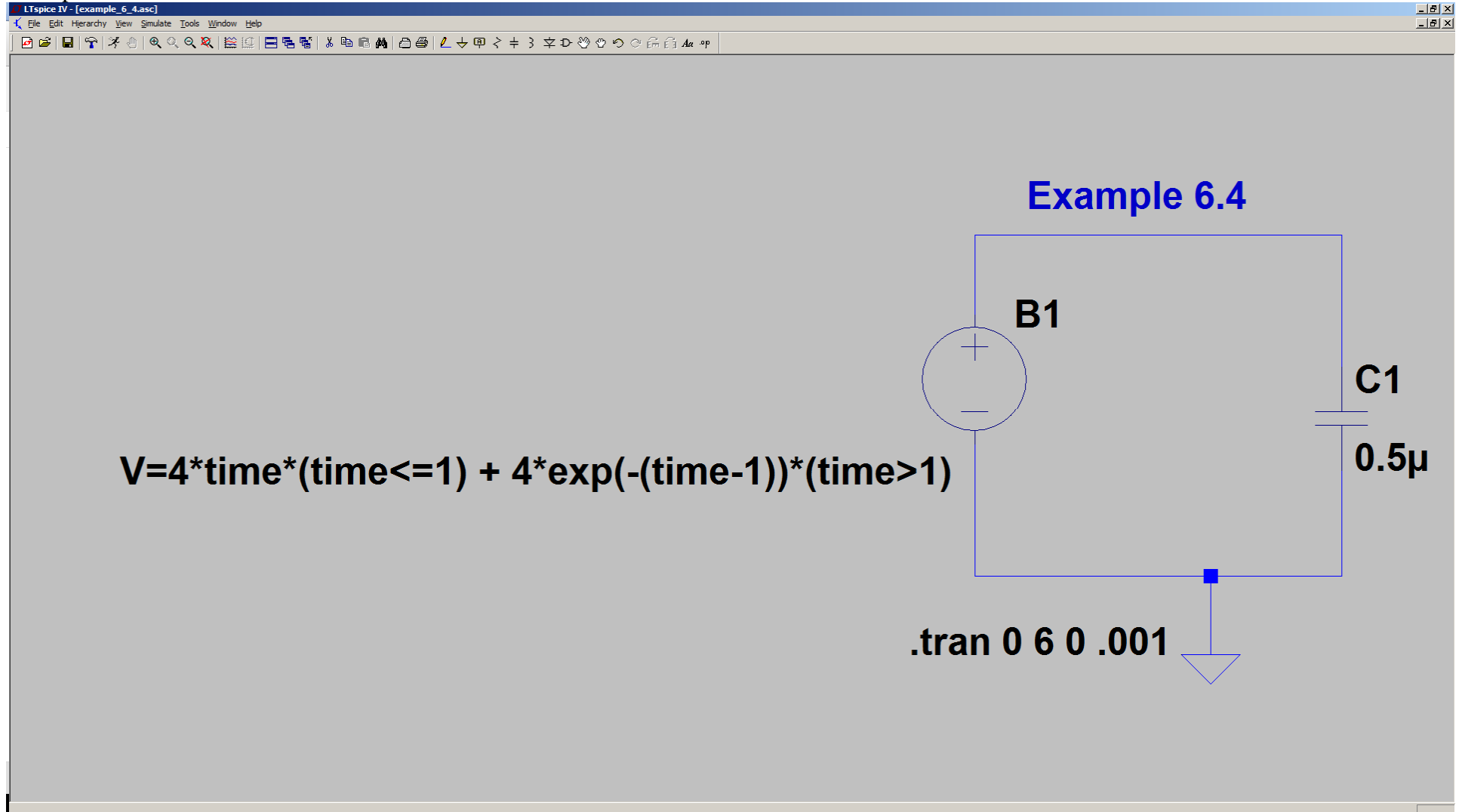

More complex behavioral voltage source


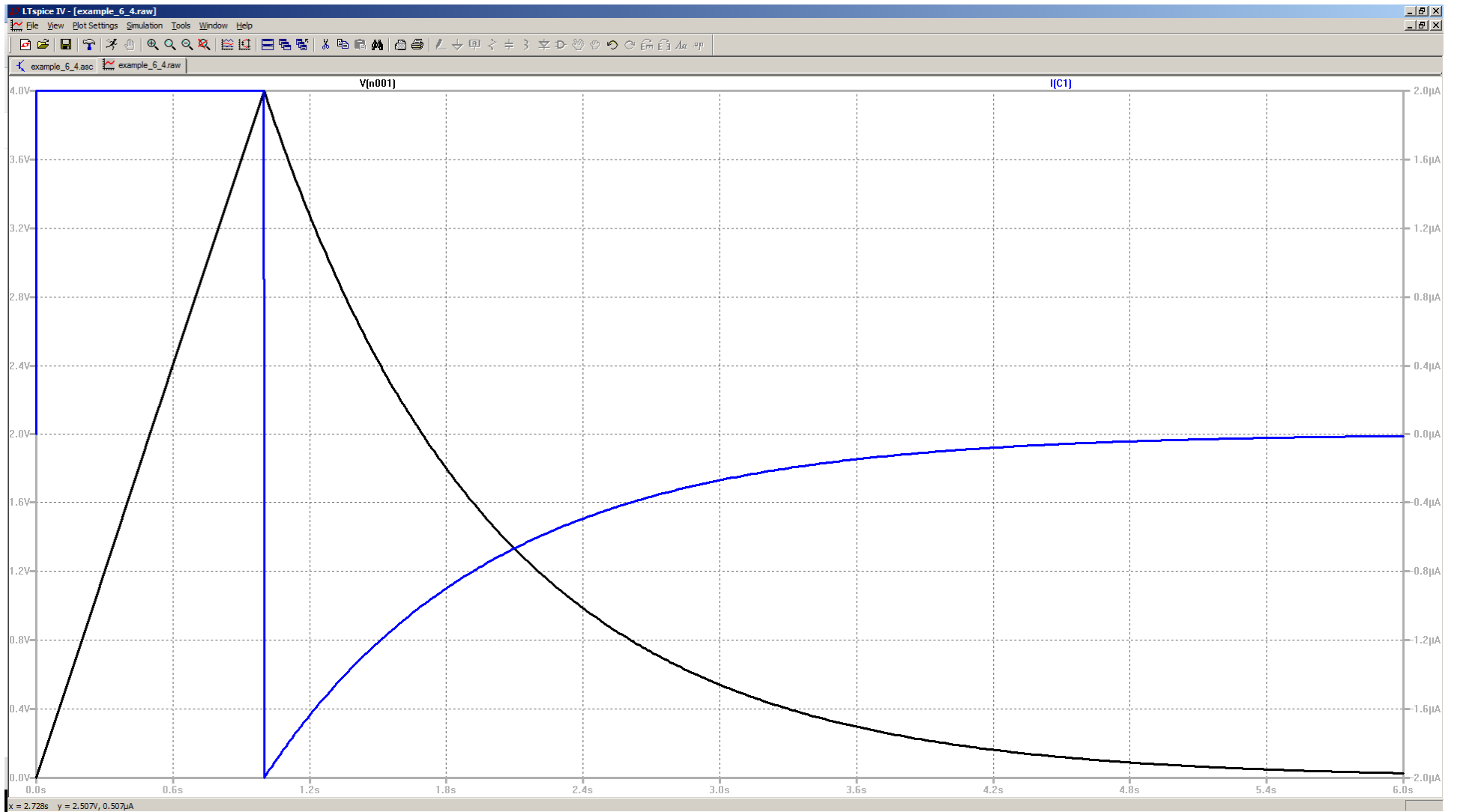
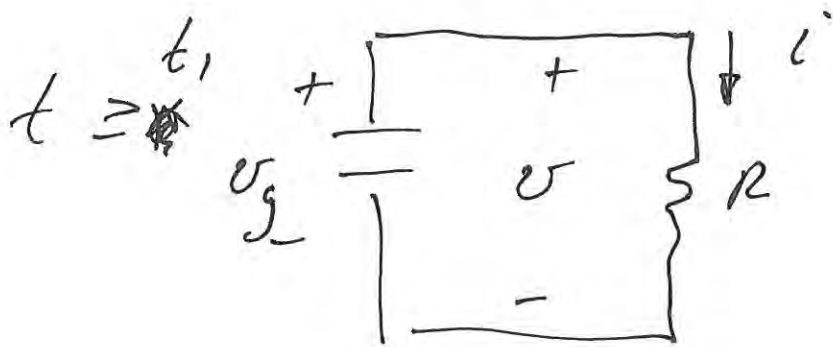
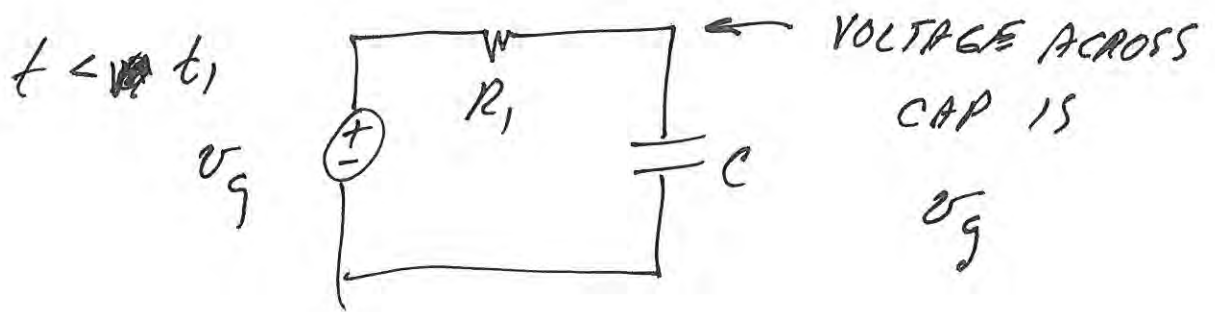


FIGURE 7.10

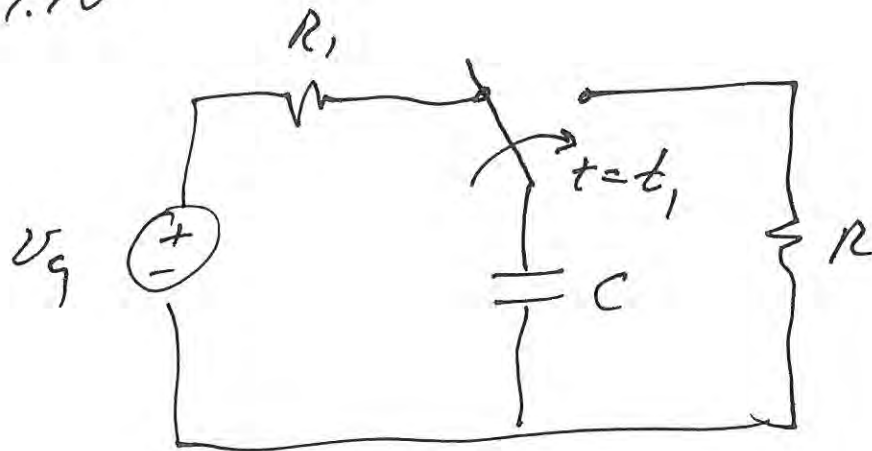

NODAL:
$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\frac{C dv}{dt} = -\frac{v}{R}$$

$$\int_{t_1}^t \frac{dv(x)}{v(x)} = - \int_{t_1}^t \frac{dq}{RC}$$

$$\ln v(x) \Big|_{t_1}^t = - \frac{(t-t_1)}{RC}$$

$$\ln \frac{v(t)}{v(t_1)} = - \frac{(t-t_1)}{RC}$$





$$v(t) = v(t_1) e^{- (t-t_1)/\tau} ; t \geq t_1$$

$t_1 =$ SWITCHING TIME

IF $t_1 = 0$

$$v(t) = v(0) e^{- t/\tau} ; t \geq 0$$



EXAMPLE 7.3

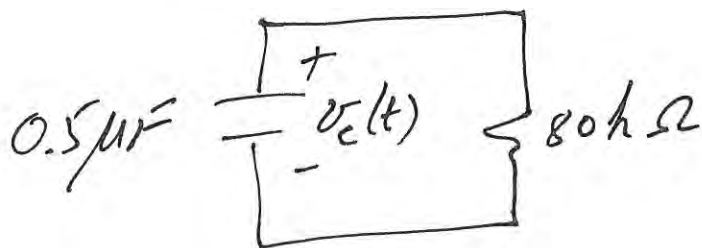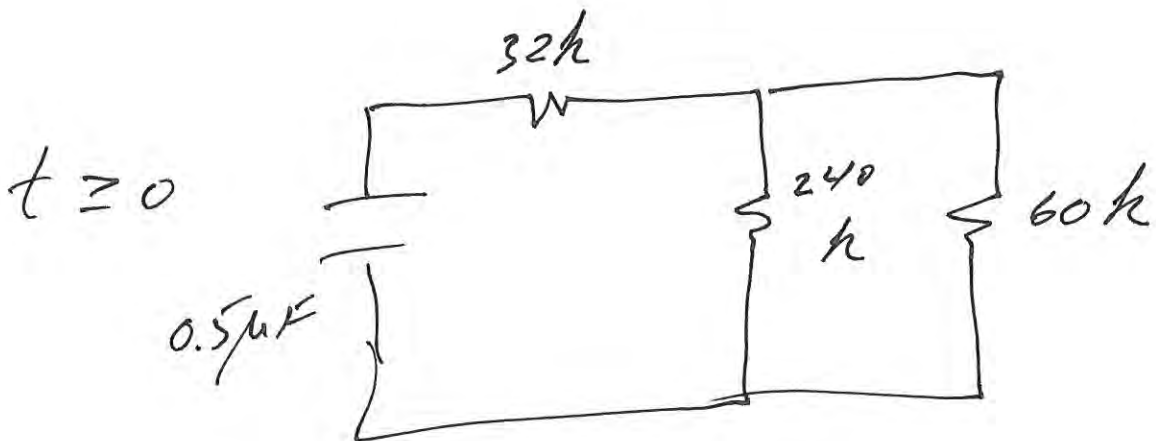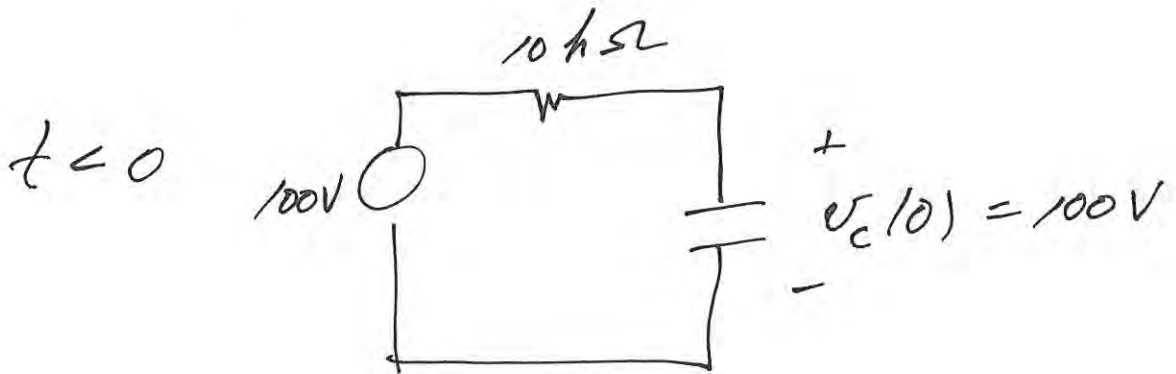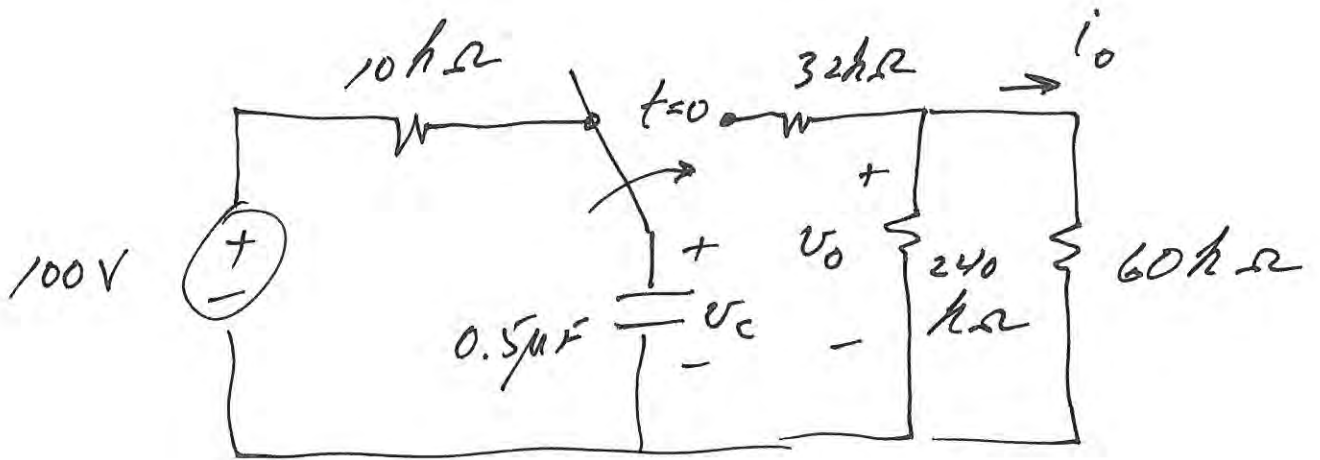

$$\tau = RC = 0.04 \text{ SEC}$$

$$v_c(t) = v_c(0) e^{-t/\tau}$$

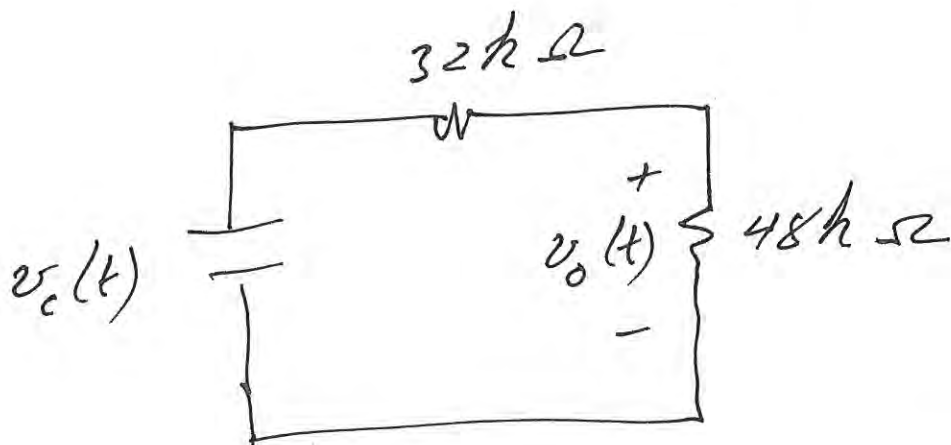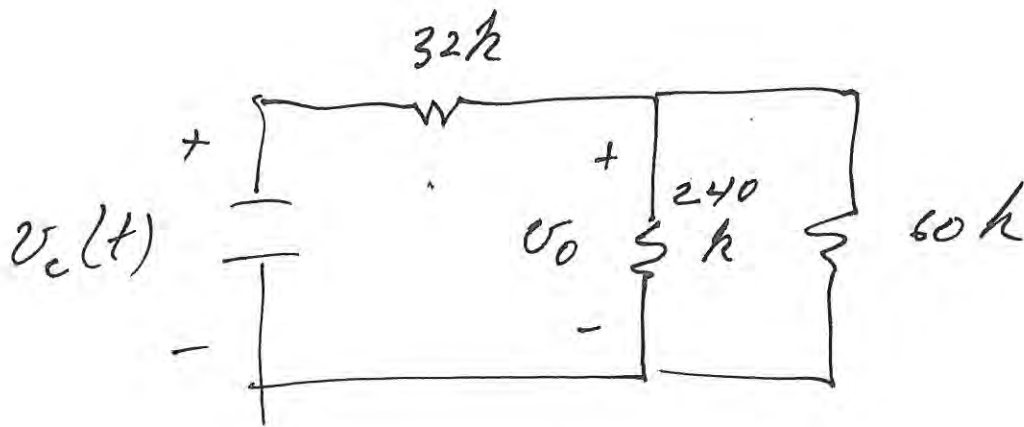
$$v_c(t) = 100 e^{-25t} \text{ V ; } t \geq 0$$





VOLTAGE DIVISION FOR $v_o(t)$:



$$v_o(t) = \frac{48k\Omega}{(32k\Omega + 48k\Omega)} v_c(t)$$

Example 7.3

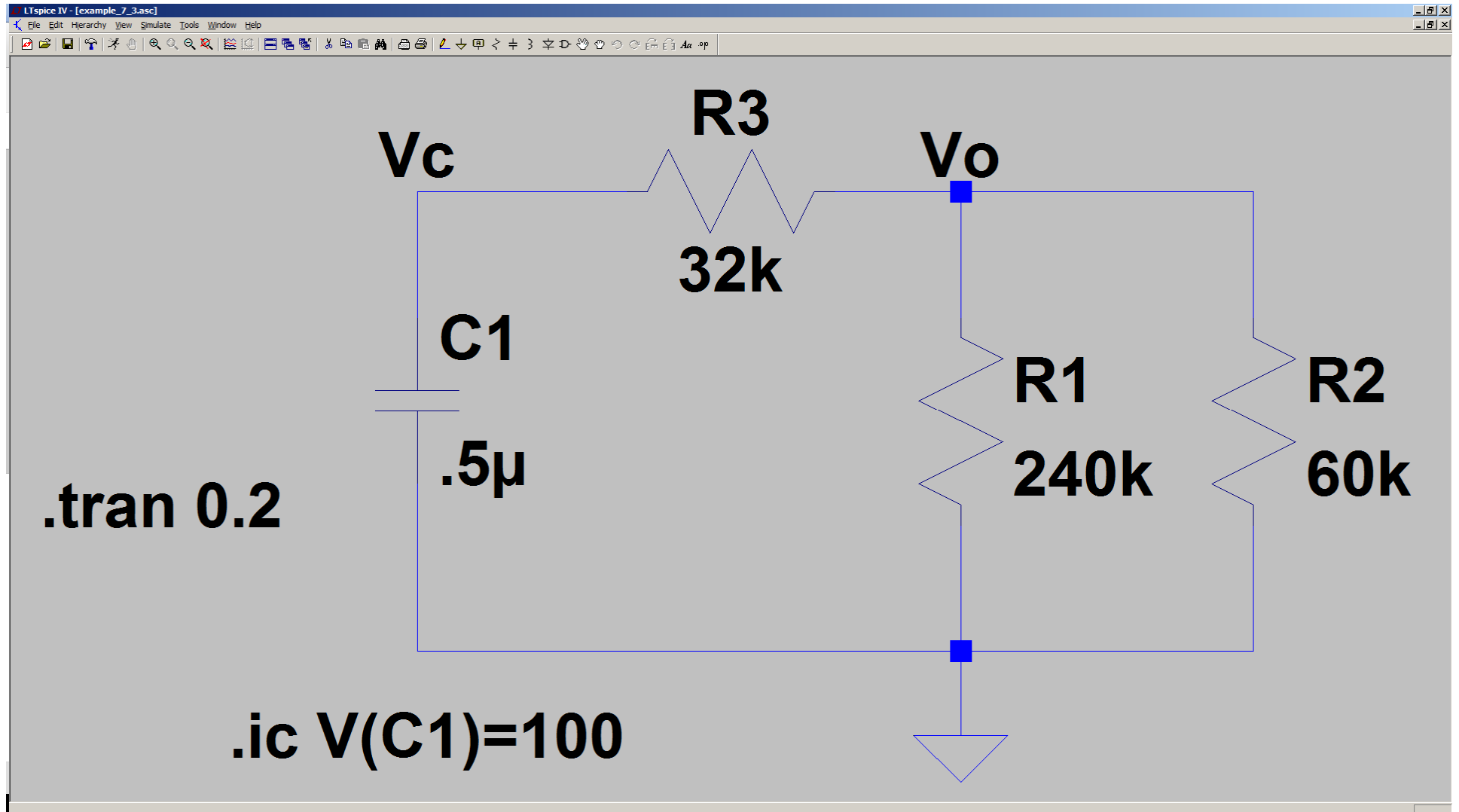

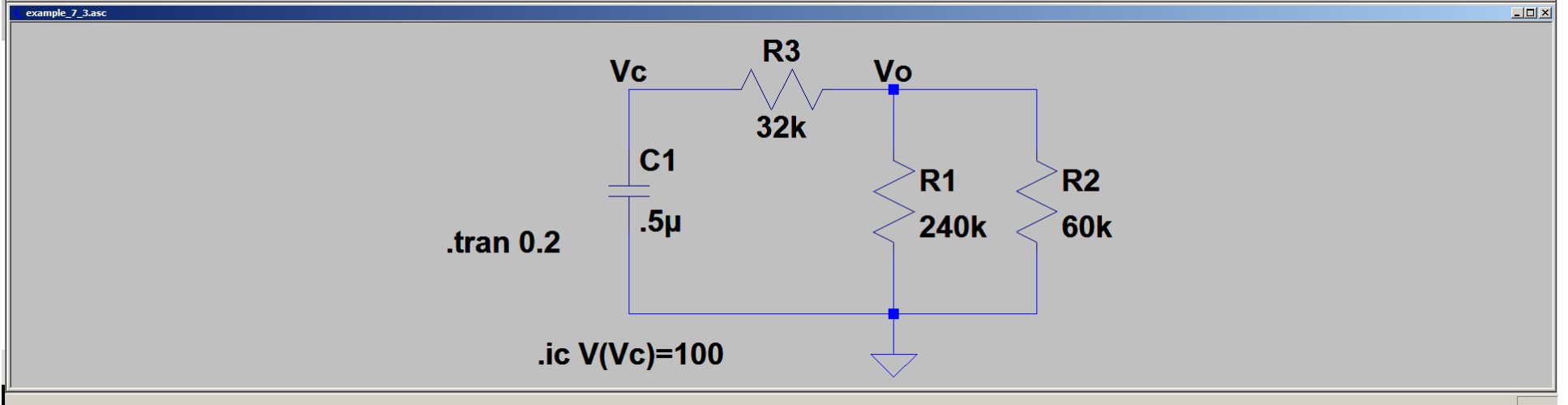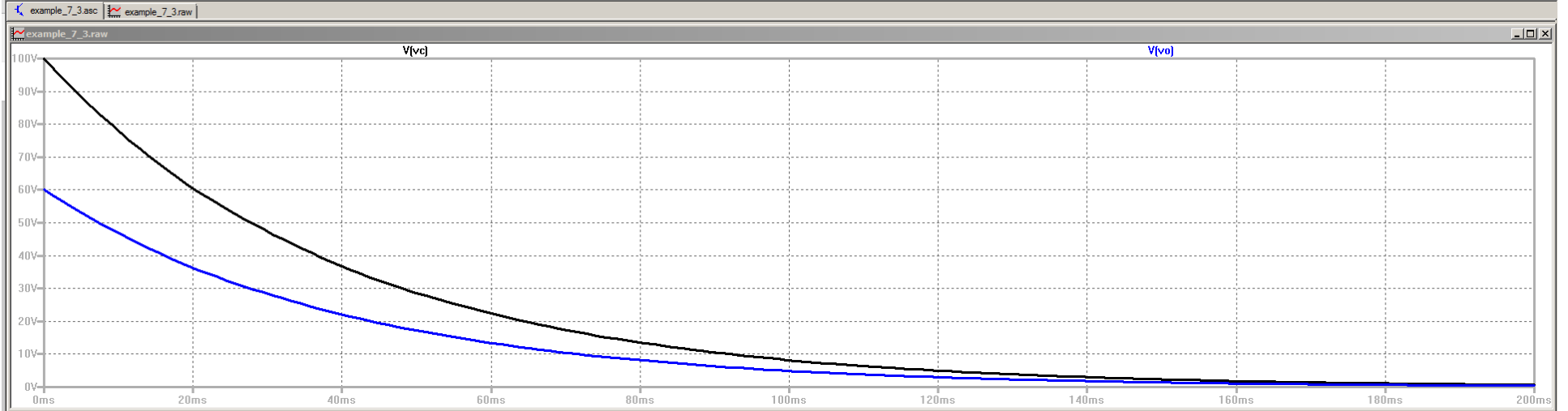

EXAMPLE 7.4 PG 223

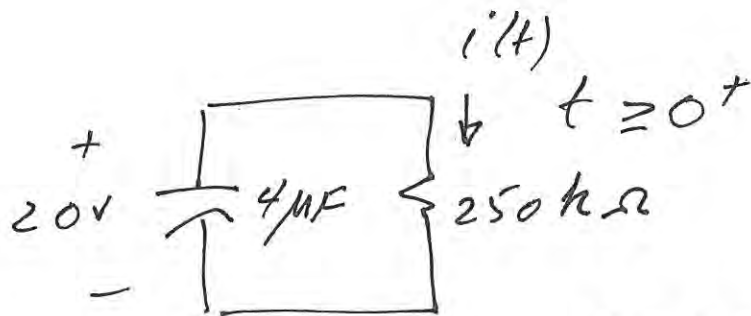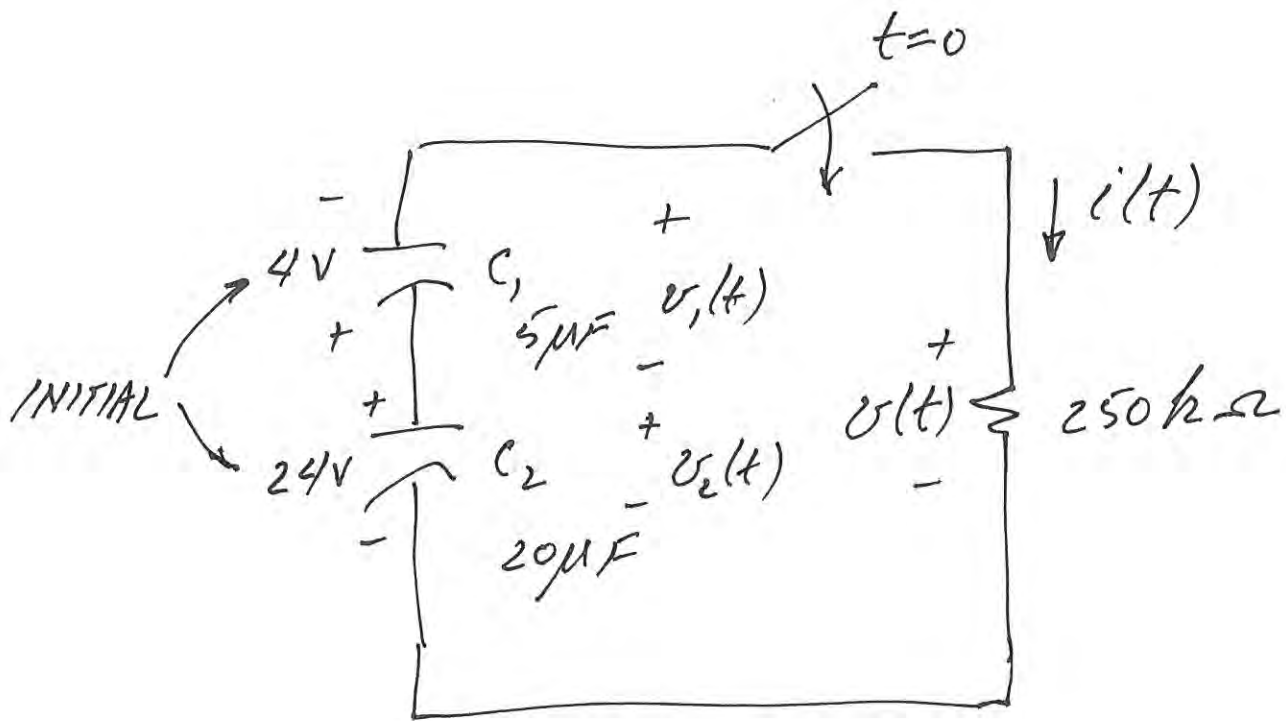

$$\tau = RC = 15$$


$$v(t) = 20 e^{-t} \text{ V}; t \geq 0^+$$

$$i(t) = \frac{v(t)}{25,000} = 80 e^{-t} \text{ } \mu\text{A}; t \geq 0^+$$

$$v_1(t) = -\frac{1}{C_1} \int_0^t i(x) dx - 4$$

$$v_2(t) = -\frac{1}{C_2} \int_0^t i(x) dx + 24$$

VOLTAGE
DIV
FOR
 v_1, v_2 ?

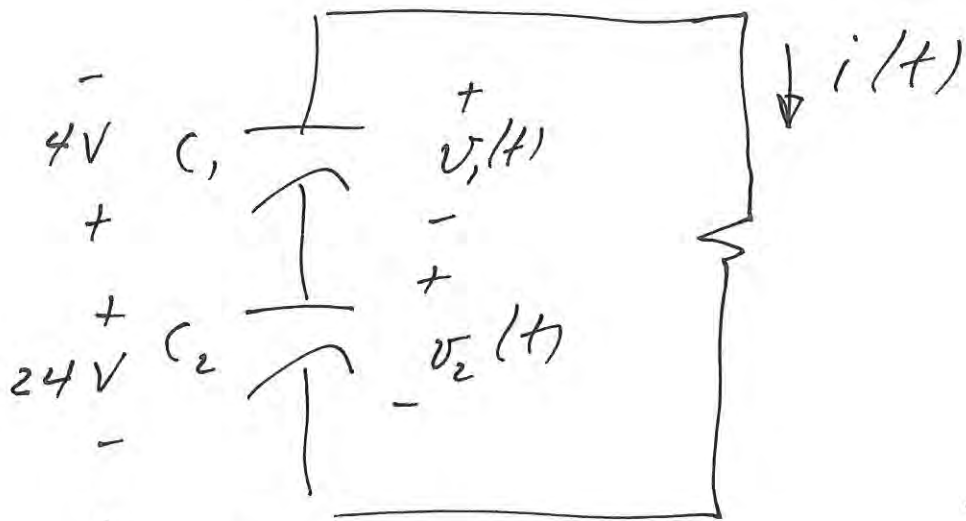

NOTE
SIGN

$$v_1 = -\frac{1}{C_1} \int_0^t i(x) dx + v_1(0^+)$$

$-4V$

$$v_2 = -\frac{1}{C_2} \int_0^t i(x) dx + v_2(0^+)$$


$+24V$

NOTE
SIGN

$$v_1(t) = (16e^{-t} - 20)V; t \geq 0$$

$$v_2(t) = (4e^{-t} + 20)V; t \geq 0$$



Example 7.4

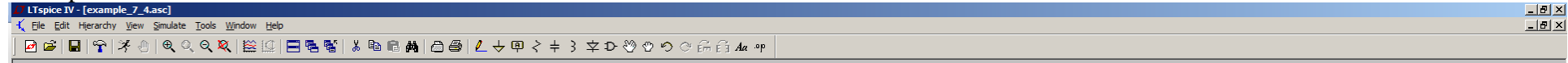

Example 7.4

```
.ic V(B)=20  
.ic V(A)=24
```

```
.tran 0 5 0 .01m
```

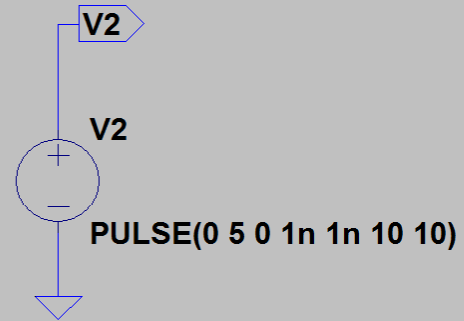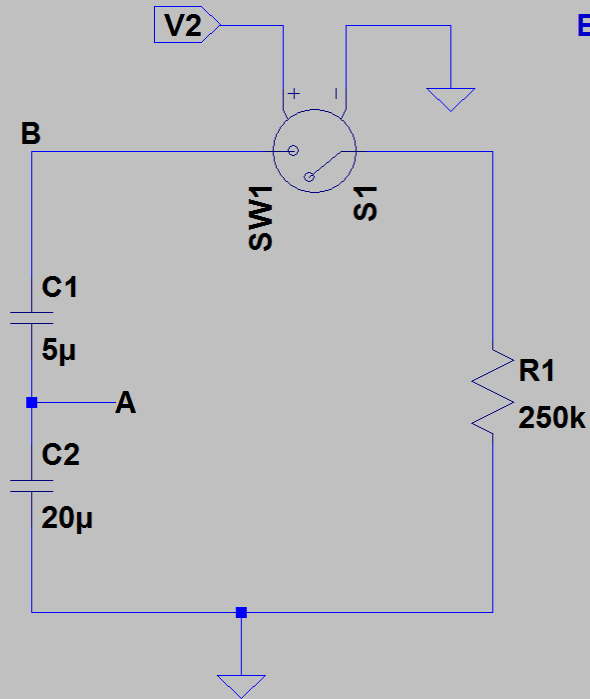

```
.model SW1 SW(Vh=0 Ron=0.001 Roff=1G Vt = 2)
```


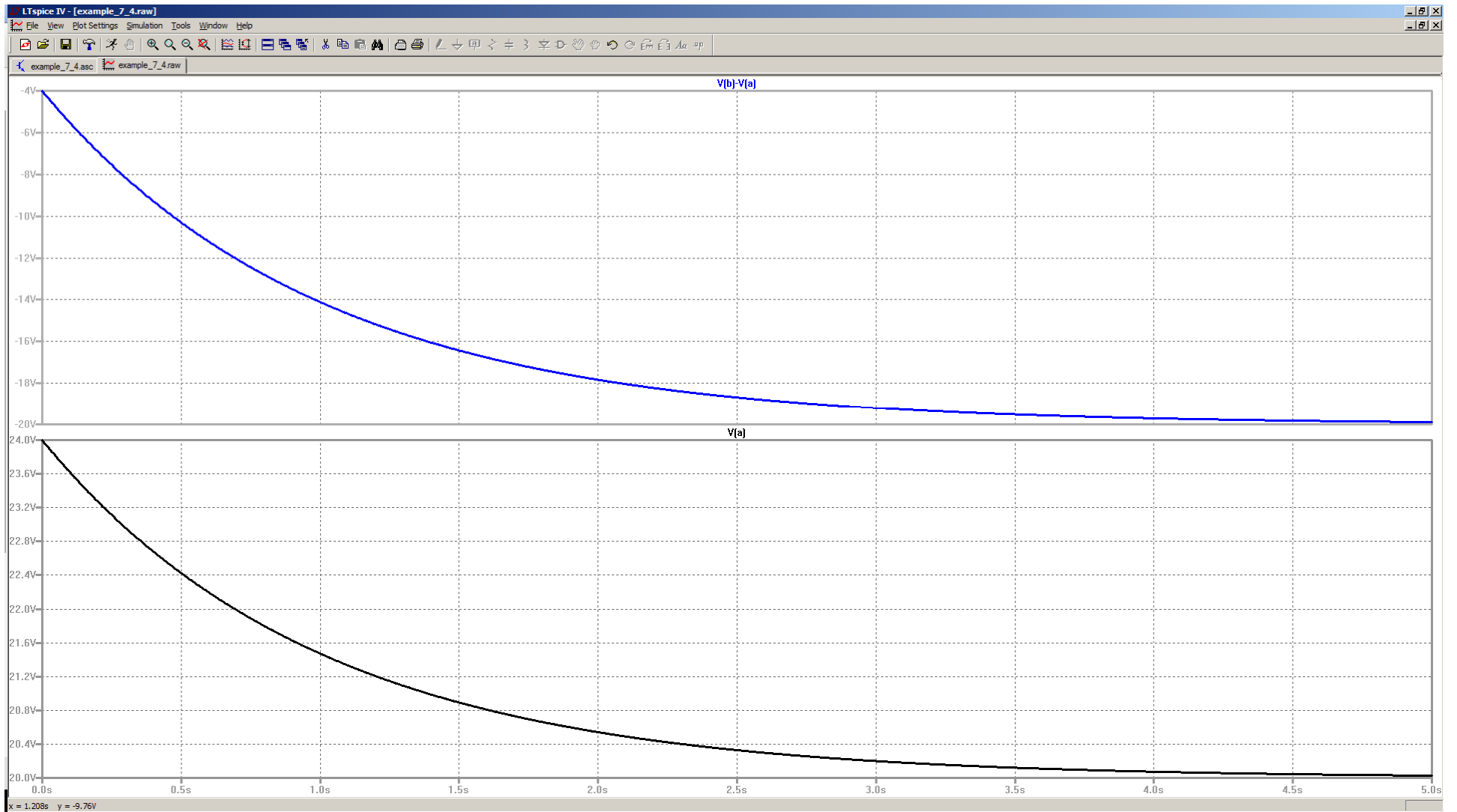


FIG 7.16 STEP RESPONSE

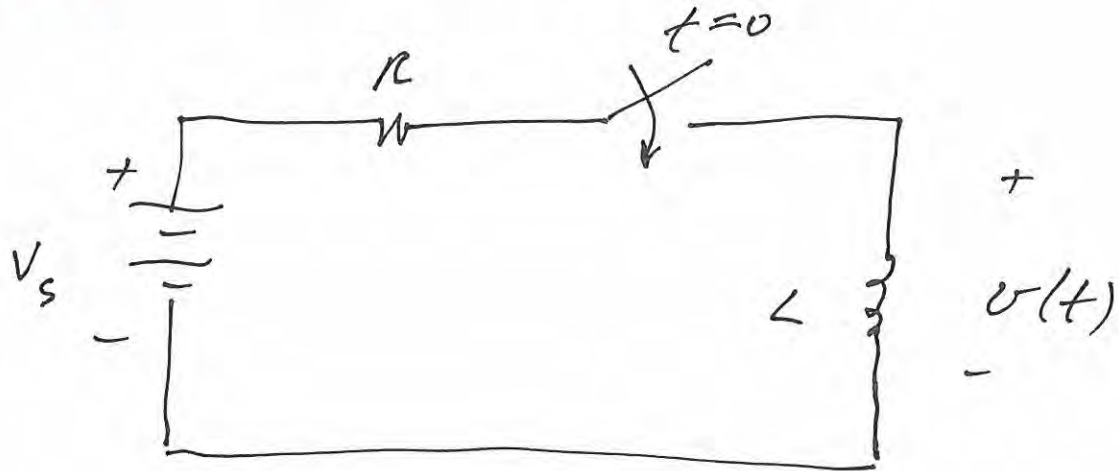

$$\text{MESH: } V_s = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt} = -\frac{Ri + V_s}{L} = -\frac{R}{L} \left(i - \frac{V_s}{R} \right)$$

$$\frac{di(t)}{i(t) - V_s/R} = -\frac{dt}{\tau} \quad \tau = \frac{L}{R}$$

$$\frac{di(x)}{i(x) - V_s/R} = -\frac{dx}{\tau}$$

$$\int_{t_0}^t \frac{di(x)}{i(x) - V_s/R} = -\frac{1}{\tau} \int_{t_0}^t dx$$

$$\ln \left[i(t) - \frac{V_s}{R} \right] \Big|_{t_0}^t = -\frac{1}{\tau} (t - t_0)$$

$$\ln \left[\frac{i(t) - \frac{V_s}{R}}{i(t_0) - \frac{V_s}{R}} \right] = -\frac{1}{\tau} (t - t_0)$$

$$i(t) = \frac{V_s}{R} + \left[i(t_0) - \frac{V_s}{R} \right] e^{-(t-t_0)/\tau}$$

THIS PROBLEM, $t_0 = 0$

$$i(t) = \frac{V_s}{R} + \left[i(0) - \frac{V_s}{R} \right] e^{-t/\tau}$$

NOTE: $i(0) = \frac{V_s}{R} + \left[i(0) - \frac{V_s}{R} \right] = i(0)$

$$i(\infty) = \frac{V_s}{R}$$

SOLUTION IS OF FORM

$$i(t) = i(\infty) + \left[i(0) - i(\infty) \right] e^{-t/\tau}$$

THIS PARTICULAR PROBLEM

$$i(0) = 0$$


$$\therefore i(t) = \frac{V_s}{R} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{R}$$

$$t \geq 0$$

FIGURE 7.16

 $t=0$

PAGE 224

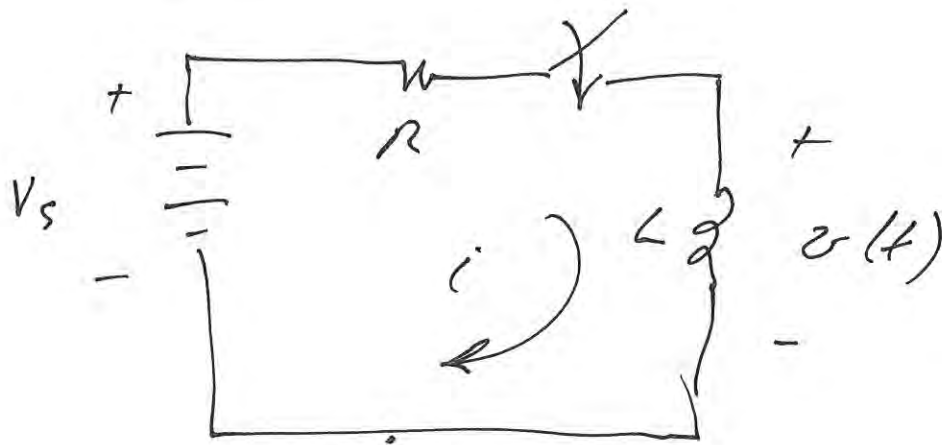ASSUME NON-ZERO $i(0^-)$

$$\text{LOOP: } V_s - iR - L \frac{di}{dt} = 0$$

$$\frac{di}{dt} = \frac{V_s - iR}{L} = -\frac{R}{L} \left(i - \frac{V_s}{R} \right)$$

$$\frac{di}{i - V_s/R} = -\frac{dt}{\tau} \quad (\tau = L/R)$$

$$\text{INTEGRATE: } \ln \left[i - \frac{V_s}{R} \right] \Big|_{i(0^+)}^{i(t)} = -\frac{t}{\tau}$$

$$\vdots$$

$$i(t) = \frac{V_s}{R} + \left[i(0^+) - \frac{V_s}{R} \right] e^{-t/\tau}$$

$$v(t) = L \frac{di(t)}{dt}$$


$$v(t) = L \frac{d}{dt} \left\{ \frac{V_s}{R} + \left[i(0^+) - \frac{V_s}{R} \right] e^{-t/\tau} \right\}$$

$$= L \left[i(0^+) - \frac{V_s}{R} \right] \left(-\frac{1}{\tau} \right) e^{-t/\tau}$$

$$v(t) = [V_s - Ri(0^+)] e^{-t/\tau} \quad (\text{EQ 7.42})$$

ALTERNATIVE APPROACH

NODAL: $i(t) = \frac{V_s - v(t)}{R}$

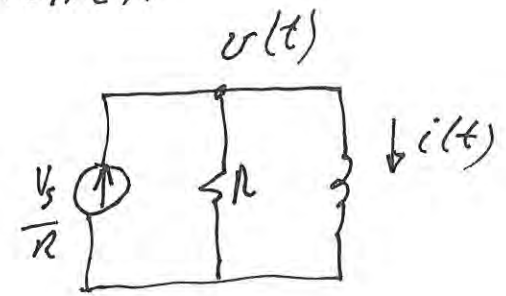

$\frac{d}{dt}$ BOTH SIDES: $\frac{di(t)}{dt} = -\frac{1}{R} \frac{dv(t)}{dt}$


BUT $v(t) = L \frac{di}{dt}$

$$\frac{1}{L} v(t) + \frac{1}{R} \frac{dv(t)}{dt} = 0$$

$$\frac{dv(t)}{v(t)} = -\frac{dt}{\tau}$$

INTEGRATE: $\ln \left[\frac{v(t)}{v(0^+)} \right] = -\frac{t}{\tau}$

$$v(t) = v(0^+) e^{-t/\tau}$$

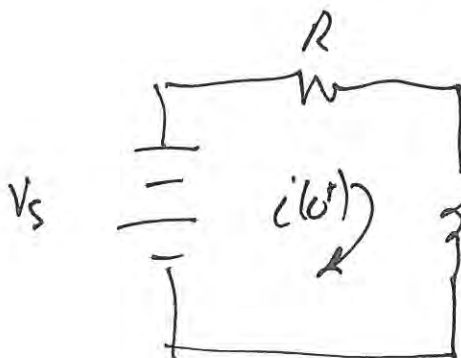

$$V_s - i(0^+)R - v(0^+) = 0$$

$$v(t) = [V_s - Ri(0^+)] e^{-t/\tau}$$

(SAME AS EQ 7.42)

SUMMARY

NODAL EQ FOR VOLTAGE


$$\frac{dv(t)}{dt} + \frac{R}{L} v(t) = 0$$

LOOP EQ FOR CURRENT

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V_s}{L}$$

? DIFFERENCE IN SOLUTIONS


EXAMPLE 7.5

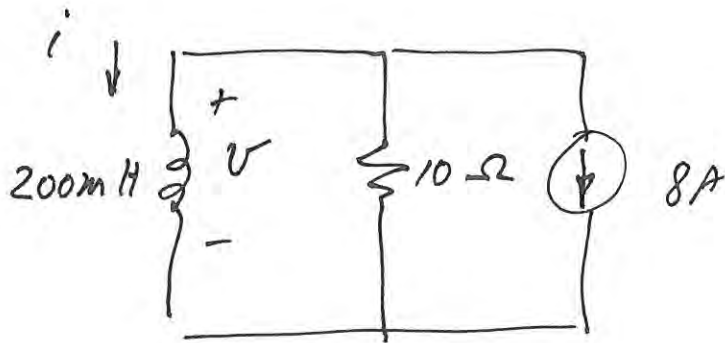

$$t < 0$$

$$i(0^-) = -8A$$

$$v(0^-) = 0V$$

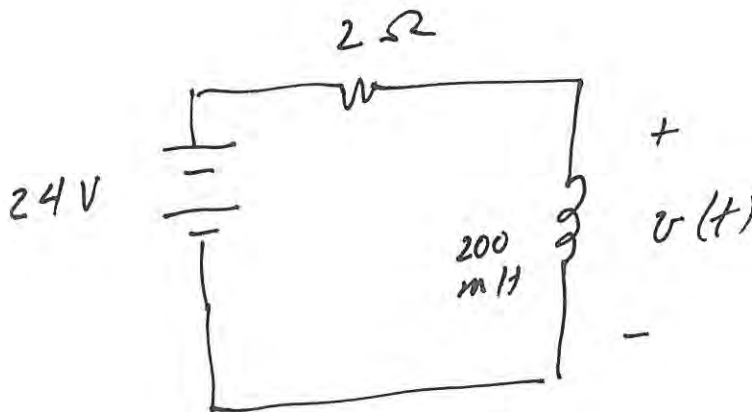

$$t \geq 0$$

$$i(0^+) = -8A$$

$$v(0^+) = ?$$

$$i(\infty) = \frac{24V}{2\Omega} = 12A$$

$$\tau = \frac{L}{R} = \frac{0.2}{2} = 0.1S$$

KNOW SOL'N OF FORM

$$i(t) = A + Be^{-t/\tau}$$

$$i(t) = A + B e^{-t/\tau}$$

$$\left. \begin{array}{l} i(0^+) = A + B \\ i(\infty) = A \end{array} \right\} \Rightarrow B = i(0^+) - i(\infty)$$


$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 12 + [-8 - 12] e^{-10t}$$

$$i(t) = 12 - 20 e^{-10t} \text{ A ; } t \geq 0^+$$


$$v(t) = L \frac{di(t)}{dt} = 0.2 \text{ H} \left(200 e^{-10t} \frac{\text{A}}{\text{s}} \right)$$
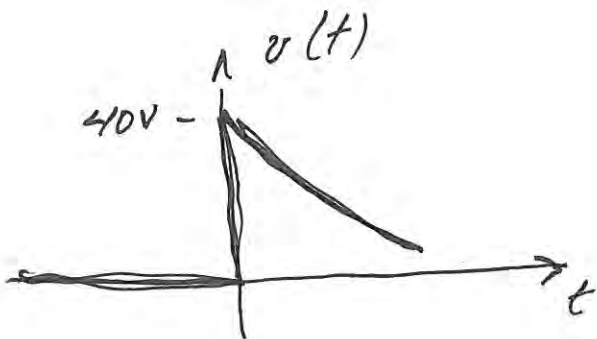
$$v(t) = 40 e^{-10t} \text{ V ; } t \geq 0^+$$




$$v(0^-) = 0$$

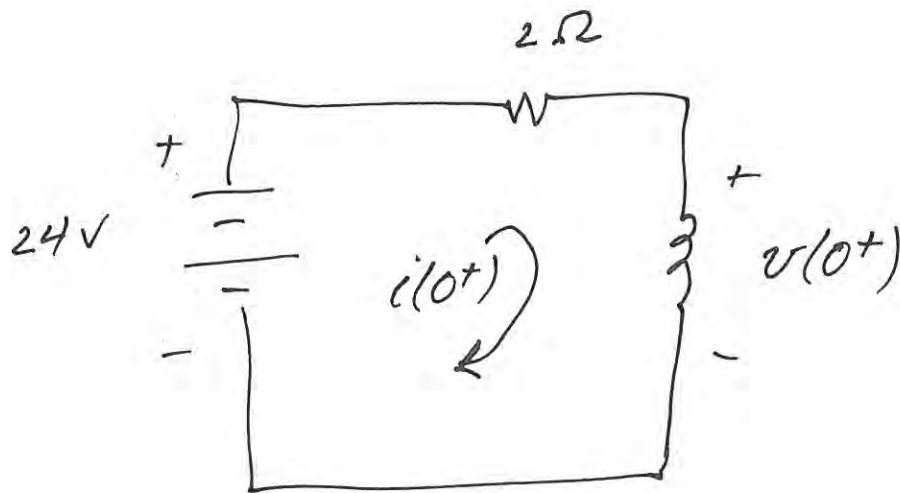CONSIDER INSTANT AFTER WHICH
SWITCH IS THROWN



LOOP EQ $24V - 2\Omega i(0^+) = v(0^+)$

$$24V + 16V = v(0^+)$$

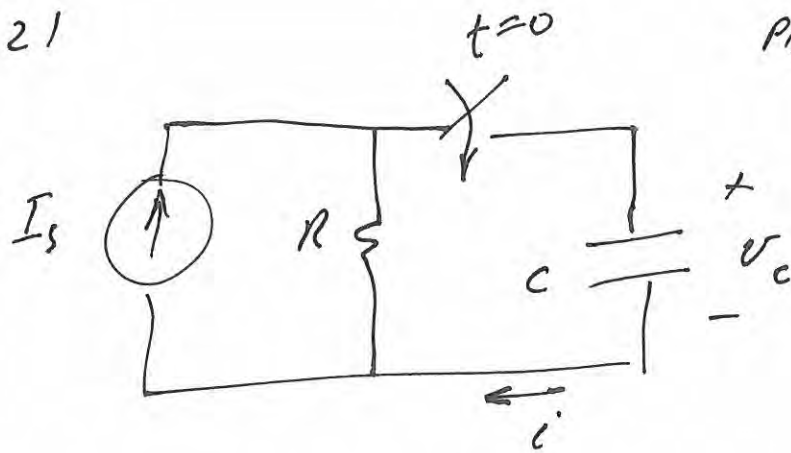

$$\text{NODAL EQ: } C \frac{dv_c}{dt} + \frac{v_c}{R} - I_s = 0$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{I_s}{C}$$

SOL'N MUST BE

$$v_c(t) = v_c(\infty) + [v_c(0^+) - v_c(\infty)] e^{-t/\tau}$$


$$v_c(\infty) = RI_s$$

$$v_c(0^+) \equiv V_0 = v_c(0^-)$$

$$v_c(t) = RI_s + (V_0 - RI_s) e^{-t/RC}; t \geq 0^+$$

SHOULD BE
 $t \geq 0$

EQUALLY VALID APPROACH

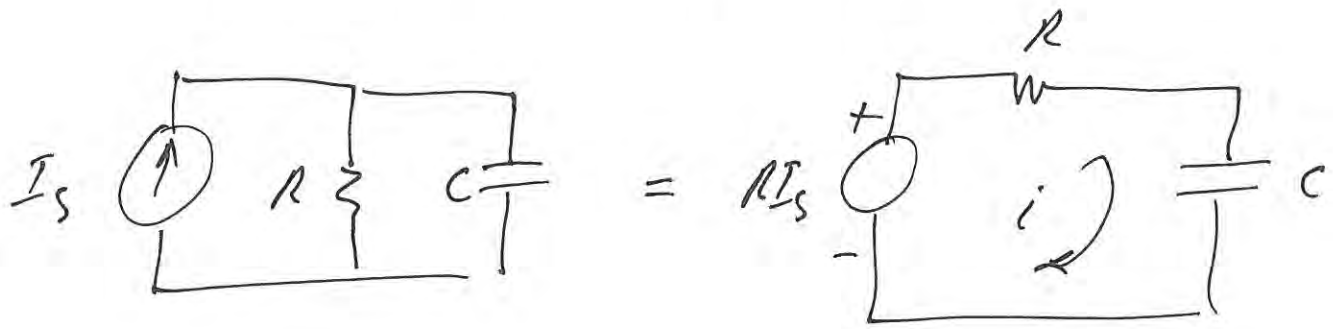

$$\text{LOOP EQ: } RI_s - Ri - \frac{1}{C} \int i(t) dt = 0$$

$\frac{d}{dt}$ BOTH SIDES:

$$-R \frac{di}{dt} - \frac{i(t)}{C} = 0$$

$$\frac{di(t)}{dt} = -\frac{1}{RC} i(t)$$

$$\frac{di(t)}{i(t)} = -\frac{dt}{\tau}$$


⋮

$$i(t) = i(0^+) e^{-t/\tau} ; t \geq 0^+$$


$$I_s - \frac{V_0}{R} \quad (\text{FROM MESH EQ } RI_s - Ri(0^+) - V_0 = 0)$$

RESISTIVE NETWORK


W DEP, INDP SOURCES

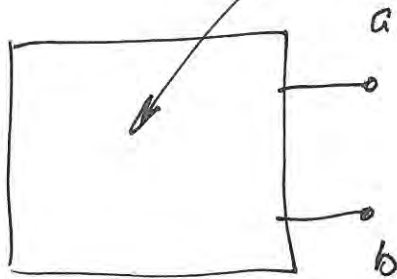

||

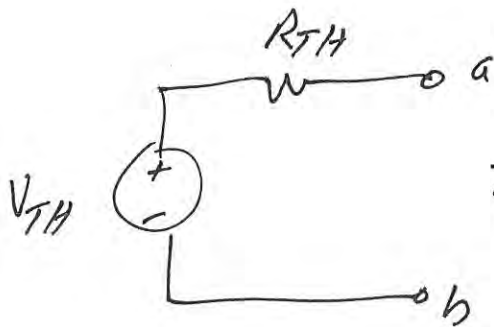


THEVENIN

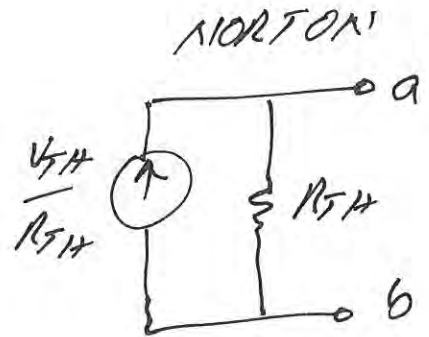


NORTON

CALCULATION :

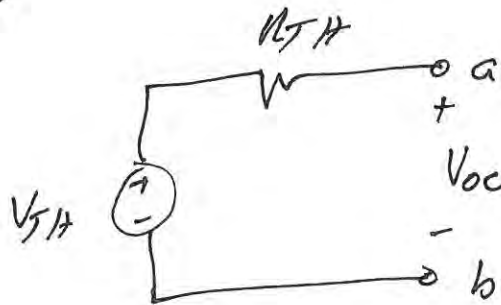
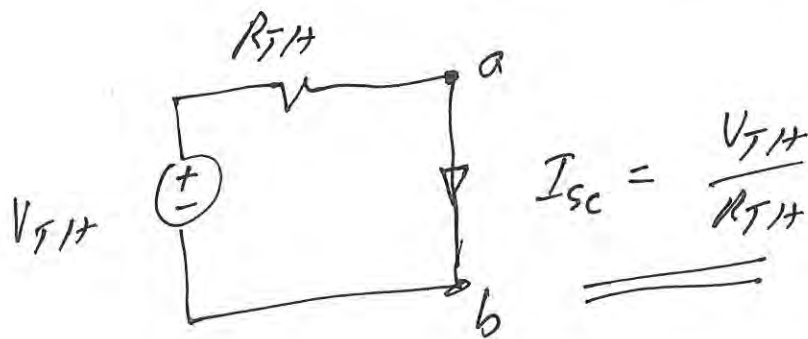
$$\underline{\underline{V_{TH} = V_{oc}}}$$




$$I_{sc} = \frac{V_{TH}}{R_{TH}}$$


$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$
$$V_{TH} = V_{oc}$$

INDP SOURCES ONLY

SHORT VOLTAGE SOURCES

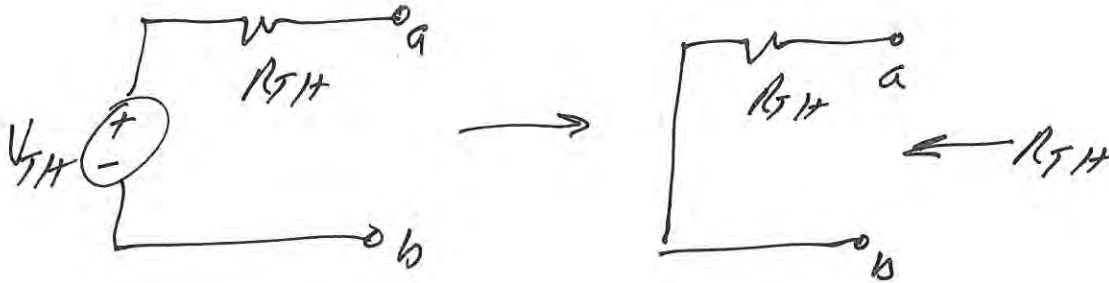


OPEN CURRENT SOURCES

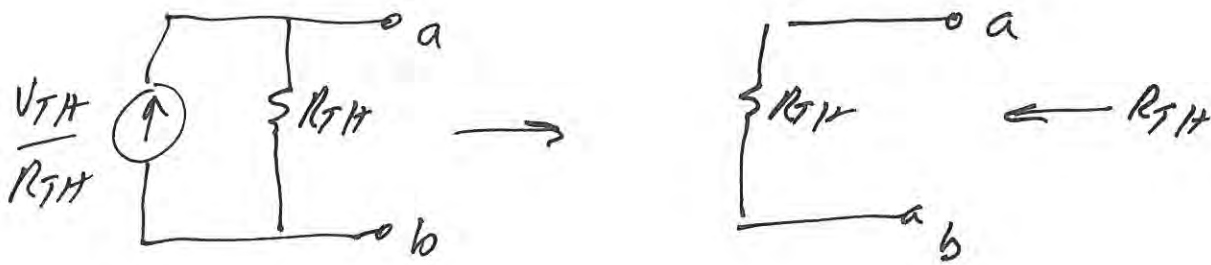

DEP SOURCES

DEACTIVATE ALL INDP SOURCES


APPL TEST SOURCE

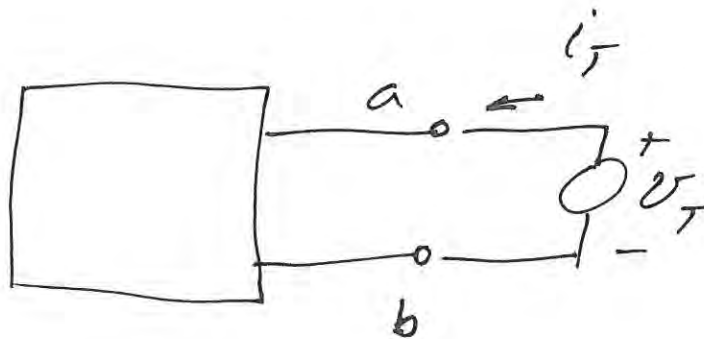


$$R_{TH} = \frac{V_T}{i_T}$$



WITH NO DEACTIVATION, GENERALLY
GET SOLUTION OF FORM

$$V_T = A i_T + B$$

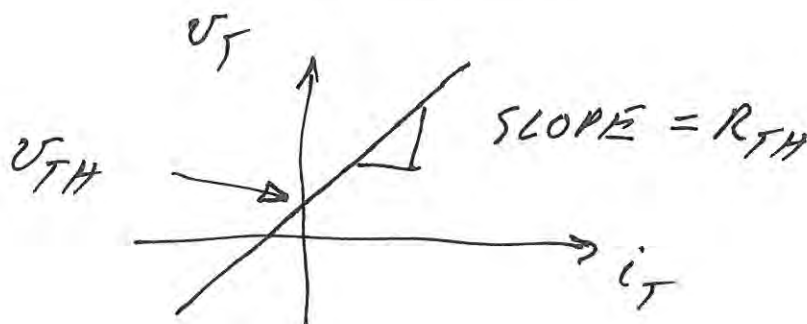

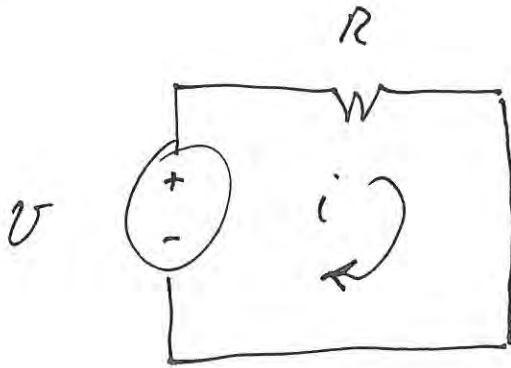

$$V = iR$$

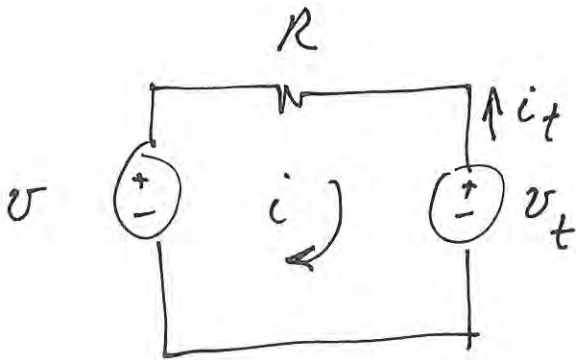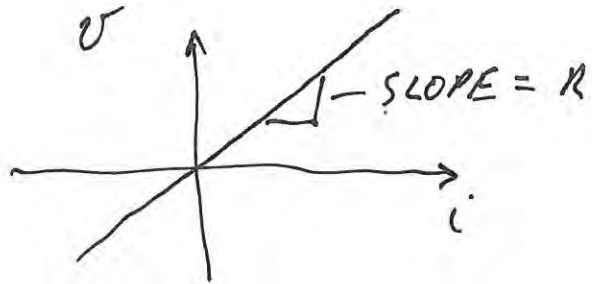



$$V - iR - V_t = 0$$

$$i = -i_t$$

$$V + i_t R - V_t = 0$$



$$V_t = i_t R + V$$

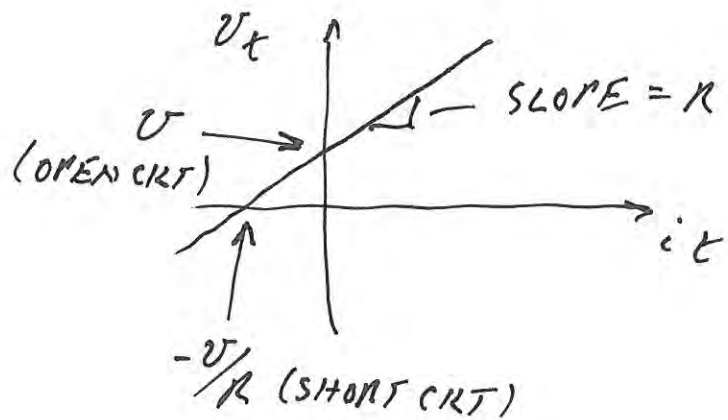

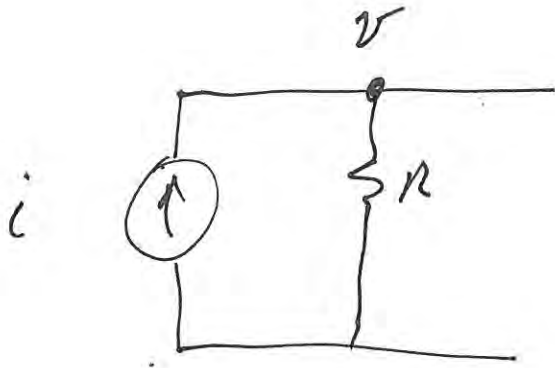


$$\frac{v}{R} - i = 0$$

$$v = iR$$

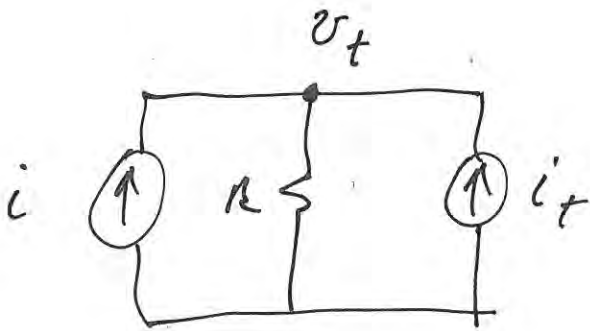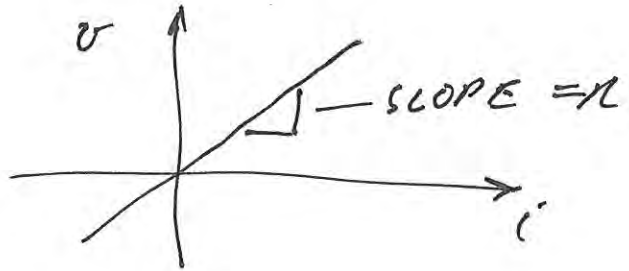


$$\frac{v_t}{R} - i - i_t = 0$$

$$v_t = iR + i_t R$$

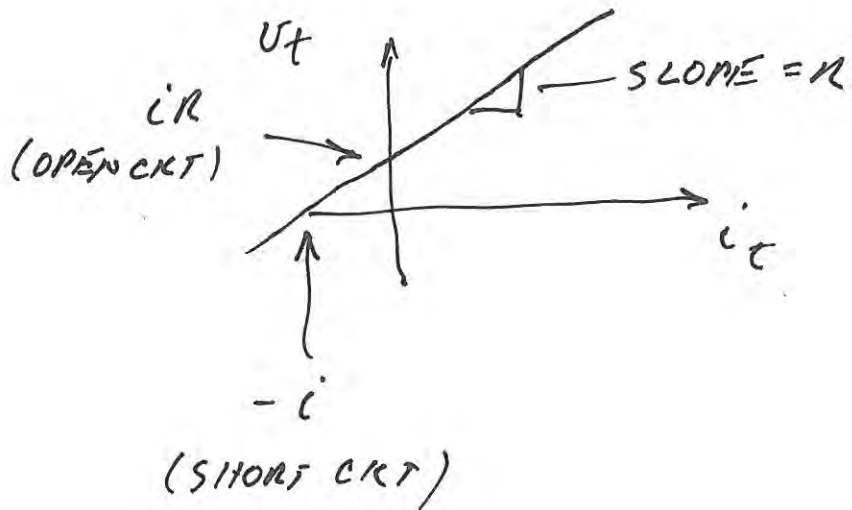

EXAMPLE 7.6

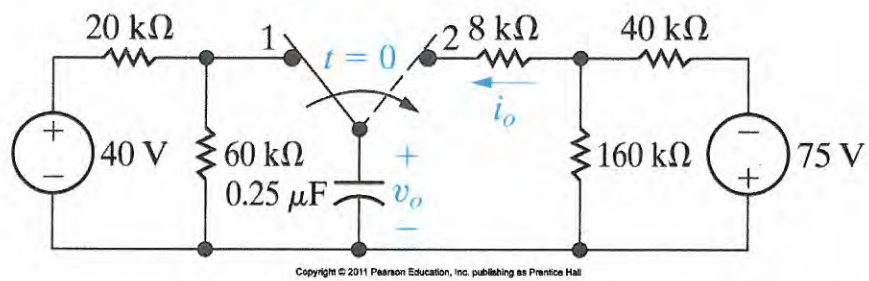

Find


a) $v_o(t)$; $t \geq 0$

b) $i_o(t)$; $t \geq 0^+$

EXAMPLE 7.6

PAGE 230

$t < 0$

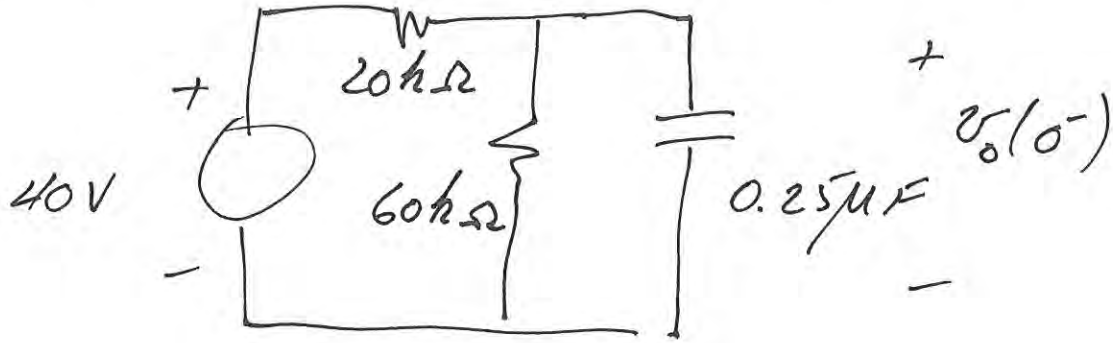






VOLTAGE DIVISION FOR $v_o(t^-)$

$$v_o(t^-) = 40\text{V} \left(\frac{60\text{k}\Omega}{20\text{k}\Omega + 60\text{k}\Omega} \right)$$

$$v_o(t^-) = 30\text{V} = v_o(t^+)$$


$t \geq 0$

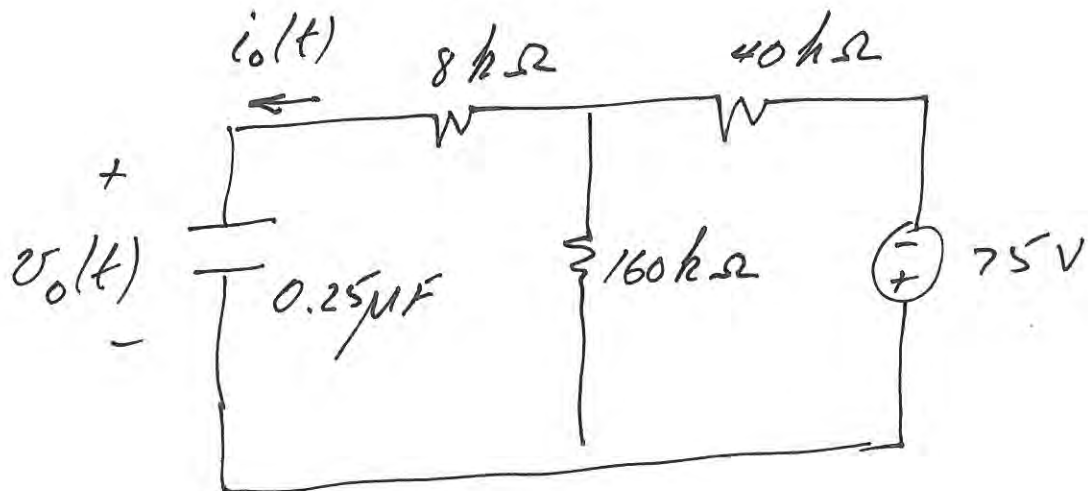

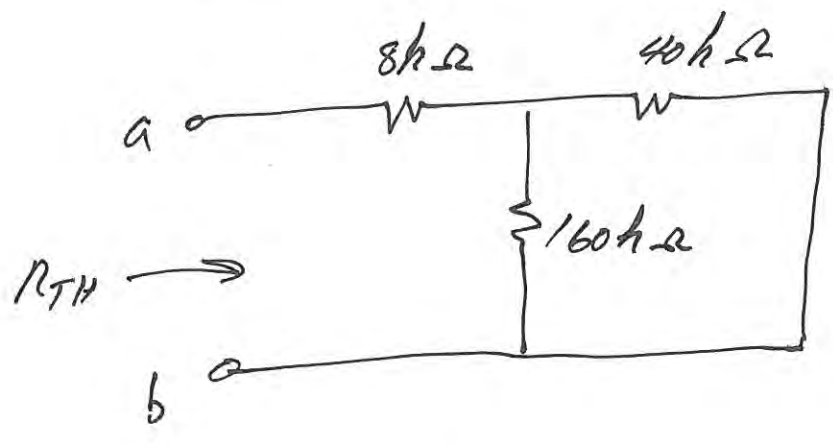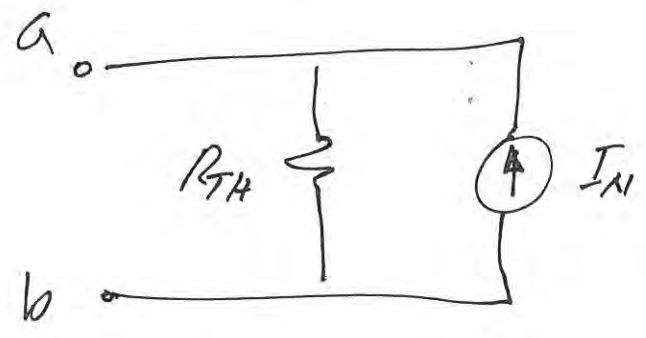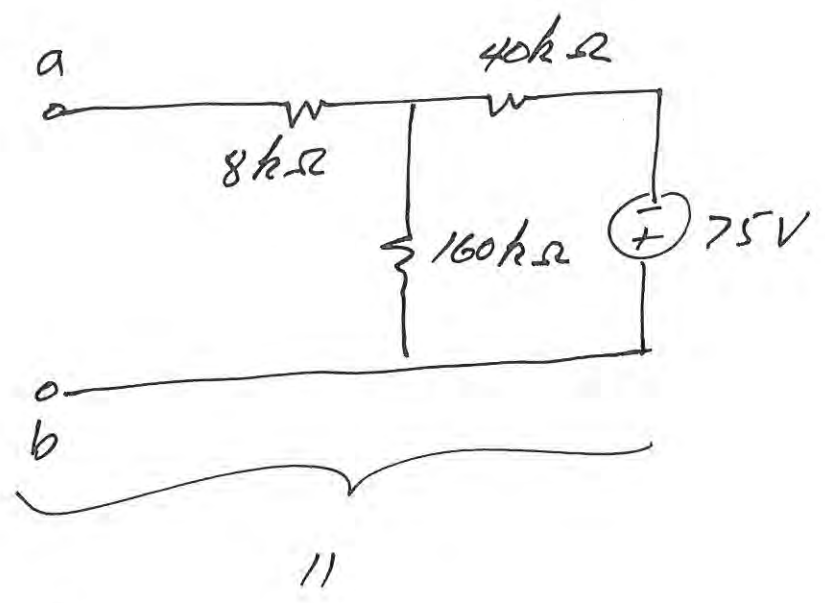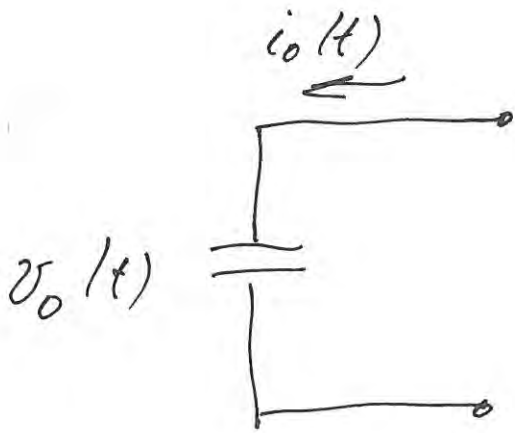


$$R_{TH} = (40k\Omega \parallel 160k\Omega) + 8k\Omega$$

$$= 40k\Omega$$

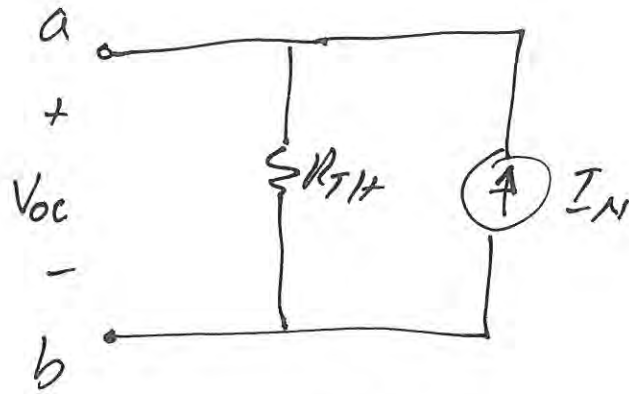

$$V_{oc} = R_{TH} I_N$$


$$I_N = \frac{V_{oc}}{R_{TH}} = ?$$

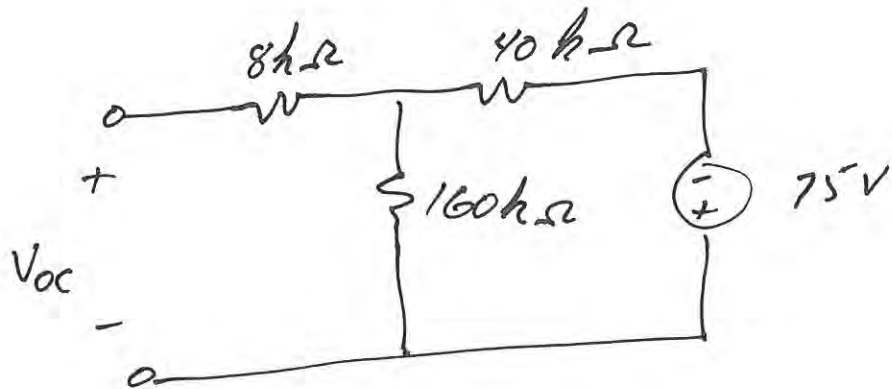

$$V_{oc} = -75V \left(\frac{160k\Omega}{160k\Omega + 40k\Omega} \right)$$

$$V_{oc} = -60V$$
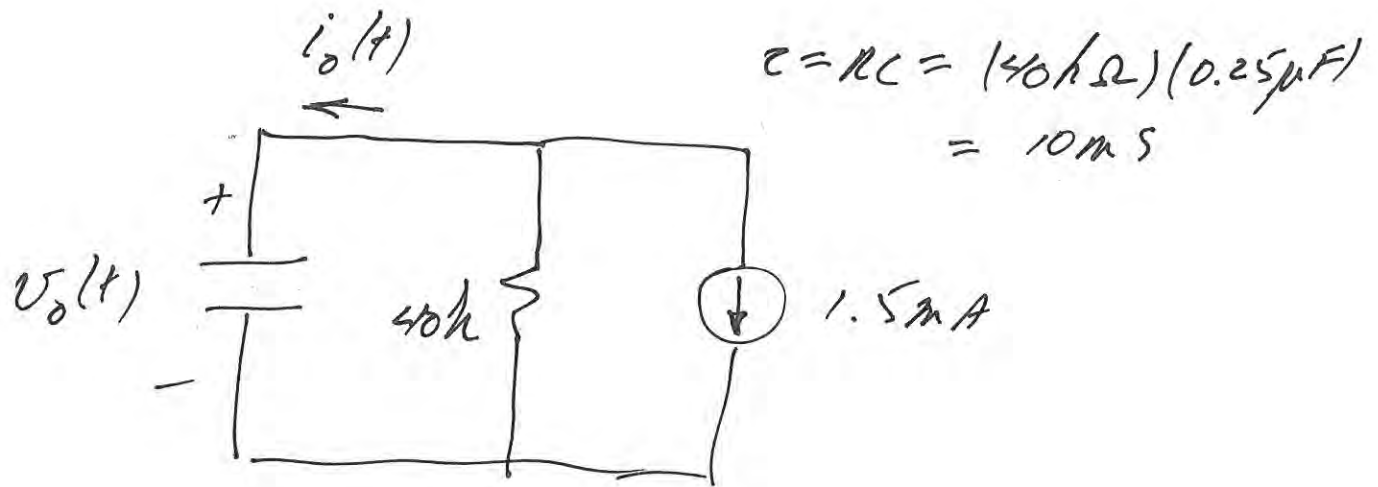
$$\Rightarrow I_N = \frac{-60V}{40k\Omega} = -1.5mA$$



$$v_o(\infty) = -1.5mA(40k\Omega) = -60V$$

$$v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau}$$

$$= -60 + [30 + 60]e^{-100t}$$

$$v_o(t) = -60 + 90e^{-100t}; t \geq 0$$


$$\begin{aligned}
 i_o(t) &= C \frac{d}{dt} v_o(t) \\
 &= 0.25 \mu\text{F} \frac{d}{dt} [-60 + 90 e^{-100t}] \\
 &= (0.25 \mu\text{F}) (-9,000 e^{-100t} \text{ V/s}) \\
 i_o(t) &= -2.25 e^{-100t} \text{ mA}
 \end{aligned}$$

? RANGE OF VALIDITY ON t






ANS: $t \geq 0^+$



WHY?

ANS:

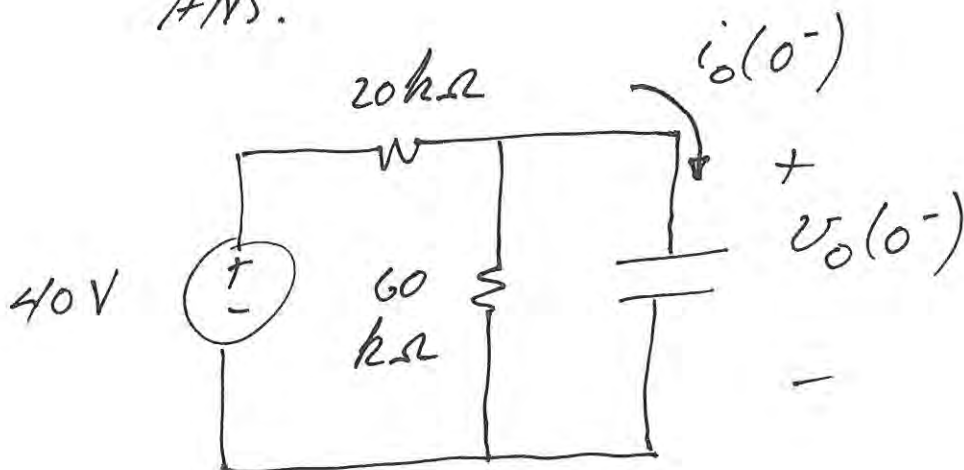

ALTERNATE

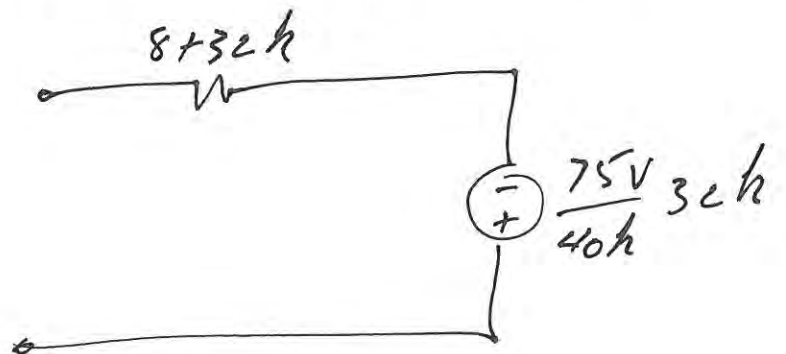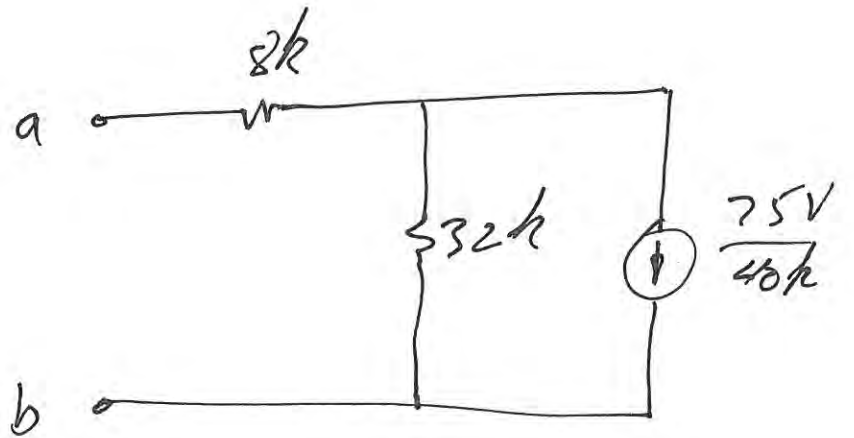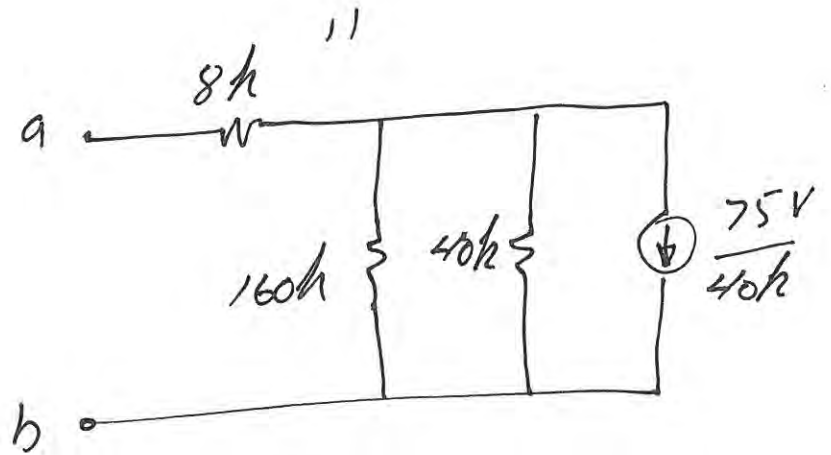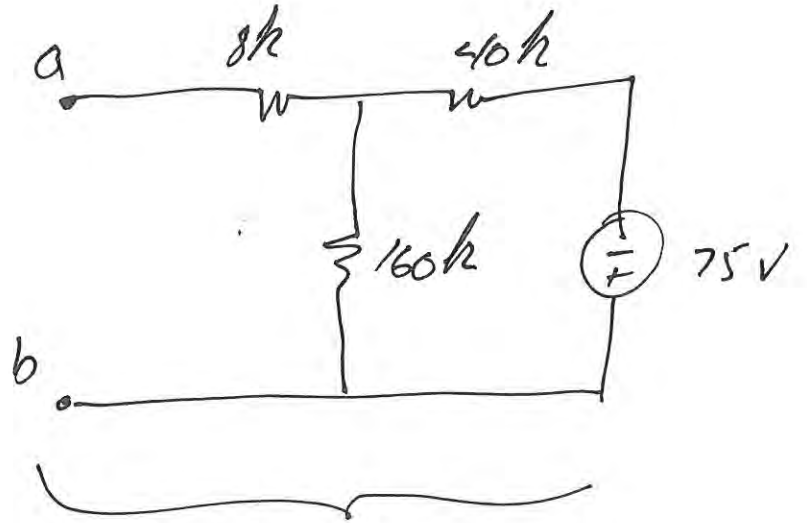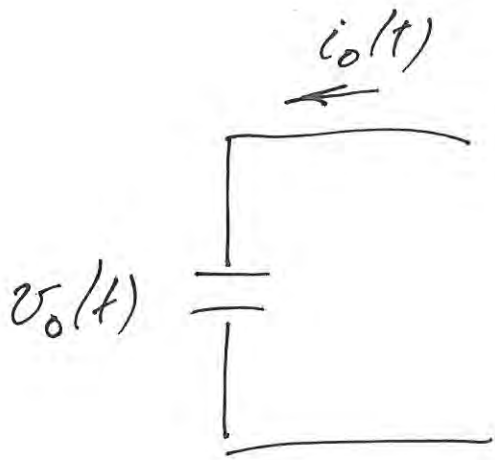

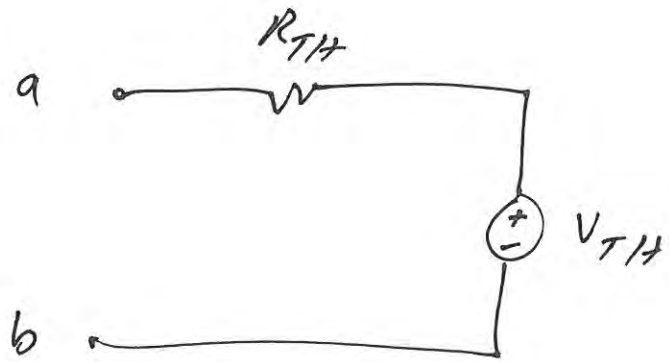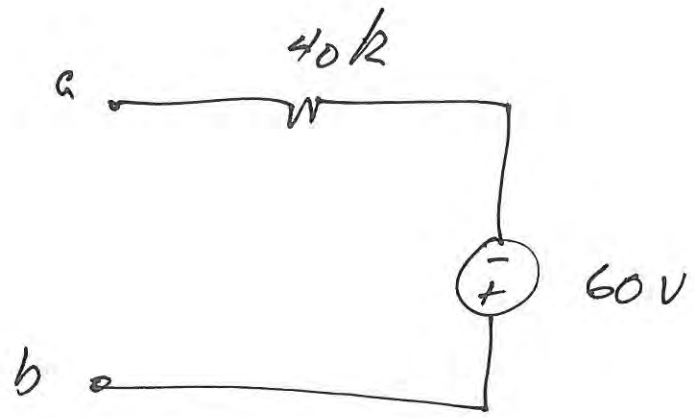

ALL DE'S OF FORM

$$\frac{dx}{dt} + \frac{x}{\tau} = K$$

FINAL VALUE OF x MUST BE CONSTANT

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t \rightarrow \infty} = 0 \Rightarrow K = \frac{x_f}{\tau}$$

$$\frac{dx}{dt} + \frac{x}{\tau} = \frac{x_f}{\tau}$$

$$\frac{dx}{dt} = -\frac{(x-x_f)}{\tau}$$

INTEGRATE: $\frac{dx}{(x-x_f)} = -\frac{dt}{\tau}$

$$\ln(x-x_f) \Big|_{t_0}^t = -\frac{(t-t_0)}{\tau}$$

$$\ln \left[\frac{x(t) - x_f}{x(t_0) - x_f} \right] = - \frac{(t - t_0)}{\tau}$$

⋮

$$x(t) = x_f + [x(t_0) - x_f] e^{-(t - t_0)/\tau}$$



↖
FINAL
VALUE

↖
VALUE AT
SWITCHING
TIME,
 $t = t_0$

APPLICATION

- 1) ID VARIABLE OF INTEREST
 - RC CKT : CAPACITOR VOLTAGE
 - RL CKT : INDUCTOR CURRENT
- } WHY?
- 2) CALC VALUE OF VARIABLE AT $t = t_0$
WORRY ABOUT t_0^- OR t_0^+ ?
 - 3) DETERMINE VALUE AS $t \rightarrow \infty$
 - 4) CALCULATE TIME CONSTANT, τ


EXAMPLE 7.7

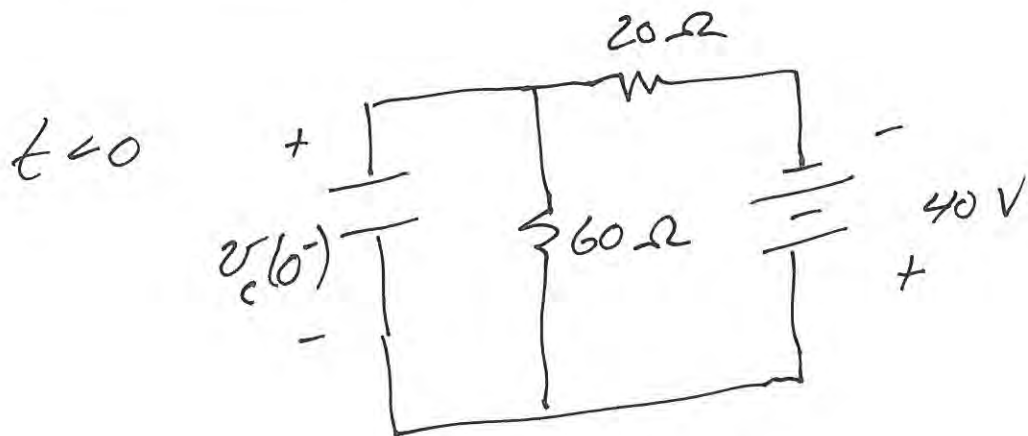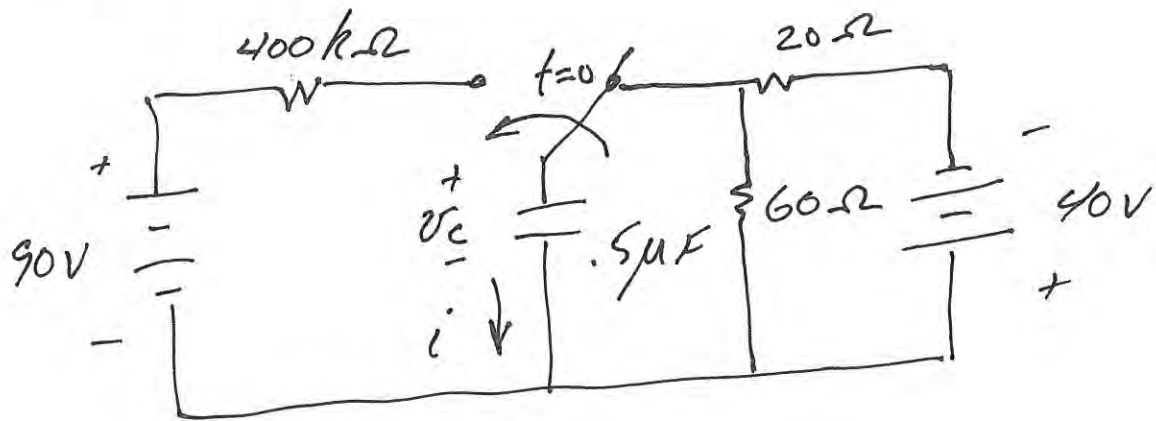

VOLTAGE DIV FOR $v_c(0^-)$:

$$v_c(0^-) = -40 \left(\frac{60}{60+20} \right)$$
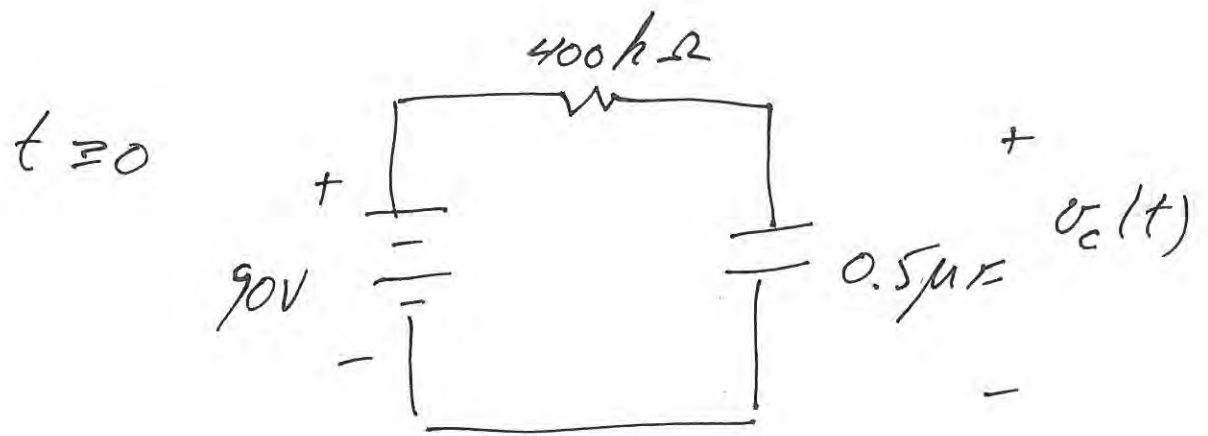
$$a) \boxed{v_c(0^-) = -30\text{V} = v_c(0^+)}$$



b) $v_c(\infty) = 90 \text{ V}$

$$\tau = RC = (400 \text{ k}\Omega)(0.5 \mu\text{F})$$

c) $\tau = 0.25 \text{ s}$

$$v_c(t) = v_f + (v(0^+) - v_f) e^{-t/\tau}$$

$$= 90 + (-30 - 90) e^{-5t} \text{ V}$$

d) $v_c(t) = 90 - 120 e^{-5t} \text{ V}; t \geq 0$

$$i = C \frac{dv_c(t)}{dt} = 0.5 \mu\text{F} \frac{d}{dt} (90 - 120e^{-5t} \text{ V})$$

$$= (0.5 \mu\text{F})(600 \text{ V/s}) e^{-5t}$$

e) $i(t) = 0.3 e^{-5t} \text{ mA}; t \geq 0^+$

WHY $t \geq 0^+$?

ANS $i(0) = 0.3 \text{ mA}$, BUT

$$i(0^-) = 0$$



? TIME AT WHICH $v_c(t) = 0$

$$v_c(t_0) = 90 - 120e^{-5t_0} = 0$$



$$\frac{90}{120} = e^{-5t_0} \rightarrow t_0 = \frac{\ln(90/120)}{-5}$$

f) $t_0 = 57.5 \text{ ms}$

9)

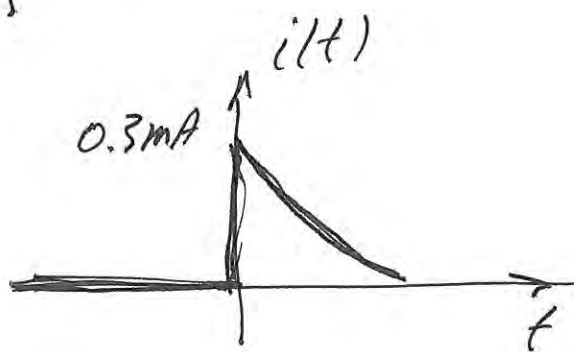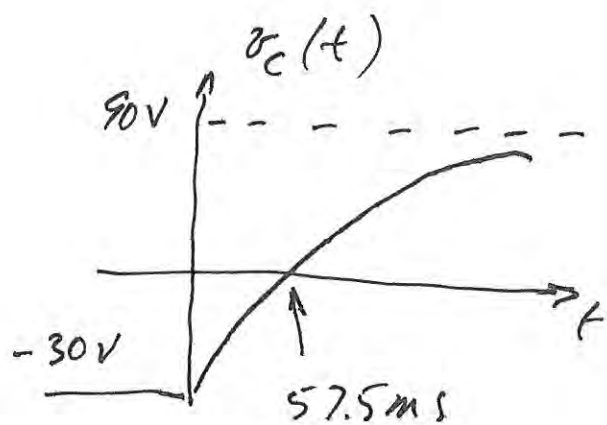


EXAMPLE 7.8

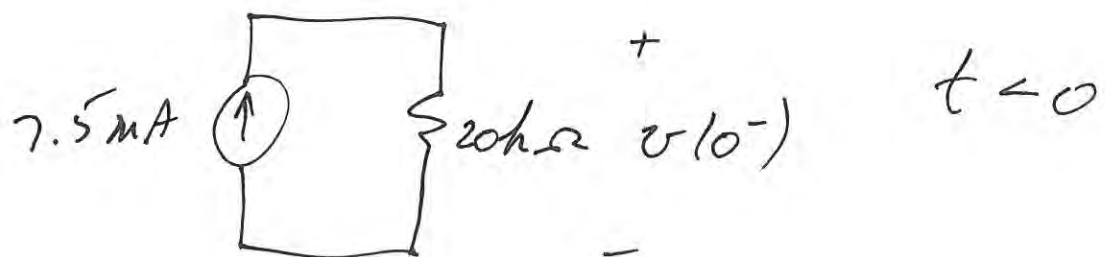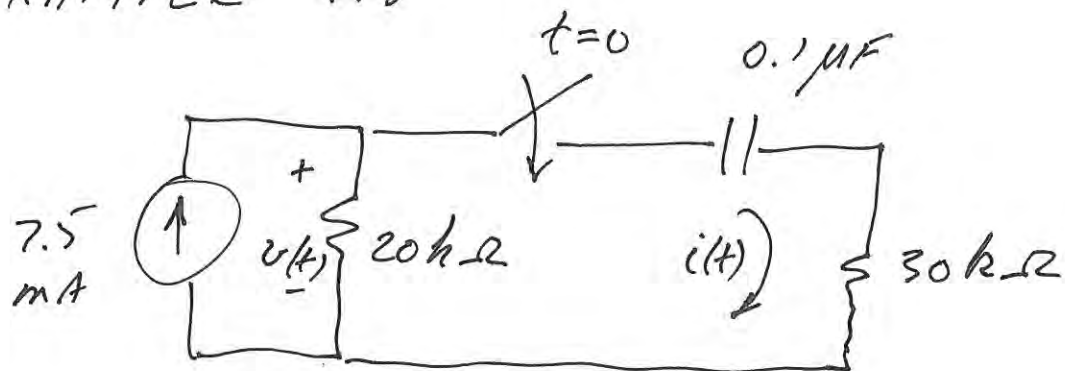


$$v(0^-) = (7.5 \text{ mA})(20 \text{ k}\Omega)$$

$$v(0^-) = 150 \text{ V}$$

$$i(0^-) = 0$$

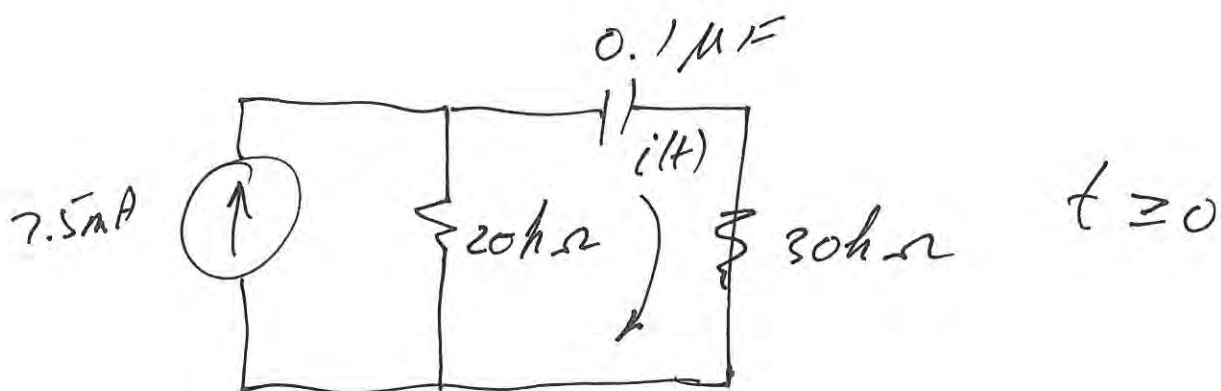

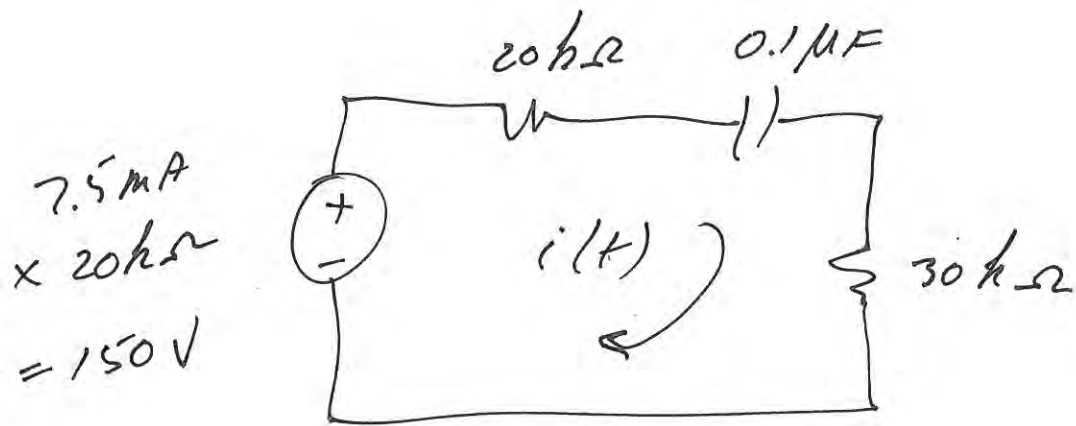

$$\tau = RC = (50 \text{ k}\Omega)(0.1 \mu\text{F})$$

$$\tau = 5 \times 10^{-3} \text{ s}$$

RECALL $i(0^-) = 0$

$$i(0^+) = \frac{150 \text{ V}}{50 \text{ k}\Omega} = 3 \text{ mA}$$


$$i(0^+) = 3 \text{ mA}$$

$$i(\infty) = 0$$

$$i(t) = i_f + [i(0^+) - i_f] e^{-200t}$$

$$i(t) = 3e^{-200t} \text{ mA}; t \geq 0^+$$

WHY $t \geq 0^+$?

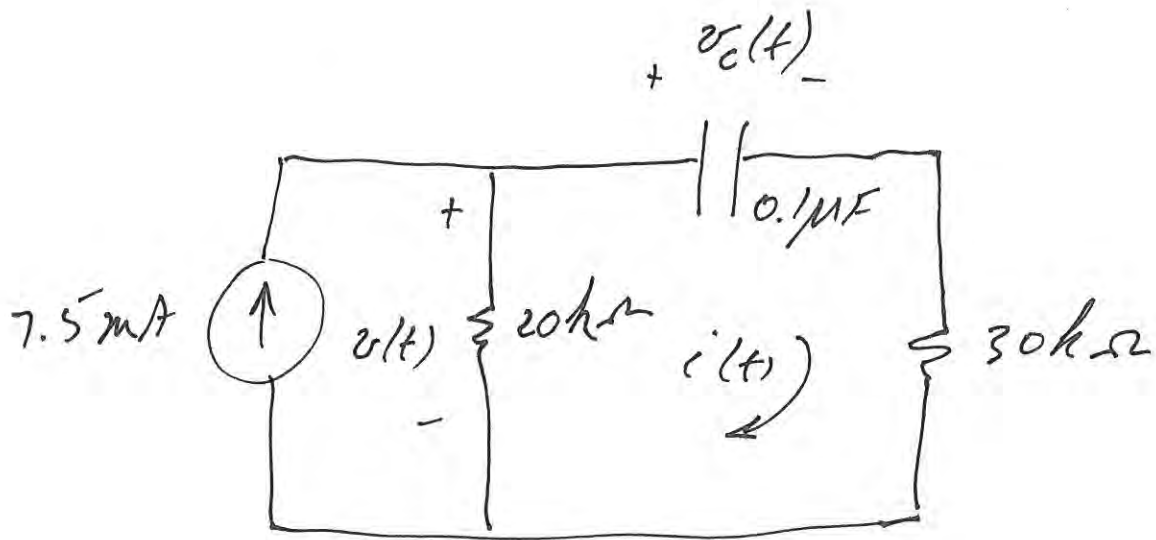

$$v_c(0^-) = 0 = v_c(0^+)$$

$$v(t) = v_c(t) + i(t) 30 \text{ k}\Omega$$

$$i(t) \Big|_{t \rightarrow \infty} = 0 \Rightarrow v_c(\infty) = (7.5 \text{ mA}) \times (20 \text{ k}\Omega) = 150 \text{ V}$$

$$v_c(t) = v_f + [v_c(0^+) - v_f] e^{-t/\tau}$$

$$v_c(t) = 150 + (0 - 150) e^{-200t} \text{ V}$$

$$v_c(t) = 150(1 - e^{-200t}) \text{ V}; \quad t \geq 0$$

WHY $t \geq 0$?

$$v(t) = v_c(t) + i(t) 30k\Omega$$

$$= 150(1 - e^{-200t}) + (30k\Omega)(3mA e^{-200t})$$


$$= 150 - 150e^{-200t} + 90e^{-200t} \text{ V}$$

$$v(t) = 150 - 60e^{-200t} \text{ V}; t \geq 0^+$$


WHY $t \geq 0^+$?

$$\begin{aligned} \text{ANS: SOLN GIVES } v(0) &= 150 - 60 \\ &= 90 \text{ V} \end{aligned}$$

BUT RECALL $v(0^-) = 150 \text{ V}$

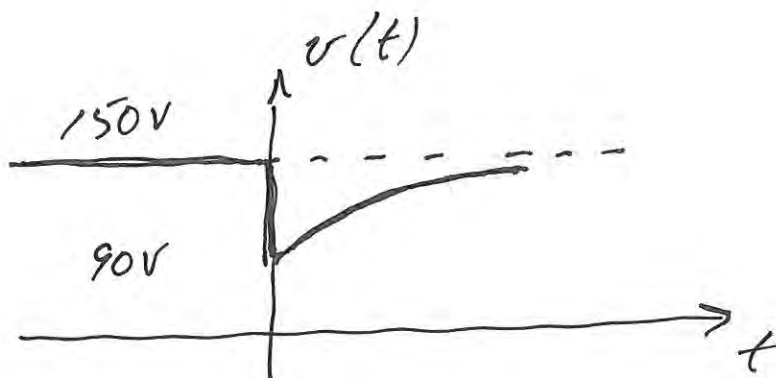

EXAMPLE 7.9

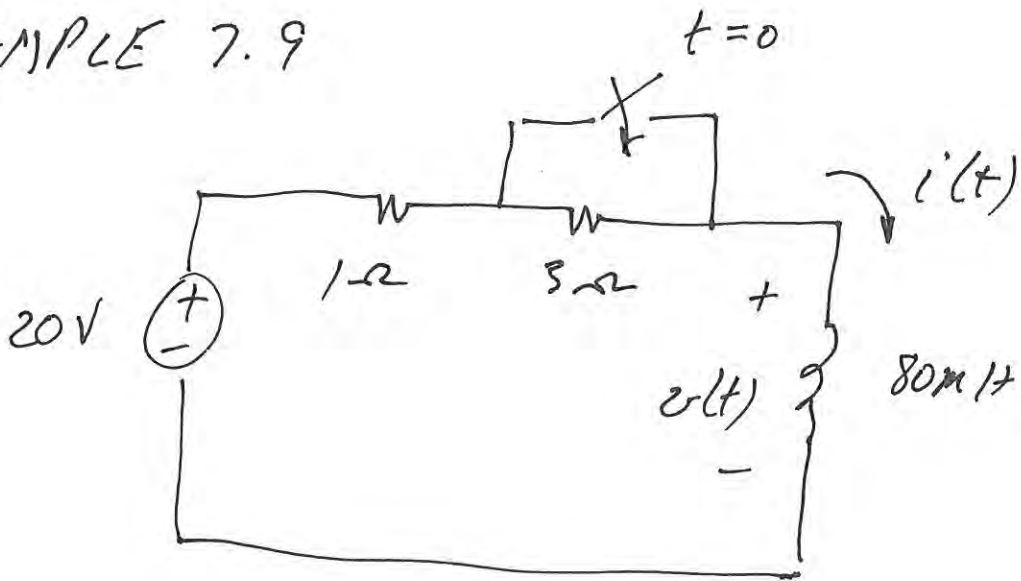


WANT: $v(t); t \geq 0^+$
 $i(t); t \geq 0$

$$v(0^-) = 0$$

$$i(0^-) = \frac{20V}{4\Omega} = 5A$$

$t \geq 0$

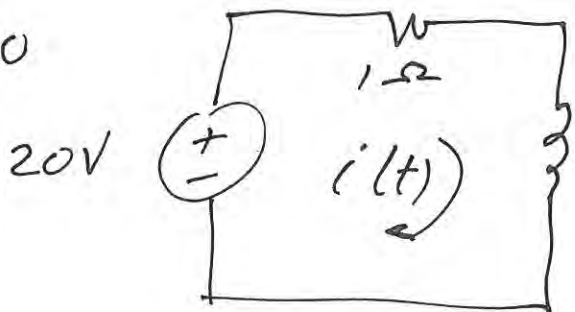

$$i(\infty) = \frac{20V}{1\Omega} = 20A$$

$$\tau = L/R = \frac{80mH}{1\Omega}$$


$$\tau = 80ms$$

$$1/\tau = 12.5 s^{-1}$$

$$i(t) = i_f + [i(0^+) - i_f] e^{-t/\tau}$$

$$= 20 + (5 - 20) e^{-12.5t} \text{ A}$$
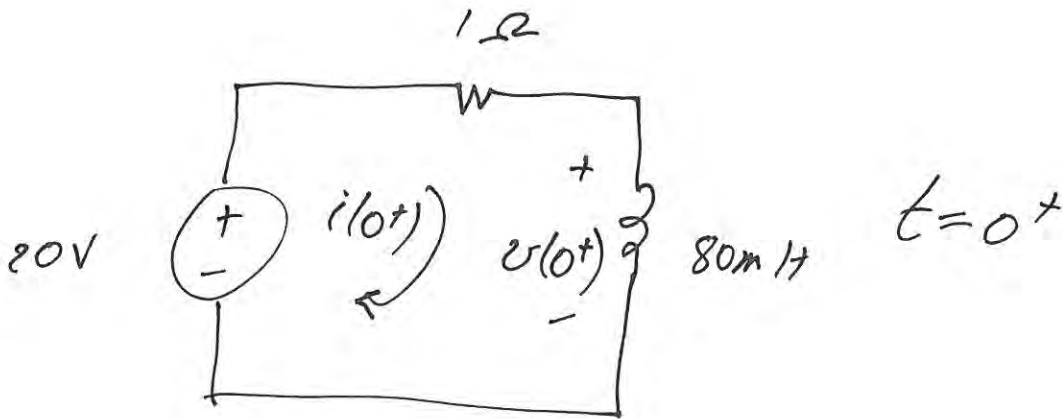
$$i(t) = 20 - 15 e^{-12.5t} \text{ A}; t \geq 0$$



$$\text{LOOP EQ: } 20 \text{ V} - i(0^+)(1 \Omega) - v(0^+) = 0$$

$$20 - 5 \text{ A}(1 \Omega) = v(0^+) = 15 \text{ V}$$


$$v(\infty) = 0$$


$$v(t) = v_f + [v(0^+) - v_f] e^{-t/\tau}$$

$$v(t) = 15 e^{-12.5t} \text{ V}; t \geq 0^+$$


WHY $t \geq 0^+$?

Example 7.9

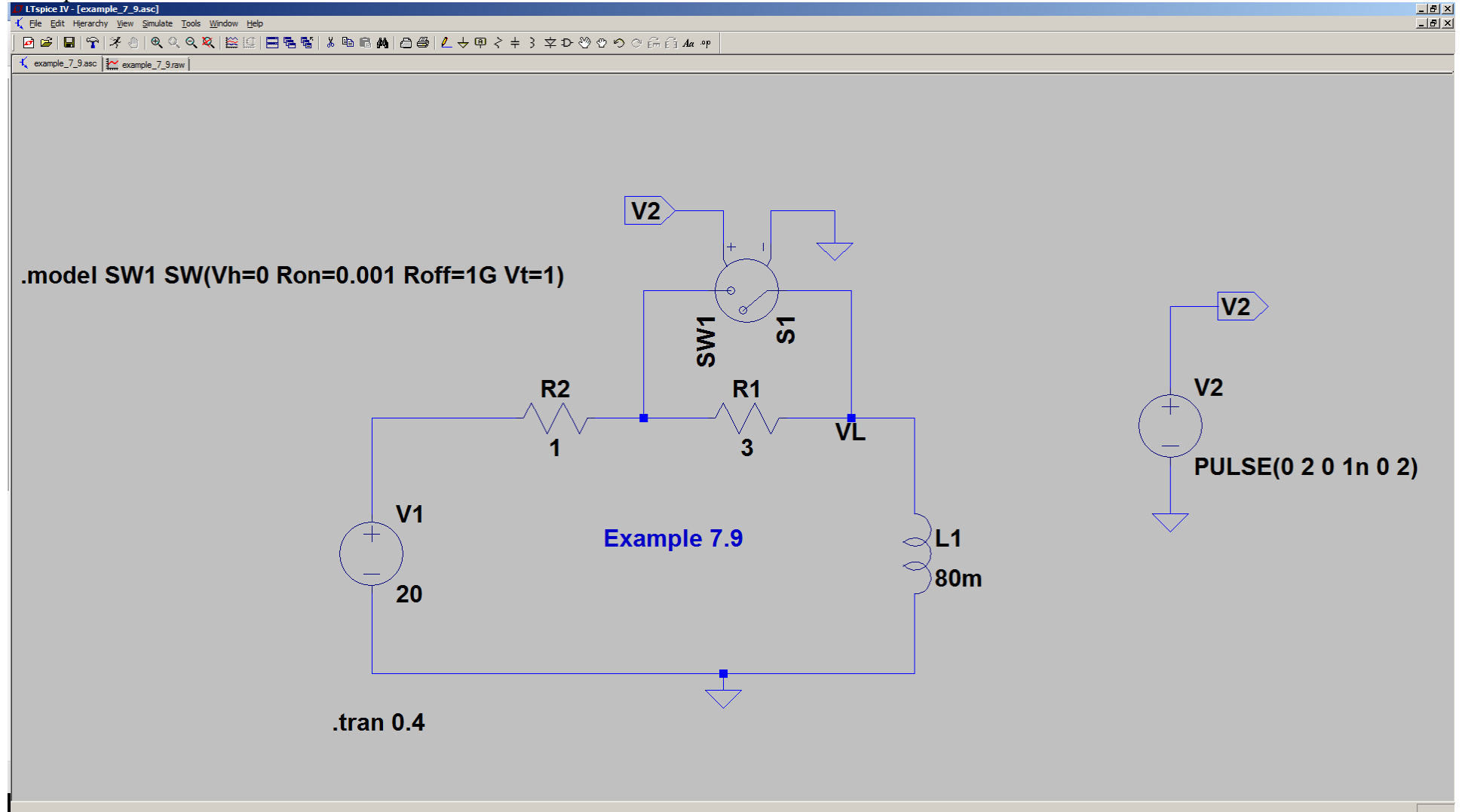


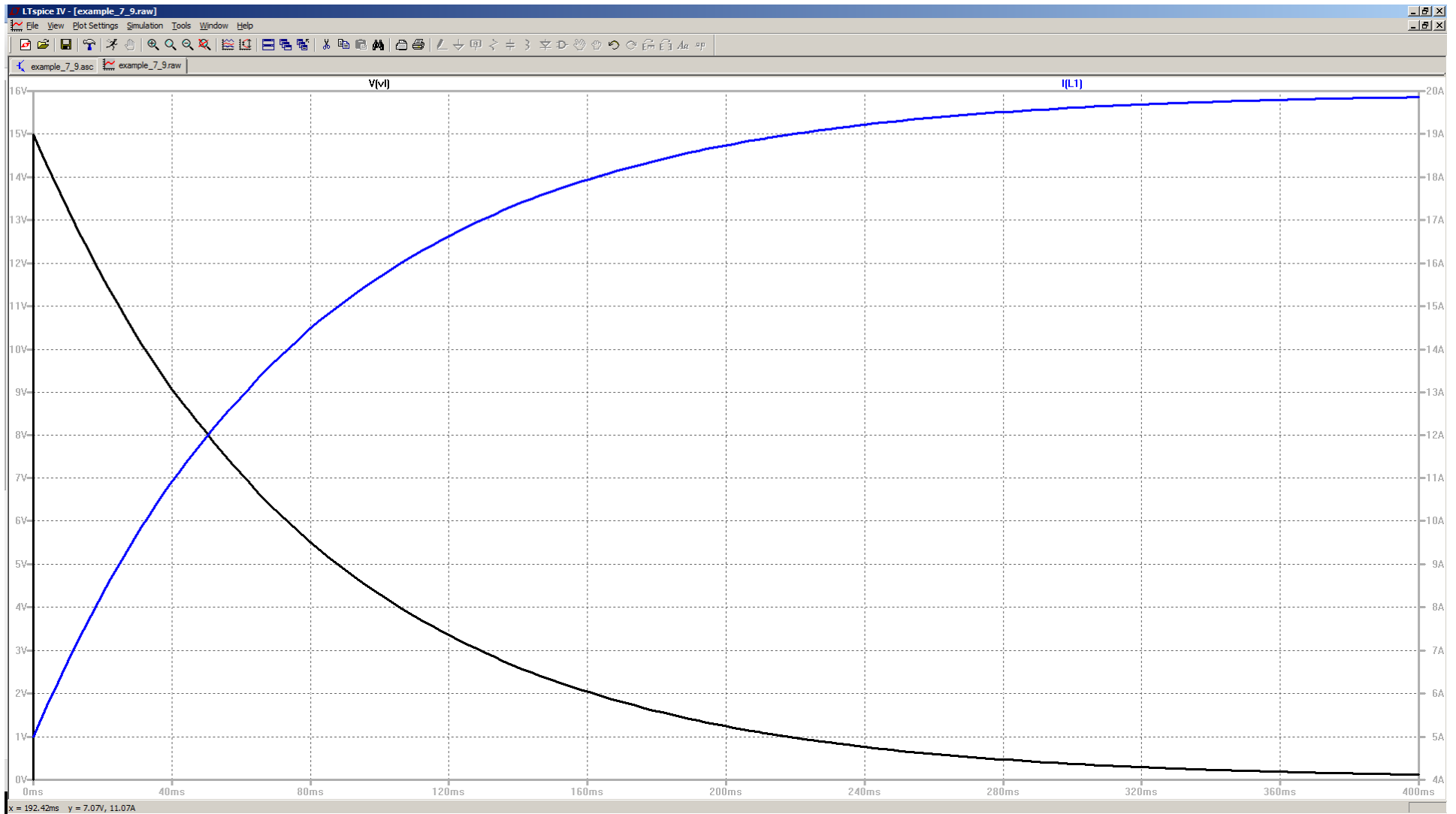

EXAMPLE 7.10

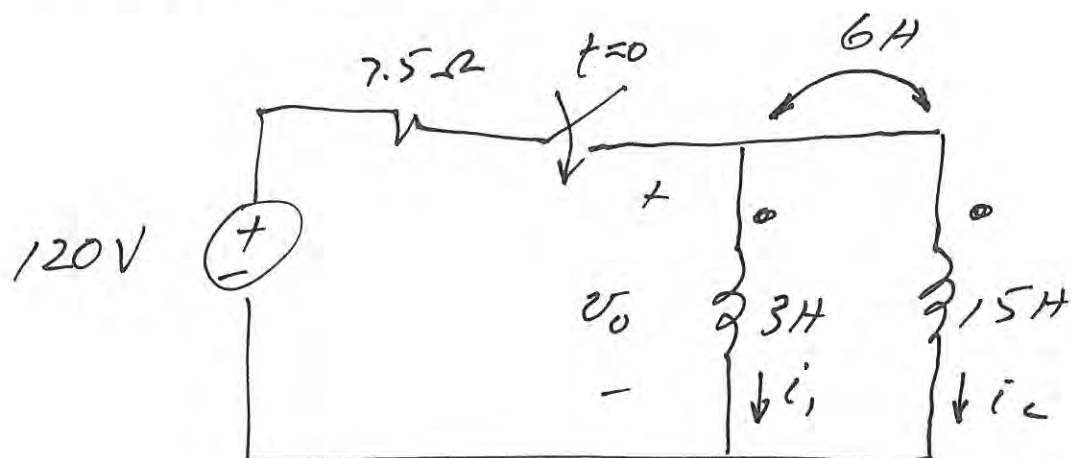

NO INITIAL STORED ENERGY

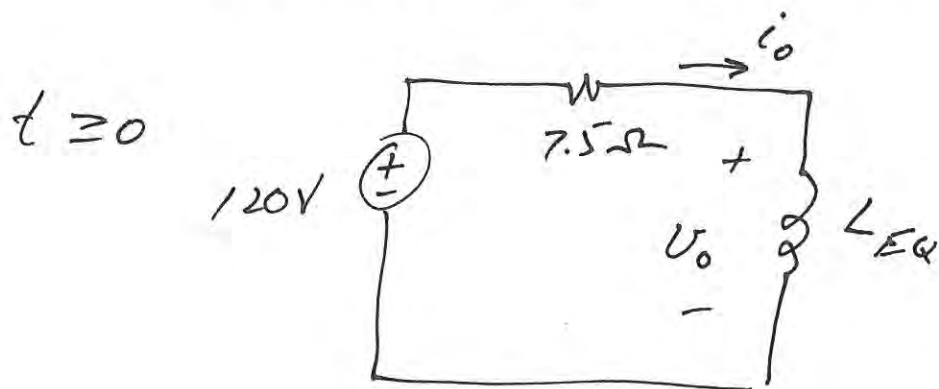

$$L_{EQ} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = 1.5H$$

$$\tau = \frac{L}{R} = \frac{1.5H}{7.5\Omega} = 0.25$$

$$i_o(0^-) = 0 = i_o(0^+)$$

$$i_o(\infty) = \frac{120V}{7.5\Omega} = 16A$$

$$i_o(t) = i_f + [i_o(0^+) - i_f] e^{-t/\tau}$$

$$i_o(t) = 16(1 - e^{-5t}) \text{ A}; t \geq 0$$

$$v_o(t) = L \frac{di_o(t)}{dt}$$

$$= 1.5 \text{ H} \frac{d}{dt} [16(1 - e^{-5t}) \text{ A}]$$

$$= (1.5 \text{ H})(-16 \text{ A})(-5/\text{s}) e^{-5t}$$


$$v_o(t) = 120 e^{-5t}; t \geq 0^+$$

WHY $t \geq 0^+$?

FROM SOL'N, $v_o(0) = 120 \text{ V}$

BUT $v_o(0^-) = 0 \text{ V}$

(DISCONTINUOUS AT $t=0$)

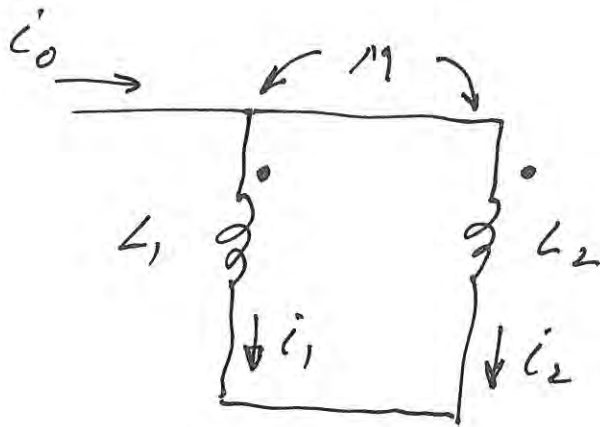

$$L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\frac{di_1}{dt} (L_1 - M) = \frac{di_2}{dt} (L_2 - M)$$

$$\frac{di_1}{dt} = -3 \frac{di_2}{dt} \quad \textcircled{A}$$

$$i_0 = i_1 + i_2 \quad \textcircled{B}$$

$$\textcircled{A} \stackrel{!}{\approx} \textcircled{B} \Rightarrow \frac{di_2}{dt} = -\frac{1}{2} \frac{di_0}{dt}$$

$$\frac{di_2}{dt} = -\frac{1}{2} \frac{d}{dt} [16(1 - e^{-5t}) A]$$

$$\frac{di_2}{dt} = -40 e^{-5t} A/s$$

$$di_2 = -40e^{-5t} dt$$

$$\int_0^t di_2 = \int_0^t (-40e^{-5x} dx)$$

$$i_2(t) - i_2(0) = \frac{-40}{-5} e^{-5x} \Big|_0^t = 8(e^{-5t} - 1)$$

$$i_2(t) = 8(e^{-5t} - 1) + \underbrace{i_2(0)}_0$$

$$\boxed{i_2(t) = 8(e^{-5t} - 1) A; t \geq 0}$$

FROM $i_0(t) = i_1(t) + i_2(t)$

$$\boxed{i_1(t) = 24(1 - e^{-5t}) A; t \geq 0}$$


RECAP

$$i_0(t) = 16(1 - e^{-5t}) \text{ A}; t \geq 0$$

$$i_1(t) = 24(1 - e^{-5t}) \text{ A}; t \geq 0$$

$$i_2(t) = -8(1 - e^{-5t}) \text{ A}; t \geq 0$$

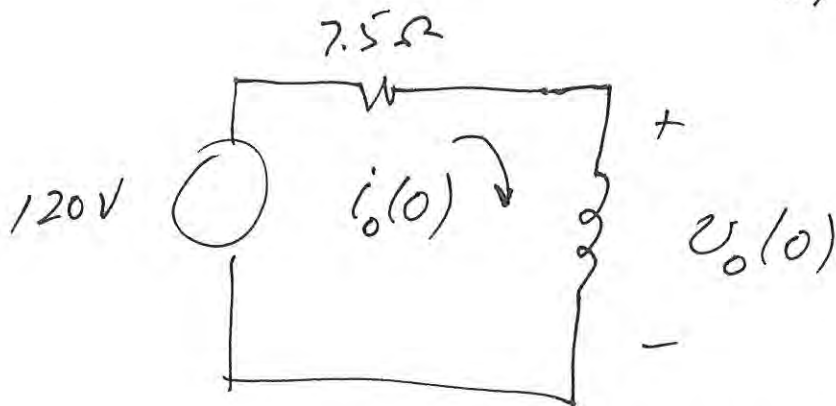$i_0(0) = i_1(0) = i_2(0)$ CONSISTENT WITH
NO STORED INITIAL
ENERGY



SOLUTION FOR $v(t)$ GIVES $v(0) = 120 \text{ V}$
(CONSISTENT WITH $i_0(0) = 0$)

IS v_0 CONSISTENT WITH i_1, i_2 ?

$$v_0(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$= 3H \frac{d}{dt} [24(1 - e^{-5t})A]$$


$$+ 6H \frac{d}{dt} [-8(1 - e^{-5t})A]$$

$$\vdots$$
$$= 120 e^{-5t} V; t \geq 0^+ \quad \underline{\underline{OK}}$$

WHAT ABOUT FINAL VALUES OF i_1, i_2 ?

$$i_1(\infty) = 24A$$

$$i_2(\infty) = -8A$$

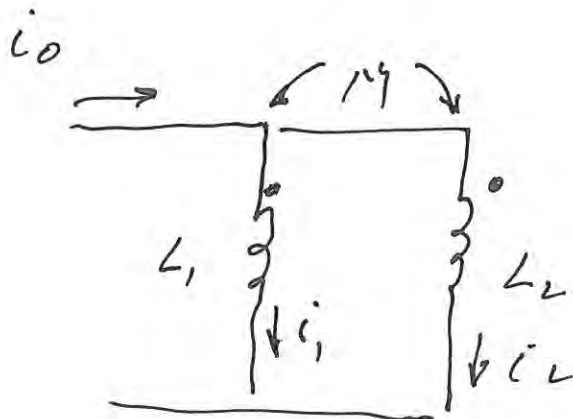

PROBLEM

PROBLEM: AS $t \rightarrow \infty$ BOTH INDUCTORS
BECOME IDEAL SHORT CIRCUITS.

\Rightarrow IT'S IMPOSSIBLE TO ESTABLISH
FINAL VALUES USING CURRENT DIV.

\rightarrow WE MUST CONSIDER FLUX LINKAGES

FLUX LINKING 3H COIL (λ_1) MUST EQUAL
FLUX LINKING 15H COIL (λ_2) BECAUSE


$$v_0 = \frac{d\lambda_1}{dt} = \frac{d\lambda_2}{dt} \quad \text{WHY?}$$

$$\text{NOW } \lambda_1 = L_1 i_1 + M i_2 = 3i_1 + 6i_2 \text{ WB-TURNS}$$

$$\lambda_2 = L_2 i_2 + M i_1 = 15i_2 + 6i_1 \text{ WB-TURNS}$$

$$L \text{ \& M IN HENRYS, } H = \frac{\text{WB}}{\text{A}} = \frac{\text{V}\cdot\text{S}}{\text{A}}$$

FARADAY'S LAW

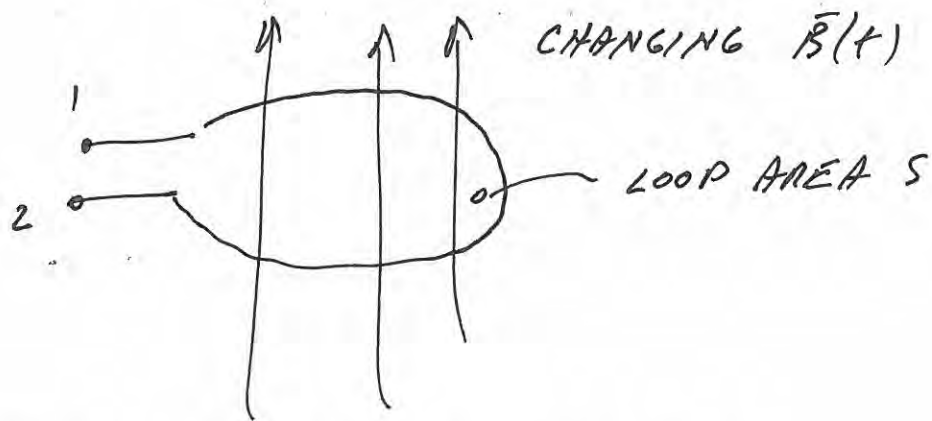

$\vec{B}(t)$ = MAGNETIC FLUX DENSITY

$$[\vec{B}(t)] = \frac{\text{Wb}}{\text{m}^2} = \text{TESLA}$$

$$\text{Wb} = \text{V} \cdot \text{S}$$

INDUCED VOLTAGE

$$V_{12} = -N \int_S \frac{\partial \vec{B}(t)}{\partial t} \cdot d\vec{S}$$

$$= (\# \text{ TURNS}) \times (\text{MAG FLUX TIME RATE}) \times \text{AREA OF CHANGE}$$

$$V = \frac{d\lambda}{dt}$$

$$\lambda = N B(t) S$$

FLUX
LINKAGE

$$[\lambda] = \text{V} \cdot \text{S}$$

USE SOL'NS FOR $i_1(t)$ & $i_2(t)$:

$$\lambda_1 = 24(1 - e^{-5t}) \text{ Wb-TURNS}$$

$$\lambda_2 = 24(1 - e^{-5t}) \text{ Wb-TURNS}$$


$$\Rightarrow \lambda_1(\infty) = \lambda_2(\infty) = 24 \text{ Wb-TURNS}$$

FINAL VALUE OF FLUX LINKING

EITHER COIL IS SAME

$$\Rightarrow i_1(\infty) \text{ \& \; } i_2(\infty) \text{ ARE CONSISTENT}$$

MAGNETICALLY COUPLED INDUCTORS

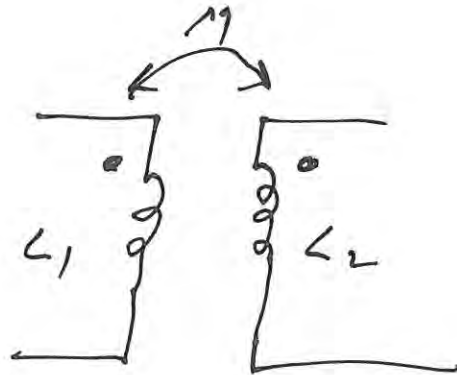

M = MUTUAL INDUCTANCE

$$M = k \sqrt{L_1 L_2}$$

↑
COUPLING COEFFICIENT

TO COUPLE INDUCTORS IN LTSPICE
USE A "K" DIRECTIVE

SYNTAX: $K \ L1 \ L2 \ k$ $|k| \leq 1$

Example 7.10



K1 L1 L2 0.89443

R1 7.5

R2 .01

V1 120


V0

L1 3


L2 15


.ic I(L1)=0
.ic I(L2)=0

.tran 1

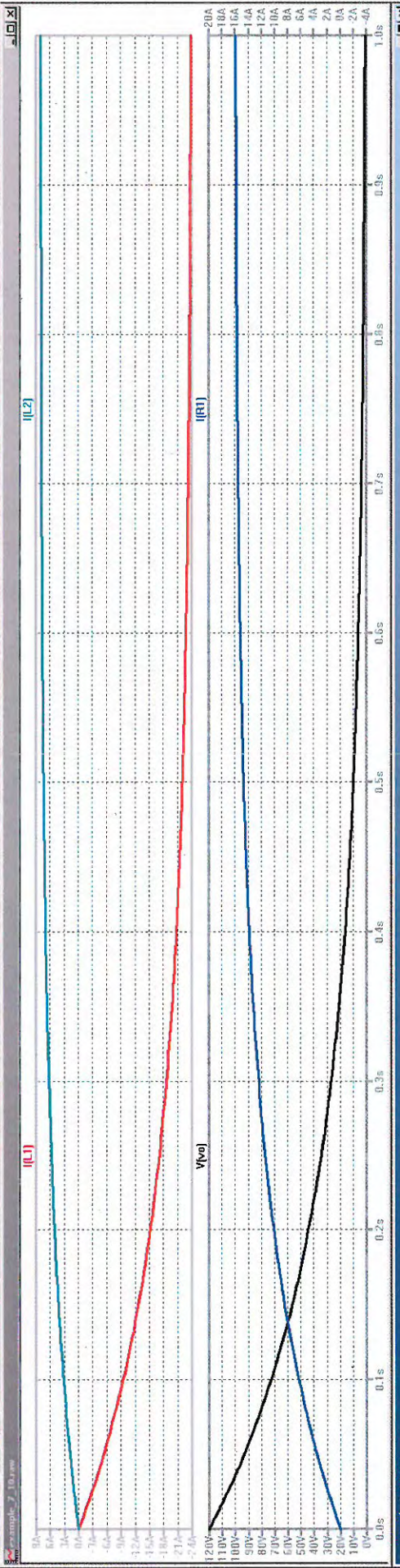

example_7_10.asc

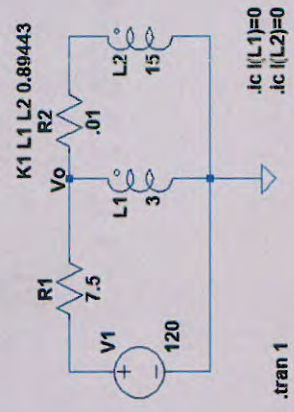

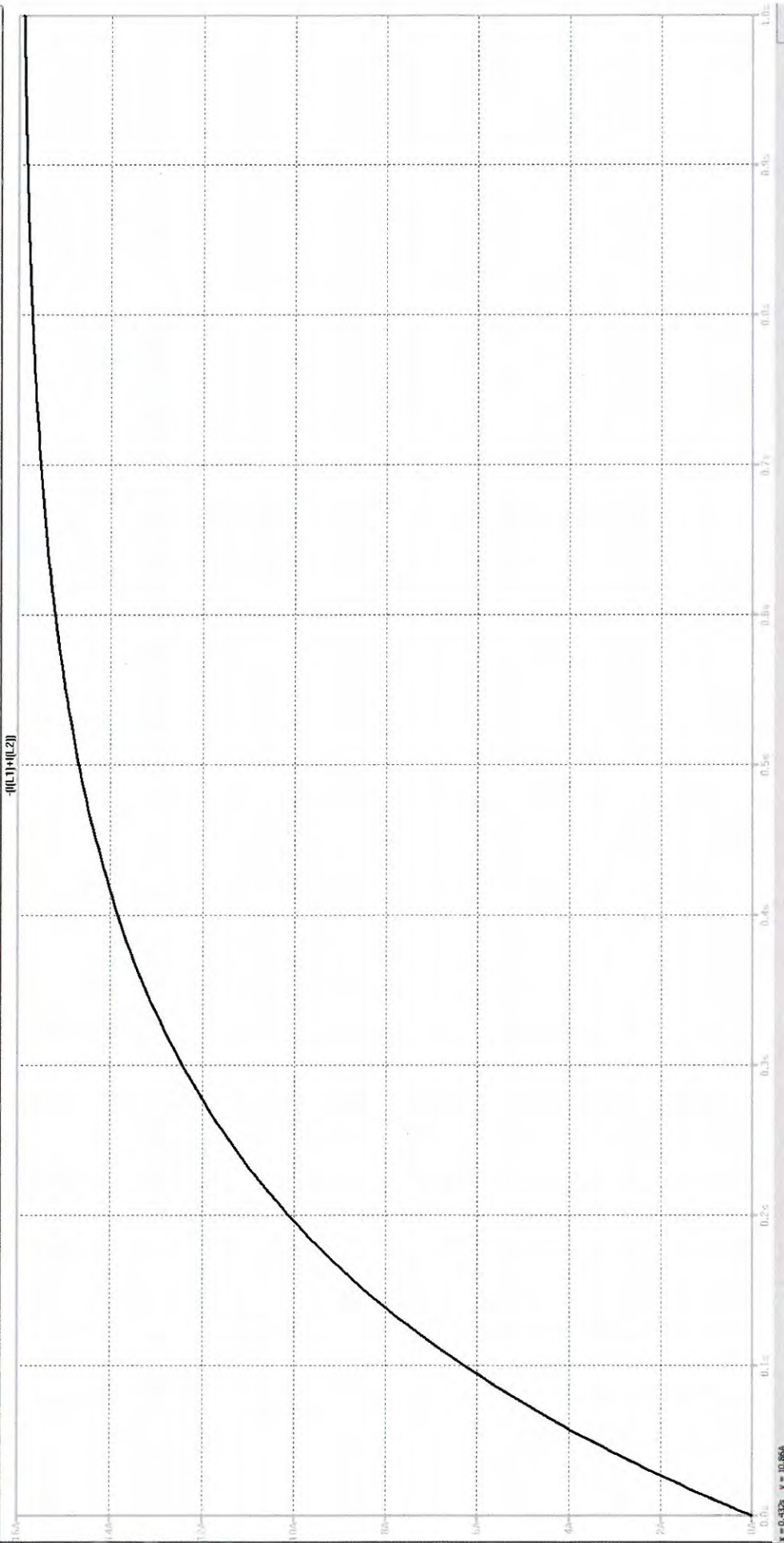

Example 7.11

Analyzing an RL Circuit that has Sequential Switching

The two switches in the circuit shown in Fig. 7.31 have been closed for a long time. At $t = 0$, switch 1 is opened. Then, 35 ms later, switch 2 is opened.

- Find $i_L(t)$ for $0 \leq t \leq 35$ ms.
- Find i_L for $t \geq 35$ ms.
- What percentage of the initial energy stored in the 150 mH inductor is dissipated in the 18 Ω resistor?
- Repeat (c) for the 3 Ω resistor.
- Repeat (c) for the 6 Ω resistor.

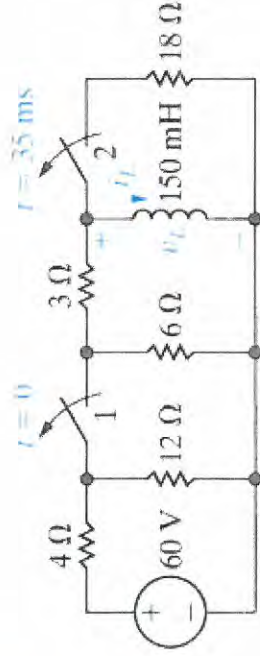


Figure 7.31 The circuit for Example 7.11.

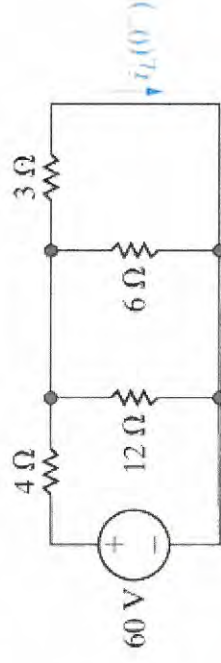


Figure 7.32 The circuit shown in Fig. 7.31, for $t < 0$.

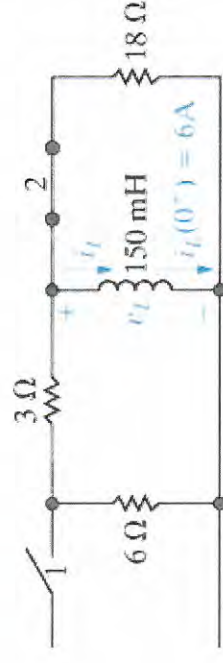






Figure 7.33 The circuit shown in Fig. 7.31, for $0 \leq t \leq 35$ ms.

- When $t = 35$ ms, the value of the inductor current is


$$i_L = 6e^{-1.4} = 1.48 \text{ A.}$$

Thus, when switch 2 is opened, the circuit reduces to the one shown in Fig. 7.34, and the

Ex 7.11 P6 237

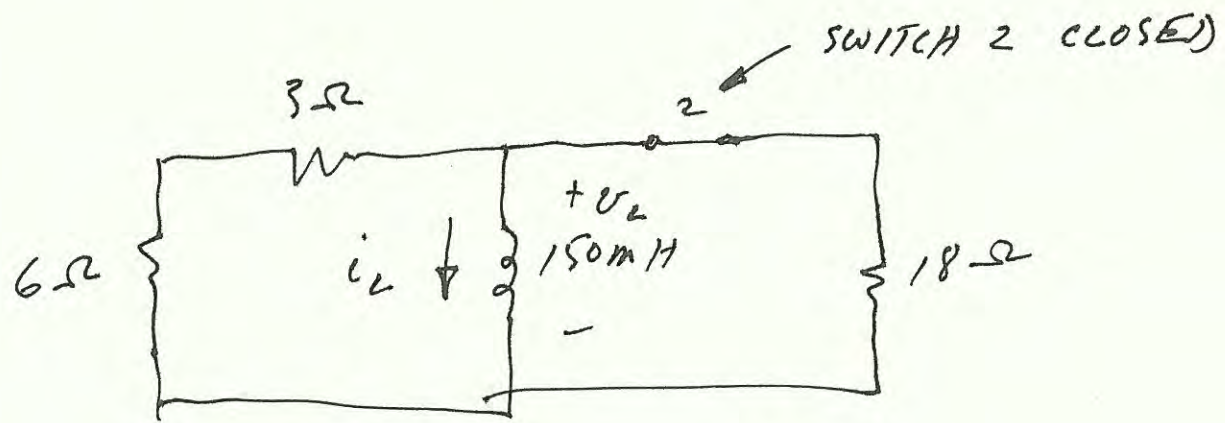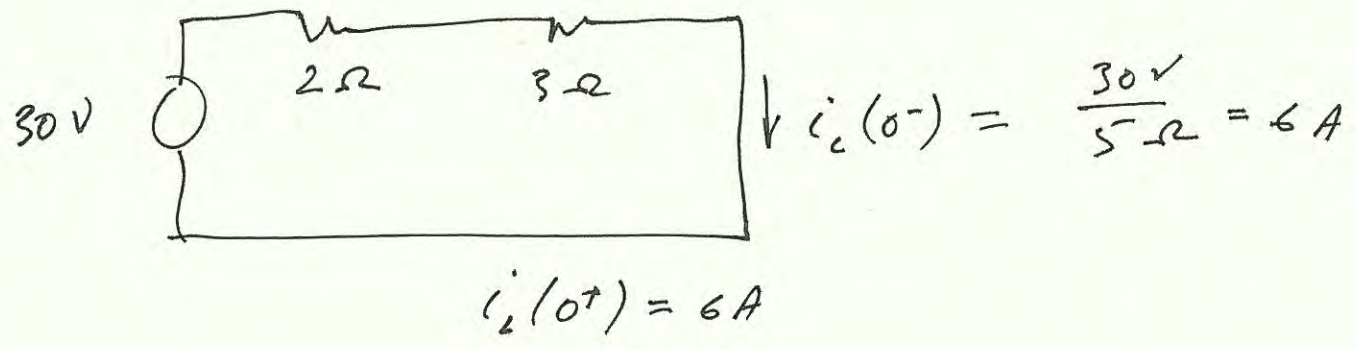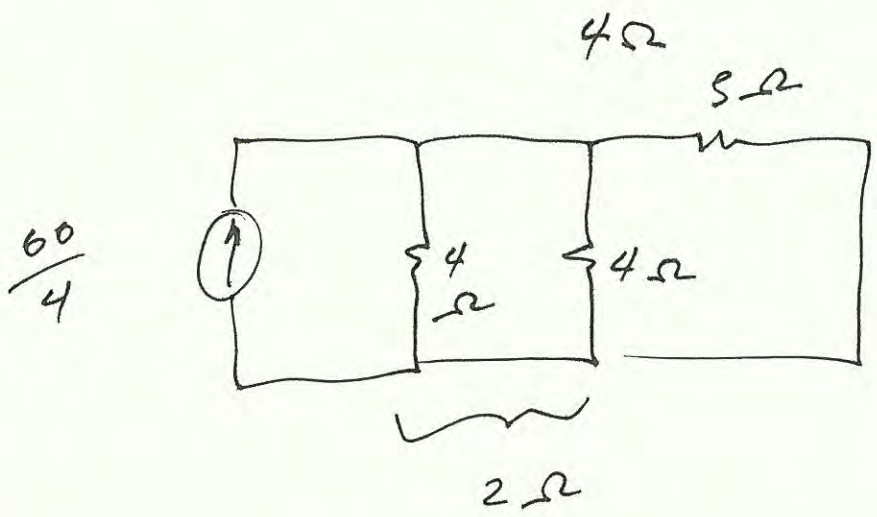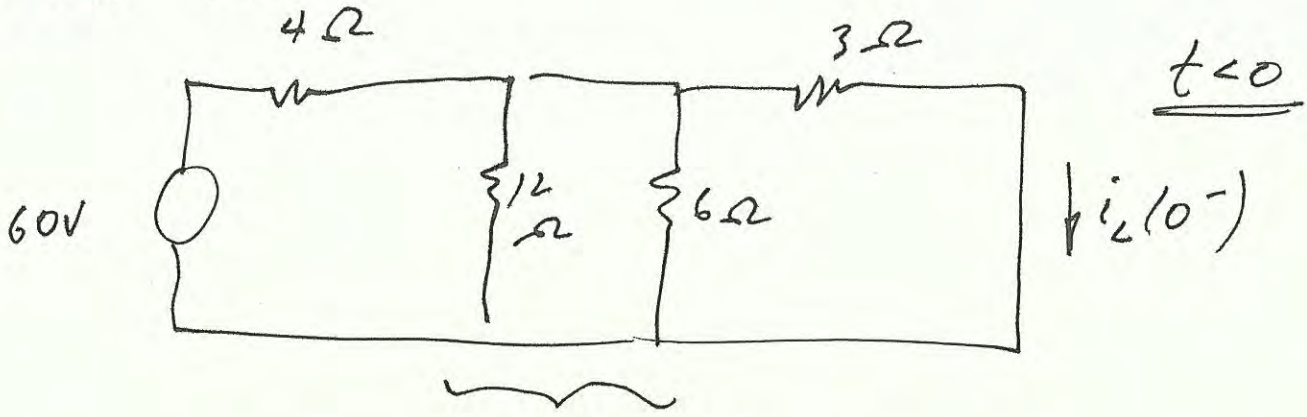

CIRCUIT FOR $0 \leq t \leq 35ms$

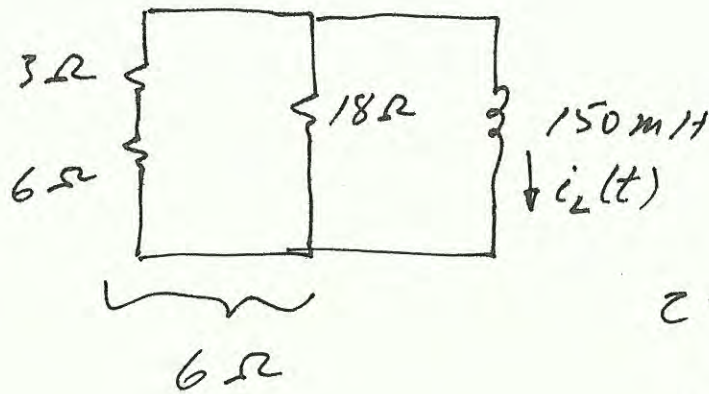


$$\tau = \frac{L}{R} = \frac{150 \text{ mH}}{6 \Omega} = 25 \text{ ms}$$

$$\frac{1}{\tau} = 40 \text{ s}^{-1}$$

$$i_L(t) = 6 e^{-40t} \text{ A}; \quad 0 \leq t \leq 35 \text{ ms} \quad *$$

(t EXPRESSED IN S)

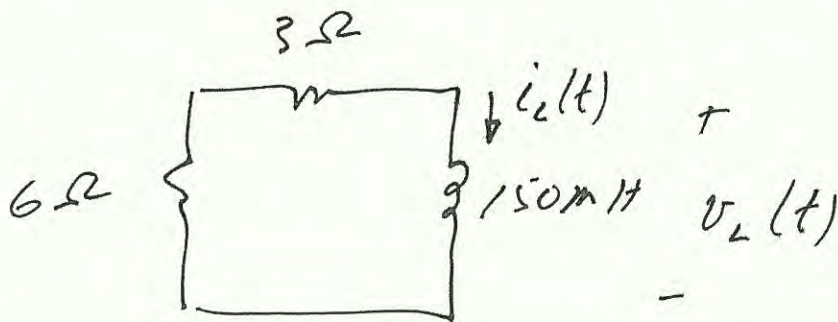AT $t = 35 \text{ ms} \equiv t_{sw}$ CKT BECOMES



WHAT IS $i_L(t) \Big|_{t=t_{sw}^-}$?

FROM * $i_L(t_{sw}^-) = i_L(t_{sw}^+) = 6 e^{-40t} \Big|_{t=35 \text{ ms}}$

$$i_L(t_{sw}^+) = 1.48 \text{ A}$$

NOW WE HAVE A NEW TIME CONSTANT

$$\tau = L/R = \frac{150 \text{ mH}}{9 \Omega} = 16.67 \text{ ms}$$

$$1/\tau = 60 \text{ s}^{-1}$$

$$i_L(t) = 1.48 e^{-(t-0.035)60} \text{ A}$$

$$35 \text{ ms} \leq t$$

NOTE EXPONENT = 0 AT SWITCHING TIME

AT THIS POINT ($t = t_{sw}$)

$$i_L(t_{sw}) = 1.48 \text{ A}$$

$$i_L(t) = 6 \exp\left(-\frac{t}{\tau_1}\right); \quad 0 \leq t \leq t_{sw}$$

$$\tau_1 = 25\text{ms}; \quad t_{sw} = 35\text{ms}$$

$$i_L(t) = 6 \exp(-40t); \quad 0 \leq t \leq t_{sw}$$


(time expressed in sec)


$$i_L(t) = 6 \exp(-0.04t); \quad 0 \leq t \leq t_{sw}$$


(time expressed in msec)


$$i_L(t) = 6 \exp\left(-\frac{t}{\tau_1}\right) \exp\left[\frac{(t-t_{sw})}{\tau_2}\right]; \quad t_{sw} \leq t$$
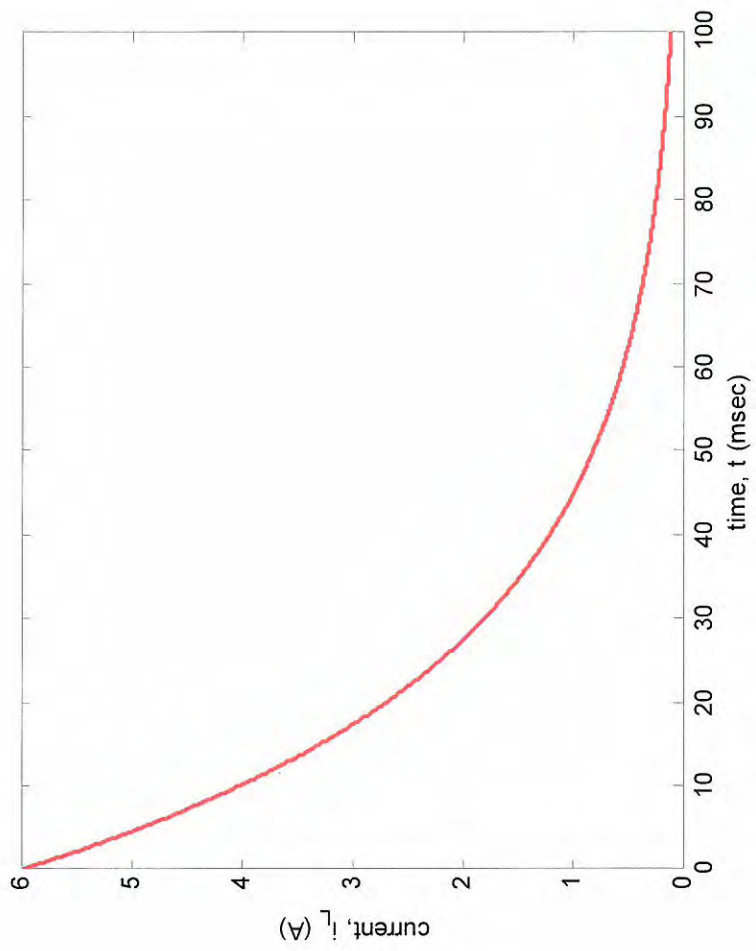
$$\tau_1 = 25\text{ms}; \quad \tau_2 = 16.67\text{ms}; \quad t_{sw} = 35\text{ms}$$



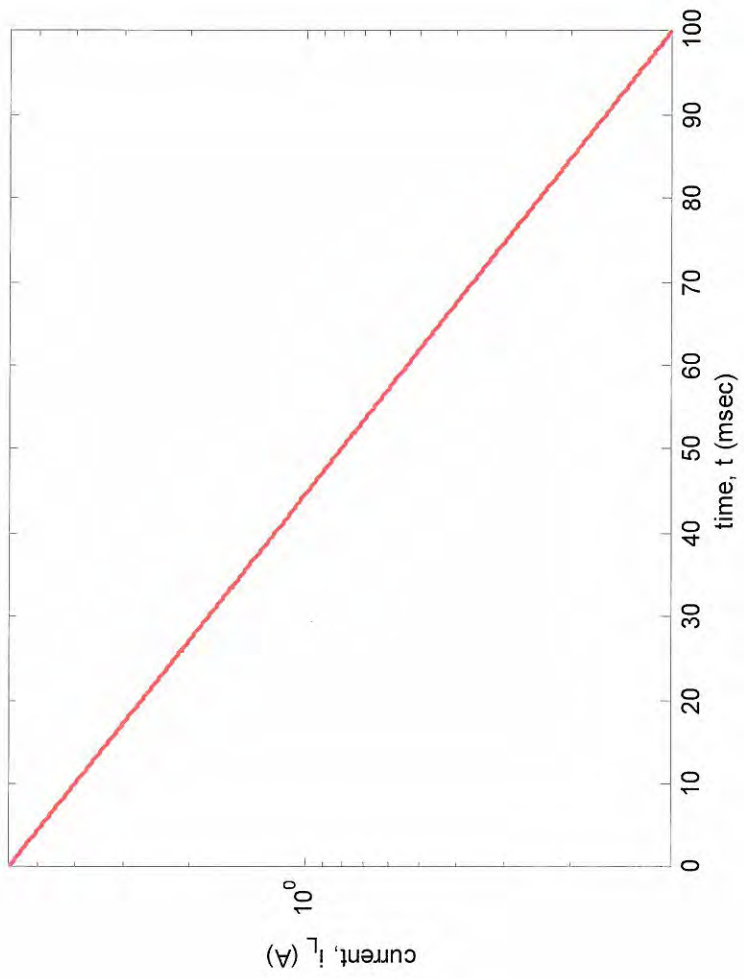

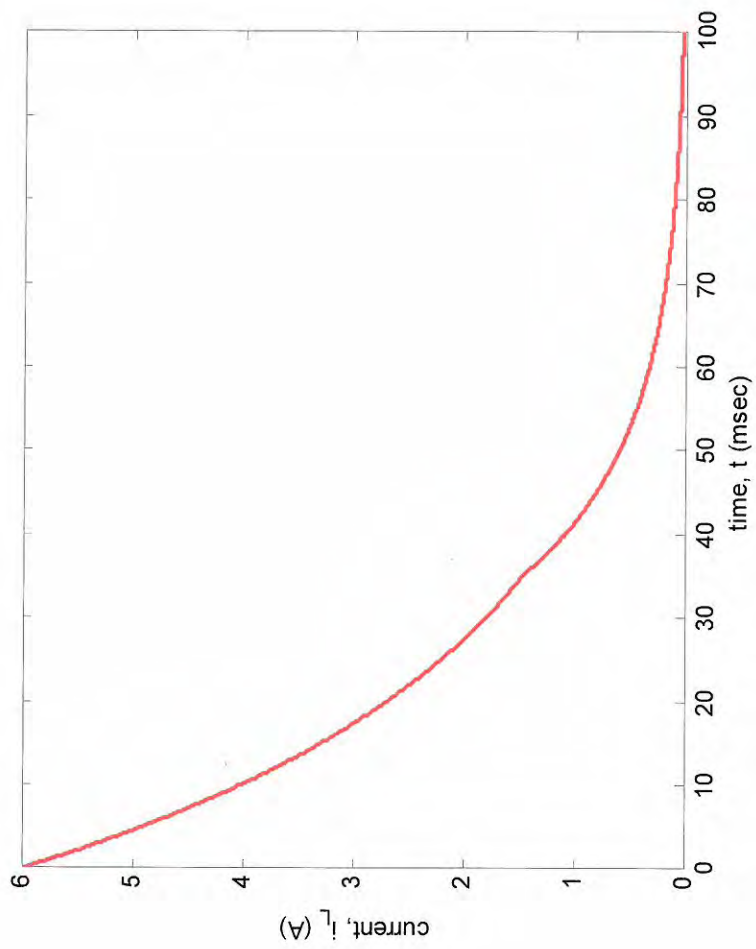

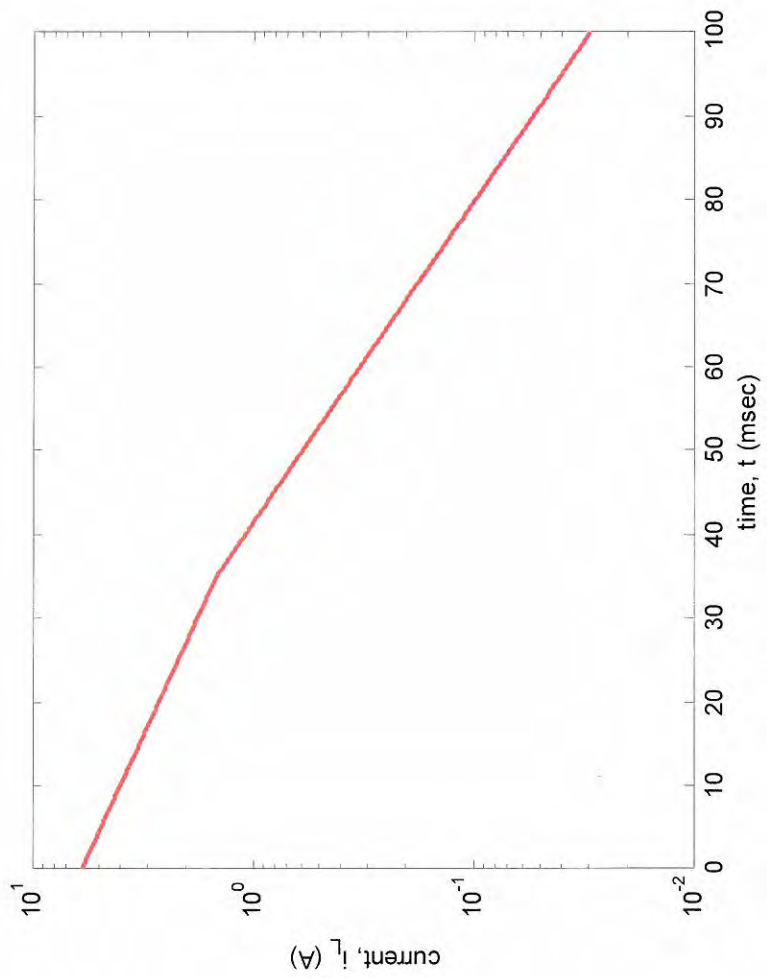

```

1  % example 7_11 in text
2  % 01/17/14 D D Duncan
3  N = 1000;
4  tmax = 100; % max time in msec
5  t = linspace(0,tmax, N); % time in msec
6  tau1 = 25; % time constant in msec
7  i_L_1 = 6*exp(-t/tau1); % current in amperes
8  figure(1); plot(t,i_L_1,'r-');
9  xlabel('time, t (msec)');
10 ylabel('current, i_L (A)');
11 figure(2); semilogy(t,i_L_1,'r-');
12 xlabel('time, t (msec)');
13 ylabel('current, i_L (A)');
14 t_sw = 35; % switching time in msec
15 tau2 = 16.67;
16 % determine array index for switching time
17 n_sw = find(t >= t_sw);
18 n_sw = n_sw(1);
19 %
20 i_L_2 = i_L_1(n_sw)*exp(-(t-t_sw)/tau2);
21 % derive composite signal from two components
22 i_L = (0 <= t & t <= t_sw).*i_L_1 + (t_sw <= t & t <= tmax).*i_L_2;
23 figure(3); plot(t,i_L,'r-');
24 xlabel('time, t (msec)');
25 ylabel('current, i_L (A)');
26 figure(4); semilogy(t,i_L,'r-');
27 xlabel('time, t (msec)');
28 ylabel('current, i_L (A)');

```