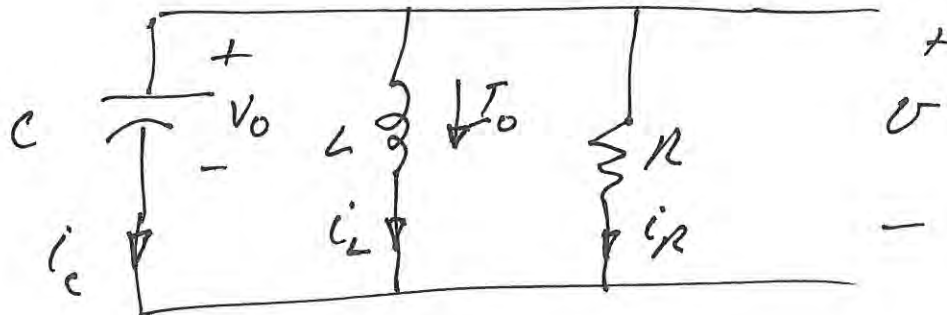


# RLC CIRCUITS



$$\frac{v}{R} + \frac{1}{L} \int_0^t v(x) dx + \frac{v}{C} + C \frac{dv}{dt} = 0$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2v}{dt^2} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

HYPOTHEESIZE A SOLUTION

$$v = Ae^{st}$$

DE BECOMES

$$As^2 e^{st} + \frac{As}{RC} e^{st} + \frac{Ae^{st}}{LC} = 0$$

$$Ae^{st} \left( s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0$$

HOW TO GUARANTEE  
SOLUTION ?

$$A = 0 ?$$

$$e^{st} = 0 ?$$

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 ?$$

"CHARACTERISTIC EQUATION"

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

HOW MANY SOLUTIONS ?

ANY LINEAR COMBINATION OF  
SOLUTIONS

IS ALSO A SOLUTION:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

ARCHITECTURE DETERMINES

$$s_1, s_2$$

INITIAL CONDITIONS DETERMINE

$$A_1, A_2$$

## STANDARD FORM

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC}$$

"NEPER" FREQ,  
PARALLEL RLC

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

RESONANT FREQ,  
PARALLEL RLC

JOHN NAPIER 1550-1617

SCOTTISH MATHEMATICIAN

(INVENTOR OF LOGARITHM)

## ✓ ASSESSMENT PROBLEM

**Objective 1**—Be able to determine the natural response and the step response of parallel  $RLC$  circuits


- 8.1 The resistance and inductance of the circuit in Fig. 8.5 are  $100\ \Omega$  and  $20\ \text{mH}$ , respectively.
- Find the value of  $C$  that makes the voltage response critically damped.
  - If  $C$  is adjusted to give a neper frequency of  $5\ \text{krad/s}$ , find the value of  $C$  and the roots of the characteristic equation.
  - If  $C$  is adjusted to give a resonant frequency of  $20\ \text{krad/s}$ , find the value of  $C$  and the roots of the characteristic equation.

**Answer:** (a)  $500\ \text{nF}$ ;

(b)  $C = 1\ \mu\text{F}$ ,  
 $s_1 = -5000 + j5000\ \text{rad/s}$ ,  
 $s_2 = -5000 - j5000\ \text{rad/s}$ ;

(c)  $C = 125\ \text{nF}$ ,  
 $s_1 = -5359\ \text{rad/s}$ ,  
 $s_2 = -74,641\ \text{rad/s}$ .

*NOTE:* Also try Chapter Problem 8.4.

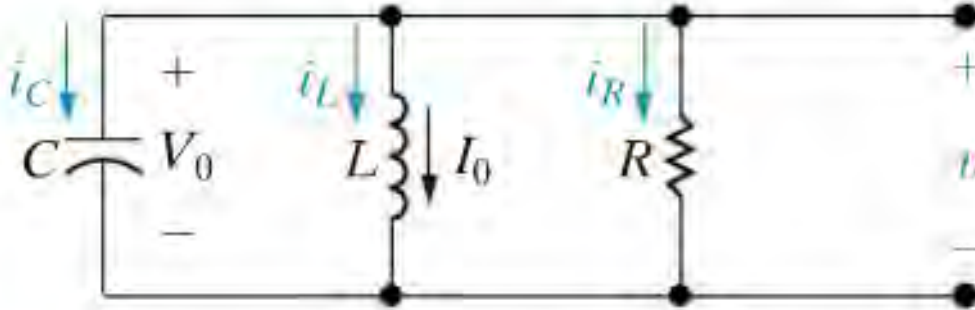

**Figure 8.5** ▲ A circuit used to illustrate the natural response of a parallel  $RLC$  circuit.

$$\left. \begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{aligned} \right\} \begin{array}{l} \text{ROOTS OF} \\ \text{CHARACTERISTIC} \\ \text{EQ} \end{array}$$

$$\alpha = \frac{1}{2RC} \quad \text{"NEPER" FREQUENCY}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{RESONANT FREQUENCY} \\ \text{(UNITS RADIANS/TIME)}$$

### 3 POSSIBLE CONDITIONS

$\omega_0^2 < \alpha^2$ : ROOTS REAL & DISTINCT  
RESPONSE "OVERDAMPED"

$\omega_0^2 > \alpha^2$ : ROOTS COMPLEX &  
CONJUGATES OF  
ONE ANOTHER  
RESPONSE "UNDERDAMPED"

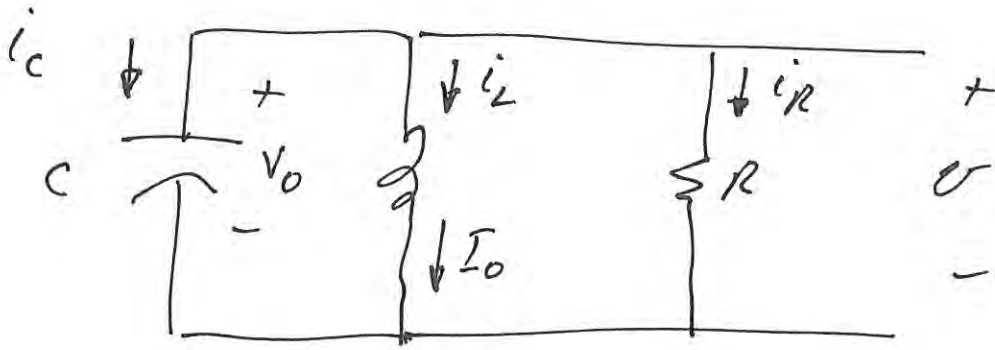$\omega_0^2 = \alpha^2$ : ROOTS REAL & IDENTICAL  
RESPONSE "CRITICALLY  
DAMPED"



SOLUTION:  $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

TWO UNKNOWN  $\Rightarrow$  NEED TWO EQUATIONS

EQ #1  $v(0^+) = A_1 + A_2$  (KNOW THIS TO BE  $V_0$ )  
WHY?

$$\frac{d}{dt} v(t) = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$\left. \frac{d}{dt} v(t) \right|_{t=0^+} = A_1 s_1 + A_2 s_2$$

APPLY KCL TO UPPER NODE:

$$i_c(0^+) + I_0 + \frac{V_0}{R} = 0$$

$\uparrow$       $\nearrow$   
 KNOWN



$$\begin{aligned} i_c(0^+) &= -\frac{V_0}{R} - I_0 \\ &= C \left. \frac{dv(t)}{dt} \right|_{t=0^+} \end{aligned}$$

EQ #2

$$C(A_1 S_1 + A_2 S_2) = -\frac{V_0}{R} - I_0$$

TWO EQ'S IN TWO UNKNOWN'S YIELD  
SOLUTIONS FOR  $A_1$  &  $A_2$

∴  $v(t)$  IS SPECIFIED


⇒ BRANCH CURRENTS

$$i_R(t) = v(t)/R$$

$$i_L(t) = \frac{1}{L} \int_0^t v(x) dx + I_0$$

$$i_c(t) = C \frac{dv(t)}{dt}$$

EXAMPLE 8.2 PG 272

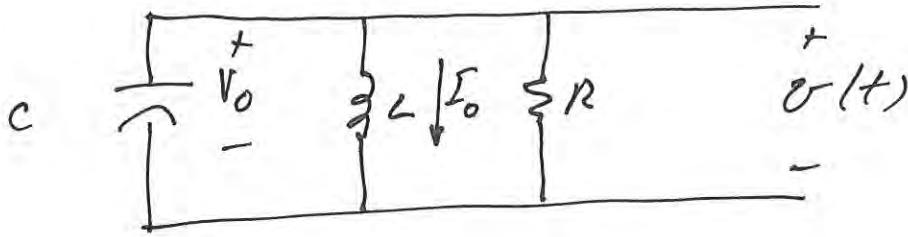

$$C = 0.2 \mu\text{F}, L = 50 \text{ mH}, R = 200 \Omega$$

$$v(0^+) = 12 \text{ V } (= V_0)$$

$$i_L(0^+) = 30 \text{ mA } (= I_0)$$

$$\text{KCL: } i_c(0^+) + i_L(0^+) + \frac{v(0^+)}{R} = 0$$

$$\begin{aligned} i_c(0^+) &= -i_L(0^+) - \frac{v(0^+)}{R} \\ &= -30 \text{ mA} - \frac{12 \text{ V}}{200 \Omega} = -90 \text{ mA} \end{aligned}$$

$$\text{GENERAL SOL'N: } v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{INITIAL COND'S: } A_1 + A_2 = V_0 \quad \textcircled{\#1}$$

$$i_c(0^+) = C(A_1 s_1 + A_2 s_2) \quad \textcircled{\#2}$$

$$s_1 = -12,500 + 7,500 = -5,000 \text{ RAD/S}$$

$$s_2 = -12,500 - 7,500 = -20,000 \text{ RAD/S}$$

(OVERDAMPED)

SUB EQ #1  
INTO EQ #2

$$A_1 = \frac{i_c(0^+)/C - V_0 s_2}{s_1 - s_2} = -14 \text{ V}$$

EQ #1

$$A_2 = V_0 - A_1 = 12 \text{ V} + 14 \text{ V}$$

$$A_2 = 26 \text{ V}$$

$$v(t) = -14 e^{-5,000t} + 26 e^{-20,000t} \text{ V}; t \geq 0$$

$$i_R(t) = v(t)/R$$

$$i_L(t) = \frac{1}{L} \int_0^t v(x) dx + I_0$$

$$= \frac{1}{50 \text{ mH}} \left\{ \frac{14}{5,000} e^{-5,000x} \Big|_0^t \right.$$

$$\left. - \frac{26}{20,000} e^{-20,000x} \Big|_0^t \right\} + I_0$$

$$i_c(t) = 56 e^{-5,000 t} - 26 e^{-20,000 t} \text{ mA}; t \geq 0$$

$$i_c(t) = C \frac{dv(t)}{dt}$$



$$= 0.2 \mu\text{F} \left\{ (14)(5,000) e^{-5,000 t} \right.$$

$$\left. - (26)(20,000) e^{-20,000 t} \right\}$$

$$i_c(t) = 14 e^{-5,000 t} - 104 e^{-20,000 t} \text{ mA}; t \geq 0$$

SHOULD BE

$t \geq 0^+$

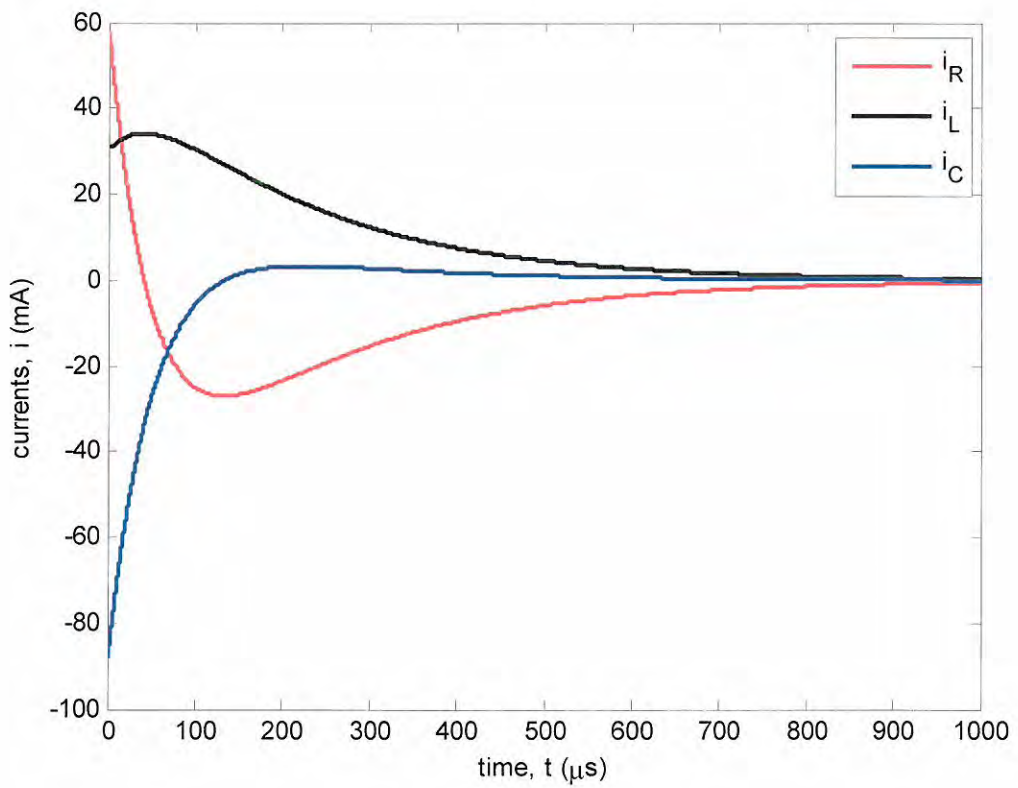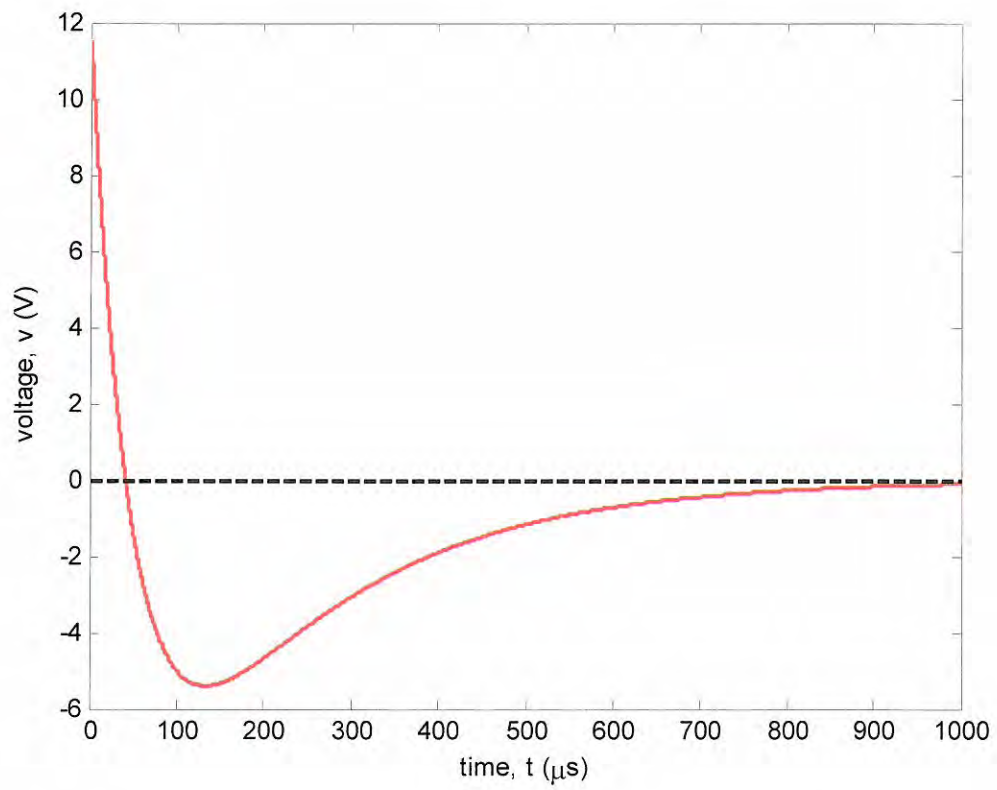


```

% example_8_2
% 01/20/14 D D Duncan
%
N = 10000;
tmax = 1000; % max time in microsec
t = linspace(1,tmax,N)*1e-6; % time in sec
v = -14*exp(-5000*t) + 26*exp(-20000*t);
figure(1);plot(t*1e6,v,'r-',[0 tmax],[0 0],'k--');
xlabel('time, t (\mus)');ylabel('voltage, v (V)');
%
i_R = v/200;
i_L = 56e-3*exp(-5000*t) - 26e-3*exp(-20000*t);
i_C = 14e-3*exp(-5000*t) - 104e-3*exp(-20000*t);
figure(2);plot(t*1e6,i_R*1000,'r-',t*1e6,i_L*1000,'k',t*1e6,i_C*1000,'b-');
xlabel('time, t (\mus)');ylabel('currents, i (mA)');
legend('i_R','i_L','i_C')


```

# Example 8.2

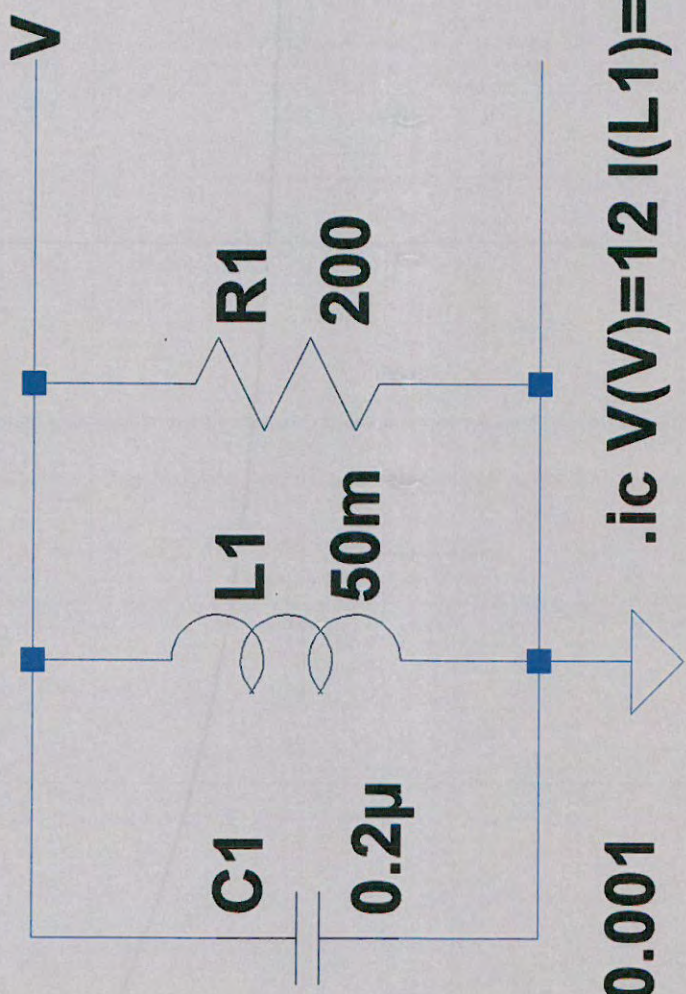


**.tran 0.001**

**.ic V(V)=12 I(L1)=30m**

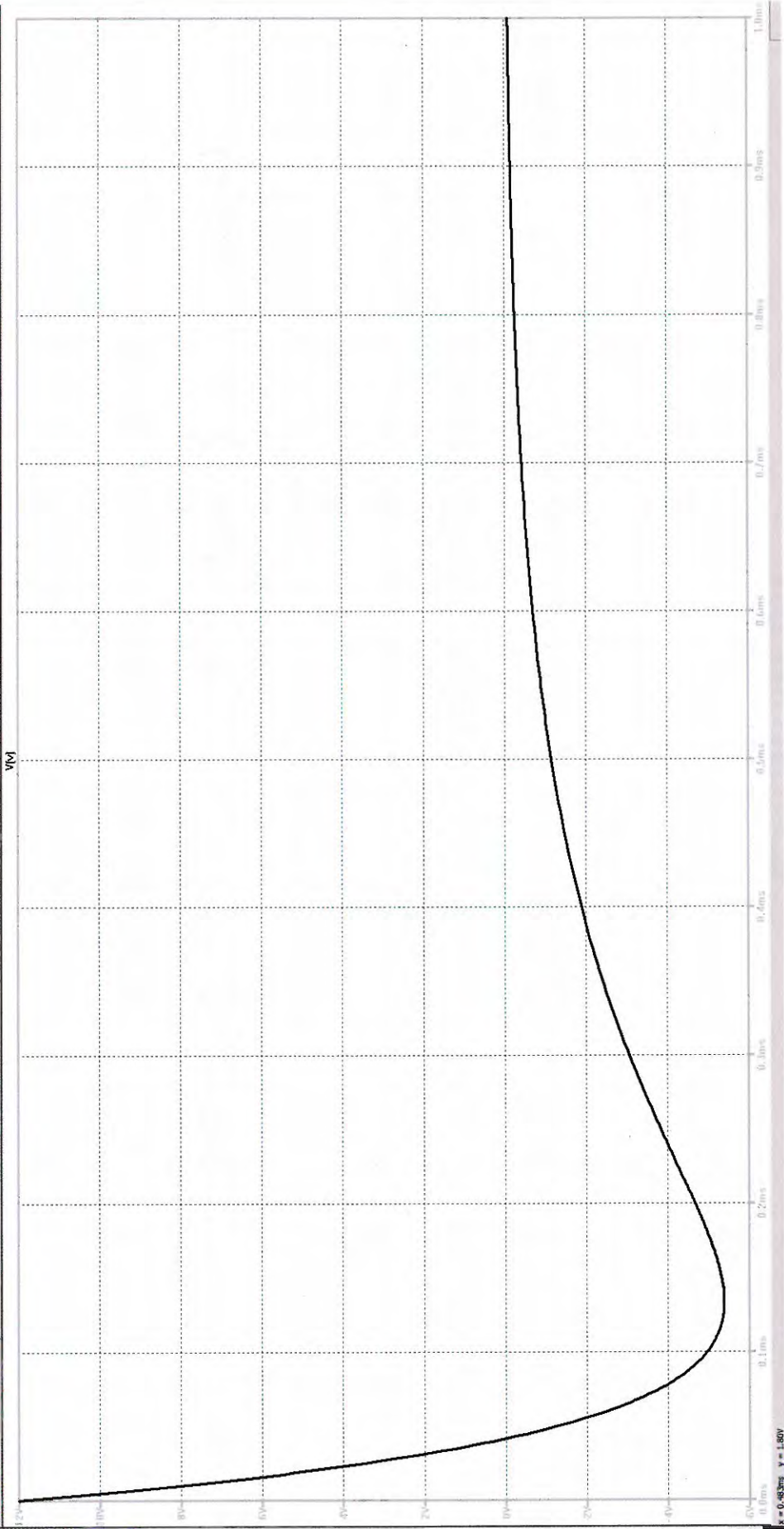



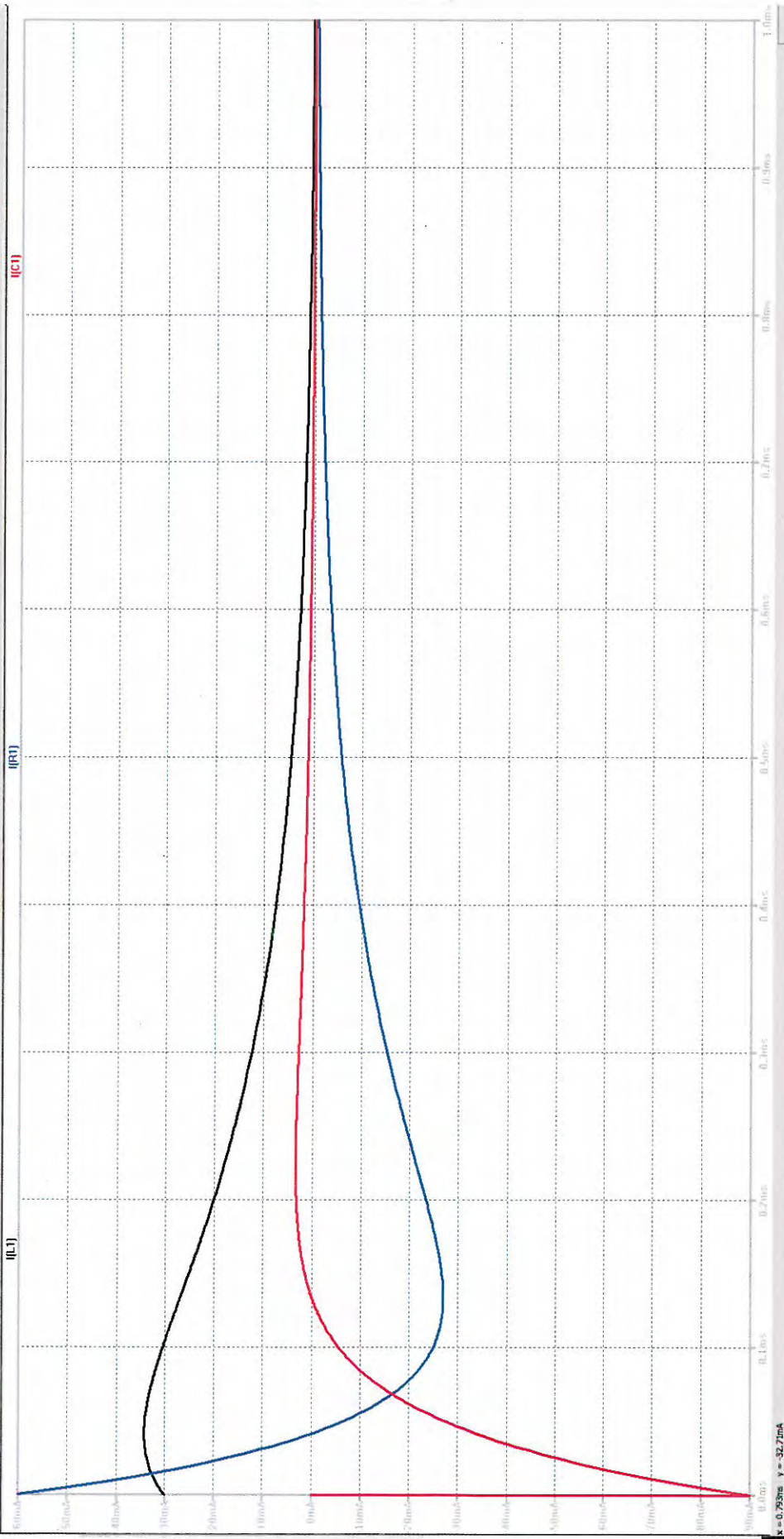

UNDER DAMPED CONDITION

$$s_i = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

UNDER DAMPING :  $\omega_0^2 > \alpha^2$

$$s_i = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

$$= -\alpha \pm j\omega_d$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

DAMPED RADIAN  
FREQUENCY

GENERAL SOLUTION:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$= A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}$$

$$\equiv \cancel{(A_1 + A_2)} e^{-\alpha t}$$

RECALL EULER IDENTITY;

$$e^{j\theta} = \cos\theta + j\sin\theta$$

⇓

$$\frac{e^{j\theta} + e^{-j\theta}}{2} = \cos\theta$$

$$\frac{e^{j\theta} - e^{-j\theta}}{2j} = \sin\theta$$

$$v(t) = A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$

$$= A_1 e^{-\alpha t} (\cos\omega_d t + j\sin\omega_d t)$$

$$+ A_2 e^{-\alpha t} (\cos\omega_d t - j\sin\omega_d t)$$


$$= e^{-\alpha t} \left[ (A_1 + A_2) \cos\omega_d t \right.$$

$$\left. + j(A_1 - A_2) \sin\omega_d t \right]$$

$$v(t) = B_1 e^{-\alpha t} \cos\omega_d t + B_2 e^{-\alpha t} \sin\omega_d t$$

CAN BE WRITTEN MORE COMPACTLY:
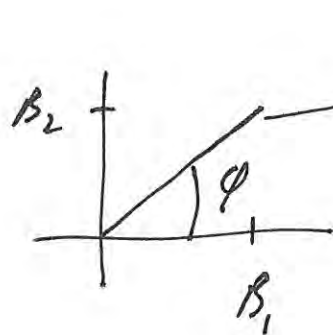
$$v(t) = \sqrt{B_1^2 + B_2^2} \left[ \frac{B_1}{\sqrt{B_1^2 + B_2^2}} \cos \omega t + \frac{B_2}{\sqrt{B_1^2 + B_2^2}} \sin \omega t \right] e^{-\alpha t}$$



$$\sqrt{B_1^2 + B_2^2}$$
$$\varphi = \text{TAN}^{-1} \frac{B_2}{B_1}$$

$$\cos \varphi = \frac{B_1}{\sqrt{B_1^2 + B_2^2}}$$

$$\sin \varphi = \frac{B_2}{\sqrt{B_1^2 + B_2^2}}$$

$$v(t) = e^{-\alpha t} \sqrt{B_1^2 + B_2^2} \underbrace{(\cos \varphi \cos \omega t + \sin \varphi \sin \omega t)}_{\cos(\omega t - \varphi)}$$

$$v(t) = \sqrt{B_1^2 + B_2^2} e^{-\alpha t} \cos(\omega t - \varphi)$$

NOTE:  $B_i$  ARE REAL BECAUSE

$v(t)$  MUST BE REAL

$$(\Rightarrow A_1 = A_2^*)$$

INITIAL CONDITIONS DETERMINE  $B_i$ :

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\boxed{v(0^+) = B_1 = V_0}$$

$$i_c(0^+) = c \left. \frac{dv}{dt} \right|_{t=0} = c \left. \frac{d}{dt} \left( B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t \right) \right|_{t=0}$$

$$i_c(0^+) = c \left( -\alpha B_1 e^{-\alpha t} \cos \omega_d t - \omega_d B_1 e^{-\alpha t} \sin \omega_d t - \alpha B_2 e^{-\alpha t} \sin \omega_d t + \omega_d B_2 e^{-\alpha t} \cos \omega_d t \right) \Big|_{t=0}$$

$$\boxed{i_c(0^+) = (-\alpha B_1 + \omega_d B_2) c}$$

## ASSESSMENT PROBLEMS


**Objective 1**—Be able to determine the natural response and the step response of parallel  $RLC$  circuits

**8.2** Use the integral relationship between  $i_L$  and  $v$  to find the expression for  $i_L$  in Fig. 8.6.


**Answer:**  $i_L(t) = (56e^{-5000t} - 26e^{-20,000t})$  mA,  $t \geq 0$ .

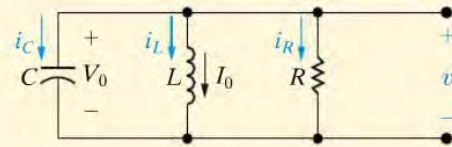**8.3** The element values in the circuit shown are  $R = 2$  k $\Omega$ ,  $L = 250$  mH, and  $C = 10$  nF. The initial current  $I_0$  in the inductor is  $-4$  A, and the initial voltage on the capacitor is  $0$  V. The output signal is the voltage  $v$ . Find (a)  $i_R(0^+)$ ; (b)  $i_C(0^+)$ ; (c)  $dv(0^+)/dt$ ; (d)  $A_1$ ; (e)  $A_2$ ; and (f)  $v(t)$  when  $t \geq 0$ .

**NOTE:** Also try Chapter Problems 8.5 and 8.13.



**Answer:** (a) 0;  
 (b) 4 A;  
 (c)  $4 \times 10^8$  V/s;  
 (d) 13,333 V;  
 (e)  $-13,333$  V;  
 (f)  $13,333(e^{-10,000t} - e^{-40,000t})$  V.

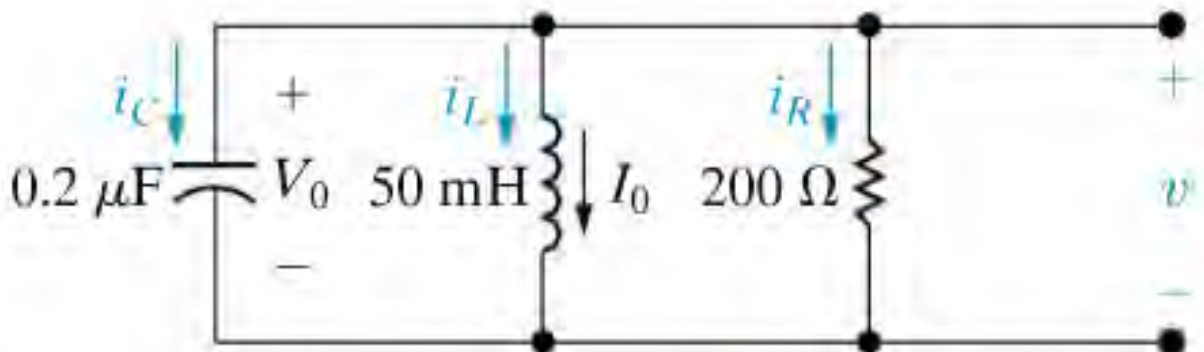

**Figure 8.6** ▲ The circuit for Example 8.2.

OVERDAMPED

$$v(t) = A_1 e^{-s_1 t} + A_2 e^{-s_2 t}$$

$$v(0) = A_1 + A_2 = v_c(0^+)$$

$$\begin{aligned} i_c(0^+) &= c \frac{dv}{dt} \Big|_{t=0} = c(A_1 s_1 + A_2 s_2) \\ &= -i_L(0^+) - \frac{v(0^+)}{R} \end{aligned}$$

---

UNDERDAMPED


$$v(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$$

$$v(0) = B_1 = v_c(0^+)$$

$$i_c(0^+) = (-\alpha B_1 + \omega_d B_2) c = -i_L(0^+) - \frac{v(0^+)}{R}$$

CHEATSHEET  
FOR  
ASSESSMENT 8.2

# EXAMPLE 8.4

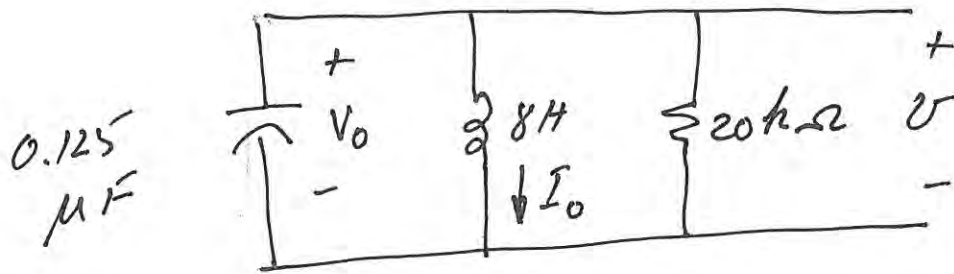

$$V_0 = 0$$

$$I_0 = -12.25 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = 200 \text{ RAD/S}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1,000 \text{ RAD/S}$$

$\omega_0 > \alpha \Rightarrow \text{UNDERDAMPED}$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 979.8 \text{ RAD/S}$$

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$



INITIAL COND'S.

$$v(0) = V_0 = \beta_1 = 0$$

$$i_c(0^+) = C\omega_d \beta_2$$

KCL:  $i_L(0^+) + i_c(0^+) + i_R(0^+) = 0$

$\uparrow$   $\uparrow$



$I_0$   $\frac{V_0}{R} = 0$

$$i_c(0^+) = -I_0 = C\omega_d \beta_2$$

$$\beta_2 = \frac{-I_0}{C\omega_d} = \frac{12.25 \text{ mA}}{(0.125 \mu\text{F})(979.8 \text{ RAD/S})}$$

$$\beta_2 \approx 100 \text{ V}$$

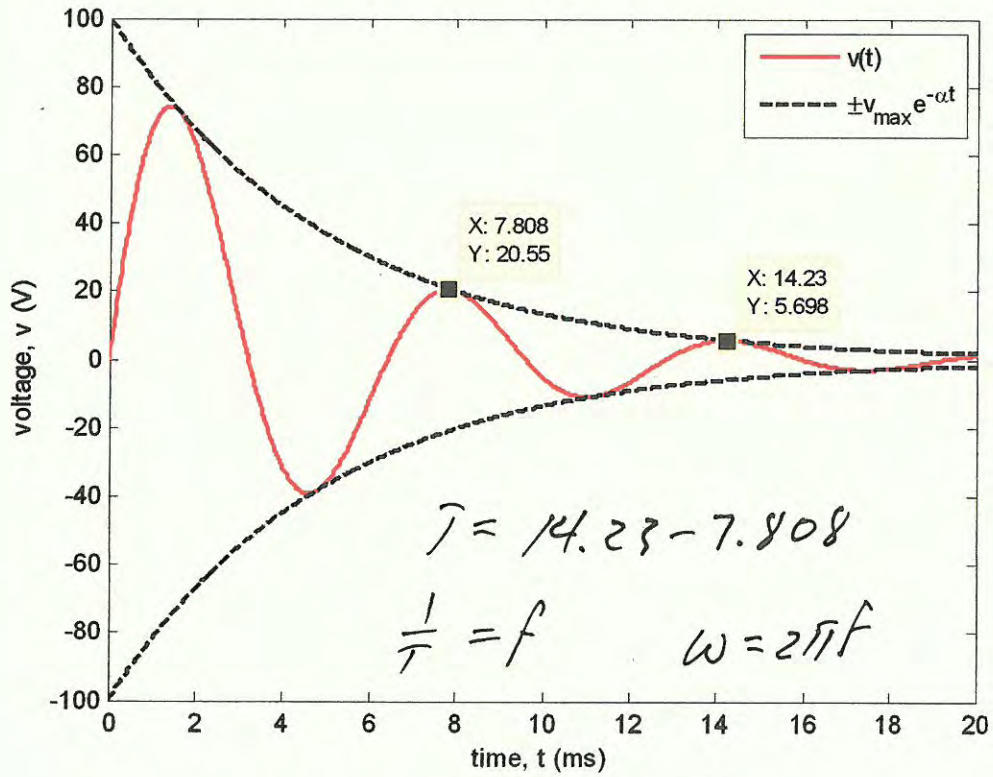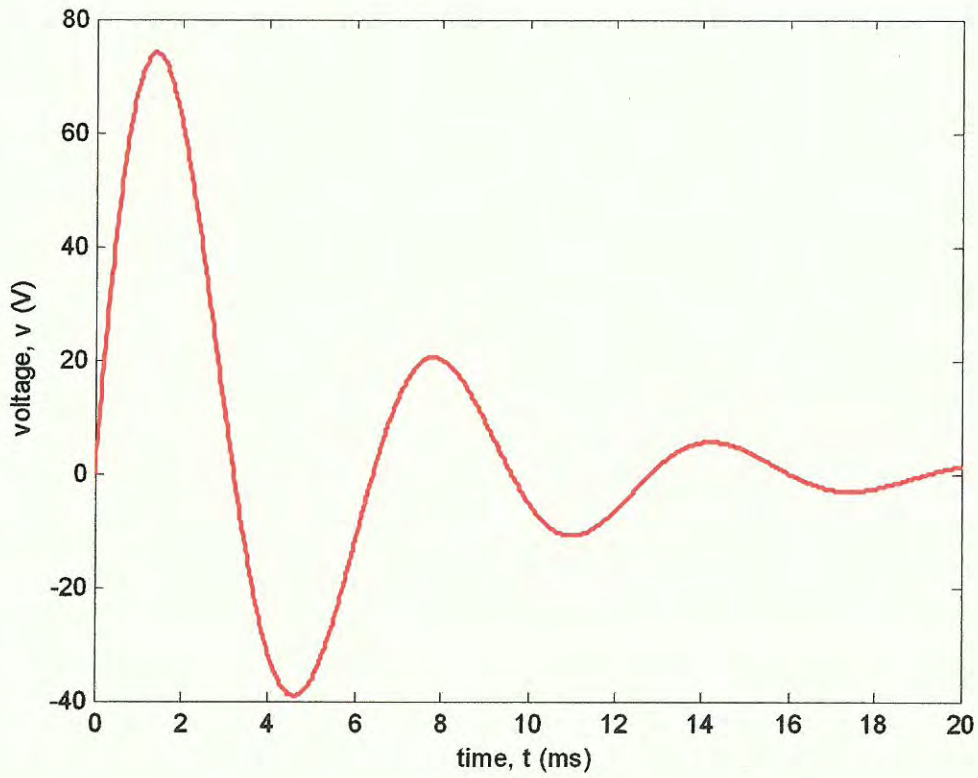
$$v(t) = 100 e^{-200t} \sin(979.8t) \text{ V}; t \geq 0$$





$$\omega_d = \frac{2\pi}{(14.23 - 7.808) \text{ ms}}$$

```
% example_8_4
% 01_20_14 D D Duncan
%
alpha = 200;
omega_d = 100*sqrt(96);
tmax = 20e-3;% max time in sec
vmax = 100;
N = 1000;
t = linspace(0,tmax,N);% time in sec
v = vmax*exp(-alpha*t).*sin(omega_d*t);% voltage in volts
figure(1);plot(t*1000,v,'r-');
xlabel('time, t (ms)');ylabel('voltage, v (V)');
envelope = vmax*exp(-alpha*t);
figure(2);plot(t*1000,v,'r-',t*1000,envelope,'k--',t*1000,-envelope,'k--');
xlabel('time, t (ms)');ylabel('voltage, v (V)');
legend('v(t)', '\pmv_{max}e^{-\alphanat}');
```

# Example 8.4

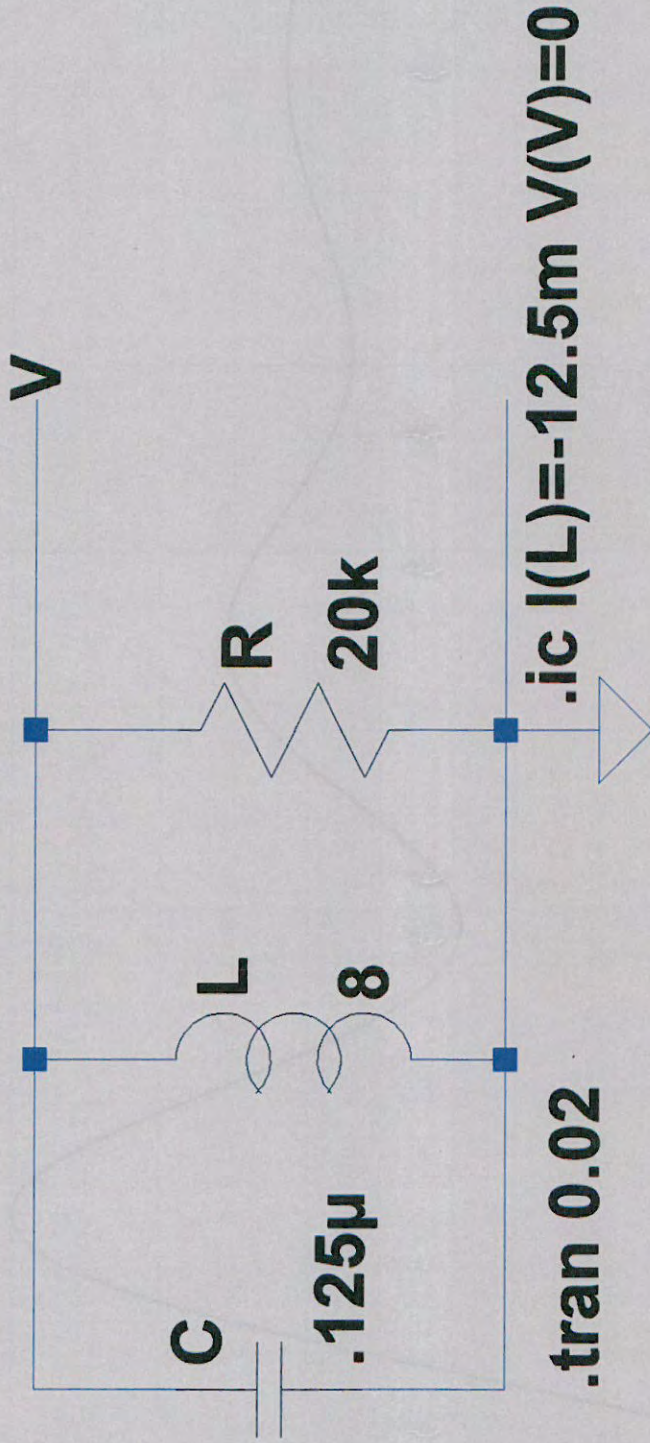

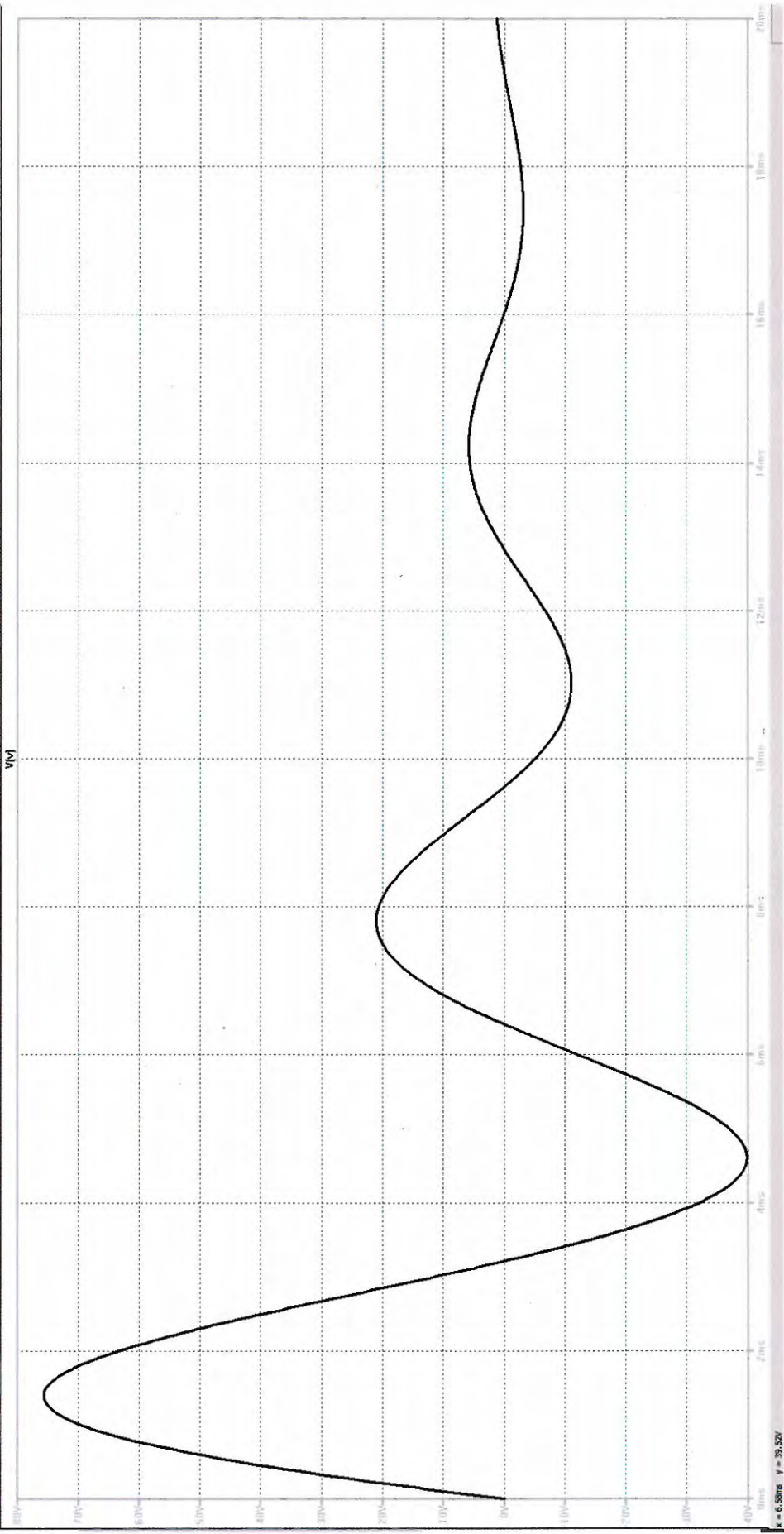

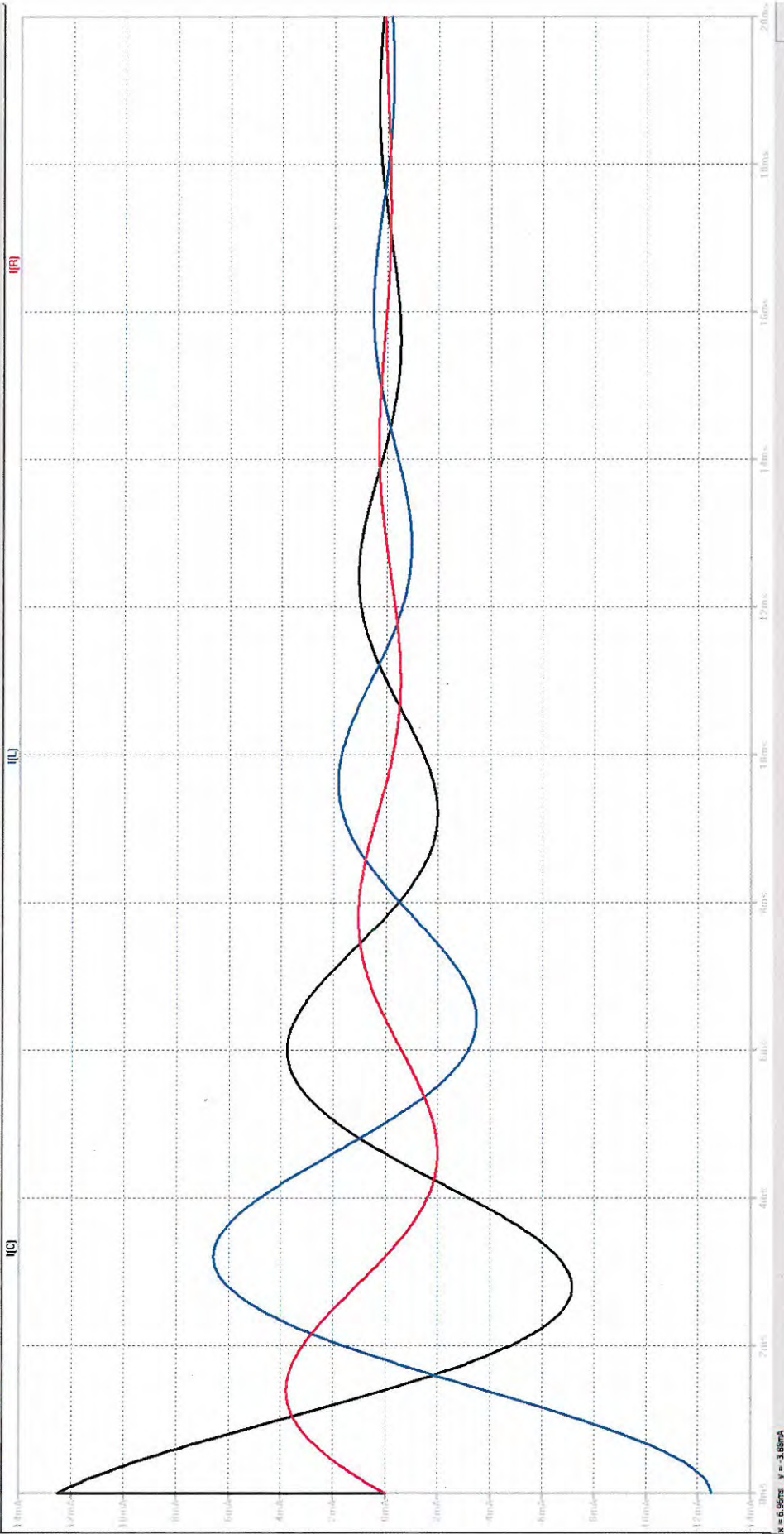

## CRITICAL DAMPING

RECALL CRITICAL DAMPING  $\Rightarrow \alpha = \omega_0$

$$\Rightarrow s_1 = s_2 = -\alpha = -\frac{1}{2RC}$$

$\Rightarrow$  GENERAL SOL'N.  $v(t) = (A_1 + A_2)t e^{-\alpha t}$

$$v(t) = A e^{-\alpha t} ?$$

ONLY 1 ARBITRARY CONSTANT

$\Rightarrow$  CANNOT SATISFY NECESSARY

(TWO) BOUNDARY, i.e., INITIAL  
CONDITIONS

$\Rightarrow$  MUST MODIFY HYPOTHESIZED  
SOLUTION FORM

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

ORIGINAL D.E.

$$\frac{d^2 v}{dt^2} + \frac{1}{rc} \frac{dv}{dt} + \frac{v}{LC} = 0$$

$$\alpha = \frac{1}{2rc}, \text{ CRITICAL DAMPING} \Rightarrow \left(\frac{1}{2rc}\right) = \frac{1}{\sqrt{LC}}$$

$= \alpha$

$$\frac{d^2 v}{dt^2} + 2\alpha \frac{dv}{dt} + \alpha^2 v = 0$$

SHOULD BE ABLE TO SHOW THAT

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

IS A SOLUTION



## INITIAL CONDITIONS

$$\boxed{v(0) = D_2 = V_0}$$


$$i_c(0^+) = c \frac{dv}{dt} \Big|_{t=0^+}$$

$$= c \frac{d}{dt} \left[ (D_1 + D_2) e^{-\alpha t} \right] \Big|_{t=0}$$

$$= c \left[ D_1 e^{-\alpha t} - \alpha (D_1 + D_2) e^{-\alpha t} \right] \Big|_{t=0}$$

$$\boxed{i_c(0^+) = c(D_1 - \alpha D_2)}$$

# EXAMPLE 8.5

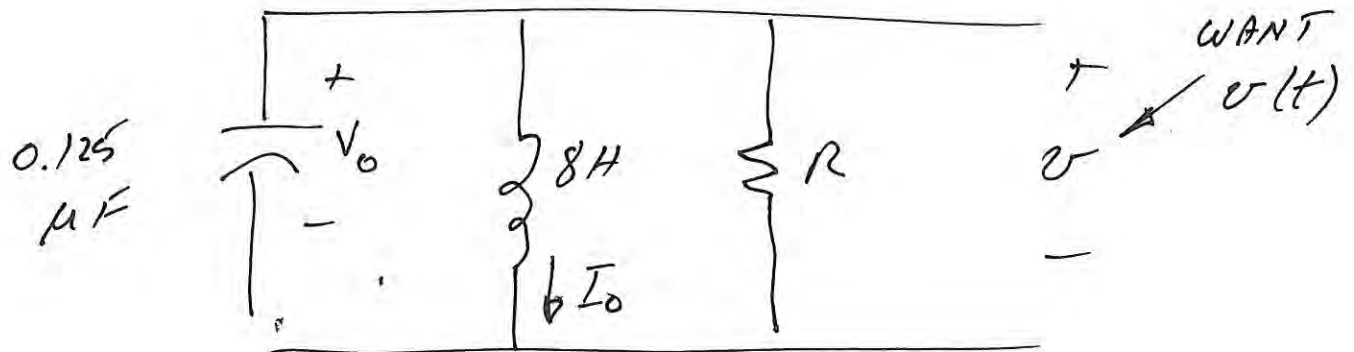

FROM EX 8.4,  $\omega_0 = \frac{1}{\sqrt{LC}} = 10^3 \text{ RAD/S}$

$$\alpha = \frac{1}{2RC}$$

FOR CRITICAL DAMPING,  $\alpha = \omega_0 = 10^3 \text{ RAD/S}$

$$\Rightarrow R = \frac{1}{2\alpha C} = 4 \text{ k}\Omega$$

FROM EX 8.4  $v_0(0^+) = 0$ ,  $I_0 = -12.25 \text{ mA}$

GENERAL FORM:

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$v(0) = D_2 = v_0(0^+) \Rightarrow D_2 = 0$$

$$\Rightarrow v(t) = D_1 t e^{-\alpha t}$$

OTHER I.C. IS

$$i_c(0^+) = c(D_1 - \alpha D_2) = cD_1$$

$$\text{KCL: } i_c(0^+) + \cancel{I_0} + \frac{v_0}{R} = 0$$

$$i_c(0^+) = -I_0$$

$$-I_0 = cD_1 \rightarrow D_1 = \frac{0.125 \text{ mA}}{0.125 \mu\text{F}} = \frac{12.25 \text{ mA}}{0.125 \mu\text{F}}$$

$$D_1 = 98,000 \quad \text{WHAT ARE UNITS?}$$

$$D_1 = \frac{-I_0}{C}$$

$$[D_1] = \frac{A}{F} = \frac{A}{C/V} = \frac{C/S}{C/V} = \frac{V}{S}$$

$$[D_1] = \frac{V}{S}$$

$$v(t) = 98,000 t e^{-1000t} \text{ V}; t \geq 0$$

$t$  IN S

$$v(t) = 98 t e^{-t} \text{ V}; t \geq 0$$

$t$  IN MS

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

WHAT HAPPENS WHEN  $s_1 = s_2$  ?

$$\text{LET } \frac{s_1 + s_2}{2} = s, \quad s_1 - s_2 = \epsilon \text{ (SMALL)}$$

$$s_1 = s + \epsilon/2, \quad s_2 = s - \epsilon/2$$

SUBSTITUTE INTO SOLUTION FORM

$$\begin{aligned} v(t) &= A_1 e^{(s + \epsilon/2)t} + A_2 e^{(s - \epsilon/2)t} \\ &= A_1 e^{st} e^{\epsilon t/2} + A_2 e^{st} e^{-\epsilon t/2} \end{aligned}$$

USE APPROXIMATION  $e^{\pm \epsilon t/2} \approx 1 \pm \frac{\epsilon t}{2}$

$$v(t) = A_1 e^{st} (1 + \frac{\epsilon t}{2}) + A_2 e^{st} (1 - \frac{\epsilon t}{2})$$

COLLECT TERMS

$$v(t) = \frac{(A_1 - A_2)\epsilon}{2} t e^{st} + (A_1 + A_2) e^{st}$$

$$v(t) = D_1 t e^{st} + D_2 e^{st}$$

## CRITICAL DAMPING

$$v(t) = D_1 e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$v(0) = D_2 = V_0$$

$$i_c(0^+) = c \left. \frac{dv(t)}{dt} \right|_{t=0^+} = c(D_1 - \alpha D_2)$$

KCL GIVES  $c(D_1 - \alpha D_2) = -\frac{I_0}{R} - \frac{v(0^+)}{R}$

$\uparrow$   
 $i_c(0^+)$

## ✓ ASSESSMENT PROBLEM


**Objective 1—Be able to determine the natural and the step response of parallel *RLC* circuits**

**8.5** The resistor in the circuit in **Assessment Problem 8.4** is adjusted for critical damping. The inductance and capacitance values are 0.4 H and 10  $\mu\text{F}$ , respectively. The initial energy stored in the circuit is 25 mJ and is distributed equally between the inductor and capacitor. Find (a)  $R$ ; (b)  $V_0$ ; (c)  $I_0$ ; (d)  $D_1$  and  $D_2$  in the solution for  $v$ ; and (e)  $i_R, t \geq 0^+$ .

**Answer:** (a) 100  $\Omega$ ;  
(b) 50 V;  
(c) 250 mA;  
(d)  $-50,000$  V/s, 50 V;  
(e)  $i_R(t) = (-500te^{-500t} + 0.50e^{-500t})$  A,  
 $t \geq 0^+$ .

*NOTE: Also try Chapter Problems 8.7 and 8.12.*

# STEP RESPONSE PARALLEL RLC

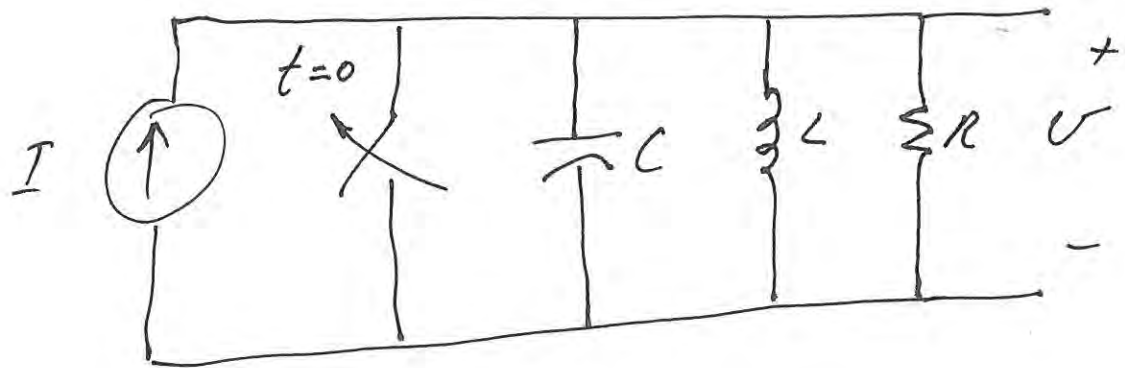

$$\text{KCL: } i_L + i_R + i_C = I$$

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

⋮

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

SOLVE BY KNOWN METHODS

("DIRECT" APPROACH)

NOTE: SOL'N = FORCED RESP.

+ NATURAL RESP.



MISSING STEPS PREVIOUS PAGE

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$v_L = L \frac{di_L}{dt} = v$$

$$\Rightarrow \frac{v}{R} = \frac{L}{R} \frac{di_L}{dt}$$

$$\Rightarrow L \frac{d^2 i_L}{dt^2} = \frac{dv}{dt}$$

$$\Rightarrow C \frac{dv}{dt} = CC \frac{d^2 i_L}{dt^2}$$

$$i_L + \frac{L}{R} \frac{di_L}{dt} + CC \frac{d^2 i_L}{dt^2} = I$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

## "INDIRECT" APPROACH

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$\frac{1}{L} \int_0^t v(\tau) d\tau + \frac{v}{R} + C \frac{dv}{dt} = I$$

$\frac{d}{dt}$  BOTH SIDES:

$$\frac{v}{L} + \frac{1}{R} \frac{dv}{dt} + C \frac{d^2v}{dt^2} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

SOLVE BY KNOWN METHODS:

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

THESE ARE NATURAL RESPONSES...


RECALL

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = \underline{I}$$

USE SOL'N. FOR  $v$ , E.G., OVERDAMPED...

$$i_L = \underline{I} + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

# STEP RESPONSE PARALLEL RLC

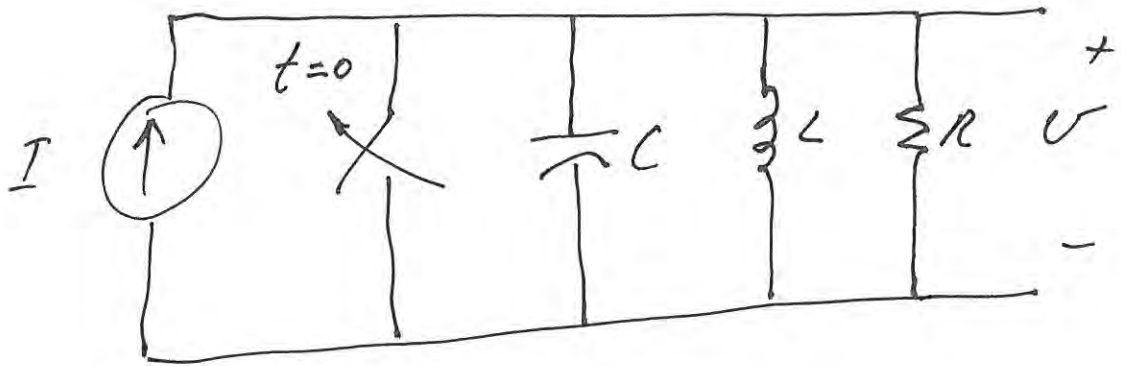

$$\text{KCL: } i_L + i_R + i_C = I$$

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

⋮

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

SOLVE BY KNOWN METHODS

("DIRECT" APPROACH)

NOTE: SOLN = FORCED RESP.

+ NATURAL RESP.

MISSING STEPS PREVIOUS PAGE

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$v_L = L \frac{di_L}{dt} = v$$

$$\Rightarrow \frac{v}{R} = \frac{L}{R} \frac{di_L}{dt}$$

$$\Rightarrow L \frac{d^2 i_L}{dt^2} = \frac{dv}{dt}$$

$$\Rightarrow C \frac{dv}{dt} = CC \frac{d^2 i_L}{dt^2}$$

$$i_L + \frac{L}{R} \frac{di_L}{dt} + CC \frac{d^2 i_L}{dt^2} = I$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

## "INDIRECT" APPROACH

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$\frac{1}{L} \int_0^t v(\tau) d\tau + \frac{v}{R} + C \frac{dv}{dt} = I$$

$\frac{d}{dt}$  BOTH SIDES:

$$\frac{v}{L} + \frac{1}{R} \frac{dv}{dt} + C \frac{d^2v}{dt^2} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

SOLVE BY KNOWN METHODS:

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

THESE ARE NATURAL RESPONSES...


RECALL

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = \underline{I}$$

USE SOL'N. FOR  $v$ , E.G., OVERDAMPED...

$$i_L = \underline{I} + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


# STEP RESPONSE // RLC CKT

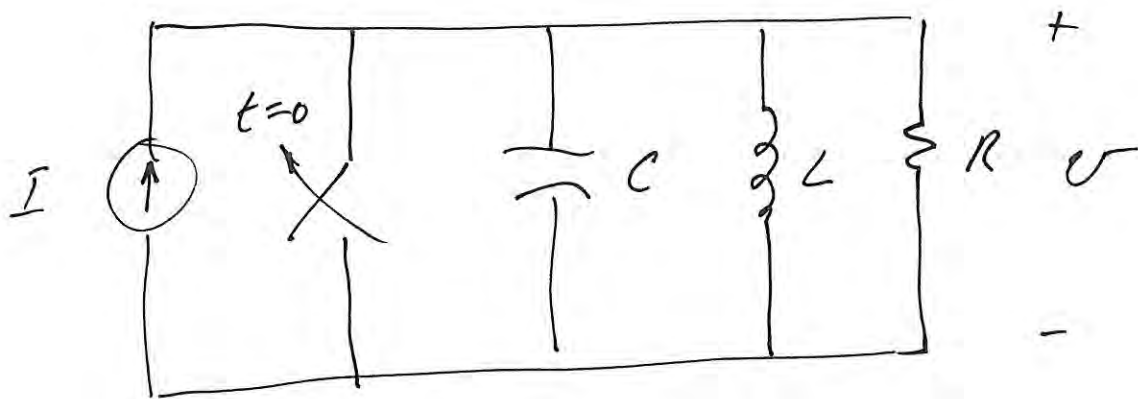

NO ENERGY STORED PRIOR TO  $t=0$


$$\Rightarrow v(0) = 0$$

$$i_L(0) = 0$$

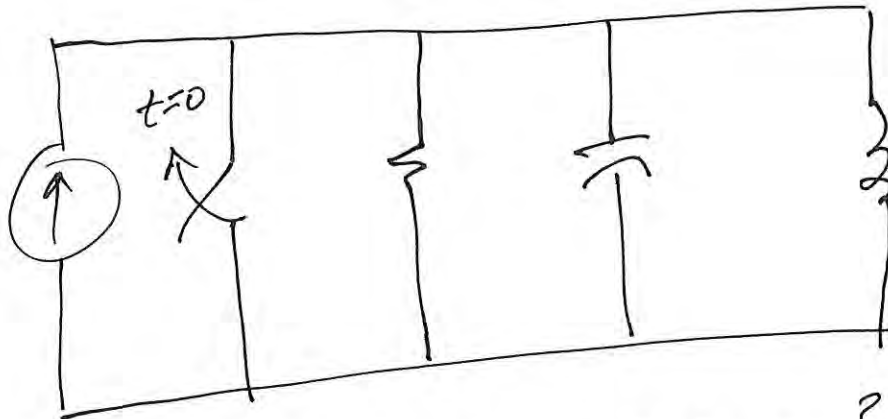


CKT EQUIVALENT ?




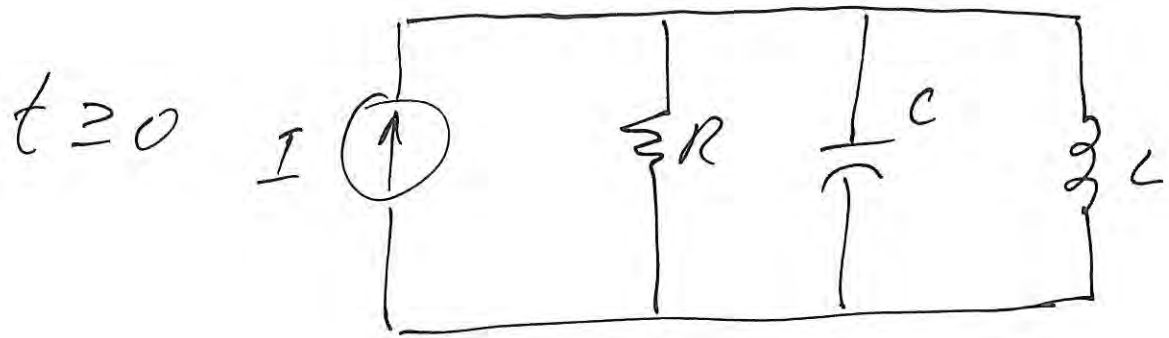



SAME AS

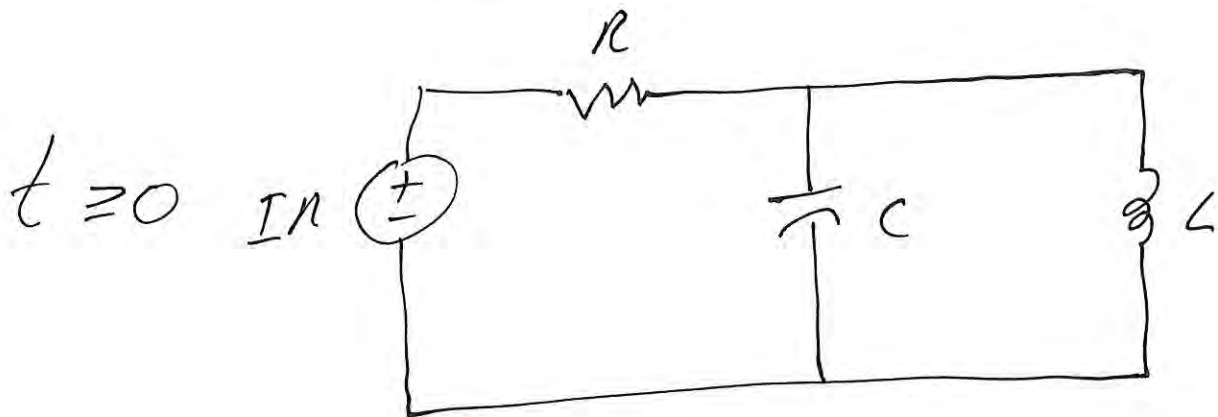

EQUIVALENT PROBLEM

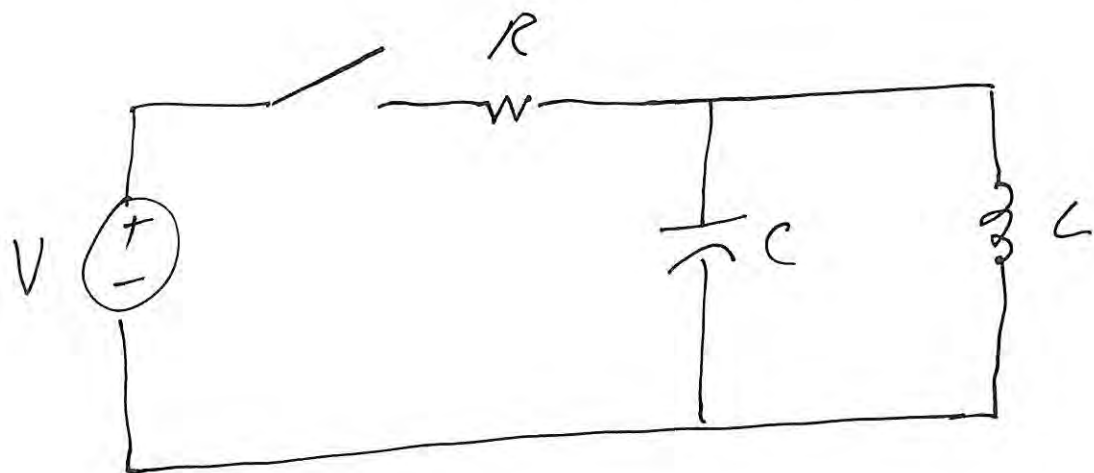

WHAT IS SWITCH OPERATION ?

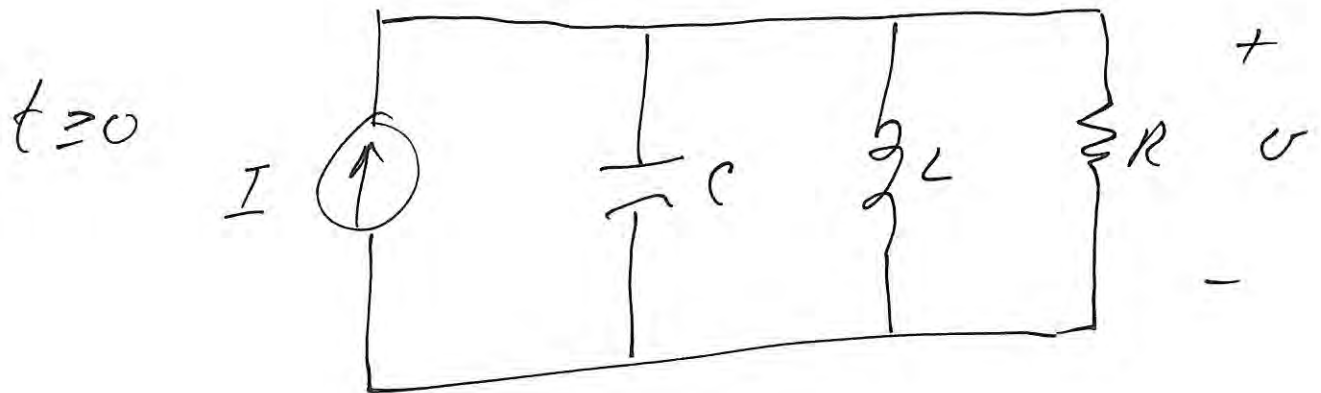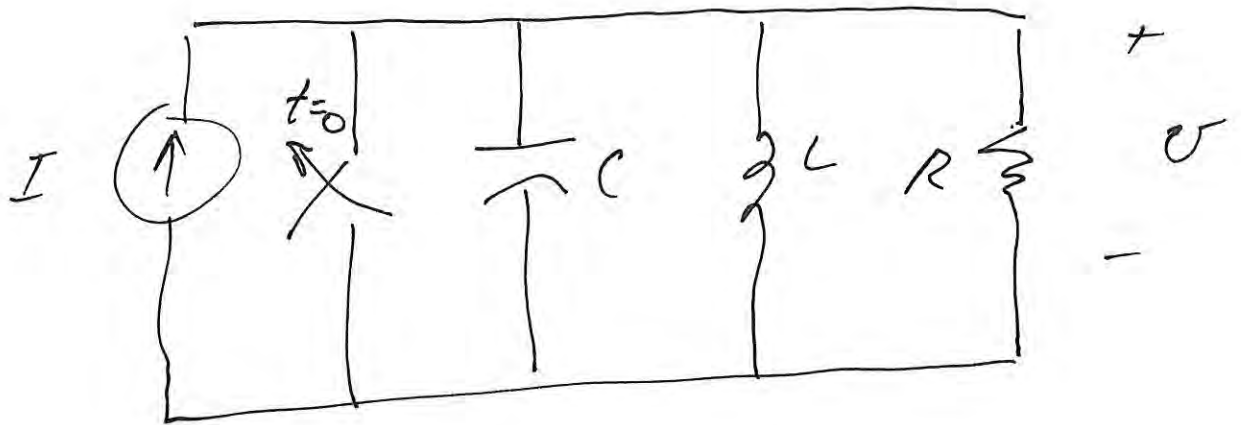

KCL:  $i_L + i_R + i_C = I$

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

RECALL  $v = L \frac{di_L}{dt} \Rightarrow \frac{dv}{dt} = L \frac{d^2 i_L}{dt^2}$

$$i_L + \frac{L}{R} \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} = I$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

NOTE INHOMOGENEOUS D.E.

AS  $t \rightarrow \infty$   $i_L(t) \rightarrow i_L(\infty)$  (CONSTANT)

$\Rightarrow$  AS  $t \rightarrow \infty$   $\frac{di_L}{dt} \rightarrow 0$

$\Rightarrow$  D.E. BECOMES

$$\frac{i_L(\infty)}{LC} = \frac{I}{LC}$$

$$\boxed{i_L(\infty) = I}$$

WHAT DOES THIS IMPLY?


COMPLETE SOLUTION OF D.E. =

HOMOGENEOUS SOLUTION

+

PARTICULAR SOLUTION

NATURAL  
RESPONSE

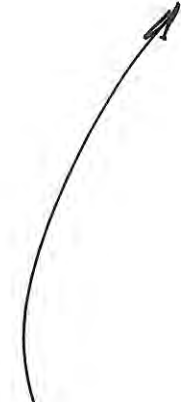

FORCED RESPONSE



WHAT IS THIS FORCED RESPONSE

?

$$i_L(t) = I_f + \text{NATURAL RESPONSE}$$

OVER DAMPED


$$i_L = I_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

UNDER DAMPED

$$i_L = I_f + e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

CRITICALLY DAMPED
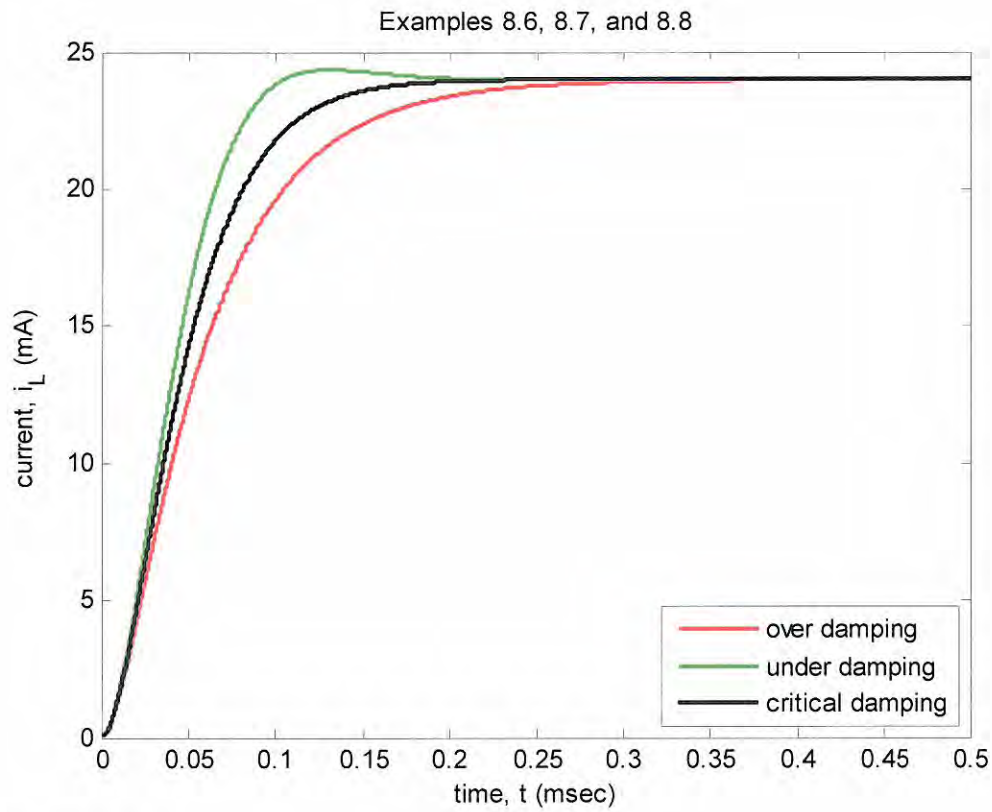
$$i_L = I_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$



over damping

$$i_L(t) = 24 - 32e^{-20,000t} + 8e^{-80,000t} \text{ mA}$$


under damping

$$i_L(t) = 24 - e^{-32,000t} (24 \cos 24,000t + 32 \sin 24,000t) \text{ mA}$$

critical damping

$$i_L(t) = 24 - e^{-40,000t} (960,000t + 24) \text{ mA}$$

Examples 8.6, 8.7, and 8.8

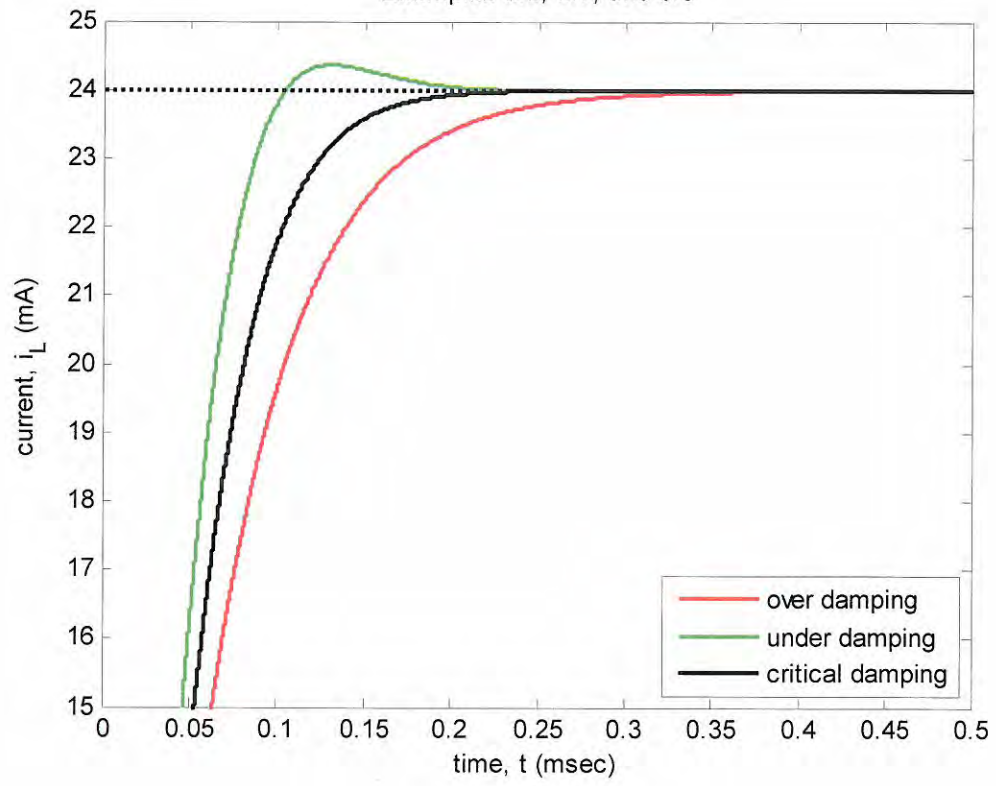

EXAMPLES 8.6 - 8.9 HAVE NO STORED  
ENERGY PRIOR TO  $t=0$


$$\Rightarrow v(0) = 0; \dot{v}_L(0) = 0$$

WHAT'S DIFFERENT FOR INITIAL ENERGY

?



# EXAMPLE 8.10

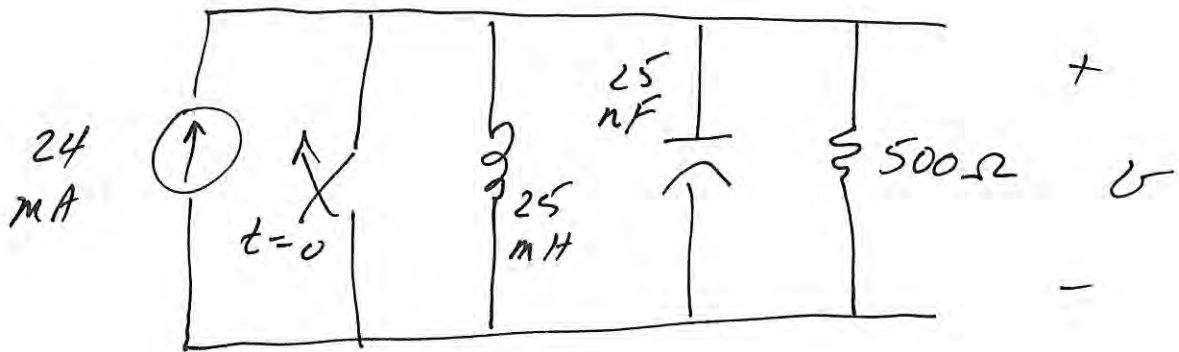

$$i_L(0) = 29 \text{ mA}$$

$$v(0) = 50 \text{ V}$$

$$\frac{1}{2RC} = 40,000$$

$$\frac{1}{\sqrt{LC}} = 40,000$$

∴ CRITICAL DAMPING

⇒ SOLN OF FORM

$$i_L(t) = I_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$\alpha = 40,000 \text{ RAD/S}$$

$$(\alpha = 40,000 \text{ NEPERS/S} \dots)$$

$$I_f = 24 \text{ mA}$$

WHY?

$$\text{INITIAL COND: } i_L(0) = 29 \text{ mA} = I_f + D_L$$

$$\Rightarrow D_L = 29 \text{ mA} - 24 \text{ mA} = 5 \text{ mA}$$

$$\text{INITIAL COND: } v(0) = L \left. \frac{di_L(t)}{dt} \right|_{t=0}$$

WHY?

$$\left. \frac{di_L(t)}{dt} \right|_{t=0} = -\alpha D_L + D_1$$

$$v(0) = 50 = 25 \text{ mH} \left( -40,000 D_L + D_1 \right)$$

$\swarrow$  5 mA

$$D_1 = 2,200 \text{ A/s}$$

$$= 2.2 \times 10^3 \text{ A/s}$$

$$= 2.2 \times 10^6 \text{ mA/s}$$


$$i_L(t) = 24 + e^{-40,000t} (2.2 \times 10^6 t + 5)$$

mA ;  $t \geq 0$

## ASSESSMENT PROBLEM

**Objective 1**—Be able to determine the natural response and the step response of parallel *RLC* circuits

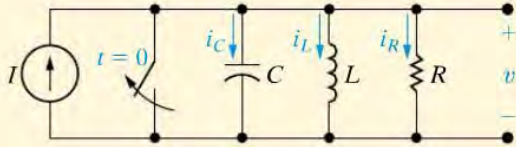
- 8.6** In the circuit shown,  $R = 500 \Omega$ ,  $L = 0.64 \text{ H}$ ,  $C = 1 \mu\text{F}$ , and  $I = -1 \text{ A}$ . The initial voltage drop across the capacitor is  $40 \text{ V}$  and the initial inductor current is  $0.5 \text{ A}$ . Find (a)  $i_R(0^+)$ ; (b)  $i_C(0^+)$ ; (c)  $di_L(0^+)/dt$ ; (d)  $s_1, s_2$ ; (e)  $i_L(t)$  for  $t \geq 0$ ; and (f)  $v(t)$  for  $t \geq 0^+$ .



**NOTE:** Also try Chapter Problems 8.27–8.29.

- Answer:**
- (a)  $80 \text{ mA}$ ;
  - (b)  $-1.58 \text{ A}$ ;
  - (c)  $62.5 \text{ A/s}$ ;
  - (d)  $(-1000 + j750) \text{ rad/s}$ ,  
 $(-1000 - j750) \text{ rad/s}$ ;
  - (e)  $[-1 + e^{-1000t}][1.5 \cos 750t + 2.0833 \sin 750t] \text{ A}$ , for  $t \geq 0$ ;
  - (f)  $e^{-1000t}(40 \cos 750t - 2053.33 \sin 750t) \text{ V}$ , for  $t \geq 0^+$ .

# SERIES RLC CKTS

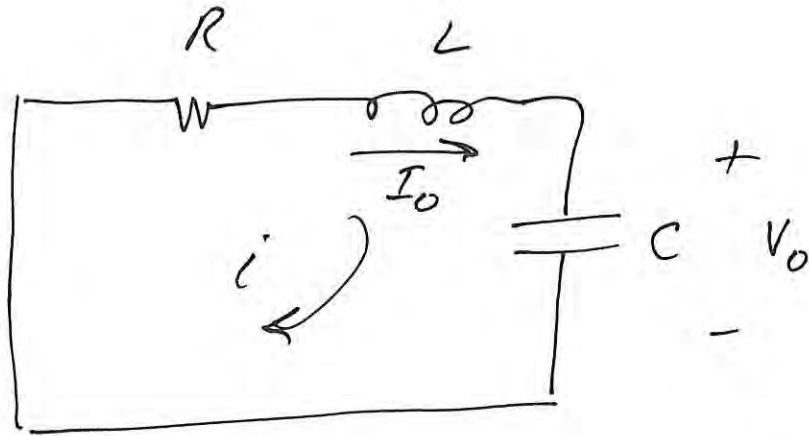

$$\text{KVL: } -iR - L \frac{di}{dt} - \frac{1}{C} \int_0^t i(\tau) d\tau - V_0 = 0$$

$\frac{d}{dt}$  BOTH SIDES:

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

STANDARD APPROACH: HYPOTHESIZE

SOL'N OF FORM  $Ae^{st}$

$$As^2 e^{st} + \frac{R}{L} A s e^{st} + \frac{A e^{st}}{LC} = 0$$

$$A e^{st} \left( s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0$$

$$s_i = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_i = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

DAMPING FACTOR:  $\alpha = \frac{R}{2L}$  RAD/S

(Np/s<sup>2</sup>)

RESONANT FREQ,  $\omega_0 = \frac{1}{\sqrt{LC}}$  RAD/S


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{OVER})$$

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \quad (\text{UNDER})$$

$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \quad (\text{CRITICAL})$$

WHAT TYPE OF RESPONSES  
ARE THESE ?

# STEP RESPONSE

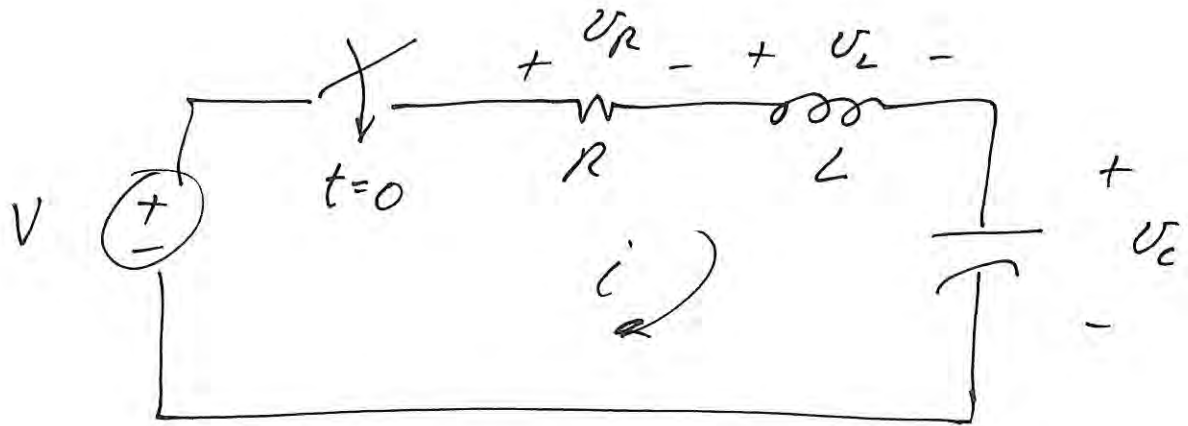

$$\text{KVL: } V - iR - L \frac{di}{dt} - v_C = 0$$

$$\text{RECALL } i = C \frac{dv_C}{dt} \Rightarrow \frac{di}{dt} = C \frac{d^2 v_C}{dt^2}$$

$$V = RC \frac{dv_C}{dt} + LC \frac{d^2 v_C}{dt^2} + v_C$$

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = \frac{V}{LC}$$

WHAT'S DIFFERENT ABOUT  
THIS GENERAL FORM?




## ✓ ASSESSMENT PROBLEMS

**Objective 2**—Be able to determine the natural response and the step response of series *RLC* circuits

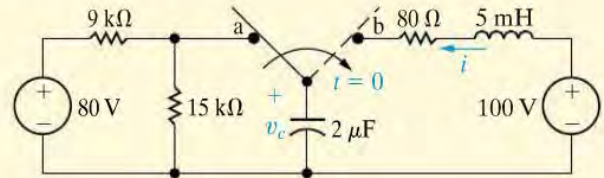**8.7** The switch in the circuit shown has been in position a for a long time. At  $t = 0$ , it moves to position b. Find (a)  $i(0^+)$ ; (b)  $v_C(0^+)$ ; (c)  $di(0^+)/dt$ ; (d)  $s_1, s_2$ ; and (e)  $i(t)$  for  $t \geq 0$ .


**Answer:** (a) 0;  
 (b) 50 V;  
 (c) 10,000 A/s;  
 (d)  $(-8000 + j6000)$  rad/s,  
 $(-8000 - j6000)$  rad/s;  
 (e)  $(1.67e^{-8000t} \sin 6000t)$  A for  $t \geq 0$ .



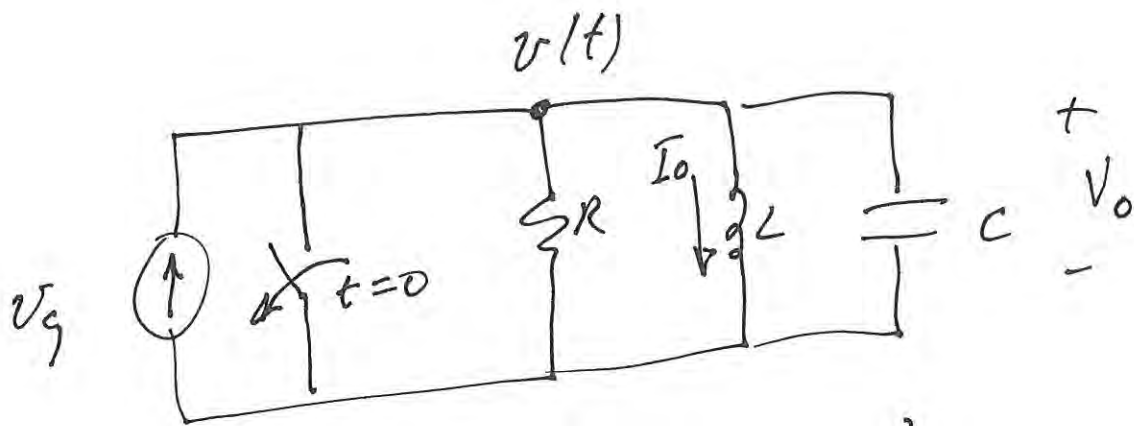**8.8** Find  $v_C(t)$  for  $t \geq 0$  for the circuit in Assessment Problem 8.7.

**Answer:**  $[100 - e^{-8000t}(50 \cos 6000t + 66.67 \sin 6000t)]$  V for  $t \geq 0$ .

*NOTE:* Also try Chapter Problems 8.49–8.51.



TYPE OF RESPONSE?

FORCED + NATURAL

FORM OF NATURAL RESPONSE?

DETERMINE  $s_{1,2}$

LOOKING FOR  $v(t)$ ?

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \text{ (e.g.)}$$

B.C.:  $v(0) = v_0 = A_1 + A_2$

$$i_c(t) = C \frac{dv(t)}{dt}; \quad i_c(0) = C \left. \frac{dv(t)}{dt} \right|_{t=0}$$

K/A KCL:  $i_R(0) + i_L(0) + i_c(0) = 0$

$$i_c(0) = -i_L(0) - i_R(0) = -I_0 - \frac{v_0}{R}$$

LOOKING FOR  $i_L(t)$ ?

$$i_L(t) = \underbrace{I_F}_{\text{FORCED}} + \underbrace{D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}}_{\text{NATURAL}} \quad (\text{e.g.})$$



$$\text{N.C.: } i_L(0) = I_F + D_2 = I_0 \rightarrow D_2 = I_0 - I_F$$

$$v(t) = L \frac{di_L(t)}{dt}$$

$$v(t)|_{t=0} = V_0 = L \left. \frac{di_L(t)}{dt} \right|_{t=0} = L(D_1 - \alpha D_2)$$

$$D_1 = \frac{V_0}{L} + \alpha D_2$$

8.53

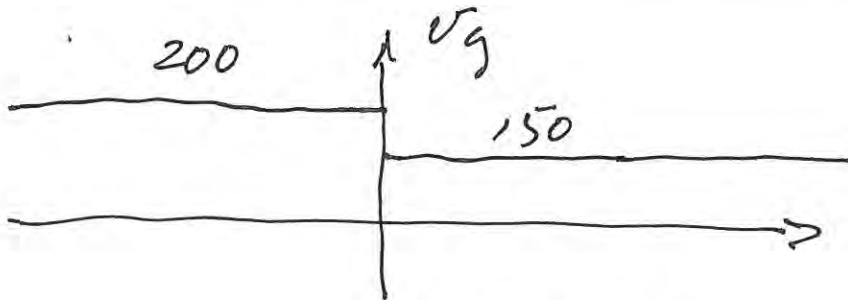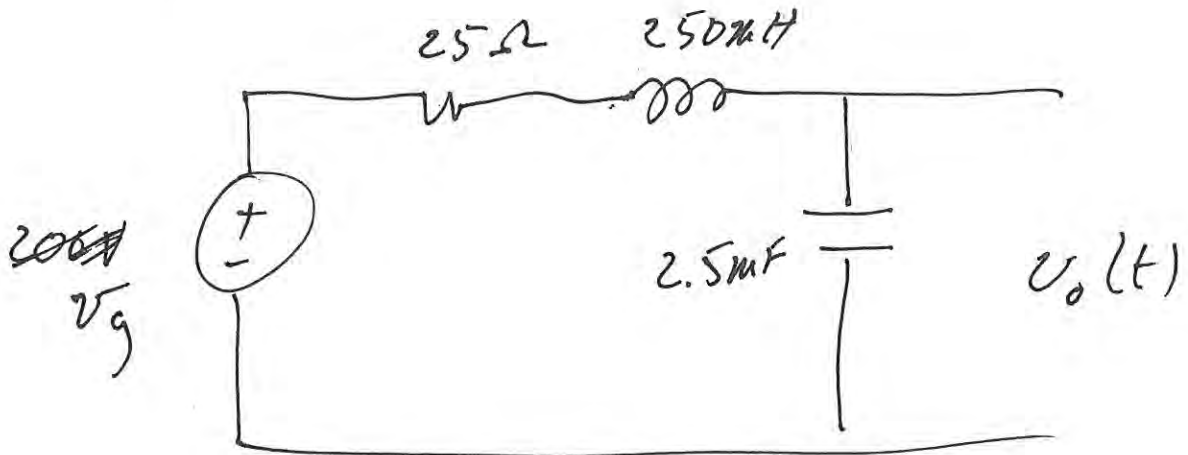

FIND  $v_o(t)$

FOR  $t < 0$ ,  $v_o(t) = v_o(0) = 200 \text{ V}$

FOR  $t \rightarrow \infty$ ,  $v_o(\infty) \rightarrow 150 \text{ V}$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha = 50 \quad \omega_0 = 40$$

$\alpha > \omega_0$   
 ~~$\omega_0 > \alpha$~~   
 0% UNDERDAMPED  
 OVERDAMPED

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_{1,2} = -50 \pm \sqrt{(50)^2 - 140}$$

$$= -50 \pm 30$$

$$= -80, -20$$

$$v_o(t) = 150V + A_1 e^{-80t} + A_2 e^{-20t}$$

$$v_o(0) = 200 = 150 + A_1 + A_2$$

$$\boxed{A_1 + A_2 = 50}$$

$$i(t) = C \frac{dv_o(t)}{dt}$$

$$i(0) = C \frac{dv_o(t)}{dt} \Big|_{t=0} = 0 \quad \text{BECAUSE}$$

LOOP CURRENT  
AT  $t=0$  IS 0  
(INDUCTOR CURRENT  
CANNOT CHANGE

$$C \frac{dv_o}{dt} \Big|_{t=0} = C \left( -80A_1 e^{-80t} - 20A_2 e^{-20t} \right) \Big|_{t=0} = 0 \quad \text{INSTANTANEOUSLY)$$

$$\boxed{-80A_1 - 20A_2 = 0}$$

$$-80A_1$$

$$A_1 + A_2 = 50$$

$$-4A_1 - A_2 = 0$$

---

$$-3A_1 = 50 \rightarrow A_1 = -\frac{50}{3}$$

$$A_2 = 50 - A_1 = 50 + \frac{50}{3}$$

$$= \frac{150 + 50}{3} = \frac{200}{3}$$


$$v_o(t) = 150 - \frac{50}{3}e^{-80t} + \frac{200}{3}e^{-20t}$$

$$\text{check } v_o(t)|_{t=0} = 150 - \frac{50}{3} + \frac{200}{3}$$

$$= 150 + \frac{150}{3} = \frac{450 + 150}{3} = \frac{600}{3}$$

$$= 200 \checkmark$$

# 8.5 TWO OP-AMPS

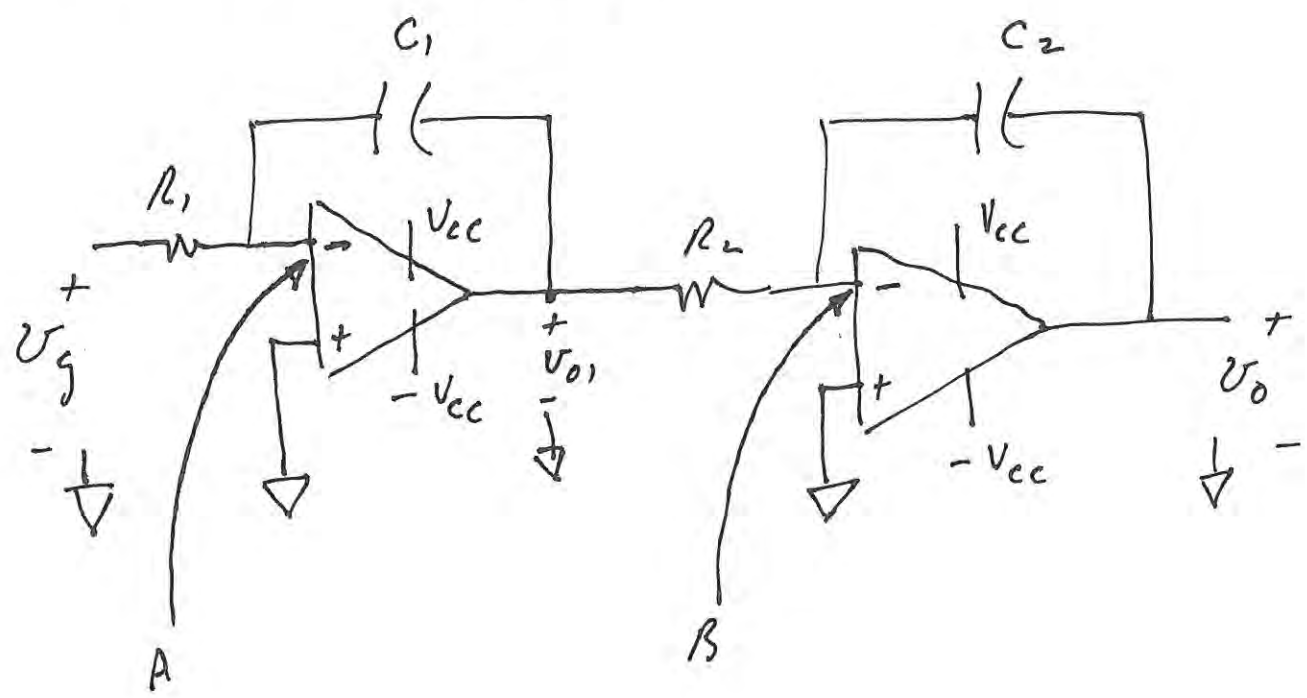

WANT: RELATIONSHIP BETWEEN  $v_o$  &  $v_g$

KCL AT NODE A:

WHY?

$$\frac{(0 - v_g)}{R_1} + C_1 \frac{d}{dt} (0 - v_{o1}) = 0$$

$$\frac{dv_{o1}}{dt} = -\frac{1}{R_1 C_1} v_g$$

WHAT DOES THIS OP-AMP DO?

KCL AT NODE B:

$$\frac{(0 - v_{o1})}{R_2} + C_2 \frac{d}{dt} (0 - v_o) = 0$$

$$\frac{dv_o}{dt} = -\frac{1}{R_2 C_2} v_{o1}$$

$\frac{d}{dt}$  BOTH SIDES:  $\frac{d^2 v_o}{dt^2} = -\frac{1}{R_2 C_2} \frac{dv_{o1}}{dt}$

RECALL EQ FOR FIRST OP-AMP:

$$\frac{dv_{o1}}{dt} = -\frac{1}{R_1 C_1} v_g$$

TOGETHER:  $\frac{d^2 v_o}{dt^2} = \frac{1}{R_1 C_1} \frac{1}{R_2 C_2} v_g$



# EXAMPLE 8.13

$$R_1 = 250 \text{ k}\Omega$$

$$R_2 = 500 \text{ k}\Omega$$

$$V_{CC1} = 5 \text{ V}$$

$$C_1 = 0.1 \mu\text{F}$$

$$C_2 = 1 \mu\text{F}$$

$$V_{CC2} = 9 \text{ V}$$

NO INITIAL ENERGY STORED

$$v_g = \begin{cases} 0; & t = 0^- \\ 25 \text{ mV}; & t = 0^+ \end{cases}$$

a) FIND  $v_o(t)$ ;  $0 \leq t \leq t_{SAT}$

b) FIND TIME TO SATURATION

$$\frac{d^2 v_o}{dt^2} = \underbrace{\left(\frac{1}{R_1 C_1}\right)}_{11} \underbrace{\left(\frac{1}{R_2 C_2}\right)}_{40} \underbrace{(v_g)}_{= 2} = 25 \text{ mV}; t = 0$$

$$\frac{d^2 v_o}{dt^2} = 2 \text{ V/s}^2; t > 0$$

HOW TO SOLVE ?

$$\frac{d^2 v_o}{dt^2} = 2 \text{ V/s}^2$$

INTEGRATE:  $\frac{dv_o}{dt} = 2t + A_1, \text{ V/s}$

INTEGRATE:  $v_o = t^2 + A_1 t + A_2 \text{ V}$

CONSTANTS FROM INITIAL COND'S.

WHAT DO WE KNOW?

VOLTAGE ACROSS A CAP CANNOT CHANGE INSTANTANEOUSLY

$$\Rightarrow \left. \frac{dv_o}{dt} \right|_{t=0} = 0 \Rightarrow (2t + A_1) \Big|_{t=0} = 0$$

$$\therefore A_1 = 0$$

SO WHAT IS  $A_2$  ?

$$v_o(t) = t^2 + v_o(0) \text{ V}$$

BECAUSE NO INITIAL STORED ENERGY,

$$v_o(0) = 0$$

NOTE NUMERICAL CONSTANT

$$v_o(t) = t^2 \text{ V}; 0 \leq t \leq t_{SAT}$$

SATURATION WHEN  $v_o(t) = V_{CC2} = 9\text{V}$

$$\Rightarrow t_{SAT} = 3\text{s}$$

CAN 1<sup>ST</sup> OP-AMP SATURATE SOONER?

RECALL FOR 1<sup>ST</sup> STAGE

$$\frac{dv_{o1}}{dt} = -\left(\frac{1}{R_1 C_1}\right)^{=40} = 25\text{mV/s}; t \geq 0$$

$$\frac{dv_{o1}}{dt} = -1\text{V/s}$$

6

$$\frac{dv_{o1}}{dt} = -1 \text{ V/s}$$

→ = 0


INTEGRATE:  $v_{o1}(t) = -1t + v_{o1}(0) \quad \text{V}$

SECOND OP-AMP SATURATES AT  $t = 3 \text{ s}$

AT THIS POINT  $v_{o1}(t_{\text{SAT}}) = -3 \text{ V}$

(WITHIN  $\pm V_{\text{CC1}}$  o o o k)

# INTEGRATING AMP W FEEDBACK RESISTORS

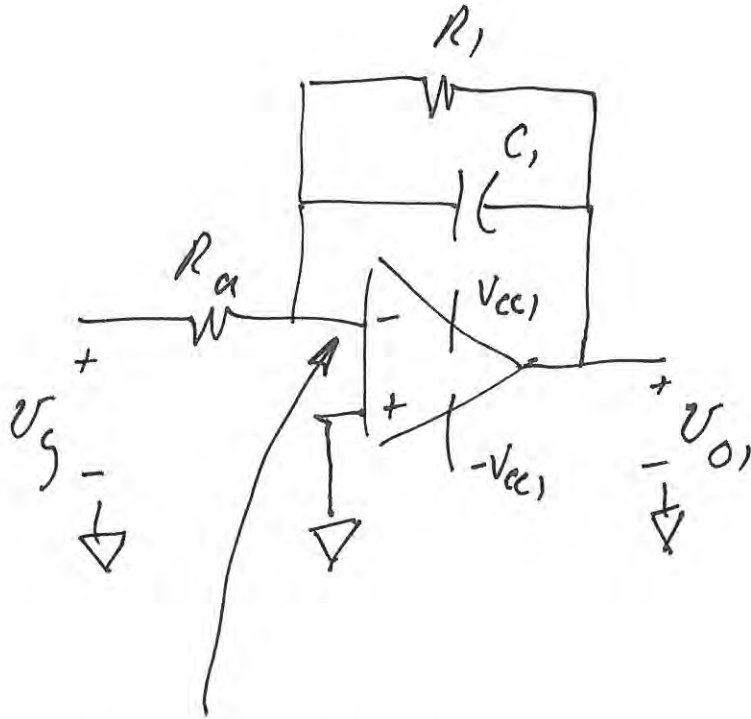

KCL: 
$$\frac{(0 - v_g)}{R_a} + \frac{(0 - v_{o1})}{R_f} + C_f \frac{d}{dt}(0 - v_{o1}) = 0$$


$$\frac{dv_{o1}}{dt} + \frac{1}{R_f C_f} v_{o1} = -\frac{v_g}{R_a C_f}$$

$(\tau_1 = R_f C_f)$

$$\frac{dv_{o1}}{dt} + \frac{v_{o1}}{\tau_1} = -\frac{v_g}{R_a C_f}$$

(I)

### SECOND STAGE

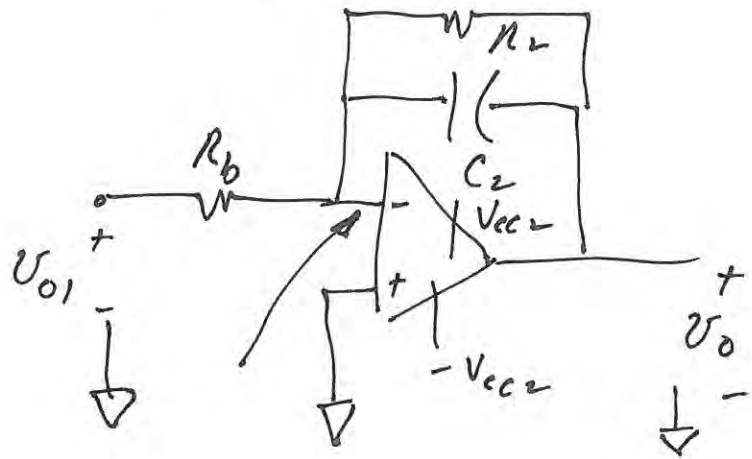

SAME FORM AS PREVIOUS:

$$\frac{dv_0}{dt} + \frac{v_0}{\tau_2} = -\frac{v_{01}}{R_b C_2} \quad \textcircled{\text{II}}$$

$\frac{d}{dt}$  BOTH SIDES:

$$\frac{d^2 v_0}{dt^2} + \frac{1}{\tau_2} \frac{dv_0}{dt} = -\frac{1}{R_b C_2} \frac{dv_{01}}{dt} \quad \textcircled{\text{II}'}$$

WITH  $\textcircled{\text{I}}$  &  $\textcircled{\text{II}'}$  ELIMINATE  $\frac{dv_{01}}{dt}$  &  $v_{01}$

$$\frac{d^2 v_0}{dt^2} + \left( \frac{1}{\tau_1} + \frac{1}{\tau_2} \right) \frac{dv_0}{dt} + \frac{v_0}{\tau_1 \tau_2} = \frac{v_g}{R_a C_1 R_b C_2}$$

DETAILS ON PREVIOUS PAGE

$$\frac{dv_{01}}{dt} + \frac{v_{01}}{\tau_1} = -\frac{v_g}{R_a C_1} \quad \textcircled{I}$$

$$\frac{dv_0}{dt} + \frac{v_0}{\tau_2} = -\frac{v_{01}}{R_b C_2} \quad \textcircled{II}$$

$$\frac{d^2 v_0}{dt^2} + \frac{1}{\tau_2} \frac{dv_0}{dt} = -\frac{1}{R_b C_2} \frac{dv_{01}}{dt} \quad \textcircled{III}$$

COMBINE  $\textcircled{I}$  &  $\textcircled{II}$ , SOLVING FOR  $\frac{dv_{01}}{dt}$

$$\frac{dv_{01}}{dt} + \frac{v_{01}}{\tau_1} = -\frac{v_g}{R_a C_1} - R_b C_2 \left( \frac{dv_0}{dt} + \frac{v_0}{\tau_2} \right)$$

$$\frac{dv_{01}}{dt} = \frac{R_b C_2}{\tau_1} \left( \frac{dv_0}{dt} + \frac{v_0}{\tau_2} \right) - \frac{v_g}{R_a C_1}$$

SUB INTO RHS OF  $\textcircled{III}$

$$\frac{d^2 v_0}{dt^2} + \frac{1}{\tau_2} \frac{dv_0}{dt} = -\frac{1}{R_b C_2} \left[ \frac{R_b C_2}{\tau_1} \left( \frac{dv_0}{dt} + \frac{v_0}{\tau_2} \right) - \frac{v_g}{R_a C_1} \right]$$

$$\frac{d^2 v_0}{dt^2} + \left( \frac{1}{\tau_1} + \frac{1}{\tau_2} \right) \frac{dv_0}{dt} + \frac{v_0}{\tau_1 \tau_2} = \frac{v_g}{R_a R_b C_1 C_2}$$

(9)

USE ESTABLISHED SOLUTION APPROACH

HYPOTHESIZE SOL'N. OF FORM

$$v_0 = Ae^{st}$$

D.E. BECOMES (HOMOGENEOUS FORM)

$$As^2 e^{st} + As\left(\frac{1}{\tau_1} + \frac{1}{\tau_2}\right)e^{st} + \frac{1}{\tau_1 \tau_2} Ae^{st} = 0$$

$$Ae^{st} \left[ s^2 + s\left(\frac{1}{\tau_1} + \frac{1}{\tau_2}\right) + \frac{1}{\tau_1 \tau_2} \right] = 0$$

CHARACTERISTIC EQ.

$$\text{ROOTS: } s_1 = -1/\tau_1 ; s_2 = -1/\tau_2$$

$$v_0 = A_1 e^{-t/\tau_1} + A_2 e^{-t/\tau_2} \text{ (IF DISTINCT)}$$

$$v_0 = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \text{ (IF NOT DISTINCT)}$$



## EXAMPLE 8.14

$$R_a = 100 \text{ k}\Omega$$

$$R_b = 25 \text{ k}\Omega$$

$$R_1 = 500 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

$$C_1 = 0.1 \mu\text{F}$$

$$C_2 = 1 \mu\text{F}$$

$$V_{\text{cc}} = \pm 6 \text{ V}$$

$$v_g = \begin{cases} 0 & ; t = 0^- \\ 250 \text{ mV} & ; t = 0^+ \end{cases}$$

NO STORED ENERGY AT  $t < 0$

$$\frac{d^2 v_o}{dt^2} + \left( \frac{1}{\tau_1} + \frac{1}{\tau_2} \right) \frac{dv_o}{dt} + \frac{v_o}{\tau_1 \tau_2} = \frac{v_g}{R_a C_1 R_b C_2}$$

$$\frac{d^2 v_o}{dt^2} + (20 + 10) \frac{dv_o}{dt} + (20)(10) v_o = 1000 \text{ V/s}^2$$

$$s_i = -1/\tau_i \quad ; \quad s_1 = -20 \text{ RAD/S}$$

$$s_2 = -10 \text{ RAD/S}$$

$$\frac{d^2 v_o}{dt^2} + 30 \frac{dv_o}{dt} + 200 v_o = 1000$$

As  $t \rightarrow \infty$   $v_o(t) \rightarrow v_o(\infty)$  (CONSTANT)

$$\Rightarrow \left. \frac{dv_o(t)}{dt} \right|_{t \rightarrow \infty} = 0$$

$$\circ \circ \quad 200 v_o(\infty) = 1000 \rightarrow v_o(\infty) = 5 \text{ V}$$

$$v_o(t) = 5 + A_1 e^{-20t} + A_2 e^{-10t}$$

INITIAL CONDS:  $v_o(0) = 5 + A_1 + A_2 = 0$

$$\left. \frac{dv_o}{dt} \right|_{t=0} = -20A_1 - 10A_2 = 0$$

INITIAL COND'S. GIVE

$$A_1 = 5 \text{ V}, A_2 = -10 \text{ V}$$

$$v_o(t) = 5(1 + e^{-20t}) - 10e^{-10t} \text{ V}; t \geq 0$$

RECALL D.E. FOR 1<sup>ST</sup> STAGE

$$\frac{dv_{o1}}{dt} + \frac{v_{o1}}{\tau_1} = -\frac{v_s}{R_a C_1}$$

$$\frac{dv_{o1}}{dt} + v_{o1}20 = 25 \text{ V/s}$$

SOLUTION?

STANDARD APPROACH FOR HOMOGENEOUS D.E.

$$v_{o1} = A e^{st}$$

$$A s e^{st} + 20 A e^{st} = 0$$

$$A e^{st}(s + 20) = 0 \Rightarrow s = -20 \text{ RAD/S}$$

FURTHER, AS  $t \rightarrow \infty$   $v_{o1}(t) \rightarrow v_{o1}(\infty)$  (CONST)

$$\Rightarrow \left. \frac{dv_{o1}}{dt} \right|_{t \rightarrow \infty} = 0$$

FOR  $t \rightarrow \infty$ , D.E. IS  $20v_{o1}(\infty) = -25$

$$v_{o1}(\infty) = -1.25V$$

$$v_{o1}(t) = Ae^{-20t} - 1.25V$$

KNOW  $v_{o1}(0) = 0 = A - 1.25$


$$\therefore v_{o1}(t) = 1.25(e^{-20t} - 1) V; t \geq 0$$

304 Natural and Step Responses of RLC Circuits

**8.64** The circuit in Fig. P8.63(b) is modified by adding a  $1\text{ M}\Omega$  resistor in parallel with the  $500\text{ nF}$  capacitor and a  $5\text{ M}\Omega$  resistor in parallel with the  $200\text{ nF}$  capacitor. As in Problem 8.63, there is no energy stored in the capacitors at the time the signal is applied. Derive the numerical expressions for  $v_o(t)$  and  $v_{o1}(t)$  for the time intervals  $0 \leq t \leq 0.5\text{ s}$  and  $t \geq 0.5\text{ s}$ .

PSPICE  
MULTISIM

Figure P8.63

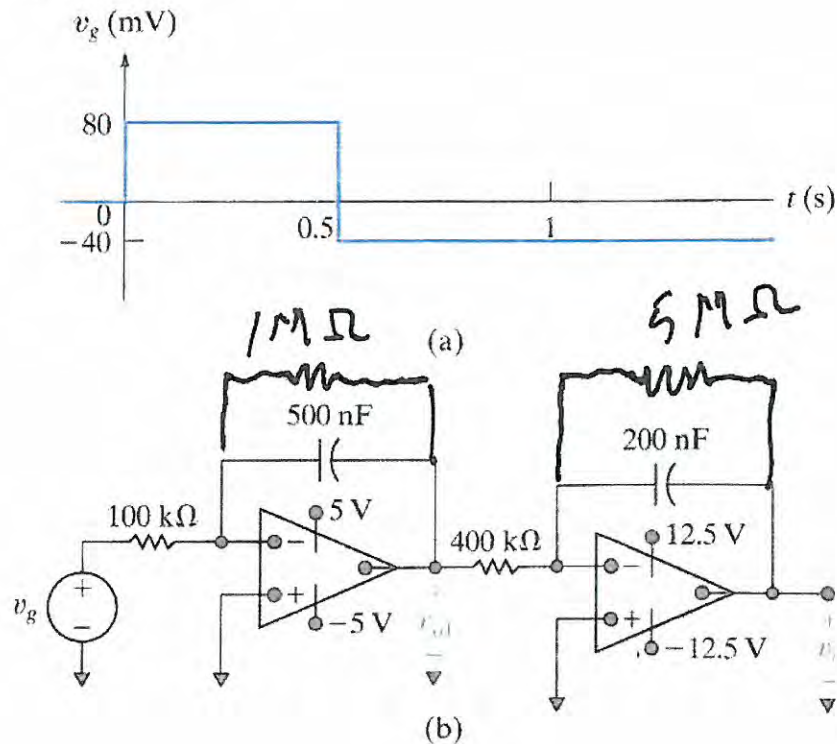

ESTABLISH D.E.

$$\frac{d^2 v_o}{dt^2} + \left( \frac{1}{\tau_1} + \frac{1}{\tau_2} \right) \frac{dv_o}{dt} + \frac{v_o}{\tau_1 \tau_2} = \frac{v_s}{R_a C_1 R_b C_2}$$

CALCULATE CONSTANTS

DETERMINE STEADY STATE SOL'N

DETERMINE NATURAL RESPONSE

APPLY INITIAL COND'S.

$$\left( v_o(0), \frac{dv_o(0)}{dt} \right)$$

~~SOL'N~~ SOL'N FOR  $t \geq 0$

DETERMINE 2<sup>ND</sup> FORCING FCN

AT TIME  $t_{sw}$

FIRST STEP SOL'N AT  $t_{sw}$  FOR

INITIAL CONDS.

$\Rightarrow$  SOL'N FOR  $t > t_{sw}$

$$\tau_1 = (1M\Omega)(500nF) = 0.5 \text{ SEC}$$

$$\tau_2 = (5M\Omega)(200nF) = 1.0 \text{ SEC}$$

$$R_a = 100k\Omega$$

$$R_b = 400k\Omega$$

$$C_1 = 500nF$$

$$C_2 = 200nF$$

$$R_a C_1, R_b C_2 = 0.004$$

D.E. IS

$$\frac{d^2 v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2v_o = 250v_g$$

STEADY STATE SOLUTION IS SUCH THAT

$$\frac{v_o(\infty)}{C_1 \tau_1} = \frac{v_g}{R_a C_1, R_b C_2}$$

$$\text{OR } v_o(\infty) = \frac{R_b C_1, R_a C_2}{R_a C_1, R_b C_2} v_g$$

$$v_o(\infty) = \frac{R_1 R_2}{R_a R_b} v_g = 125 v_g$$

COMPLETE SOL'N =

STEADY STATE SOL'N + NATURAL RESP

NATURAL RESPONSE IS SOLUTION TO HOMOGENEOUS EQ

$$\frac{d^2 v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2v_o = 0$$

HYPOTHESIZE SOL'N  $v_o(t) = A e^{st}$

D.E. BECOMES

$$A s^2 e^{st} + 3A s e^{st} + 2A e^{st} = 0$$

$$A e^{st} (s^2 + 3s + 2) = 0$$

$$s_i = \frac{-3 \pm \sqrt{9-8}}{2} = \frac{-3 \pm 1}{2}$$

$$s_i = -2, -1 \quad (\text{OVERDAMPED})$$

$$v_o(t) = v_F + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



- DIGRESSION -

WE ALSO NEED  $v_{o1}(t)$ :

$$\frac{dv_{o1}}{dt} + \frac{v_{o1}}{\tau_1} = -\frac{v_g}{R_a C_1}$$

STEADY STATE SOL'N SUCH THAT

$$\frac{v_{o1}(\infty)}{\tau_1} = -\frac{v_g}{R_a C_1} \rightarrow v_{o1}(\infty) = -\frac{R_1}{R_a} v_g$$

$$v_{o1}(\infty) = -10v_g$$

SOLUTION FORM IS


$$v_{o1}(t) = v_{o1}(\infty) + A e^{-\tau_1 t}$$

INITIAL CONDITION IS  $v_{o1}(0) = 0$

(VOLTAGE ACROSS CAP.  
CANNOT CHANGE INSTANTANEOUSLY)

$$v_{o1}(t) = -10v_g + 10v_g e^{-2t}$$
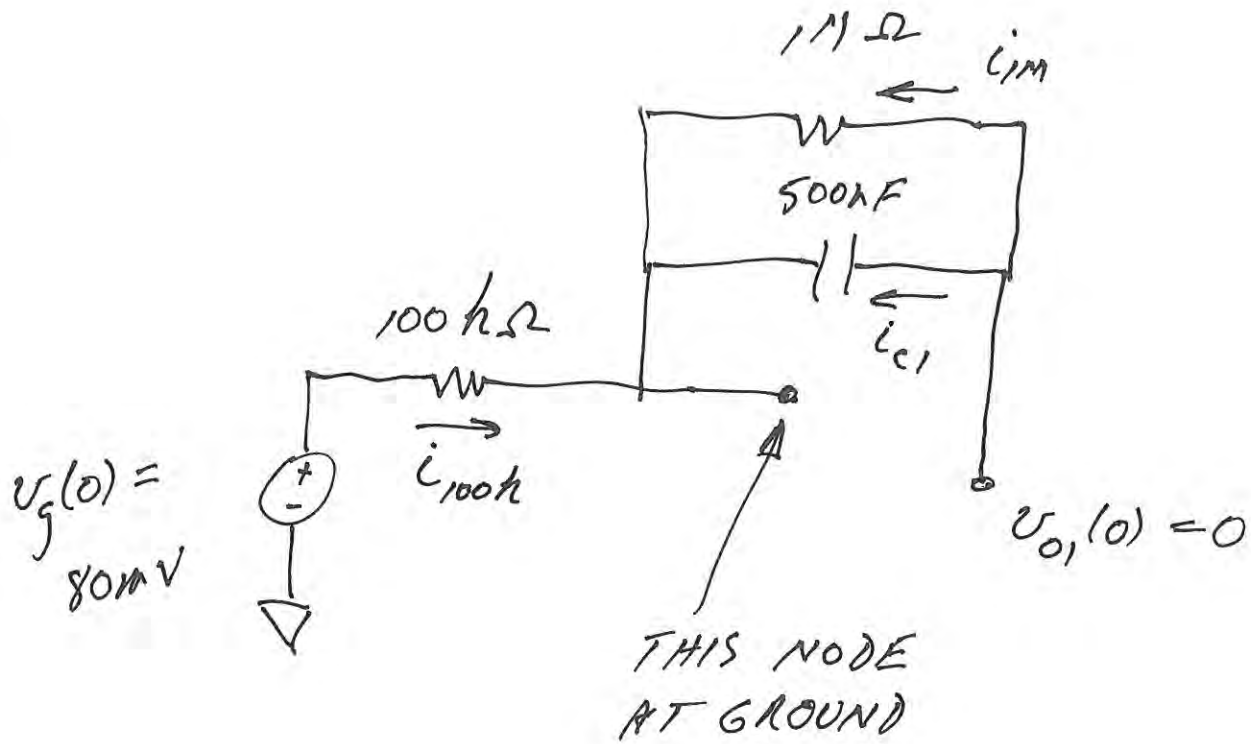
$$\frac{dv_{o1}(t)}{dt} = -20v_g e^{-2t}$$



OBSVIOUSLY  $i_{1M} = \frac{0V}{1M\Omega} = 0$

$$i_{c1}(0) = C \left. \frac{dv_{o1}(t)}{dt} \right|_{t=0}$$

$$= (500\text{nF})(-20)(80\text{mV}) = -0.8\mu\text{A}$$

$$i_{100k}(0) = \frac{80\text{mV}}{100k\Omega} = 0.8\mu\text{A}$$

CURRENTS CHECK ✓

— END DIGRESSION —

$$v_o(t) = 125v_g + A_1 e^{-2t} + A_2 e^{-t}$$


INITIAL COND:

- ①  $v_o(0) = 125v_g + A_1 + A_2 = 0$  (NO INITIAL ENERGY, VOLTAGE ACROSS CAPACITOR CANNOT CHANGE INSTANTANEOUSLY)

WE NEED ANOTHER EQUATION FOR SECOND UNKNOWN: HAS TO BE

$$c_2 \left. \frac{dv_o(t)}{dt} \right|_{t=0}$$

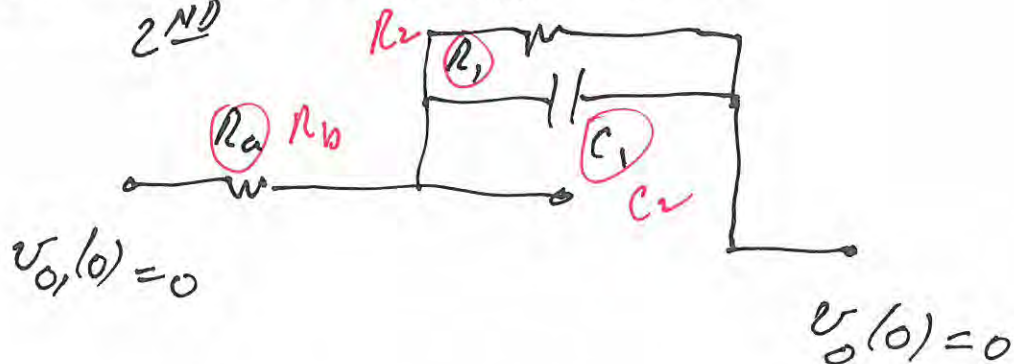~~1ST~~  
INSPECT ~~1ST~~ STAGE AT  $t=0$   
2ND



NO CURRENT FLOWS THROUGH FEEDBACK CKT AT  $t=0$

$$\therefore c_2 \left. \frac{dv_o(t)}{dt} \right|_{t=0} = 0$$

$$\left. \frac{dv_o(t)}{dt} \right|_{t=0} = \left. -2A_1 e^{-2t} - A_2 e^{-t} \right|_{t=0}$$

$$(2) \quad -2A_1 - A_2 = 0$$

WITH EQ'S (1) & (2),

$$A_1 = 125V_5$$

$$A_2 = -250V_5$$

$$v_o(t) = 125V_5 + 125V_5 e^{-2t} - 250V_5 e^{-t}; t \geq 0$$

$$v_{o1}(t) = -10V_5 + 10V_5 e^{-2t}; t \geq 0$$

NOW FOR  $0 \leq t \leq 0.5s$ ,  $V_5 = 80mV$

$$v_o(t) = 10 + 10e^{-2t} - 20e^{-t} \text{ V}; 0 \leq t \leq 0.5s$$

$$v_{o1}(t) = -0.8 + 0.8e^{-2t} \text{ V}; 0 \leq t \leq 0.5s$$

AT  $t=0.5$ , THE SOURCE IS SWITCHED TO

$$v_s = -40\text{mV}$$

THE ABOVE SOLUTIONS EVALUATED AT  $t=0.5$  BECOME THE INITIAL CONDITIONS FOR THE SOLUTIONS OF THE SAME FORM

$$v_o(t) \Big|_{t=0.5} = 10 + 10e^{-1} - 20e^{-0.5} \\ = 1.5482\text{V}$$

$$v_o(t) = v_o(\infty) + A_1 e^{-2(t-0.5)} + A_2 e^{-(t-0.5)}$$

$$\text{RECALL } v_o(\infty) = 125 v_s$$

$$\text{NOW } v_s = -40\text{mV} \Rightarrow v_o(\infty) = -5\text{V}$$

INITIAL CONDITION IS


$$v_o(t) \Big|_{t=0.5} = -5 + A_1 + A_2 = 1.5482\text{V} \quad (3)$$

AGAIN, WE NEED A 2<sup>ND</sup> EQ :

$$C_2 \frac{dv_o(t)}{dt} \Big|_{t=0.5} = C_2(-2A_1, -A_2) = i_{C_2}(0.5)$$

NEED TO DETERMINE  $i_{c2}$  AT  $t = 0.5$   
 INSPECT 2<sup>ND</sup> STAGE AT  $t = 0.5$

NOTE  $v_{o1}(0.5) = -0.8 + 0.8e^{-1}$

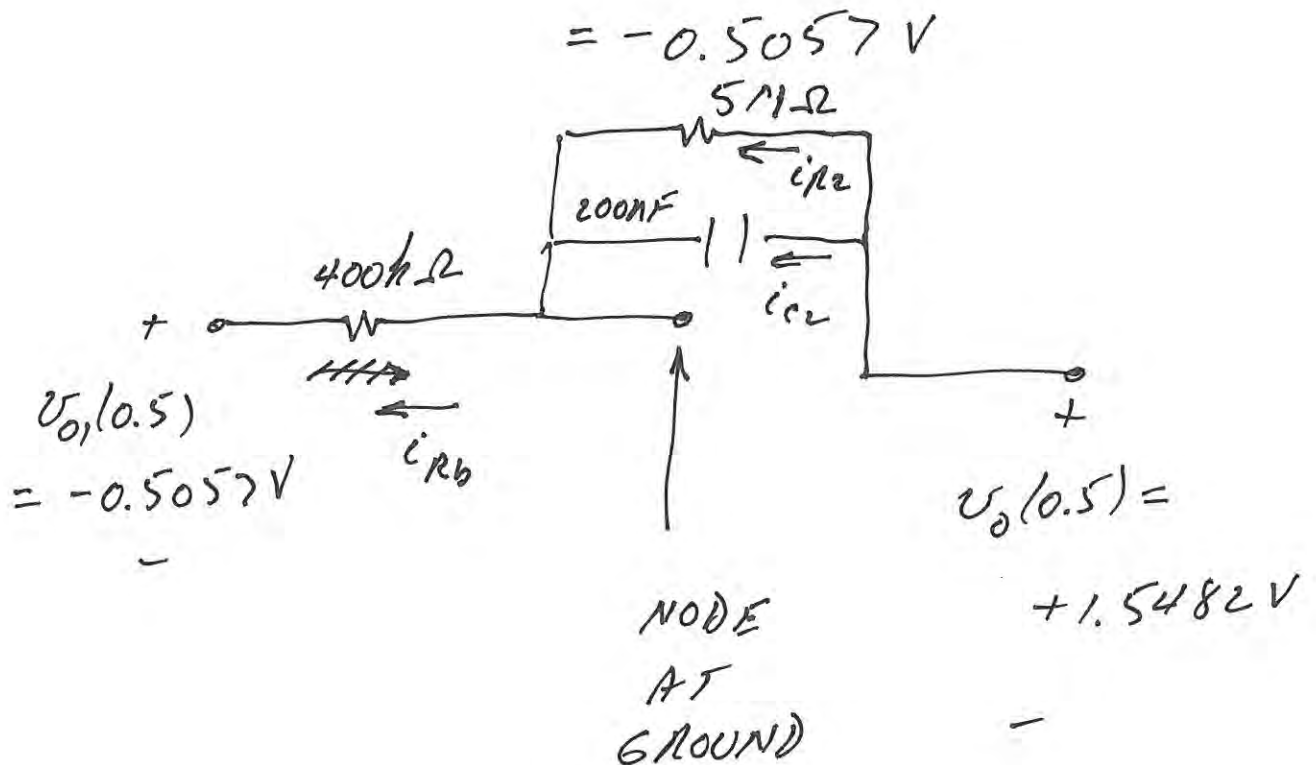

$$i_{R2}(0.5) = \frac{1.5482V}{511\Omega} = 0.30964\mu A$$

$$i_{Rb}(0.5) = \frac{0.5057V}{400k\Omega} = 1.2643\mu A$$

$$i_{c2}(0.5) = i_{Rb}(0) - i_{R2}(0.5) = 0.9546\mu A$$

2<sup>ND</sup> EQUATION IS

$$C_2(-2A_1, -A_2) = i_{C_2}(0.5)$$

$$-2A_1, -A_2 = \frac{0.9546 \mu A}{200 \mu F}$$

(4)

$$-2A_1, -A_2 = 4.7731$$

EQUATIONS (3) & (4) GIVE

$$A_1 = -11.3211 V$$


$$A_2 = 17.8691 V$$

$$v_o(t) = -5 - 11.3211 e^{-2(t-0.5)} + 17.8691 e^{-(t-0.5)} V$$


$$0.5 \leq t < \infty$$
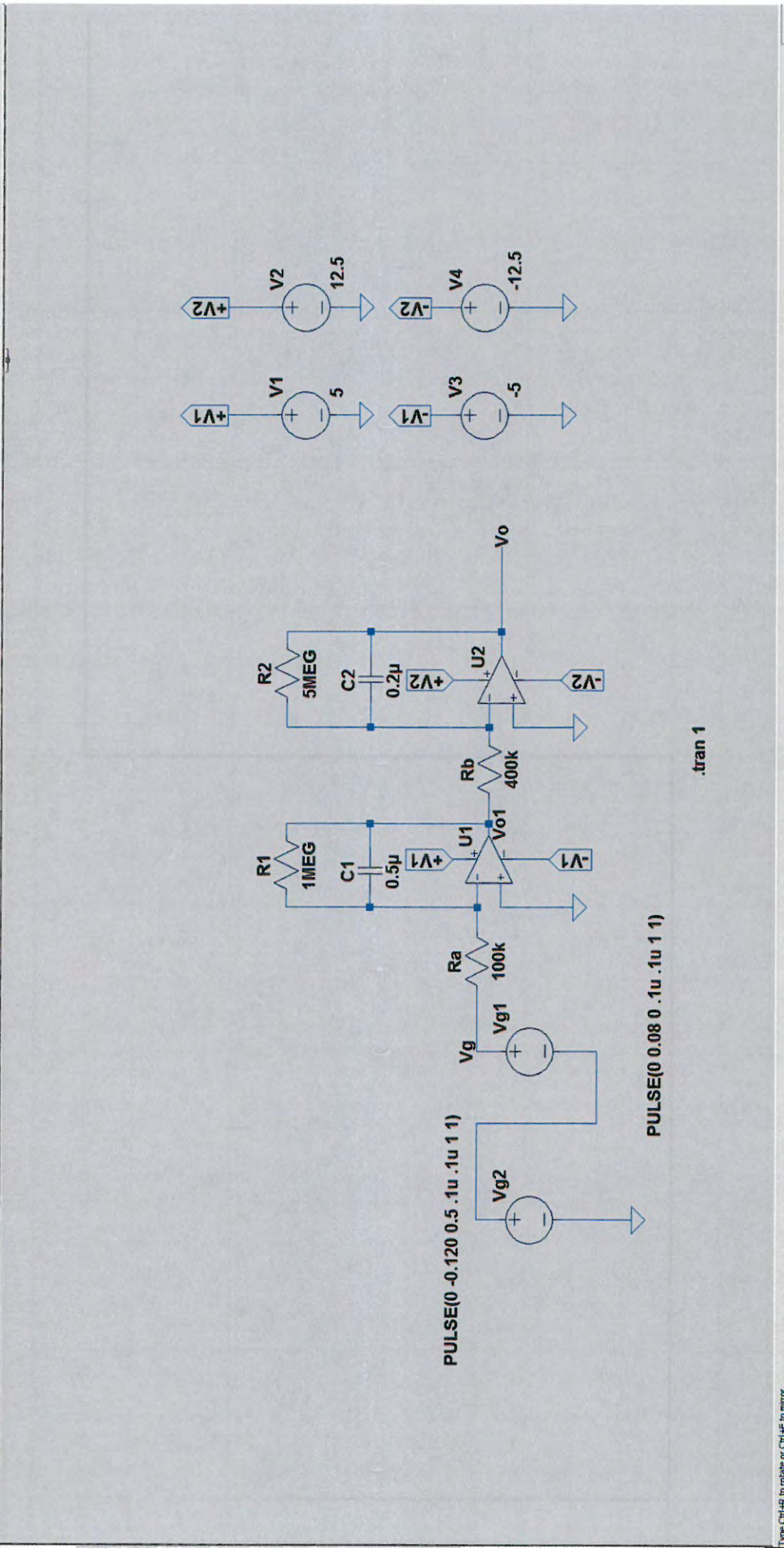
# Problem 8.64, 9<sup>th</sup> edition


LTSpice IV - [problem\_8\_64\_9ed.lvs]  
 File Edit Hierarchy View Simulate Tools Window Help  
 problem\_8\_64\_9ed.asy problem\_8\_64\_9ed.raw






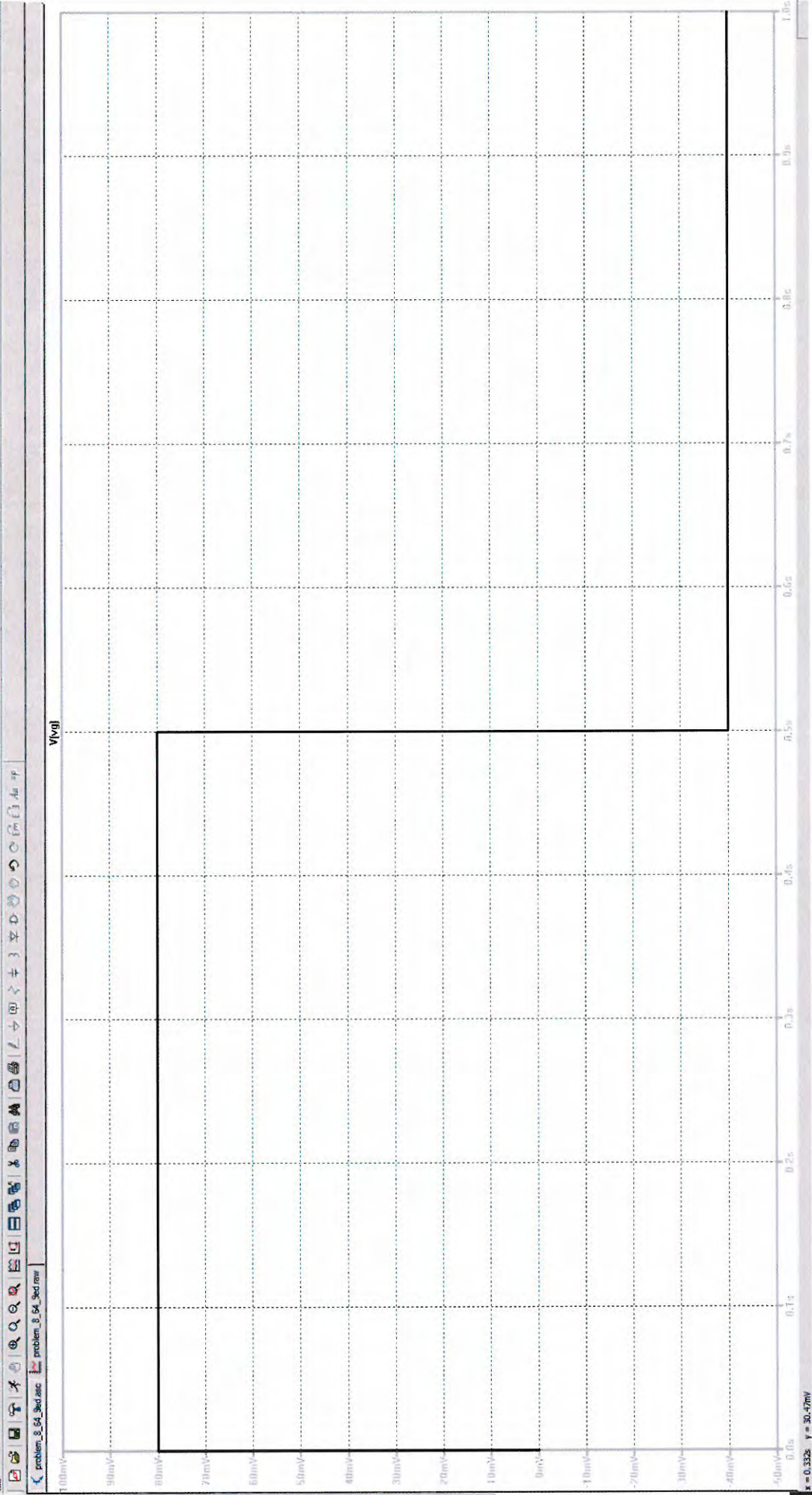

Source waveform

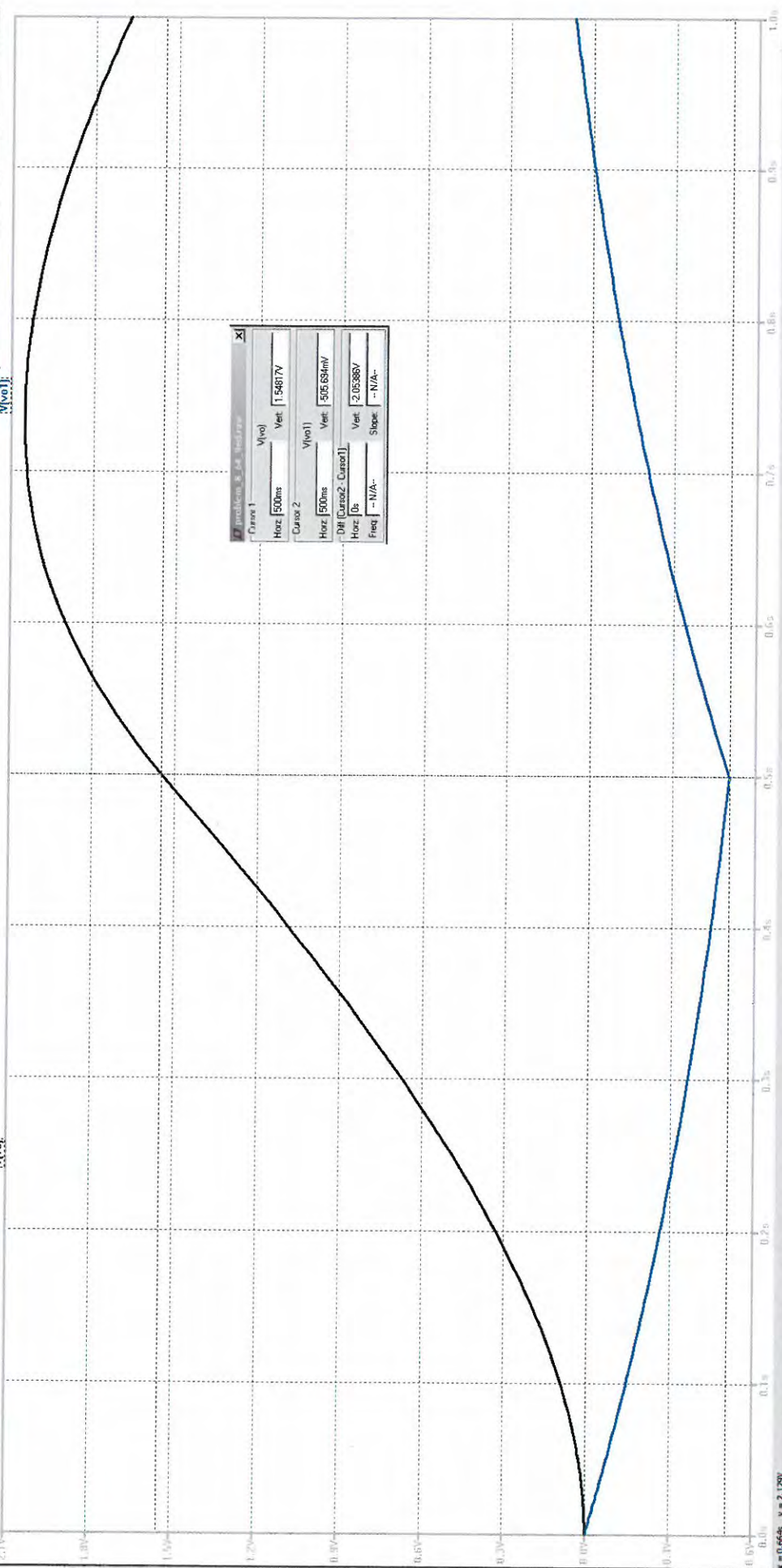


Total solution for stages 1 and 2

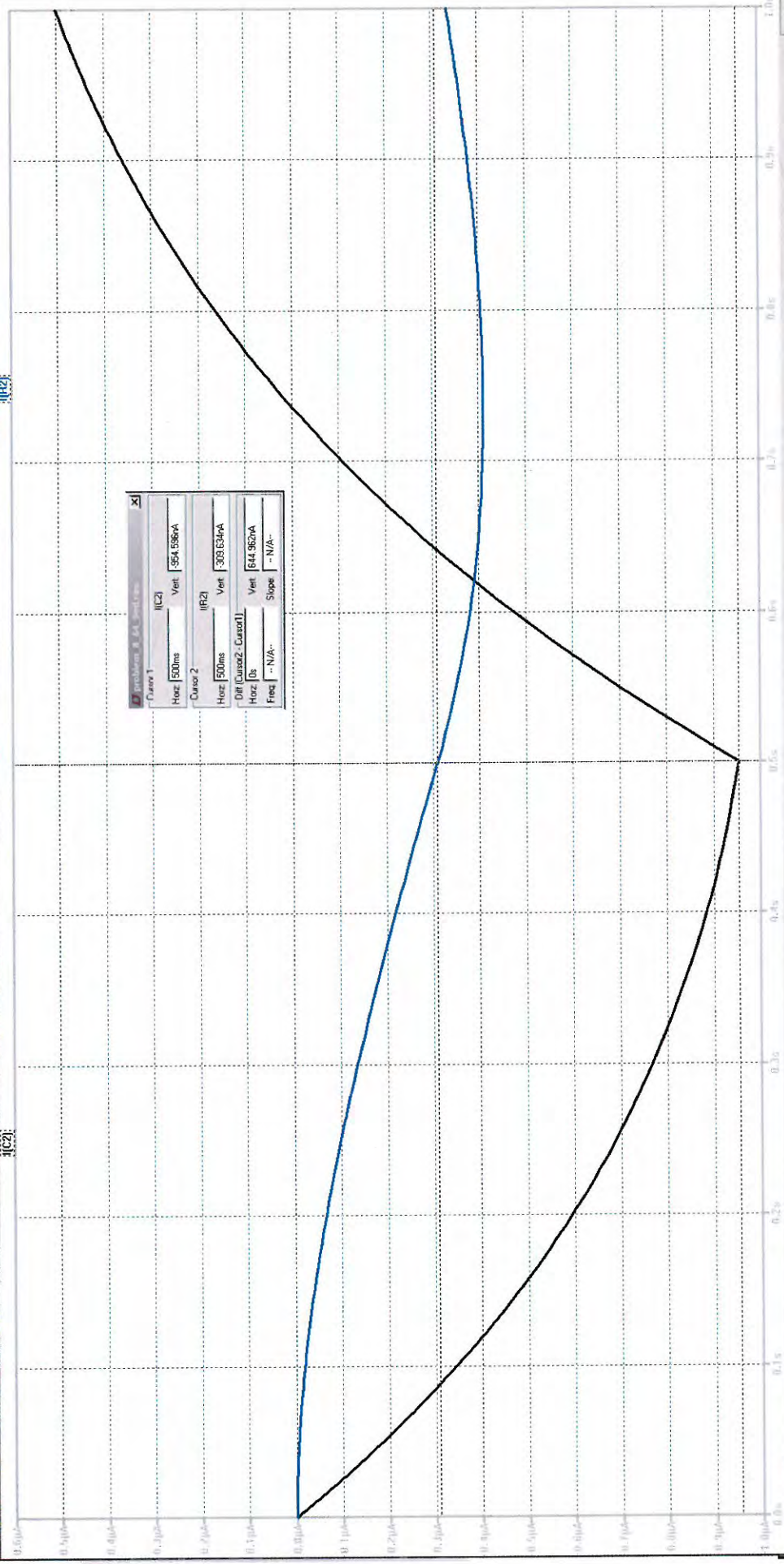

I = 0.512u V = 0.513uA

Feedback currents in stage 2

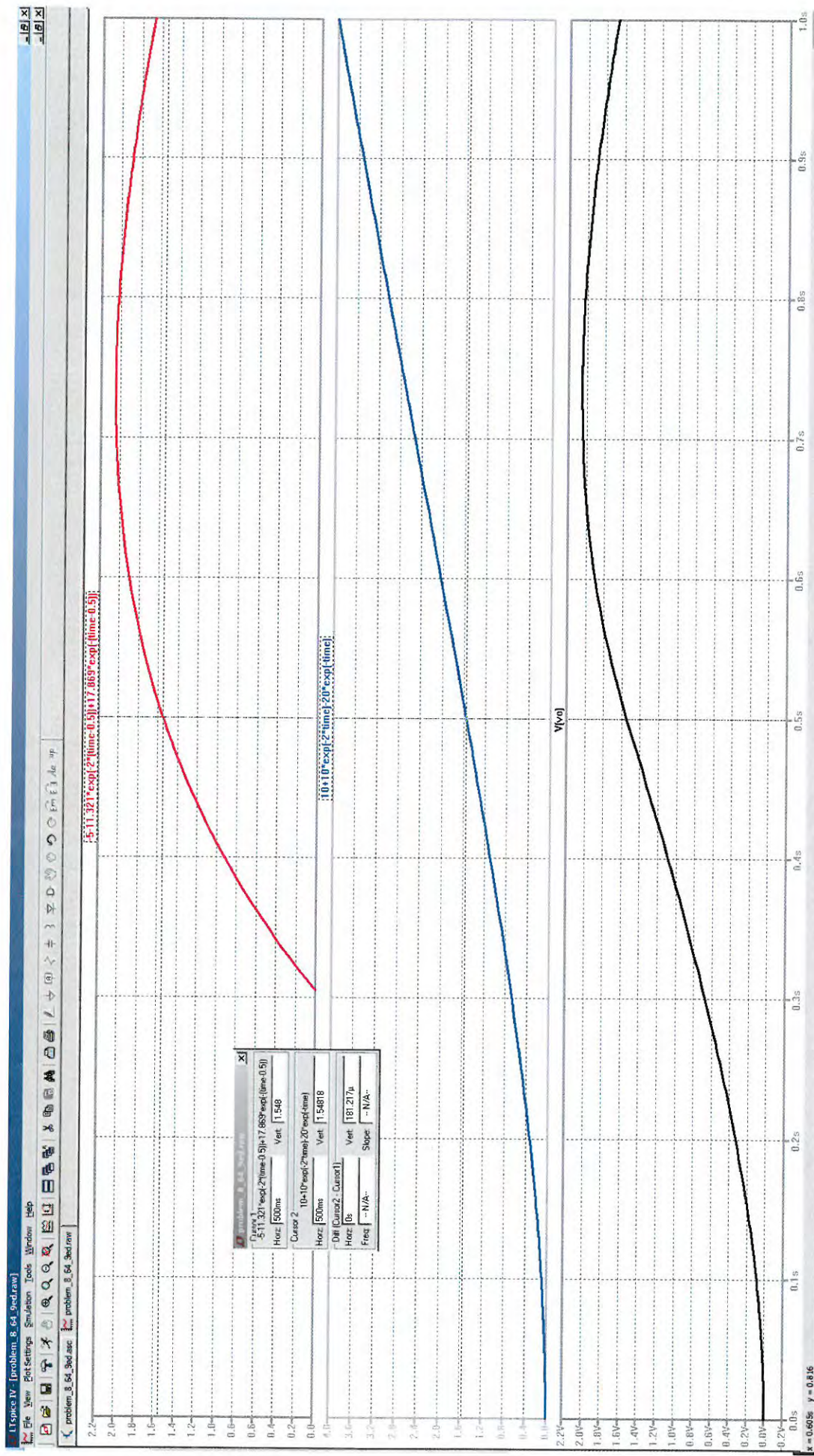

Total solution (bottom), solution for  $t > 0.5$  (top) and for  $0 < t < 0.5$  (middle)



