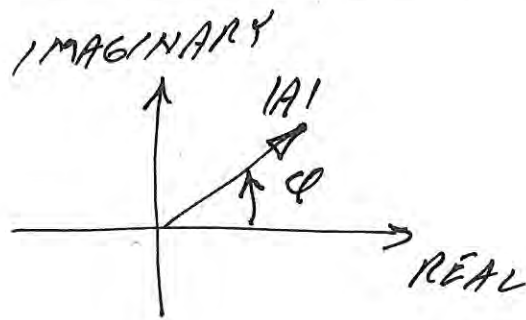


PHASORS

WE REPRESENT A POINT IN THE COMPLEX PLANE AS A VECTOR




THIS VECTOR HAS REAL & IMAGINARY COMPONENTS

$$A = A_r + jA_i$$

$$A^* = A_r - jA_i$$

EQUIVALENTLY WE CAN WRITE

$$A = |A| e^{j\phi} ; \phi = \tan^{-1} \left[\frac{\text{Im}(A)}{\text{Re}(A)} \right]$$

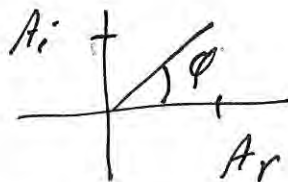


$$\begin{aligned} |A| &= \sqrt{A \cdot A^*} \\ &= \sqrt{A_r^2 + A_i^2} \end{aligned}$$

THIS EQUIVALENCE CAN BE SEEN
USING EULER'S IDENTITY

$$|A|e^{j\phi} = \sqrt{A_r^2 + A_i^2} (\cos\phi + j\sin\phi)$$

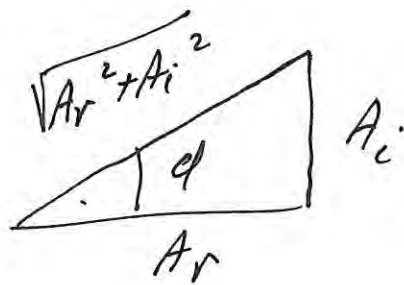BUT WHAT IS $\cos\phi = \cos(\tan^{-1} A_i/A_r)$?



$$\cos\phi = \frac{A_r}{\sqrt{A_r^2 + A_i^2}}$$

$$\sin\phi = \frac{A_i}{\sqrt{A_r^2 + A_i^2}}$$

$$\therefore |A|e^{j\phi} = \sqrt{A_r^2 + A_i^2} \left(\frac{A_r}{\sqrt{A_r^2 + A_i^2}} + j \frac{A_i}{\sqrt{A_r^2 + A_i^2}} \right)$$

$$= A_r + jA_i$$

Q.E.D.

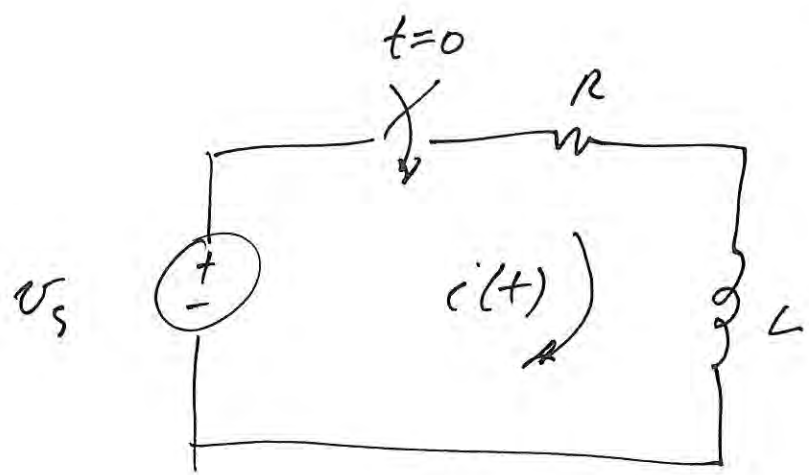


FIG 9.5

KVL AFTER SWITCH IS THROWN

$$v_s - Ri(t) - L \frac{di(t)}{dt} = 0$$

HERE $v_s = V_m \cos(\omega t + \phi)$

D.E. IS $Ri(t) + L \frac{di(t)}{dt} = V_m \cos(\omega t + \phi)$

SINCE SWITCHED, KNOW SOL'N OF FORM

$i(t) = i_h(t) + i_p(t)$

← HOMOGENEOUS SOL'N.

← PARTICULAR SOL'N.

KNOW: $i_h(t) = Ae^{-t/\tau}$, $\tau = L/R$

IN PAST PROBLEMS i_p WAS CONST. WHY?

HERE THE PARTICULAR SOL'N IS A FUNCTION OF TIME. WHY?

WE KNOW PARTICULAR SOL'N HAS GENERAL FORM OF FORCING FUNCTION.

DOES THIS SUGGEST $i_p(t) = K \cos(\omega t + \phi)$?

EASIER WAY

$$i_p(t) = \text{Re} \left\{ B e^{j(\omega t + \phi)} \right\}$$

↑
CAN BE COMPLEX

APPROACH: IGNORE $\text{Re}\{\dots\}$ BUT TAKE REAL PART OF FINAL ANSWER.

$$\text{LET } i_p(t) = B e^{j(\omega t + \phi)}$$

WHEN ALL DONE WITH ALGEBRAIC MANIPULATIONS, KEEP ONLY REAL PART

$$\text{USE } i_p(t) = B e^{j(\omega t + \phi)} \quad (3)$$

IN D.E.:


$$R B e^{j(\omega t + \phi)} + L j \omega B e^{j(\omega t + \phi)} = V_m e^{j(\omega t + \phi)}$$

$$B (R + j \omega L) e^{j(\omega t + \phi)} = V_m e^{j(\omega t + \phi)}$$

$$[B(R + j \omega L) - V_m] e^{j(\omega t + \phi)} = 0$$

$$\therefore B = \frac{V_m}{R + j \omega L} \quad (\text{NOTE COMPLEX})$$


WRITE $B = |B| e^{-j\theta}$, FIND $|B|, \theta$

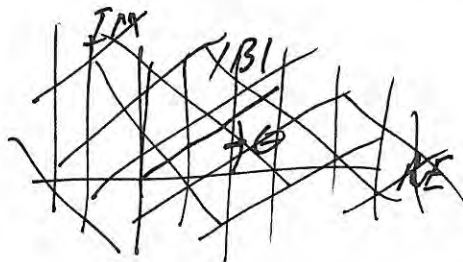

$$B = \frac{V_m}{R + j \omega L} \frac{R - j \omega L}{R - j \omega L} = V_m \frac{(R - j \omega L)}{R^2 + (\omega L)^2}$$

$$= \frac{V_m \sqrt{R^2 + (\omega L)^2} e^{-j\theta}}{R^2 + (\omega L)^2} = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} e^{-j\theta}$$

(4)

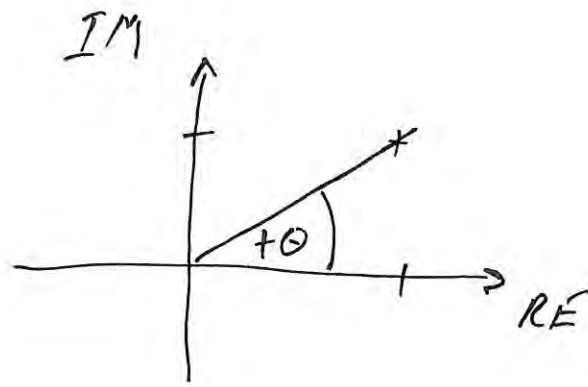

$$+\theta = \text{TAN}^{-1} \frac{\omega L}{R}$$

$$i_p(t) = \text{Re} \left\{ B e^{j(\omega t + \varphi)} \right\}$$

$$= \text{Re} \left\{ \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} e^{-j\theta} e^{j(\omega t + \varphi)} \right\}$$

$$i_p(t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \varphi - \theta)$$

$$i(t) = i_h(t) + i_p(t)$$

$$= A e^{-t/\tau} + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \varphi - \theta)$$

$$i(0) = 0 = A + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\varphi - \theta)$$

5

$$i(t) = \frac{-V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\phi - \theta) e^{-t/\tau}$$


$$+ \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \phi - \theta)$$

$$B = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} e^{-j\theta}, \quad \theta = \tan^{-1} \frac{\omega L}{R}$$

CAN YOU SHOW THIS IS EQUAL TO

$$\frac{V_m}{R + j\omega L} \quad ?$$

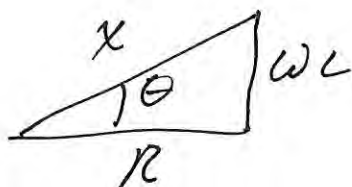USE $e^{-j\theta} = \cos\theta - j\sin\theta$




FIND x

①

SINUSOIDAL SOURCES



$$v(t) = V_m \cos(\omega t)$$

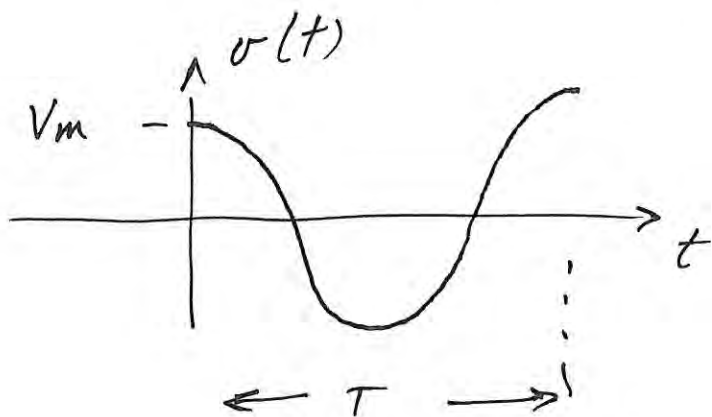


$$T = \text{PERIOD} : v(t) = V_m \cos(2\pi f t)$$

$$T = 1/f : v(t) = V_m \cos(2\pi \frac{t}{T})$$

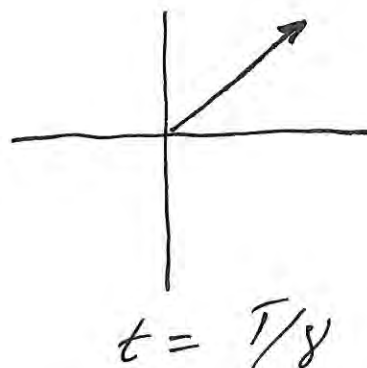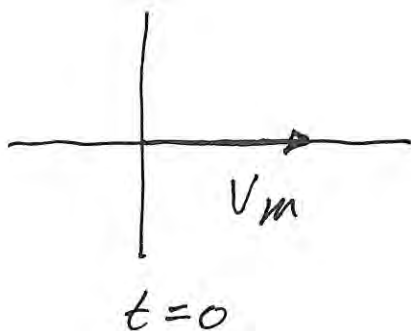WHEN t GOES THROUGH A TIME EQUAL TO PERIOD, PHASE CHANGES BY 2π RADIANS OR 360°




(2)

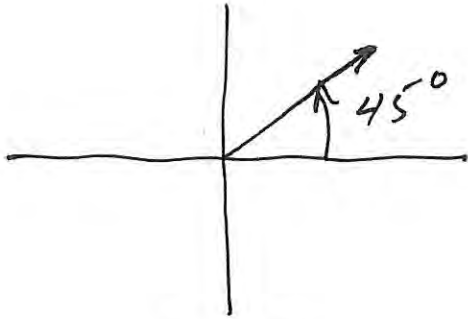

$$\frac{T}{8} \times \frac{360^\circ}{T} = 45^\circ$$

$$t = T/8$$

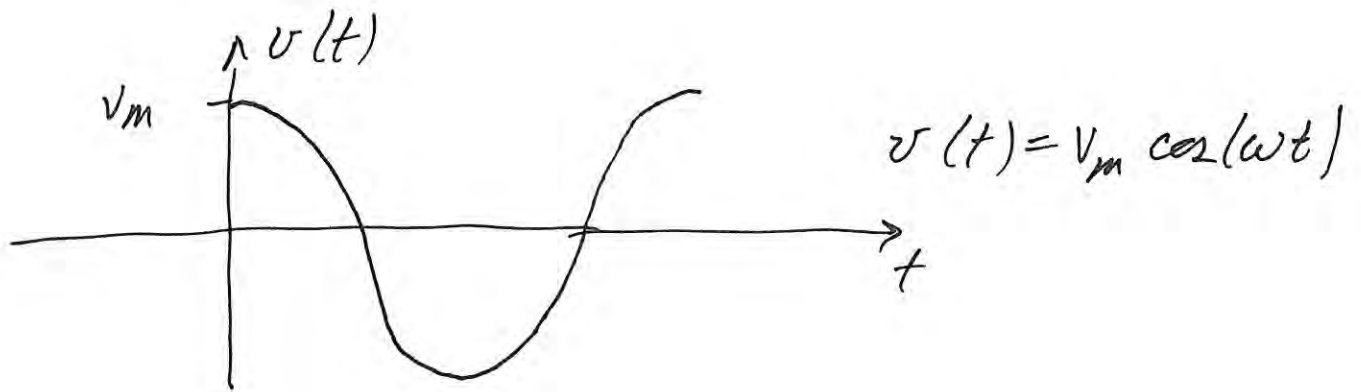

WHERE IS $v(t) = v_m$ (MAX VALUE)

ANS: AT $t = 0$

(ACTUALLY WHEN ARGUMENT

OF COS IS ZERO

$\cos(\dots)$)

(3)

WHAT IF WE ADD A PHASE?

$$v(t) = v_m \cos(\omega t + \phi)$$

WHERE IS MAX?

ANS: WHERE $\omega t + \phi = 0$

$$\text{OR } t = \frac{-\phi}{\omega} = \frac{-\phi}{2\pi f} = \frac{-\phi}{2\pi} T$$

WITH $[\phi] = \text{RADIAN}$, $[T] = \text{SEC}$,

$$[t] = \text{SEC}$$

WHAT IF ϕ IS IN DEGREES?, ϕ°



ANS: MAX IS AT $t = \frac{-\phi^\circ}{360} T$

NOTE SIGN ON t

⇒ ADDING PHASE SHIFTS WAVEFORM
TO THE LEFT

SAY $v(t) = V_m \sin(\omega t)$

HOW DO WE REPRESENT THIS AS A COS?

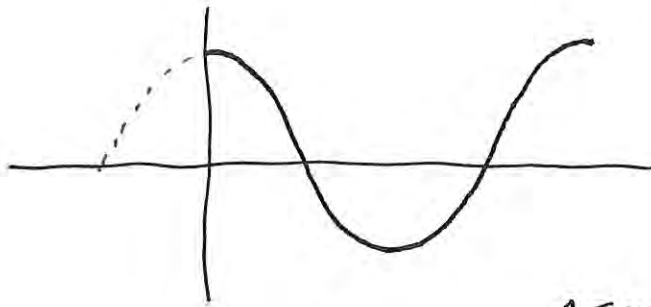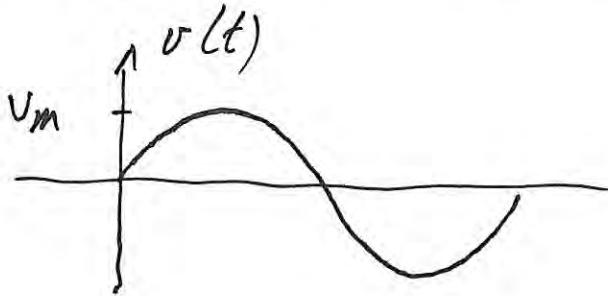

$$V_m \cos(\omega t)$$

REMEMBER: SUBTRACTING
PHASE SHIFTS TO THE
RIGHT

HOW FAR DO WE NEED TO SHIFT

$$V_m \cos(\omega t)$$

TO THE RIGHT TO MAKE IT
LOOK LIKE $V_m \sin(\omega t)$?

ANS: 90°

$$\therefore V_m \sin(\omega t) = V_m \cos(\omega t - 90^\circ)$$

5

CONCLUSION: GIVEN A SIGNAL


$$V_m \sin(\omega t + \theta)$$

WE CAN WRITE THIS AS THE
EQUIVALENT COSINE

$$V_m \cos(\omega t + \theta - 90^\circ)$$

WHERE MIGHT WE MAKE
USE OF THIS TRANSLATION

?

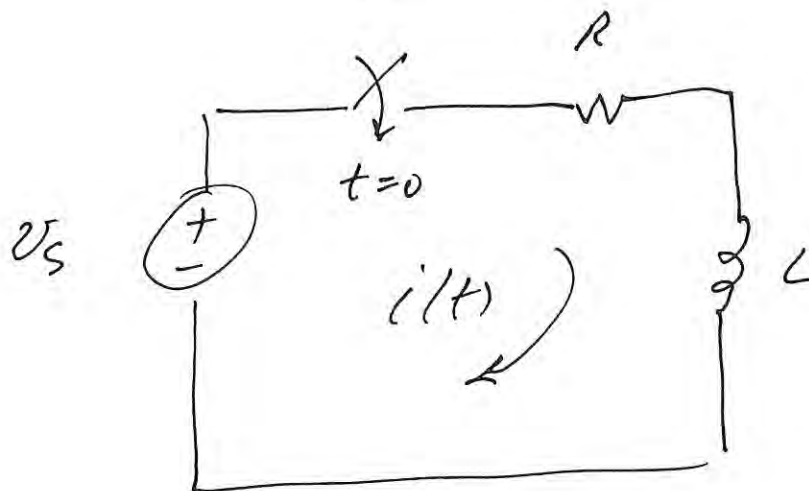

WHAT IF $v_s = V_m \sin(\omega t + \theta)$?

RMS VALUES

$$V_{RMS} = \left\{ \frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt \right\}^{1/2}$$

$$= \left\{ \frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt \right\}^{1/2}$$

NOTE INTEGRATION OVER PERIOD



THIS DEF VALID FOR ANY t_0

$$V_{RMS} = \left\{ \frac{1}{T} V_m^2 \frac{T}{2} \right\}^{1/2}$$

$$V_{RMS} = V_m / \sqrt{2}$$

ONLY FOR SINUSOIDS!

FOOTNOTE

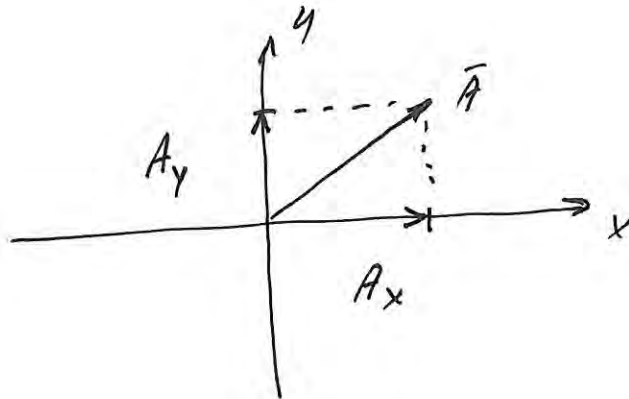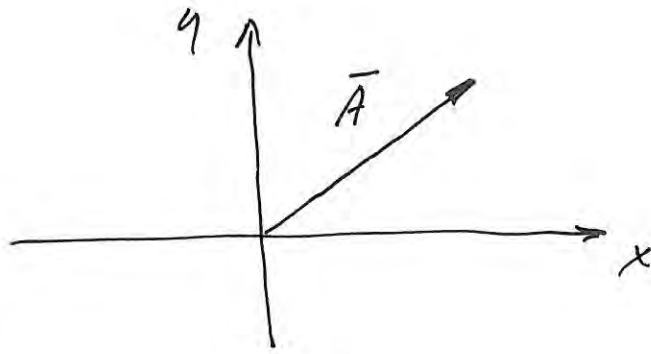


$$\bar{A} = \hat{x} A_x + \hat{y} A_y \quad (\hat{x}, \hat{y}) \text{ UNIT VECTORS}$$

CARTESIAN

CAN ALSO CONSIDER POLAR FORM

$$\bar{A} = |\bar{A}| \angle \theta \quad ; \quad \theta = \tan^{-1}(A_y/A_x)$$

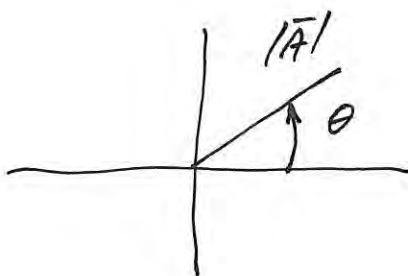


PHASORS... AGAIN

$$V_r + j V_i = \sqrt{V_r^2 + V_i^2} e^{j\theta}$$

$$\theta = \text{TAN}^{-1}(V_i/V_r)$$

CARTESIAN
FORM

POLAR
FORM

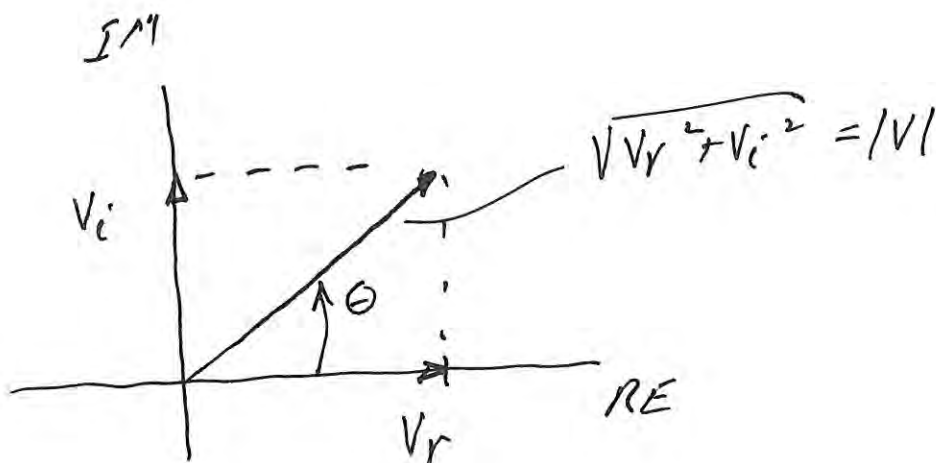

EULER'S IDENTITY $e^{j\theta} = \cos\theta + j\sin\theta$

$$|V| e^{j\theta} = |V| \cos\theta + j|V| \sin\theta$$

$$= |V| \frac{V_r}{|V|} + j|V| \frac{V_i}{|V|} = V_r + jV_i$$

SIGNAL REPRESENTATION

CONVENTION: $v(t) = V_m \cos(\omega t + \phi)$

RESULT: $v(t) = V_m \operatorname{Re} \{ e^{j(\omega t + \phi)} \}$

$$= \operatorname{Re} \{ V_m e^{j(\omega t + \phi)} \}$$

$$= \operatorname{Re} \{ \underbrace{V_m e^{j\phi}} e^{j\omega t} \}$$

COMPLEX NUMBER
REPRESENTING AMPLITUDE
AND PHASE OF SIGNAL

WE CALL $V_m e^{j\phi}$ THE PHASOR REPRESENTATION
OR "PHASOR TRANSFORM"
OF THE SIGNAL;

$$\bar{V} = V_m e^{j\phi} \equiv \mathcal{P} \{ V_m \cos(\omega t + \phi) \}$$

REPRESENTED IN TEXT
IN BOLD NOTATION

$$\bar{V} = V_m e^{j\phi} \equiv \underbrace{\mathcal{P}\{V_m \cos(\omega t + \phi)\}}$$

"PHASOR TRANSFORM"
OF SIGNAL, $V_m \cos(\omega t + \phi)$

NOTE $\bar{V} = V_m \cos \phi + j V_m \sin \phi$

WE OFTEN MAKE USE OF NOTATION

$$e^{j\phi} = \angle \phi^\circ \quad \angle \phi^\circ$$

$$\bar{V} = V_m \angle \phi^\circ$$

WHAT ABOUT INVERSE TRANSFORM?

$$\mathcal{P}\{V_m \cos(\omega t + \varphi)\} = V_m e^{j\varphi}$$

\mathcal{P}^{-1} TO BOTH SIDES

$$\mathcal{P}^{-1}\{\mathcal{P}\{V_m \cos(\omega t + \varphi)\}\} = \mathcal{P}^{-1}\{V_m e^{j\varphi}\}$$

$$V_m \cos(\omega t + \varphi) = \mathcal{P}^{-1}\{V_m e^{j\varphi}\}$$


WHAT'S THIS? ↗

$$\begin{aligned} \text{ANS: } \mathcal{P}^{-1}\{V_m e^{j\varphi}\} &= \text{Re}\{V_m e^{j\varphi} e^{j\omega t}\} \\ &= \text{Re}\{V_m e^{j(\omega t + \varphi)}\} \end{aligned}$$

$$V_m \cos(\omega t + \varphi) \xleftrightarrow{\mathcal{P}} V_m e^{j\varphi}$$

TIME DOMAIN

FREQUENCY
DOMAIN

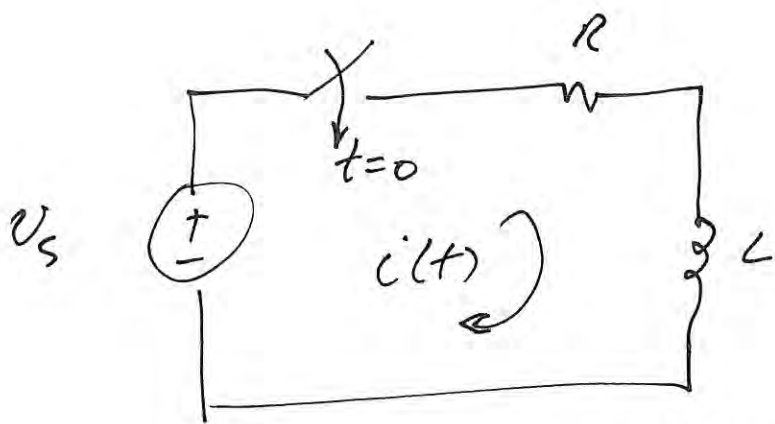

$$v_s - Ri(t) - L \frac{di(t)}{dt} = 0$$

$$v_s = V_m \cos(\omega t + \phi)$$

RECALL S.S. SOLUTION IS OF FORM

$$i_{ss}(t) = \text{Re} \left\{ I_m e^{j\beta} e^{j\omega t} \right\}$$

$$\text{Re} \left\{ RI_m e^{j\beta} e^{j\omega t} \right\} + \text{Re} \left\{ j\omega L I_m e^{j\beta} e^{j\omega t} \right\}$$

$$= \text{Re} \left\{ V_m e^{j\phi} e^{j\omega t} \right\}$$

$$\text{Re} \left\{ (j\omega L + R) I_m e^{j\beta} e^{j\omega t} \right\} = \text{Re} \left\{ V_m e^{j\phi} e^{j\omega t} \right\}$$

MORE SIMPLY

$$(j\omega L + R) I_m e^{j\beta} e^{j\omega t} = V_m e^{j\phi} e^{j\omega t}$$

(TAKE REAL PART LATER)

KEEP IN MIND WHAT WE'RE SOLVING FOR...

$$(j\omega L + R) I_m e^{j\beta} = V_m e^{j\phi}$$

$$I_m e^{j\beta} = \frac{V_m e^{j\phi}}{j\omega L + R}$$

$$= \frac{V_m}{\sqrt{(\omega L)^2 + R^2}} e^{-j\theta} e^{j\phi}$$

~~$$I_m e^{j\beta} = \frac{V_m}{\sqrt{(\omega L)^2 + R^2}} e^{j(\phi - \theta)}$$~~

$$\mathcal{P}^{-1}\{I_m e^{j\beta}\} = \frac{V_m}{\sqrt{(\omega L)^2 + R^2}} \cos(\omega t + \phi - \theta)$$

$$\theta = \text{TAN}^{-1}(\omega L / R)$$

$$v(t) = V_m \cos(\omega t + \phi)$$

PHASOR TRANSFORM

$$\bar{V} \equiv \mathcal{P}\{V_m \cos(\omega t + \phi)\} = V_m e^{j\phi}$$

$$\text{NOTE: } V_m \cos(\omega t + \phi) = \text{Re}\{V_m e^{j(\omega t + \phi)}\}$$

$$= \text{Re}\{V_m e^{j\phi} e^{j\omega t}\}$$

$$= \text{Re}\{\bar{V} e^{j\omega t}\}$$

\Rightarrow PHASOR TRANSFORM DESCRIBES THE

SIGNAL COMPONENT AT THE ~~COMPLEX~~

FREQUENCY ~~$e^{j\omega t}$~~ ω

INVERSE PHASOR TRANSFORM

$$\mathcal{P}^{-1}\{\bar{v}\} = \mathcal{P}^{-1}\{V_m e^{j\varphi}\}$$

$$\mathcal{P}^{-1}\{V_m e^{j\varphi}\} = \mathcal{R}\{V_m e^{j\varphi} e^{j\omega t}\}$$

$$= \mathcal{R}\{V_m e^{j(\omega t + \varphi)}\}$$

$$= V_m \cos(\omega t + \varphi)$$

$$\mathcal{P}^{-1}\{\bar{v}\} = V_m \cos(\omega t + \varphi)$$

$$\bar{v} = V_m e^{j\varphi}$$

$$V_m \cos(\omega t + \phi) \xleftrightarrow{\mathcal{P}} V_m e^{j\phi}$$

TIME DOMAIN FREQUENCY DOMAIN

ASSESSMENT PROBLEMS

Objective 1—Understand phasor concepts and be able to perform a phasor transform and an inverse phasor transform

9.1 Find the phasor transform of each trigonometric function:

a) $v = 170 \cos(377t - 40^\circ)$ V.

b) $i = 10 \sin(1000t + 20^\circ)$ A.

c) $i = [5 \cos(\omega t + 36.87^\circ) + 10 \cos(\omega t - 53.13^\circ)]$ A.

d) $v = [300 \cos(20,000\pi t + 45^\circ) - 100 \sin(20,000\pi t + 30^\circ)]$ mV.

Answer: (a) $170 \angle -40^\circ$ V;

(b) $10 \angle -70^\circ$ A;

(c) $11.18 \angle -26.57^\circ$ A;

(d) $339.90 \angle 61.51^\circ$ mV.

9.2 Find the time-domain expression corresponding to each phasor:

a) $\mathbf{V} = 18.6 \angle -54^\circ$ V.

b) $\mathbf{I} = (20 \angle 45^\circ - 50 \angle -30^\circ)$ mA.

c) $\mathbf{V} = (20 + j80 - 30 \angle 15^\circ)$ V.

Answer: (a) $18.6 \cos(\omega t - 54^\circ)$ V;


(b) $48.81 \cos(\omega t + 126.68^\circ)$ mA;

(c) $72.79 \cos(\omega t + 97.08^\circ)$ V.

NOTE: Also try Chapter Problem 9.11.

HOW DO WE USE THE CONCEPT OF A PHASOR TRANSFORM?

\bar{V} - \bar{I} RELATIONSHIPS

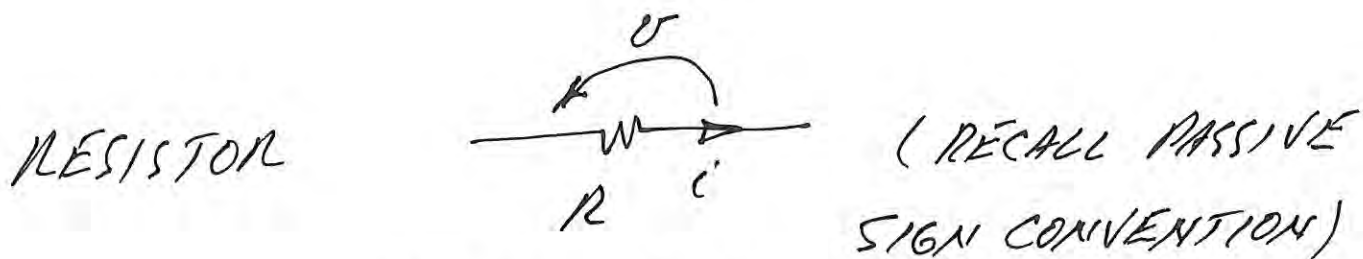


$$i = I_m \cos(\omega t + \theta_i)$$

$$v = R I_m \cos(\omega t + \theta_i)$$

↑
PHASE ANGLE OF CURRENT

$$\mathcal{P}\{v\} \equiv \bar{V} = R I_m e^{j\theta_i} = R \bar{I}$$


$$\boxed{\bar{V} = R \bar{I}}$$

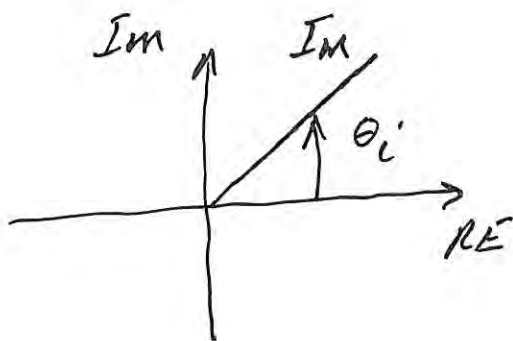

\bar{V} & \bar{I} ARE
IN PHASE

WHY?

INDUCTORS

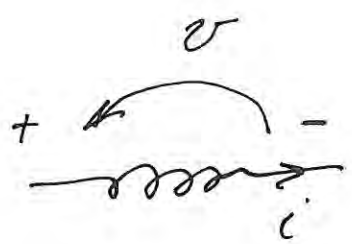

$$v = L \frac{di}{dt}$$

WITH $i = I_m \cos(\omega t + \theta_i)$

$$v = L \frac{d}{dt} I_m \cos(\omega t + \theta_i)$$

$$= -\omega L I_m \sin(\omega t + \theta_i)$$

BY CONVENTION, WE NEED TO EXPRESS
IN TERMS OF COSINE
WHY?

RECALL: SHIFT TO RIGHT BY
SUBTRACTING PHASE


$$v = -\omega L I_m \cos(\omega t + \theta_i - 90^\circ)$$

$$\mathcal{P}\{v\} = -\omega L I_m e^{j(\theta_i - 90^\circ)}$$

$$P\{v\} = \bar{V} = -\omega L e^{-j90^\circ} \underbrace{I_m e^{j\theta_i}}_{\bar{I}}$$



WHAT IS e^{-j90°

$$e^{-j90^\circ} = -j$$

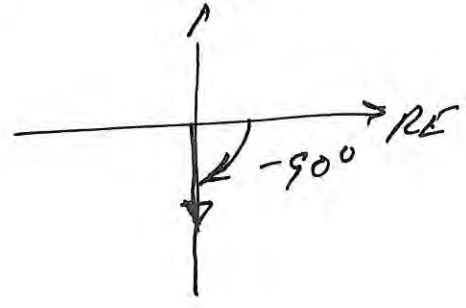

$$\boxed{\bar{V} = j\omega L \bar{I}}$$

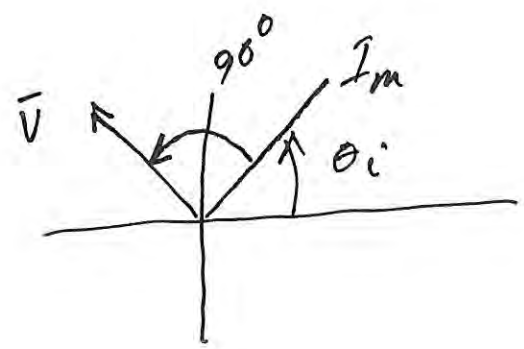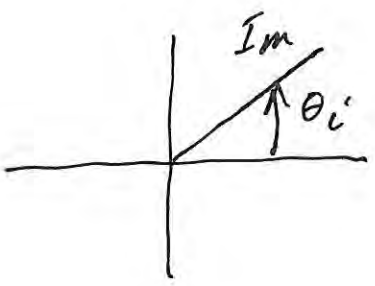
NOTE $j\omega L = \omega L e^{j90^\circ}$



NOTE \bar{V} is \bar{I} OUT OF PHASE BY 90°

DOES VOLTAGE LEAD OR LAG?

CAPACITORS

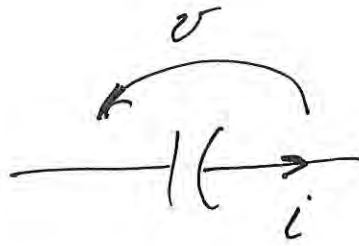

$$i = c \frac{dv}{dt}$$

WITH $v = V_m \cos(\omega t + \theta_v)$

↑
PHASE ANGLE
OF VOLTAGE


$$i = -\omega c V_m \sin(\omega t + \theta_v)$$

AS BEFORE,

$$\bar{I} = j\omega c \bar{V}$$

$$\boxed{\bar{V} = \frac{1}{j\omega c} \bar{I}}$$

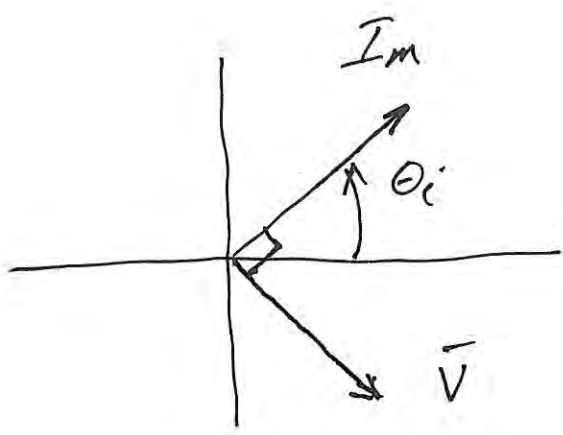NOTE $\frac{1}{j\omega c} = \frac{1}{\omega c} e^{-j90^\circ}$



NOTE \bar{V} & \bar{I} OUT OF PHASE BY 90°
DOES VOLTAGE LEAD OR LAG?

RESISTOR $\bar{V} = R \bar{I}$


INDUCTOR $\bar{V} = j\omega L \bar{I}$

CAPACITOR $\bar{V} = \frac{1}{j\omega C} \bar{I}$

ALL OF FORM

$$\bar{V} = z \bar{I}$$

↑
"IMPEDANCE"

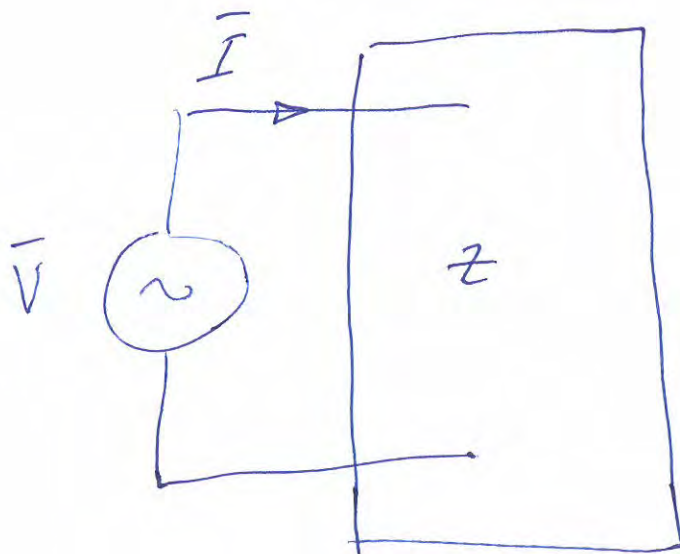

FOR IDEAL RESISTORS, INDUCTORS,
CAPACITORS, Z IS EITHER COMPLETELY
REAL OR PURELY IMAGINARY.


FOR A GENERAL CIRCUIT, Z IS
COMPLEX.

$$\text{Im}\{Z\} \equiv \text{"REACTANCE"} = X$$

FOR RESISTOR, REACTANCE = 0

FOR INDUCTOR, REACTANCE = ωL

FOR CAPACITOR, REACTANCE = $-1/\omega C$

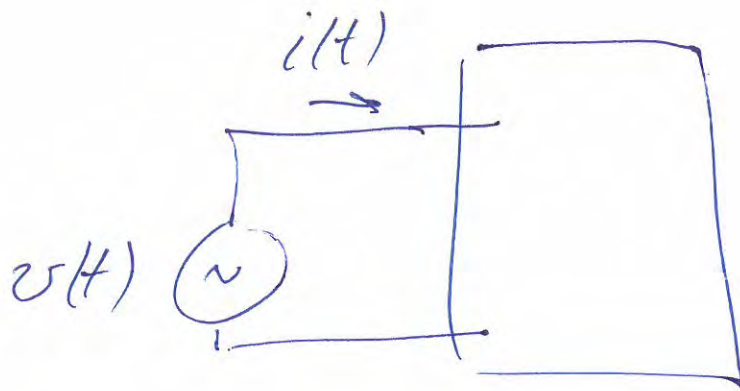

$$v(t) = V_m \cos(\omega t + \phi)$$

$$i(t) = I_m \cos(\omega t + \phi + \theta)$$


WHAT IS THE IMPEDANCE?

WHAT IS THE REACTANCE?

ASSESSMENT PROBLEMS

Objective 2—Be able to transform a circuit with a sinusoidal source into the frequency domain using phasor concepts

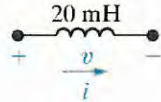
- 9.3** The current in the 20 mH inductor is $10 \cos(10,000t + 30^\circ)$ mA. Calculate (a) the inductive reactance; (b) the impedance of the inductor; (c) the phasor voltage \mathbf{V} ; and (d) the steady-state expression for $v(t)$.



- Answer:** (a) 200Ω ;
(b) $j200 \Omega$;
(c) $2 \angle 120^\circ$ V;
(d) $2 \cos(10,000t + 120^\circ)$ V.

NOTE: Also try Chapter Problems 9.12 and 9.13.

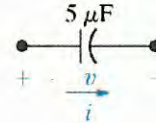- 9.4** The voltage across the terminals of the $5 \mu\text{F}$ capacitor is $30 \cos(4000t + 25^\circ)$ V. Calculate (a) the capacitive reactance; (b) the impedance of the capacitor; (c) the phasor current \mathbf{I} ; and (d) the steady-state expression for $i(t)$.



- Answer:** (a) -50Ω ;
(b) $-j50 \Omega$;
(c) $0.6 \angle 115^\circ$ A;
(d) $0.6 \cos(4000t + 115^\circ)$ A.

SPECIFICATION OF SINUSOIDAL SOURCE

$$\text{SINE}(V_{\text{OFFSET}}, V_m, f, t_d, \theta, \varphi)$$

DELAY

DAMPING FACTOR (1/s)

EXAMPLE: WANT $20\cos(800t + 25^\circ)$

USE $\text{SINE}(0, 20, 127.3, 0, 0, 115)$

$$800 = 2\pi f$$

$$\Rightarrow f = 800 / 2\pi$$


$$\text{SINE}(x + 90^\circ) = \text{COSINE}(x)$$

$$\text{SINE}(25 + 90) = \text{COSINE}(25)$$

$$\text{SINE}(115) = \text{COSINE}(25)$$

KVL IN THE FREQ DOMAIN

①

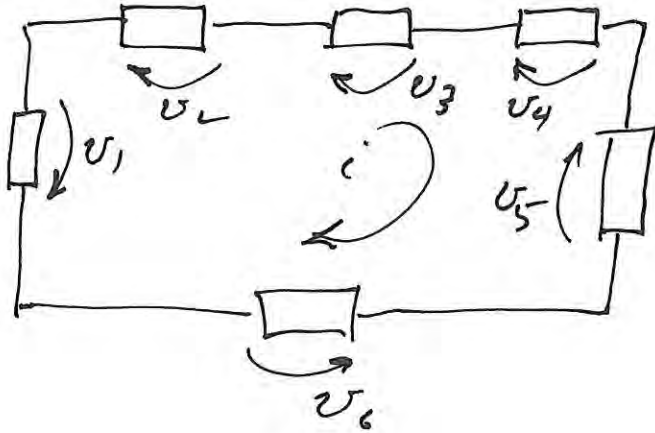

$$\text{KVL: } v_1 + v_2 \dots + v_6 = 0 \quad (\text{TIME DOMAIN})$$

$$v_{m1} \cos(\omega t + \theta_1) + v_{m2} \cos(\omega t + \theta_2)$$

$$+ \dots + v_{m6} \cos(\omega t + \theta_6) = 0$$

USING EULER'S IDENTITY:

$$\text{Re} \{ v_{m1} e^{j(\omega t + \theta_1)} \} + \text{Re} \{ v_{m2} e^{j(\omega t + \theta_2)} \}$$

$$+ \dots + \text{Re} \{ v_{m6} e^{j(\omega t + \theta_6)} \} = 0$$

BECAUSE $\text{Re} \{ A \} + \text{Re} \{ B \} = \text{Re} \{ A + B \}$

WE CAN WRITE

$$\operatorname{Re} \left\{ V_{m1} e^{j(\omega t + \theta_1)} + \dots + V_{m6} e^{j(\omega t + \theta_6)} \right\} = 0$$

OR

$$\operatorname{Re} \left\{ (V_{m1} e^{j\theta_1} + \dots + V_{m6} e^{j\theta_6}) e^{j\omega t} \right\} = 0$$

THE ONLY WAY TO SATISFY THIS EQ
FOR AN ARBITRARY TIME IS TO SET
THE TERMS


$$(V_{m1} e^{j\theta_1} + \dots + V_{m6} e^{j\theta_6}) = 0$$

OR

$$\boxed{\bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_6 = 0} \quad \text{KVL}$$

(FREQUENCY DOMAIN)

KCL

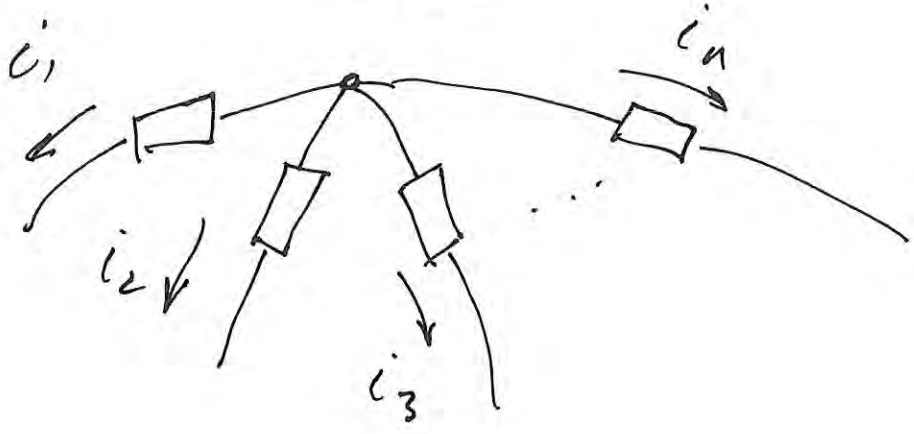


ON BASIS OF PREVIOUS, WE HAVE

$$i_1 + i_2 + \dots + i_n = 0 \quad \text{TIME DOMAIN}$$

$$\bar{I}_1 + \bar{I}_2 + \dots + \bar{I}_n = 0 \quad \text{FREQ DOMAIN}$$

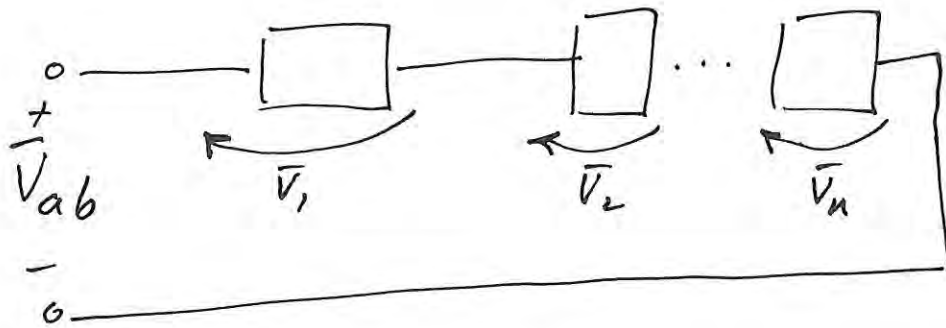IMPLICATIONS OF KVL & KCL IN THE FREQUENCY DOMAIN



KVL: $\bar{V}_{ab} = \bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_n$

BUT WE'VE ESTABLISHED THAT REGARDLESS OF COMPONENT, THE \bar{V} - \bar{I} RELATIONSHIPS ARE ALL OF THE FORM

$$\bar{V} = z\bar{I}$$

SINCE THERE'S ONLY ONE CURRENT IN THIS MESH EQ,

$$\bar{V}_i = z_i \bar{I}$$

(5)

$$\begin{aligned}\bar{V}_{ab} &= z_1 \bar{I} + z_2 \bar{I} + \dots + z_n \bar{I} \\ &= (z_1 + z_2 + \dots + z_n) \bar{I}\end{aligned}$$


GOOD NEWS: SERIES COMBINATIONS

COMBINE JUST LIKE RESISTORS

BAD NEWS: WE HAVE TO ADD COMPLEX

NUMBERS (SMALL PRICE TO PAY)

EXAMPLE 9.6

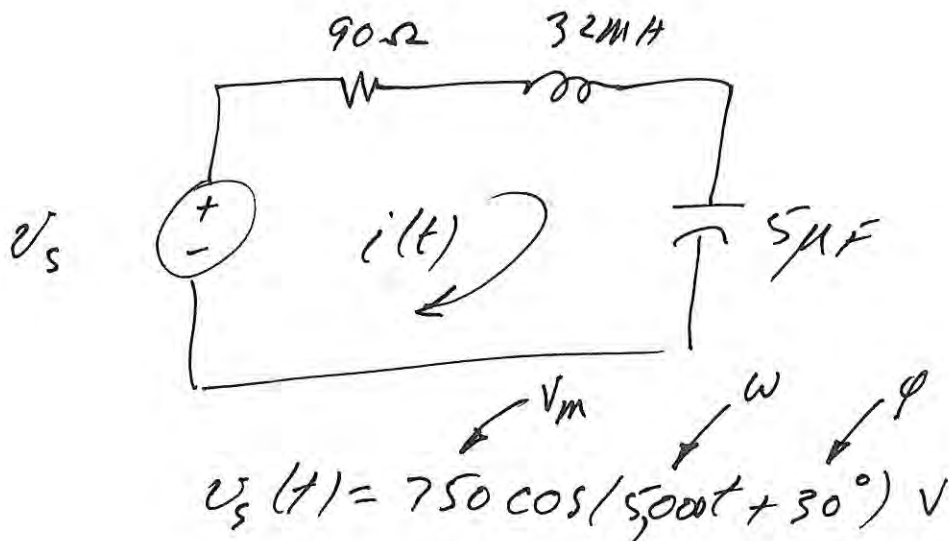

(6)

TIME DOMAIN

$$v_s(t) = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i(x) dx$$

FREQUENCY DOMAIN

$$\begin{aligned} \bar{V}_s &= z_R \bar{I} + z_L \bar{I} + z_C \bar{I} \\ &= (z_R + z_L + z_C) \bar{I} \end{aligned}$$

$$\bar{I} = \frac{\bar{V}_s}{z_{EQ}}$$

$$i(t) = \mathcal{P}^{-1} \left\{ \frac{\bar{V}_s}{z_{EQ}} \right\}$$

$$z_R = 90 \Omega$$

$$\begin{aligned} z_L &= j\omega L = j(5000 \text{ RAD/S})(32 \text{ mH}) \\ &= j160 \Omega \end{aligned}$$

$$z_C = \frac{-j}{\omega C} = -j40 \Omega$$

$$z_{EQ} = 90 \Omega + j160 \Omega - j40 \Omega = (90 + j120) \Omega$$

(7)

$$z_{EQ} = (90 + j120) \Omega$$

$$= \sqrt{(90)^2 + (120)^2} e^{j\theta}$$

$$\theta = \tan^{-1}\left(\frac{120}{90}\right) = 53.13^\circ$$

$$z_{EQ} = 150 e^{j53.13^\circ}$$

$$z_{EQ} = 150 \angle 53.13^\circ$$

$$\bar{V}_s = \mathcal{P}\{750 \cos(5,000t + 30^\circ)\}$$

$$= 750 e^{j30^\circ}$$

$$\bar{I} = \frac{\bar{V}_s}{z_{EQ}} = \frac{750 e^{j30^\circ}}{150 e^{j53.13^\circ}}$$


$$= 5 e^{-j23.13^\circ}$$

$$i(t) = \mathcal{P}^{-1}\{5 e^{-j23.13^\circ}\}$$


$$i(t) = 5 \cos(5,000t - 23.13^\circ) \text{ A}$$

$$v_s(t) = 750 \cos(5,000t + 30^\circ) \text{ V}$$
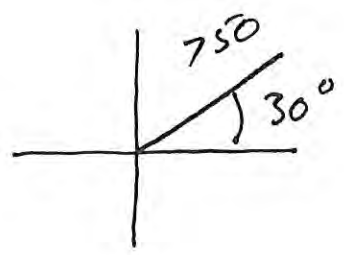
$$i(t) = 5 \cos(5,000t - 23.13^\circ) \text{ A}$$



$v_s(t)$

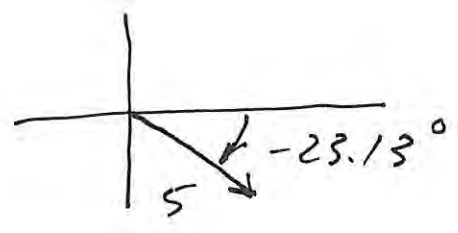

$i(t)$

$$Z_{EQ} = 150 \angle 53.13$$

$$= 150 \cos(53.13) + j150 \sin(53.13)$$

$$= 90 + j120 \Omega$$

WHAT IS THE CHARACTER OF THIS IMPEDANCE?

DOES IT HAVE AN INDUCTIVE OR A CAPACITIVE REACTANCE?

$$Z_{EQ} = R + j\omega L - j/\omega C$$

WHAT HAPPENS IF

$$j\omega L - j/\omega C = 0 \quad ?$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

WHERE HAVE WE SEEN THIS
FORMULA BEFORE?

WHAT WAS THIS CALLED?


WHY DO YOU SUPPOSE IT HAS THIS NAME?

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(132\text{mH})(5\mu\text{F})}} = 2,500\text{RAD/S}$$

$$f_0 = \frac{\omega_0}{2\pi} = 397.89\text{Hz}$$

$$\text{MAX MESH CURRENT} = \frac{750\text{V}}{90\Omega} = 8.33\text{A}$$


Example 9.6

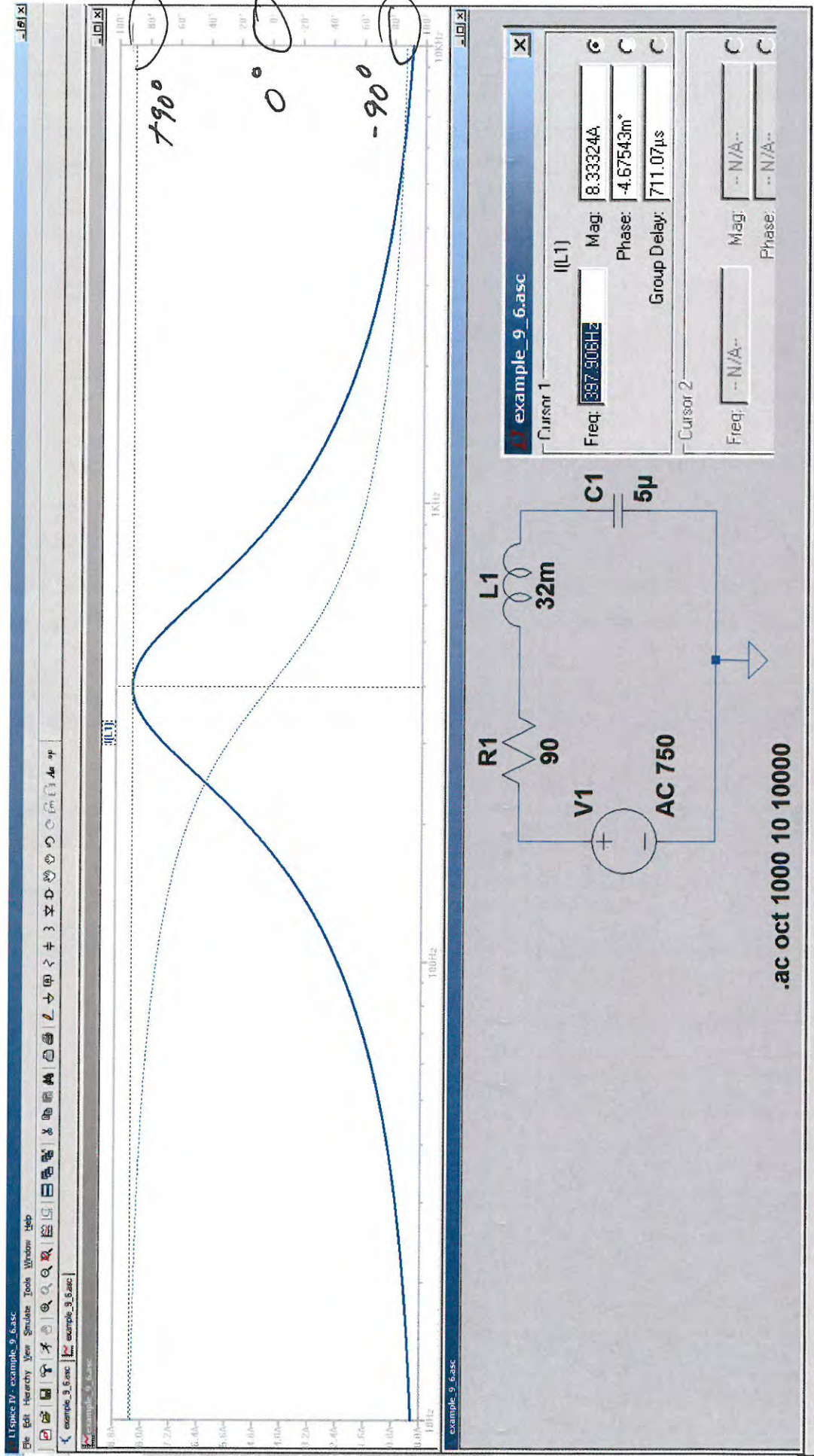

What is illustrated here?
 What conclusions can you draw?

AC CURRENT LEADS BY 90°
 AC CURRENT LAGS BY 90°

TRANSIENT RESP

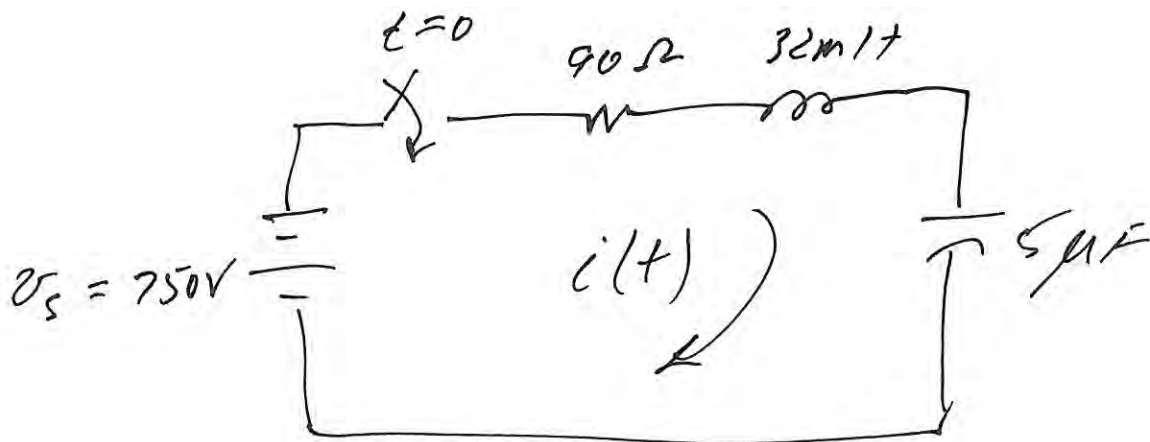

TIME DOMAIN

$$t \geq 0 \quad v_s = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i(x) dx$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(32mH)(5\mu F)} = 6.25 \times 10^6 \text{ (RAD/S)}^2$$

$\omega_0 = 2,500 \text{ RAD/S}$

$$\alpha = \frac{R}{2L} = \frac{90}{2(32mH)} = 1,406 \text{ NP/S}$$

$$s_{1,2} = -1,406 \pm \sqrt{(1,406)^2 - 6.25 \times 10^6}$$

$$= -1,406 \pm j 2,067$$

UNDER DAMPED

$$i(t) = B_1 e^{-\alpha t} \cos \omega_0 t + B_2 e^{-\alpha t} \sin \omega_0 t$$


INITIAL COND'S.

ASSUME NO STORED ENERGY

$$\Rightarrow i(0) = 0 \quad \text{WHY?}$$

$$\Rightarrow B_1 = 0$$

CKT AT $t=0^+$

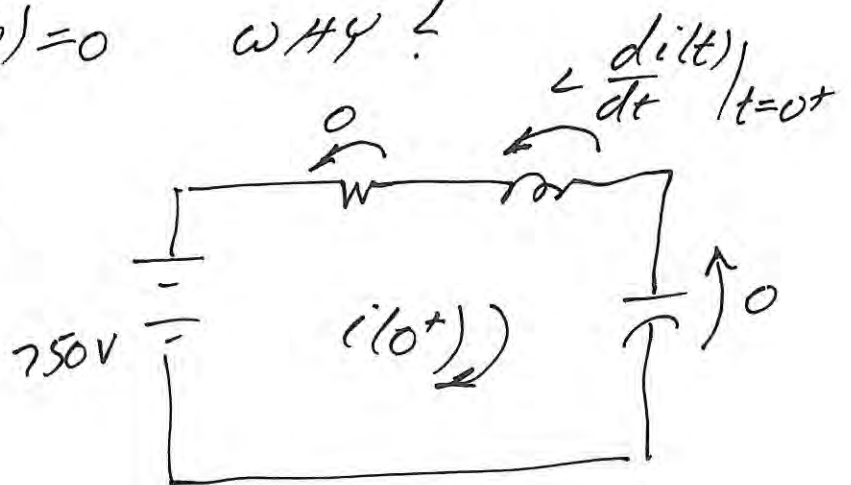

$$\text{KVL: } 750V = L \frac{di(t)}{dt} \Big|_{t=0^+}$$

$$\frac{750V}{32mH} = -\alpha B_1 + \omega_0 B_2$$

$$= \omega_0 B_2$$

$$B_2 = \frac{750V}{32mH(2,500)} = 9.375 A$$

$$i(t) = 9.375 e^{-1,406t} \text{ A}$$


PULSE ANALYSIS

STOP TIME = 20ms

PULSE WIDTH 5ms }
PULSE PERIOD = 10ms } 50% DUTY CYCLE

PULSE RISE TIME = 0.1μs

PULSE FALL TIME = 0.1μs

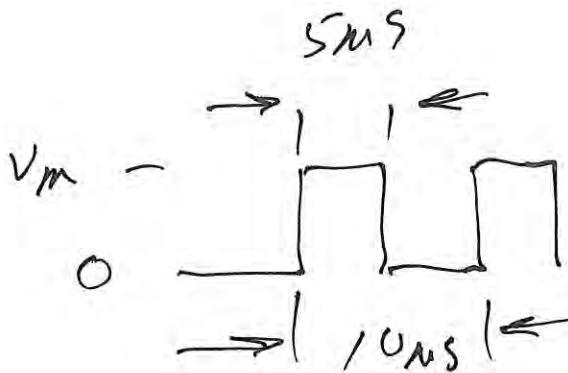

$$i(t) = 9.375 e^{-7,406t} \sin 2,500t \quad A$$

$$2,500 = 2\pi f = \frac{2\pi}{T}$$



$$T = \frac{2\pi}{2,500} = 2.513 \text{ms}$$





SQ WAVE PERIOD = 10ms





PULSE WIDTH = 5ms





HOW MANY OSCILLATIONS IN 5ms ?


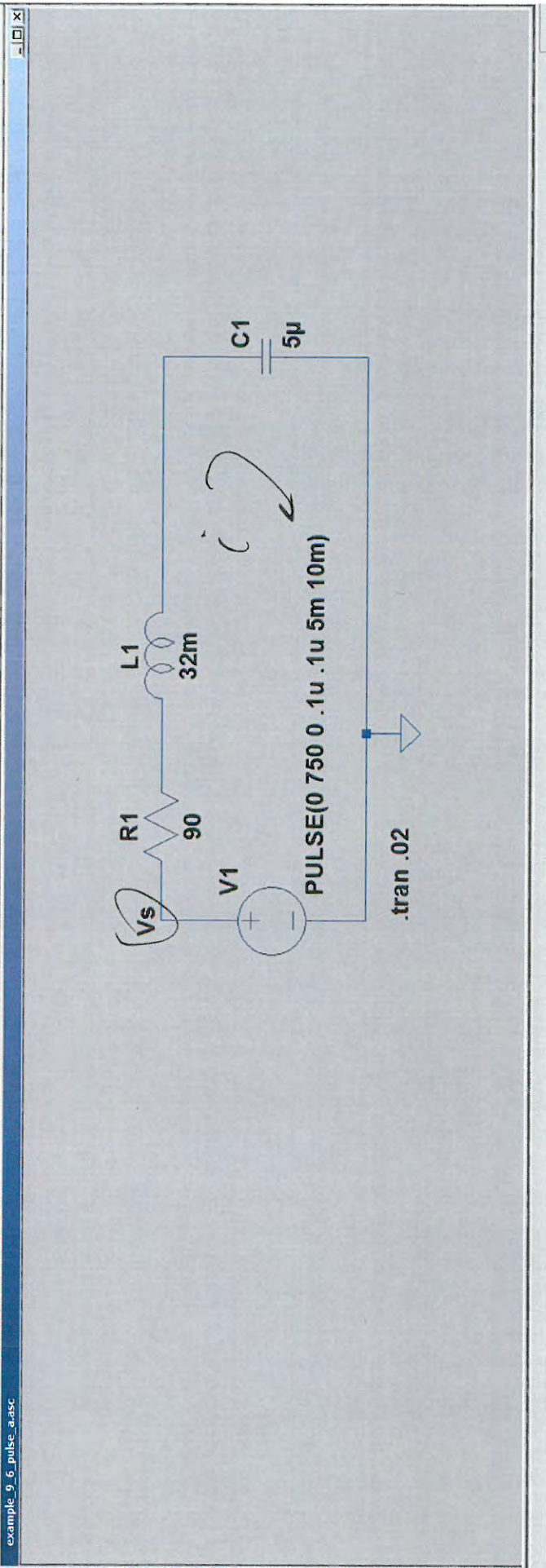
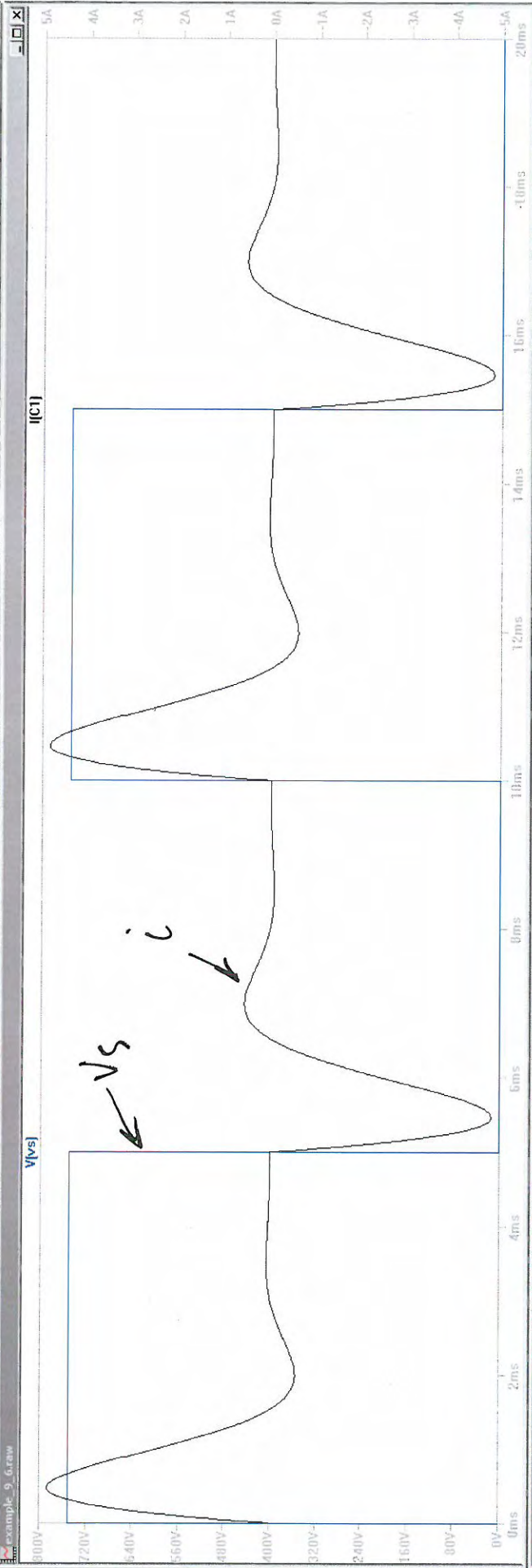
$$\frac{5 \times 10^{-3}}{2.513 \times 10^{-3}} \approx \underline{\underline{2}}$$



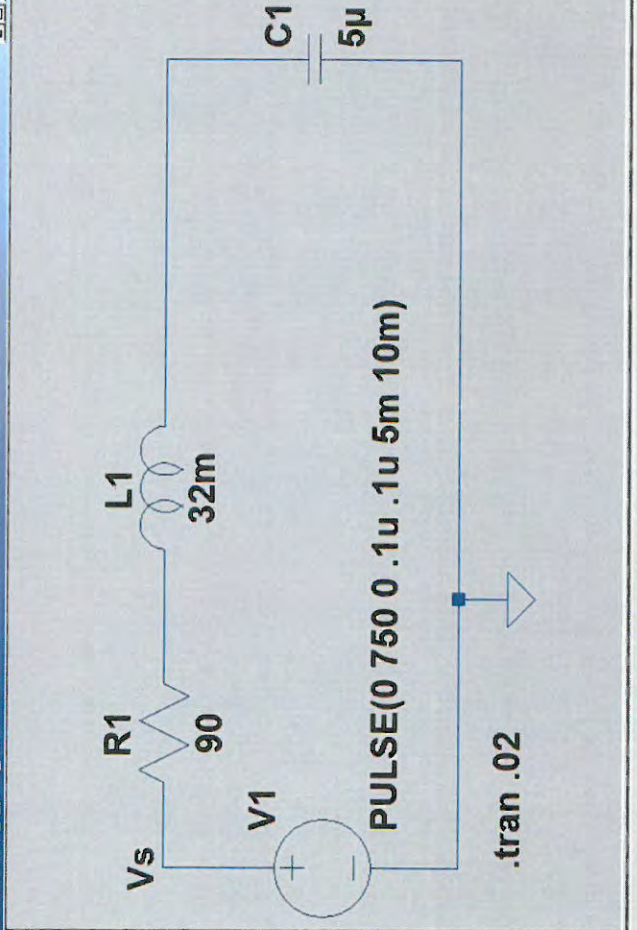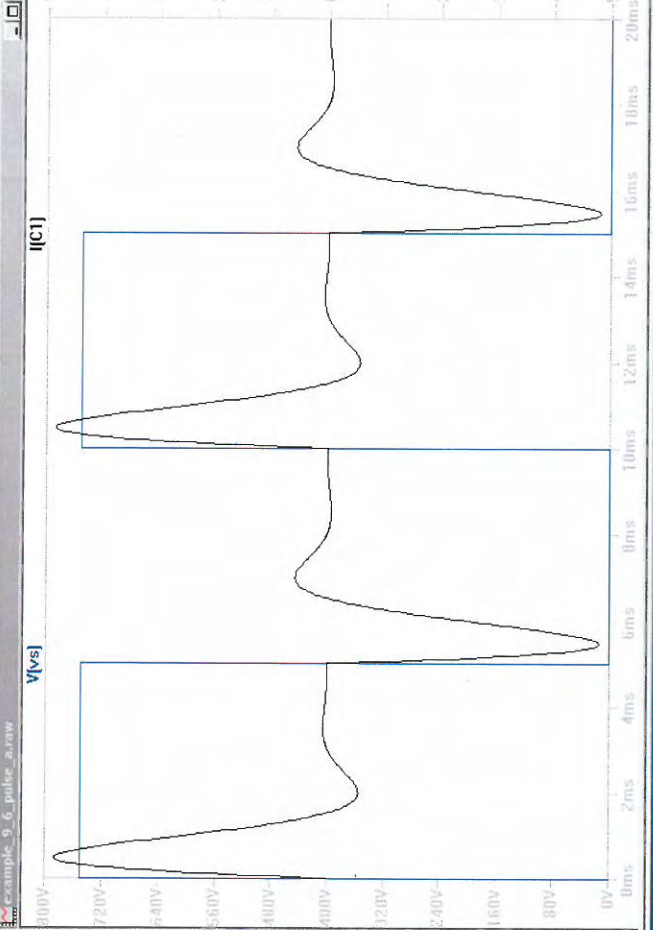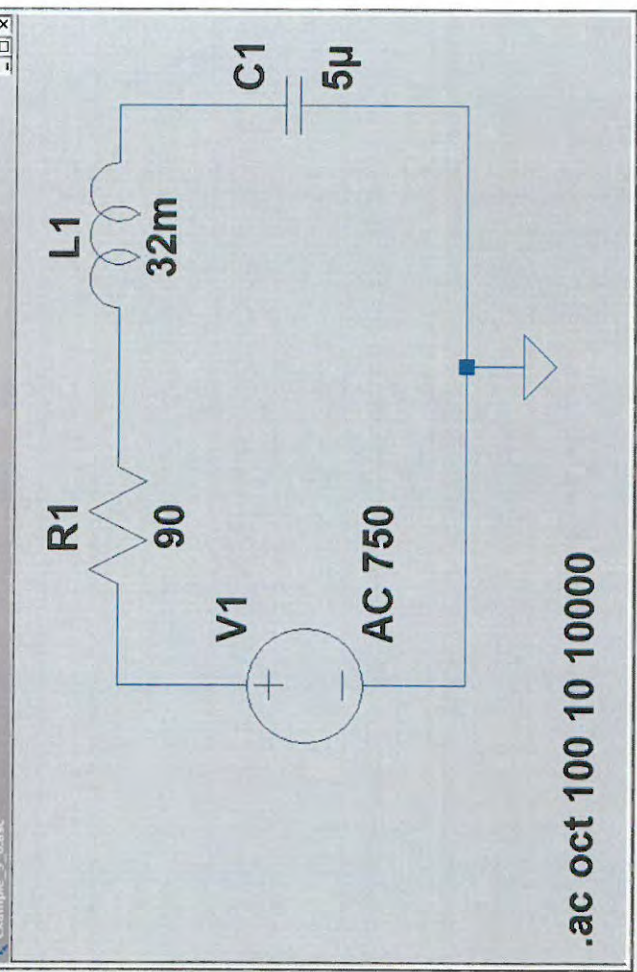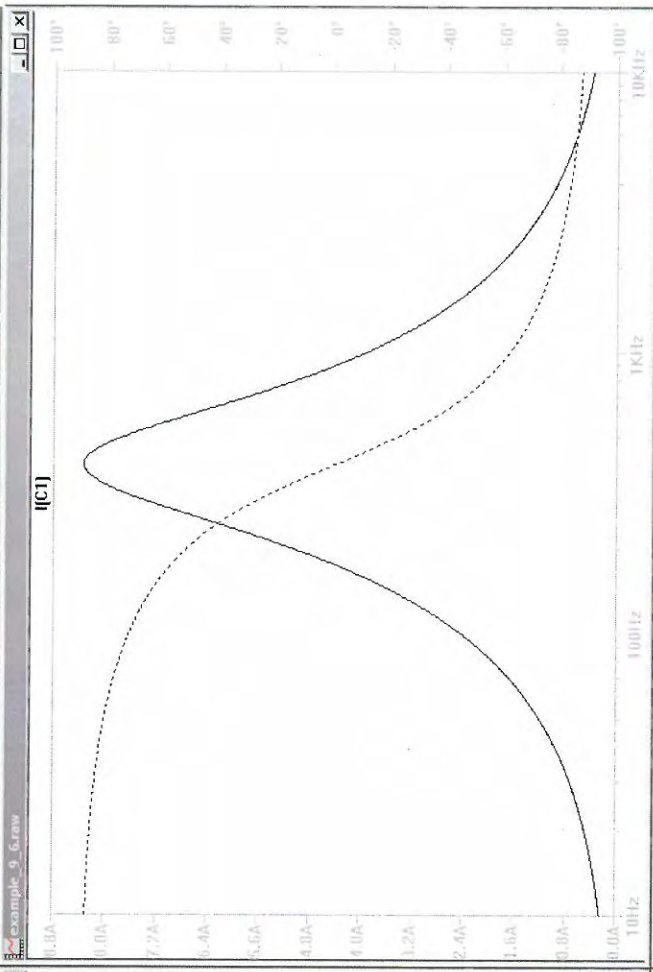


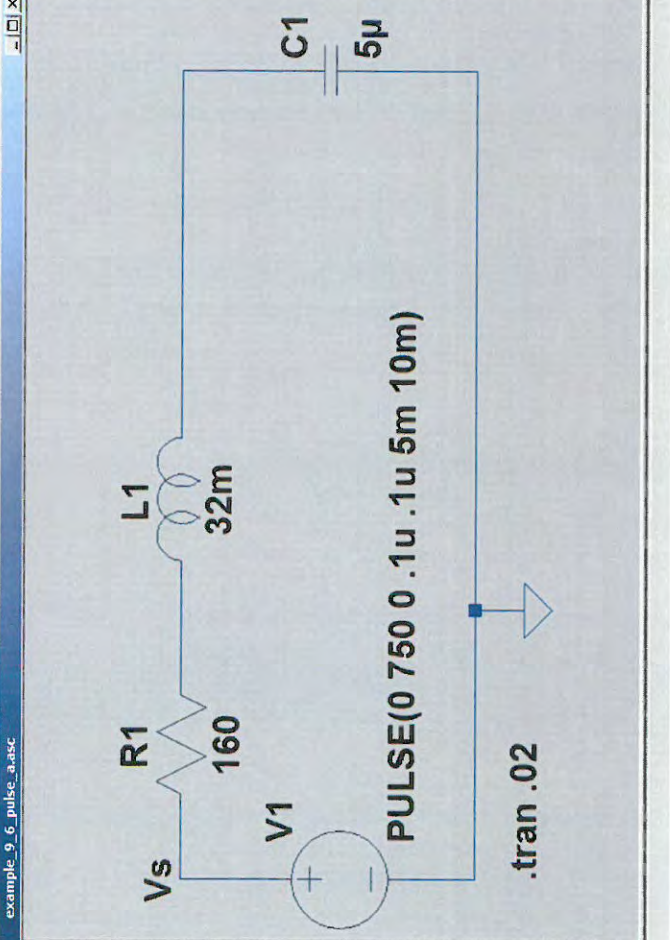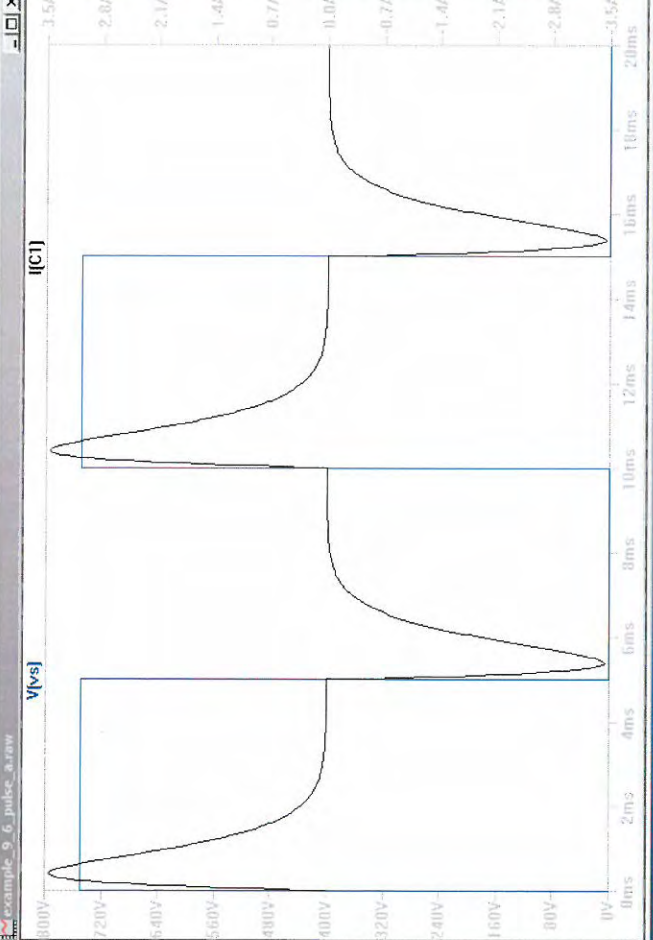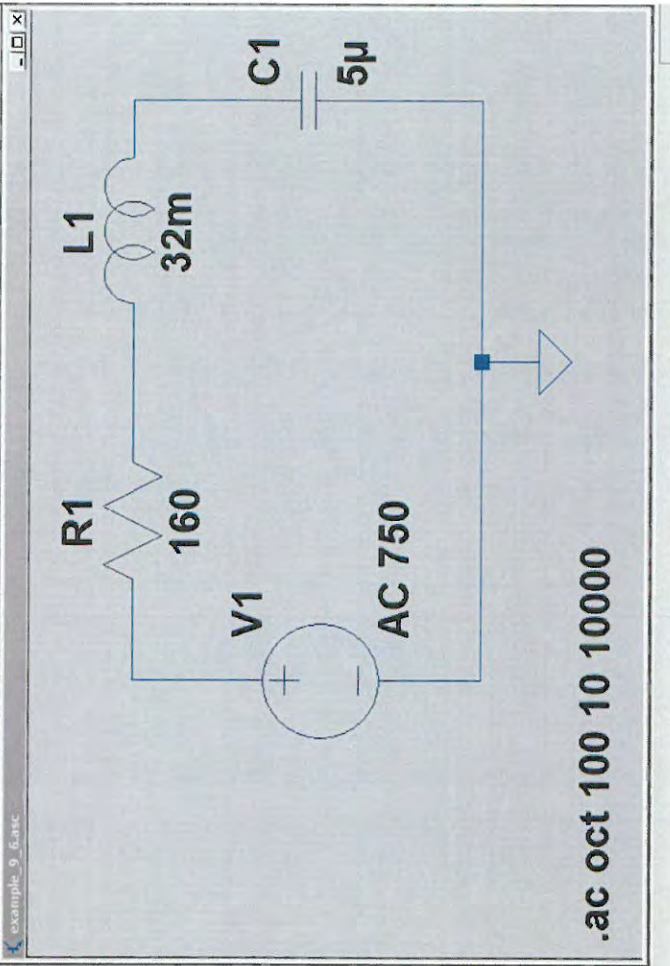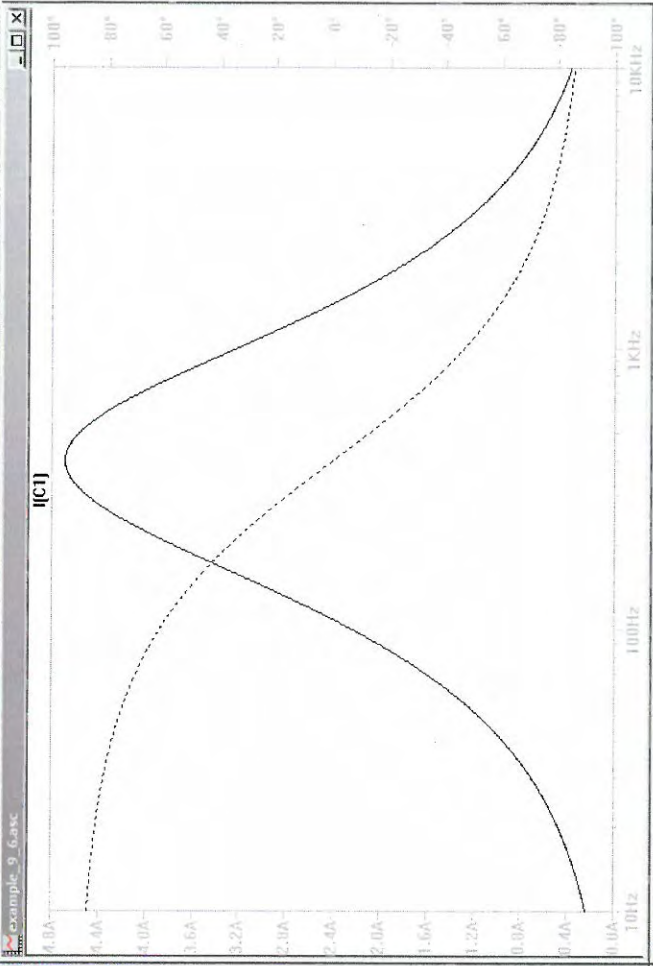

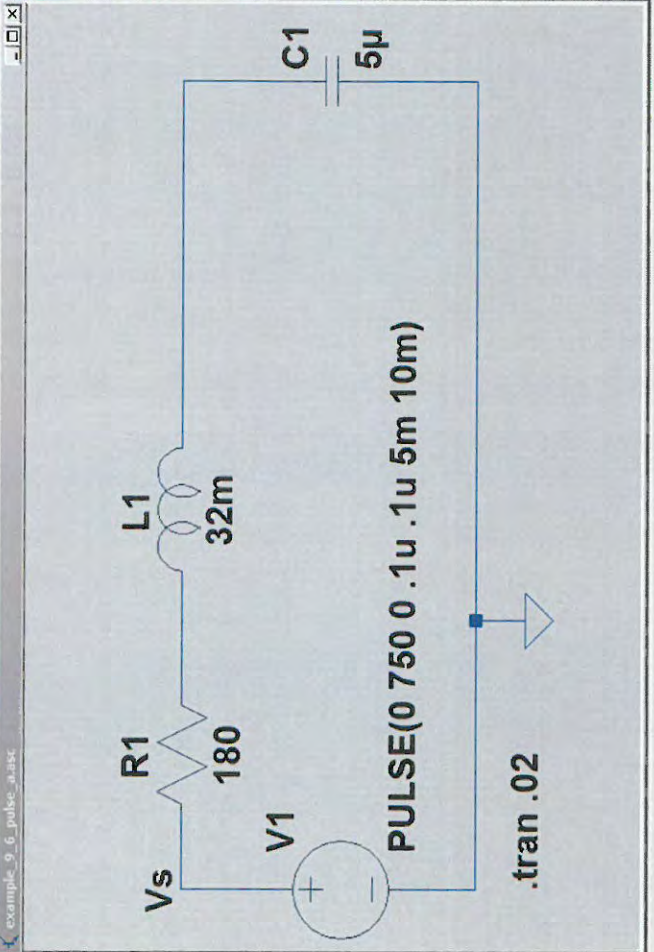
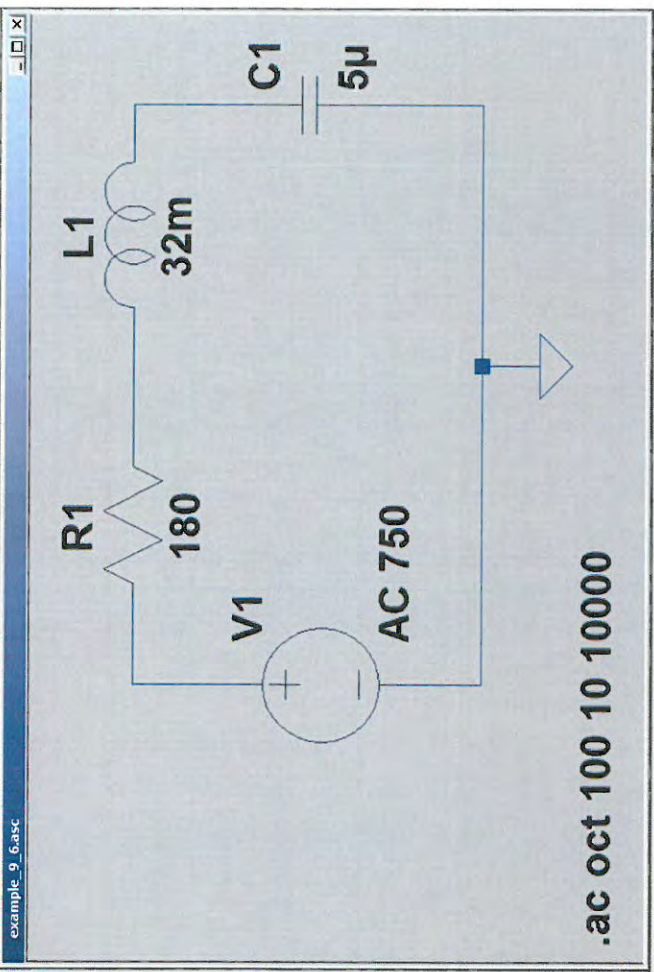
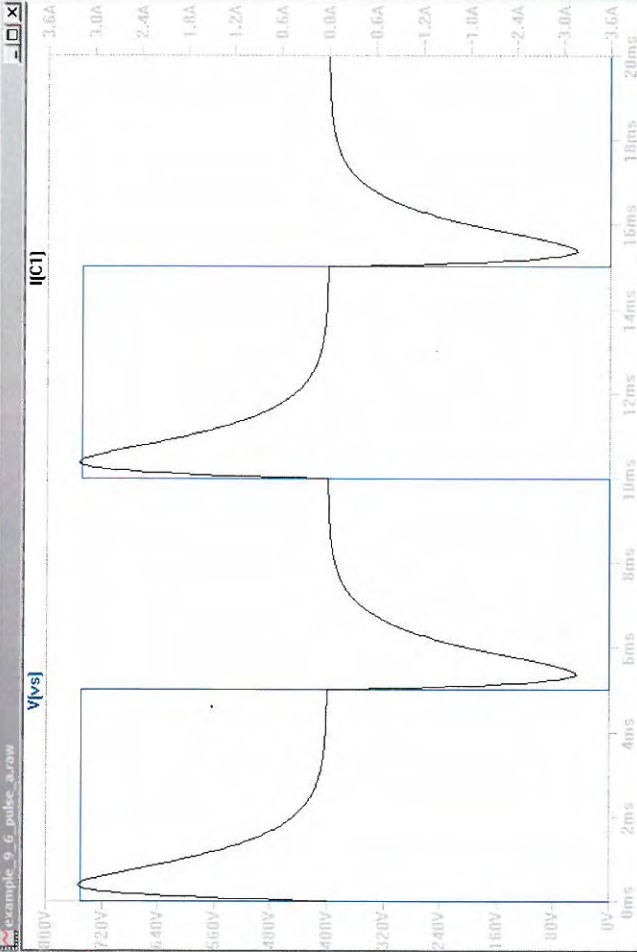
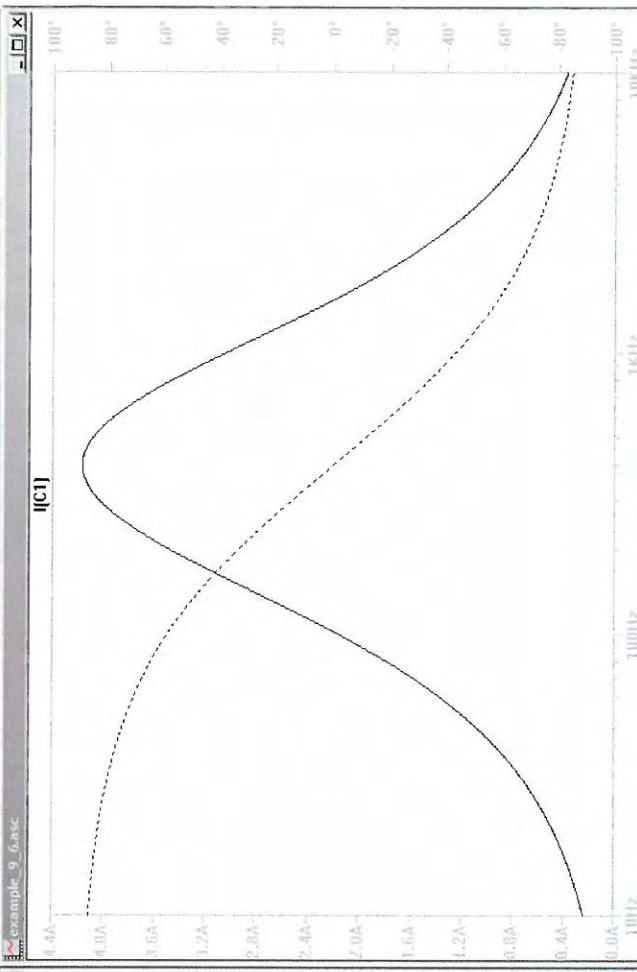


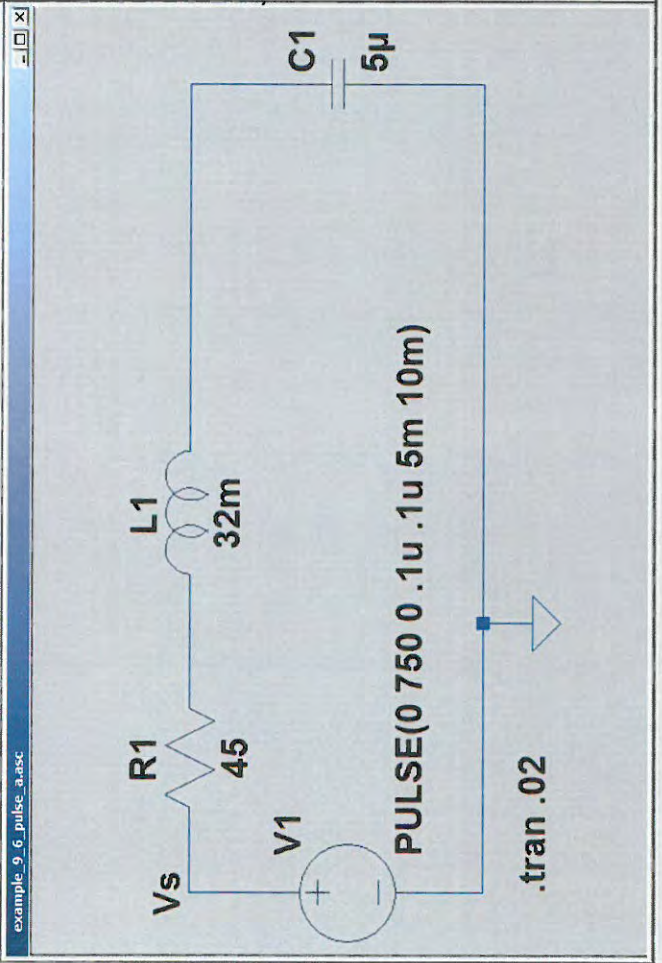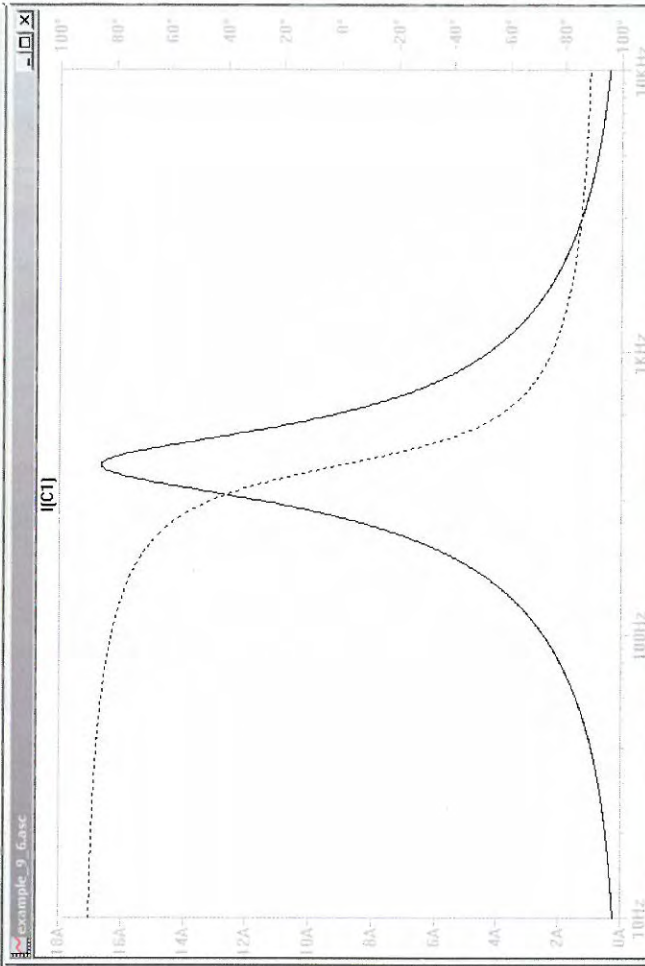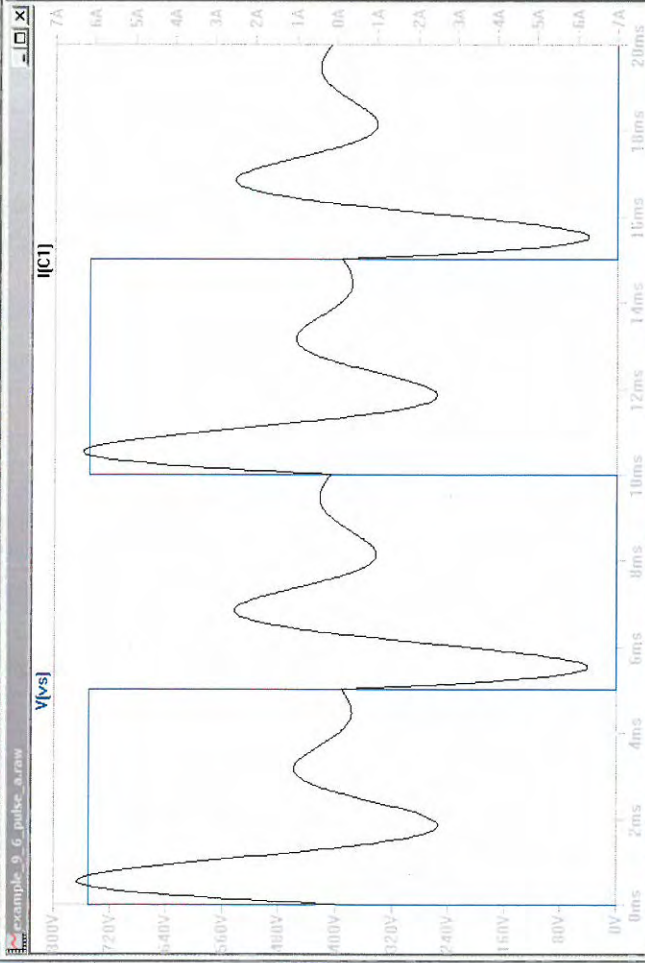


.tran .02

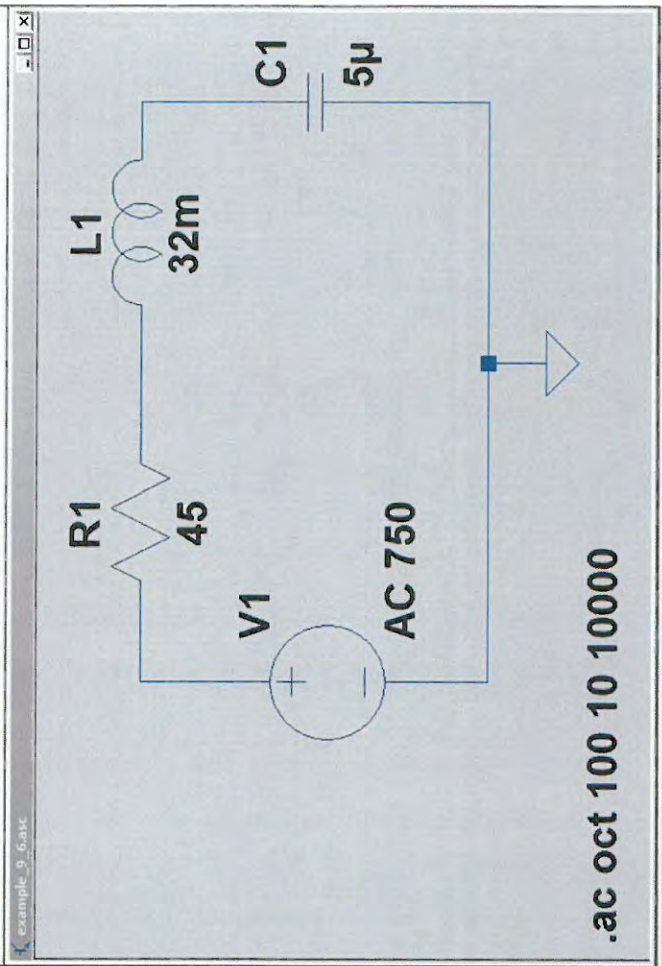

.ac oct 100 10 10000

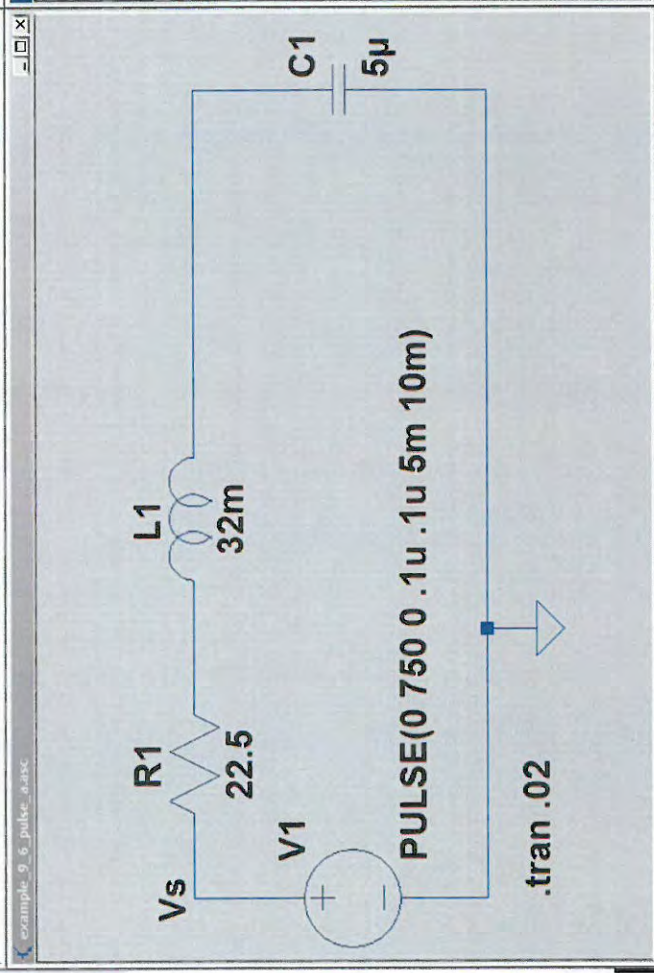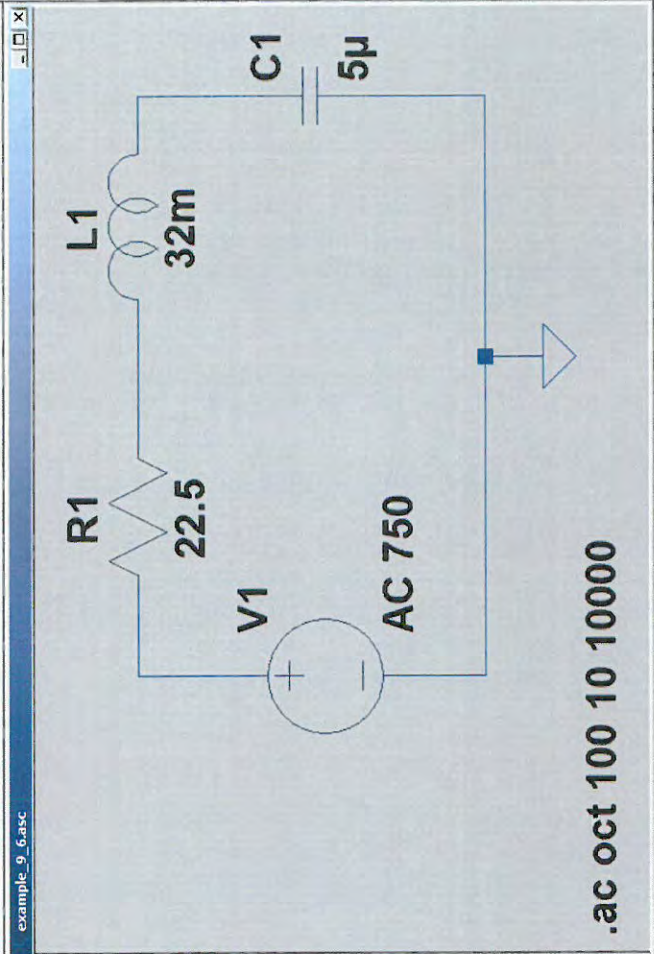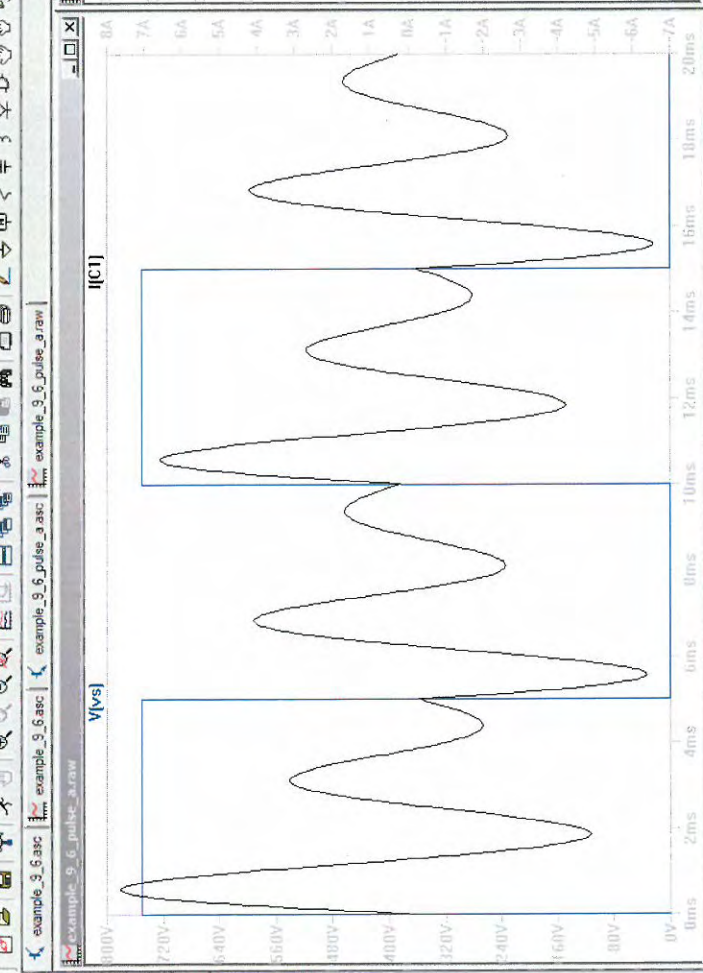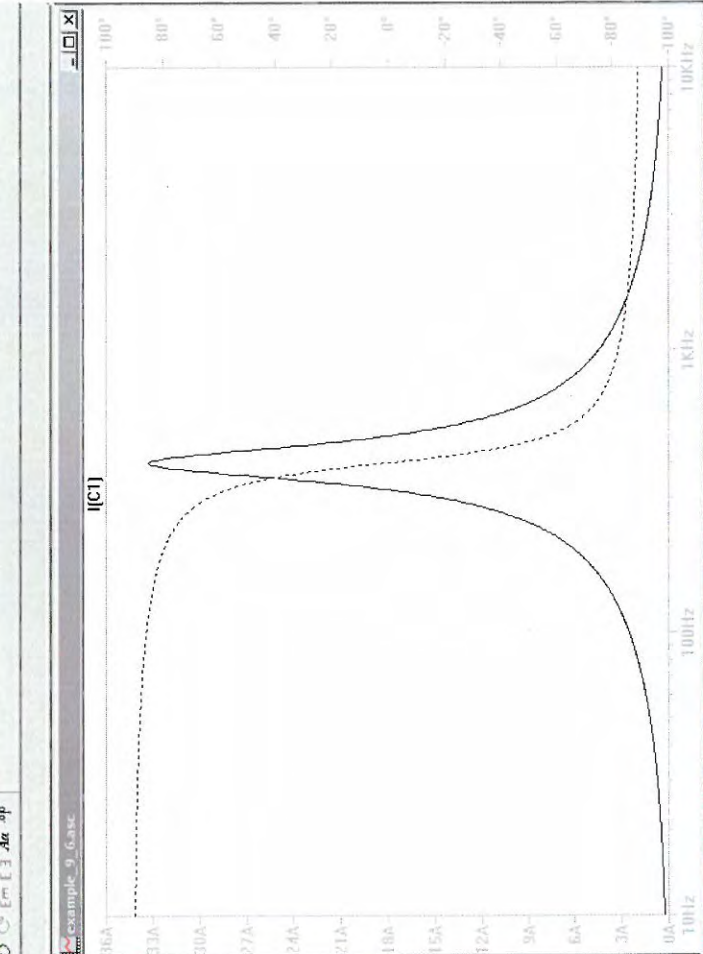

EXAMPLE

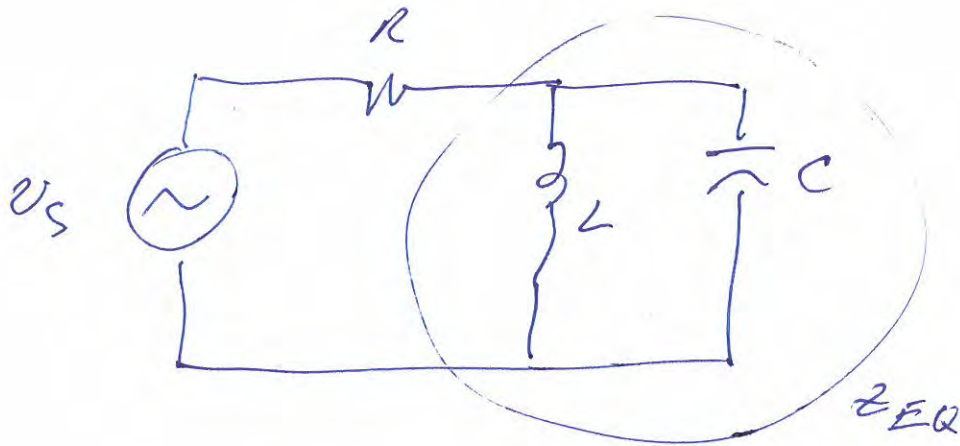

$$v_s(t) = 2 \cos(\omega t) \text{ V}$$

$$z_{EQ} = \frac{j\omega L / j\omega C}{j\omega L + 1/j\omega C} = \frac{j\omega L}{-\omega^2 LC + 1}$$

$$LC = 1/\omega_0^2$$





$$\omega_0 = \frac{1}{\sqrt{LC}}$$





$$z_{EQ} = \frac{j\omega L}{1 - (\omega/\omega_0)^2}$$





$\omega < \omega_0$ REACTANCE POSITIVE





$\omega = \omega_0$ $z_{EQ} \rightarrow \infty$

$\omega > \omega_0$ REACTANCE NEGATIVE

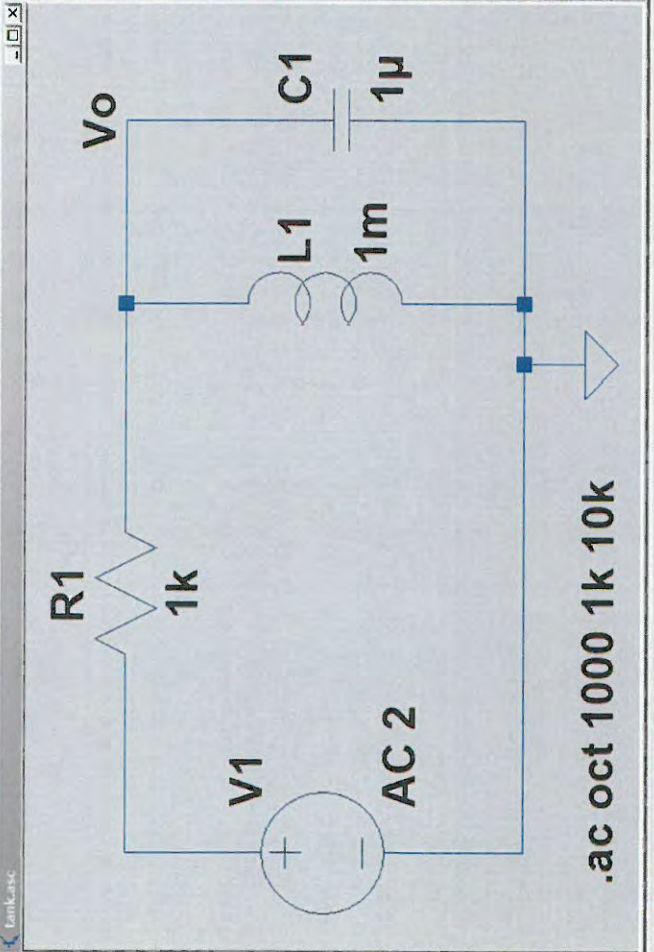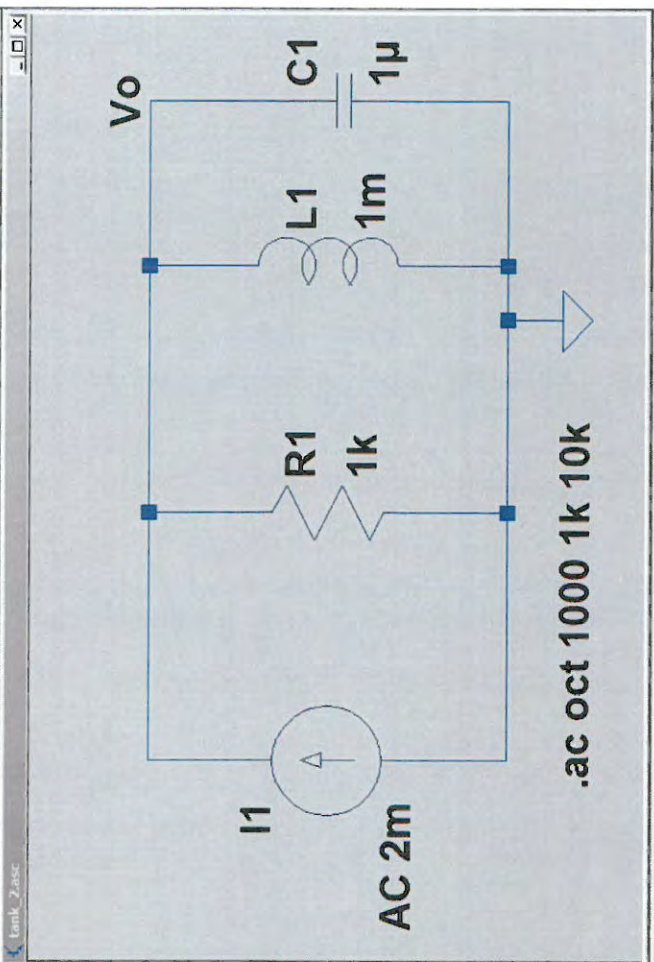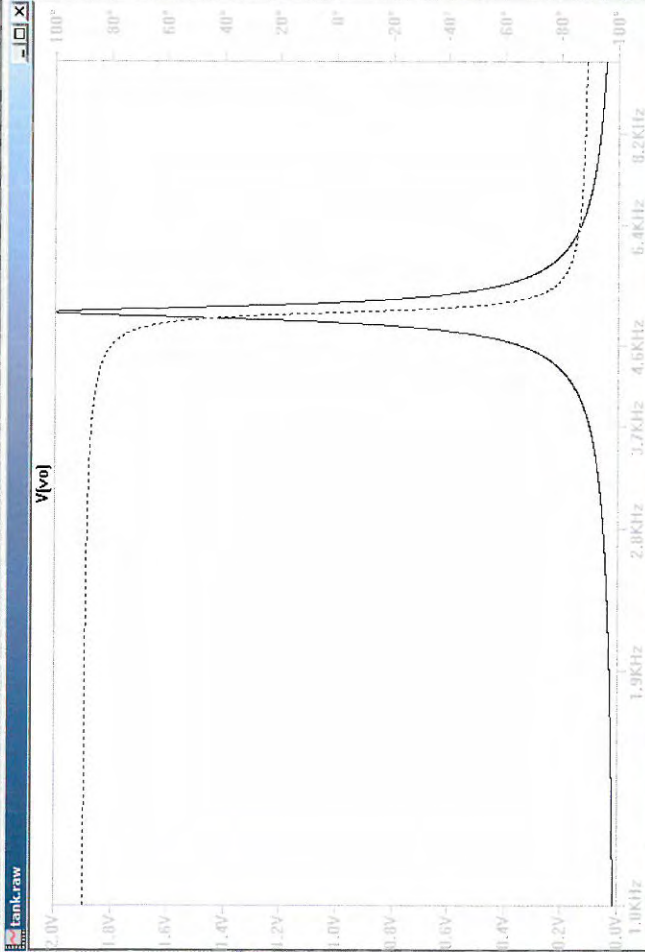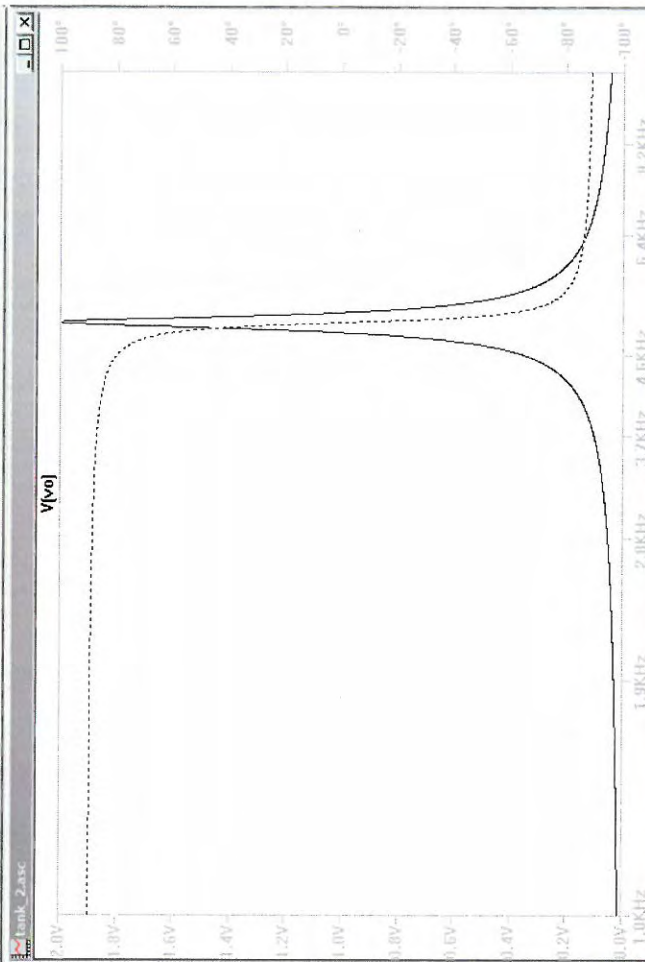

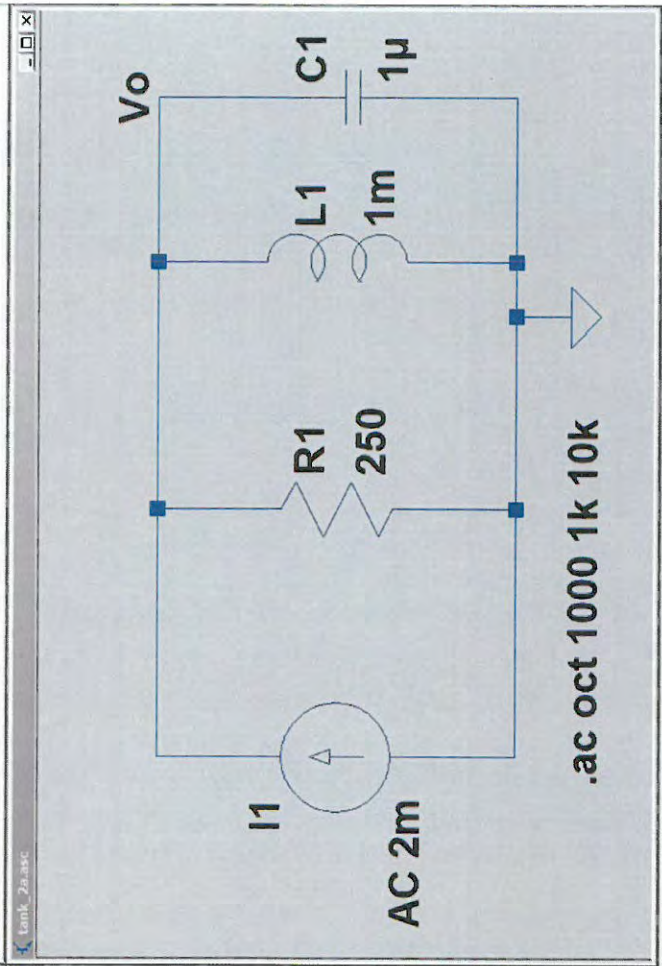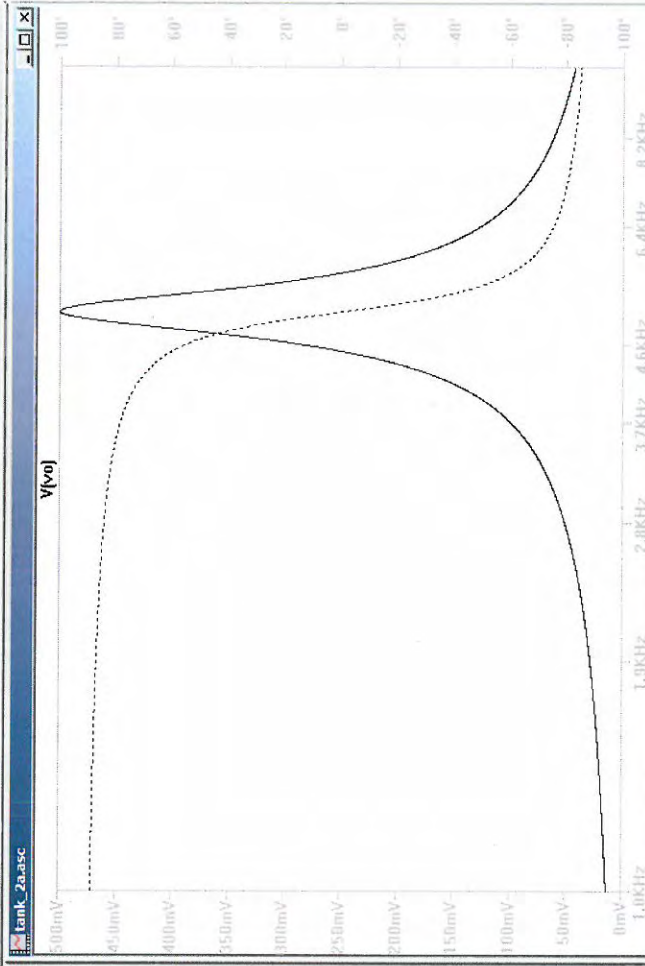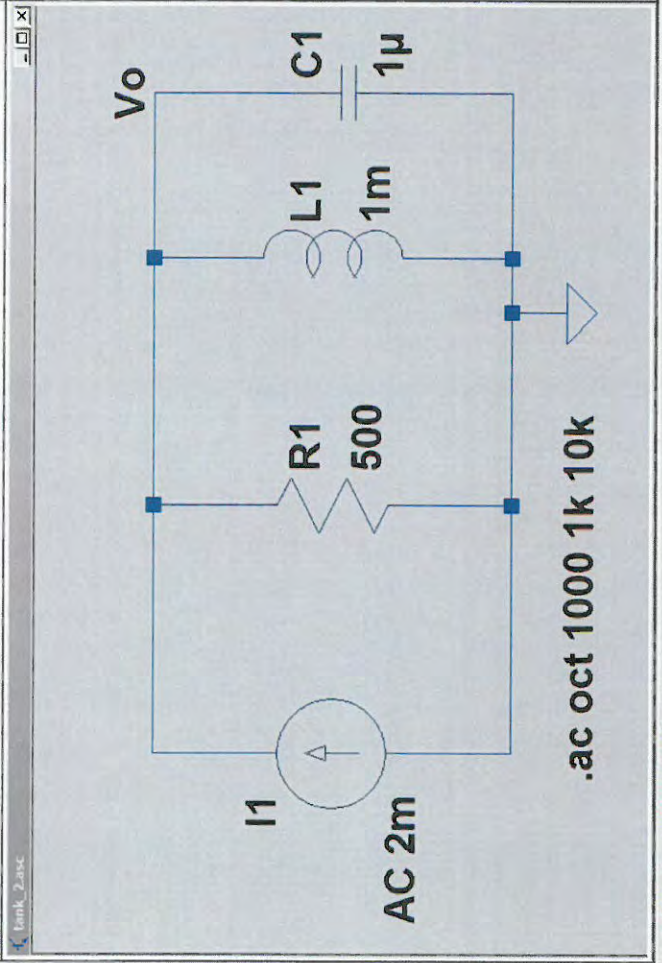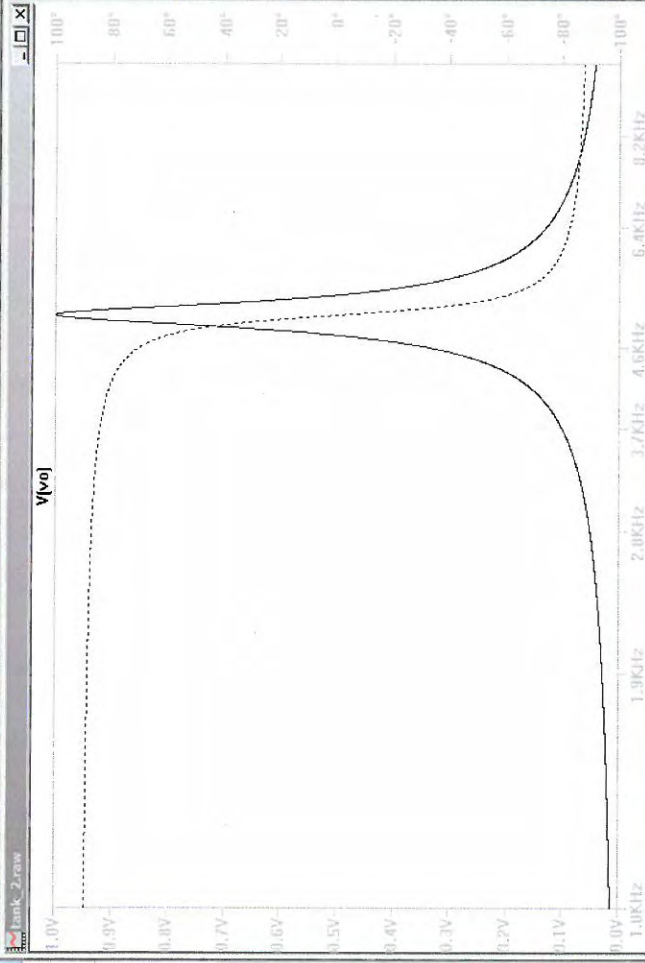

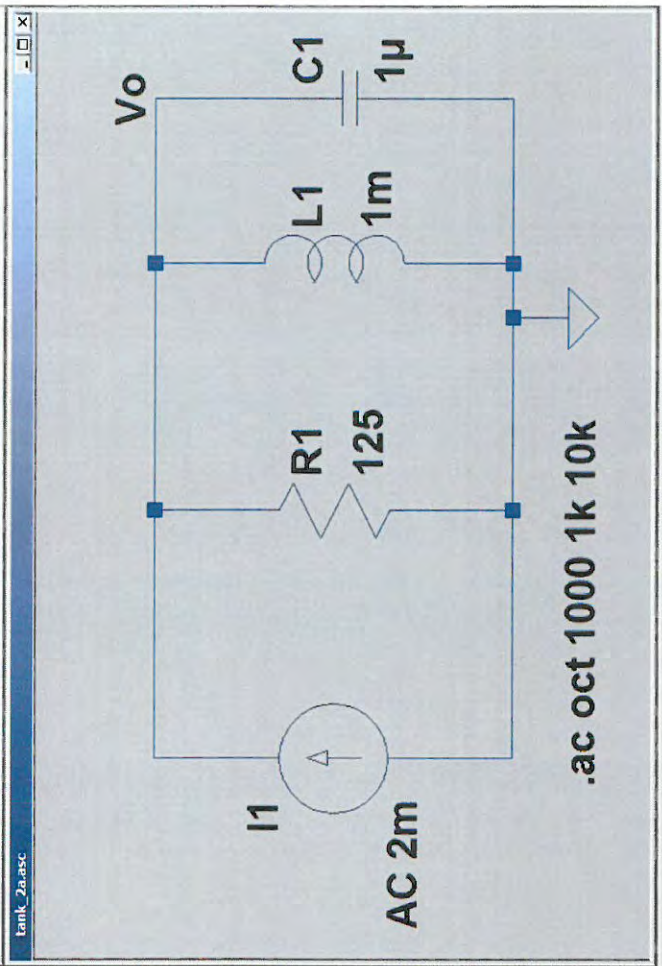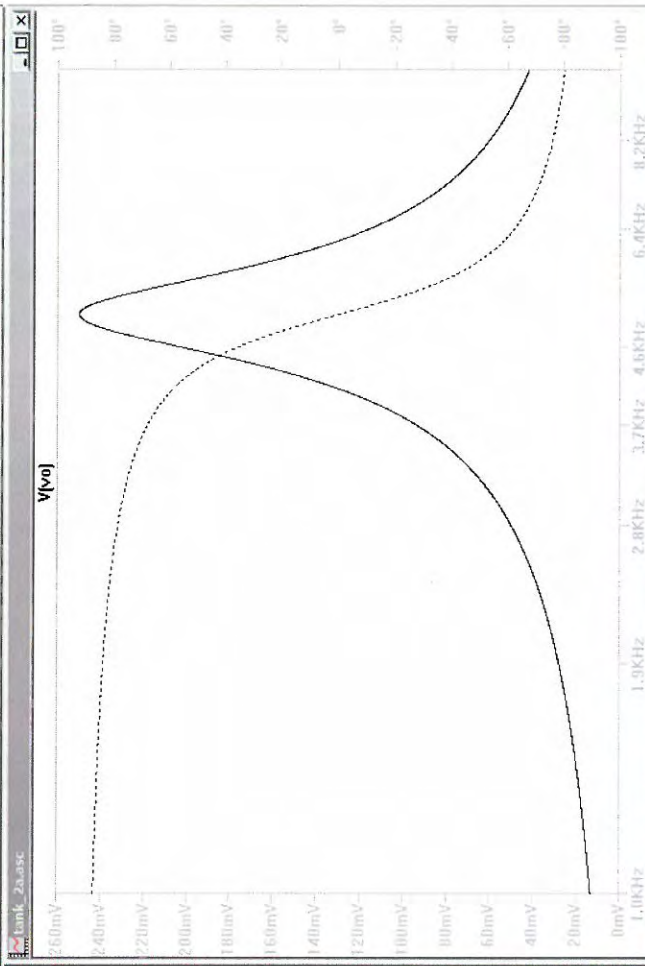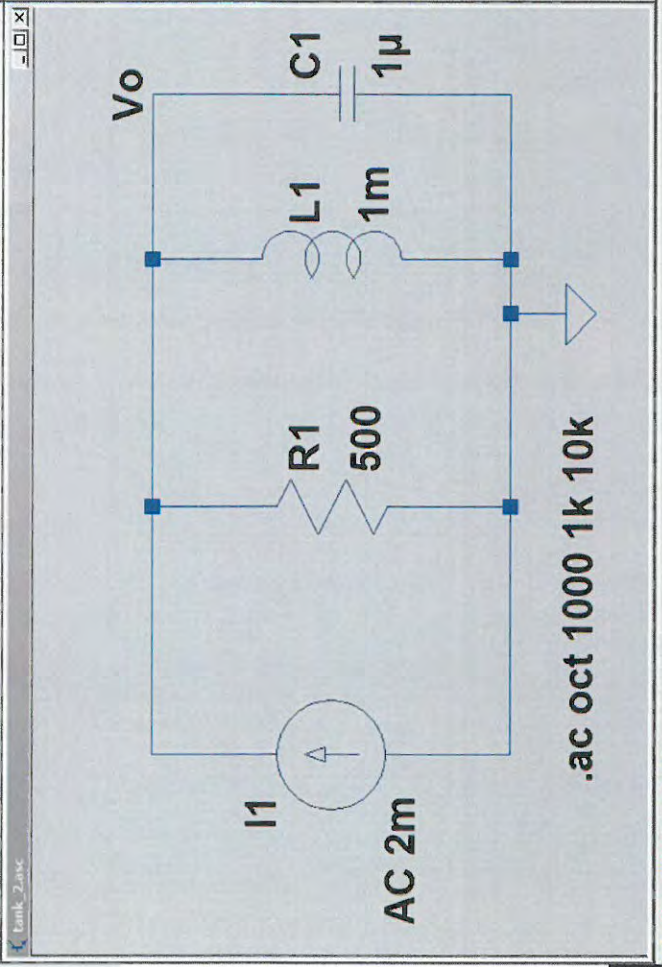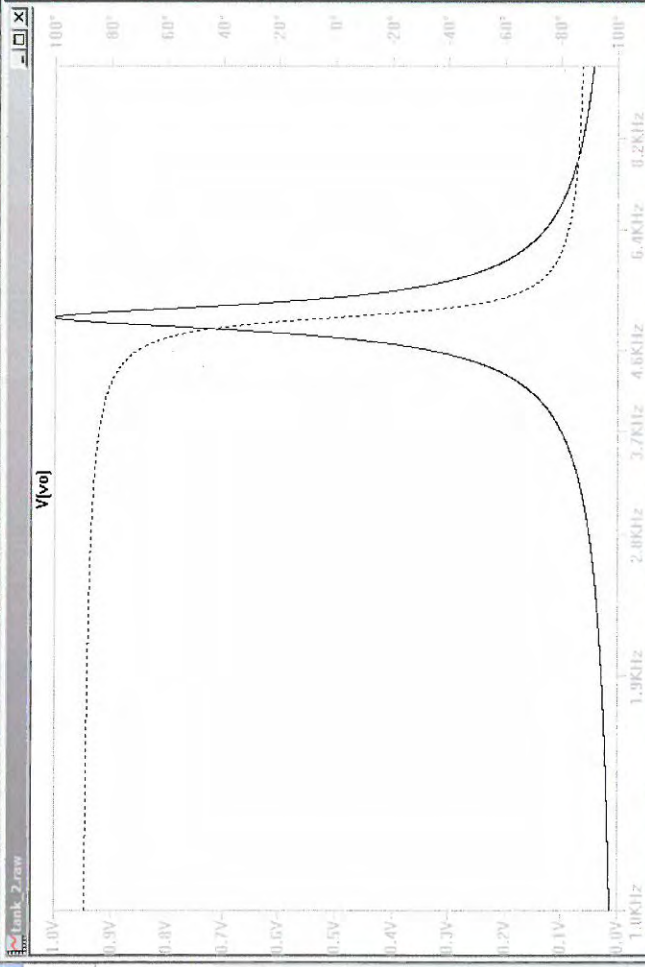

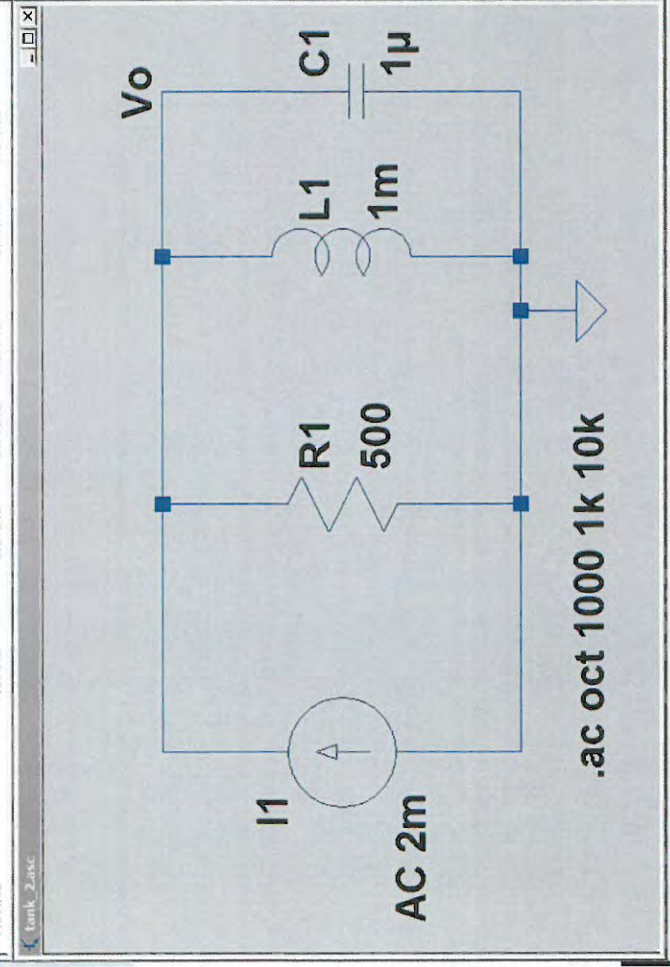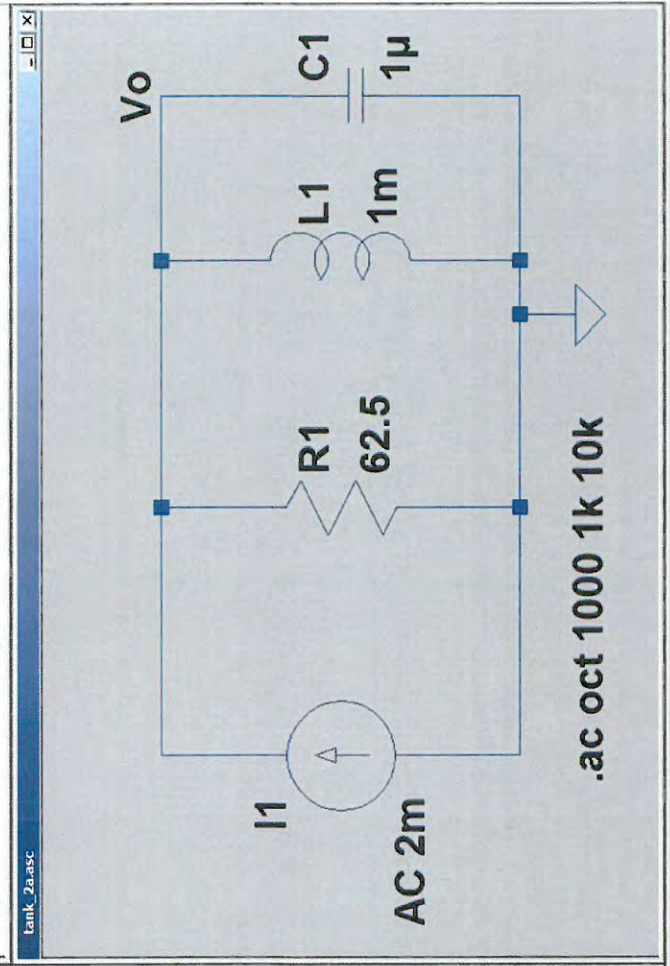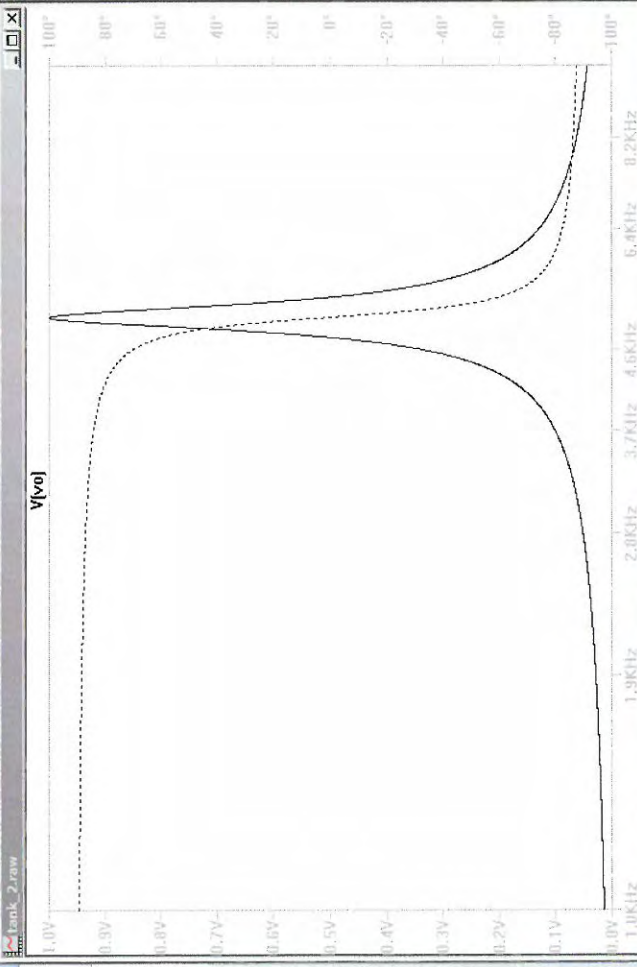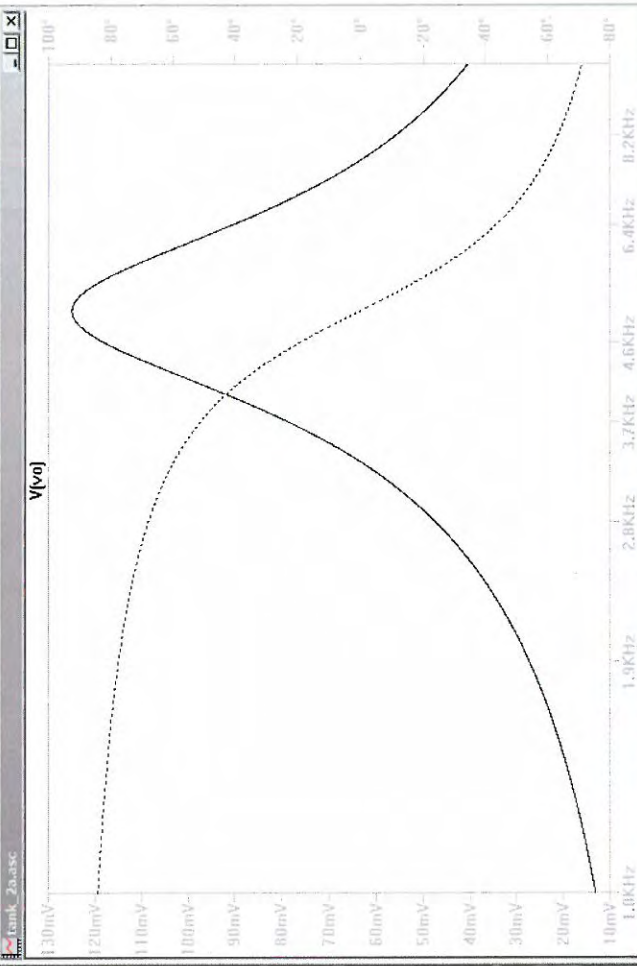

SERIES RLC ($\alpha = \frac{R}{2L}$)

$R \uparrow$ $\alpha \uparrow$ $Q \downarrow$ RINGING \downarrow

PARALLEL RLC ($\alpha = \frac{1}{2RC}$)

$R \uparrow$ $\alpha \downarrow$ $Q \uparrow$ RINGING \uparrow

CRITICAL DAMPING


$$\text{SERIES RLC: } \alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}$$


$$\alpha = \omega_0 \Rightarrow R = \frac{2L}{\sqrt{LC}}, \boxed{R = 2\sqrt{\frac{L}{C}}}$$

$$\text{PARALLEL RLC: } \alpha = \frac{1}{2RC}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha = \omega_0 \Rightarrow \frac{\sqrt{LC}}{2C} = R, \boxed{R = \frac{1}{2}\sqrt{\frac{L}{C}}}$$


Example 9.7

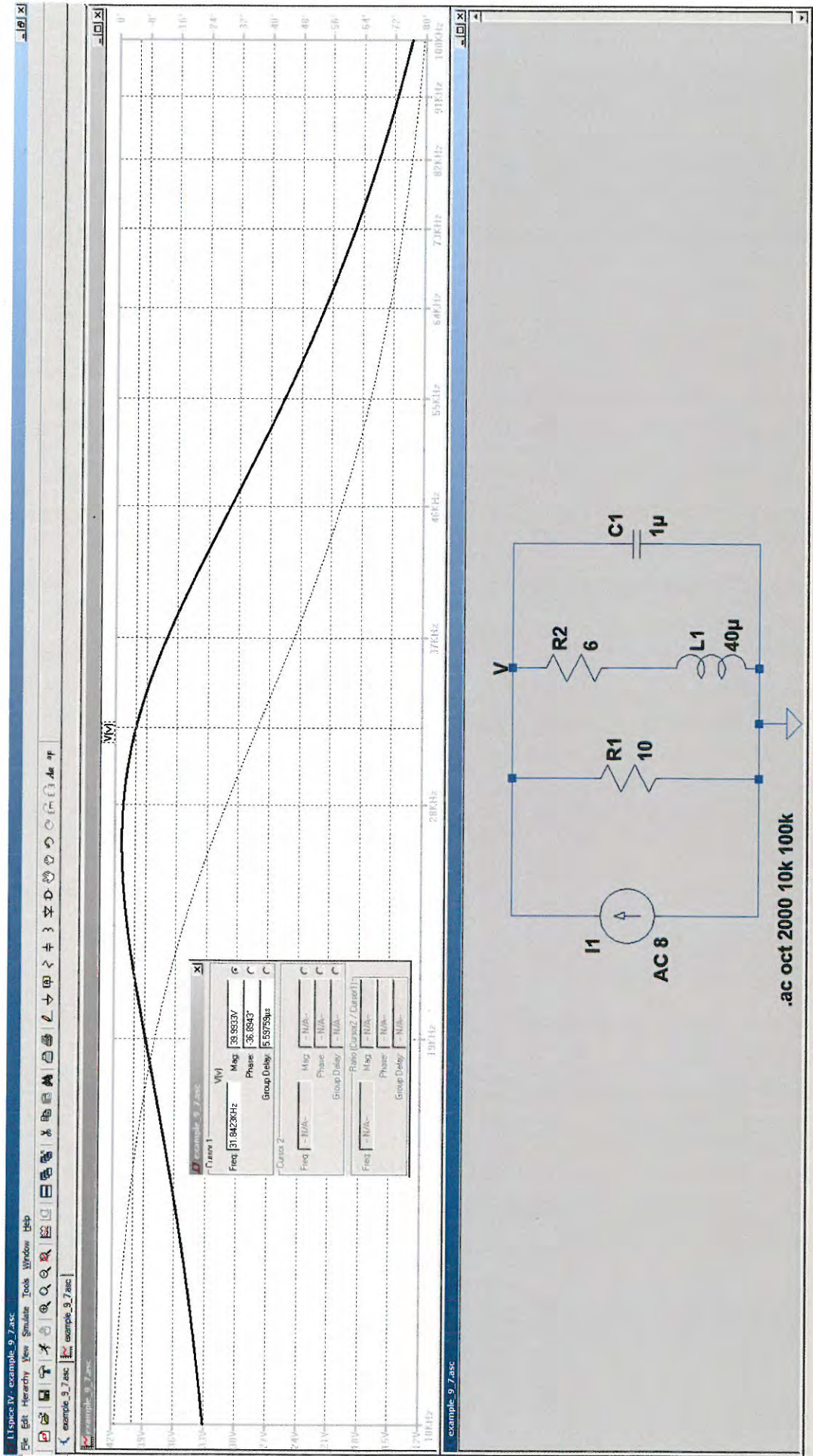

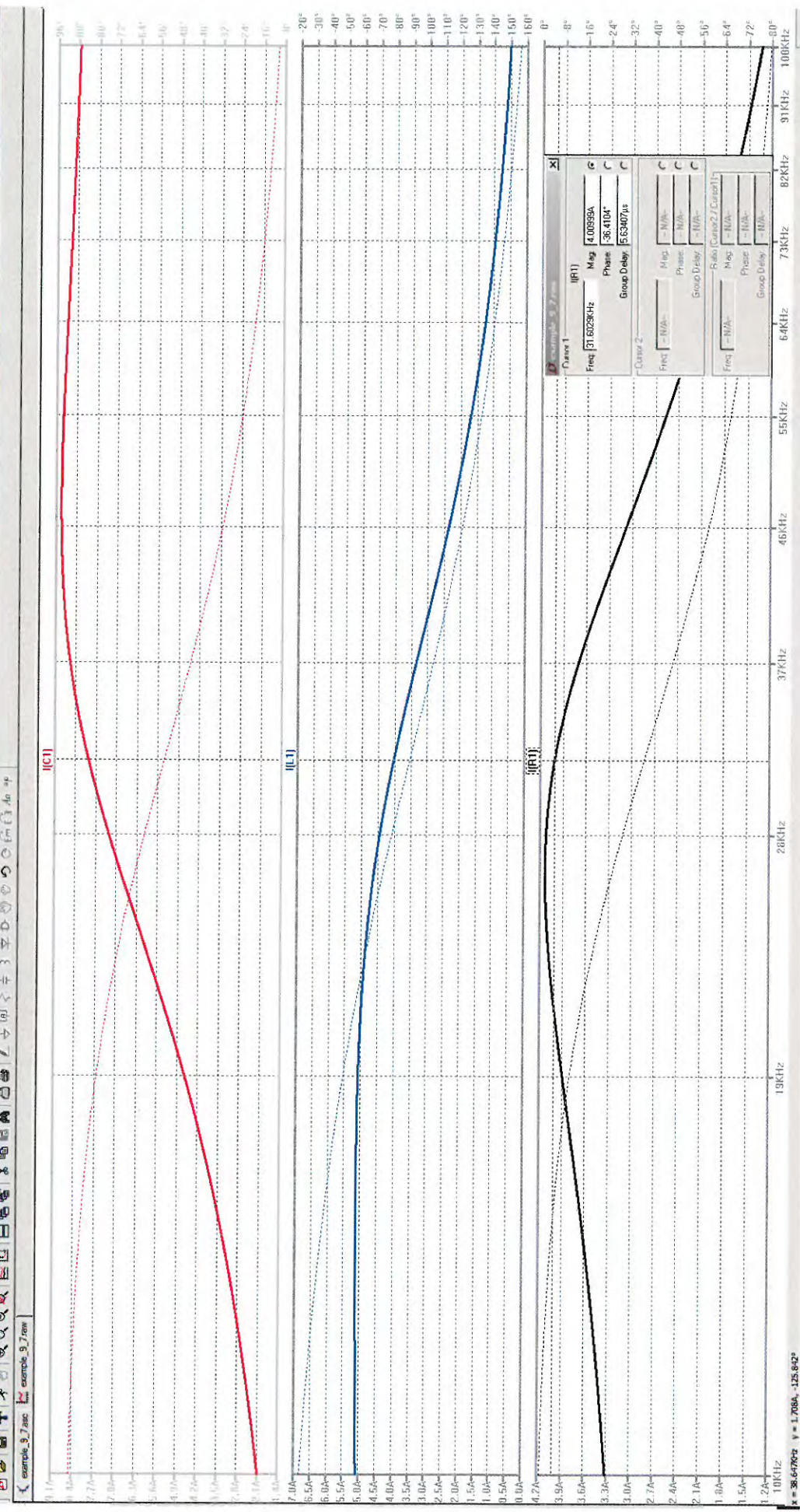

x = 36.6776Hz y = 1.708A -125.842°

$\Delta \leftrightarrow Y$

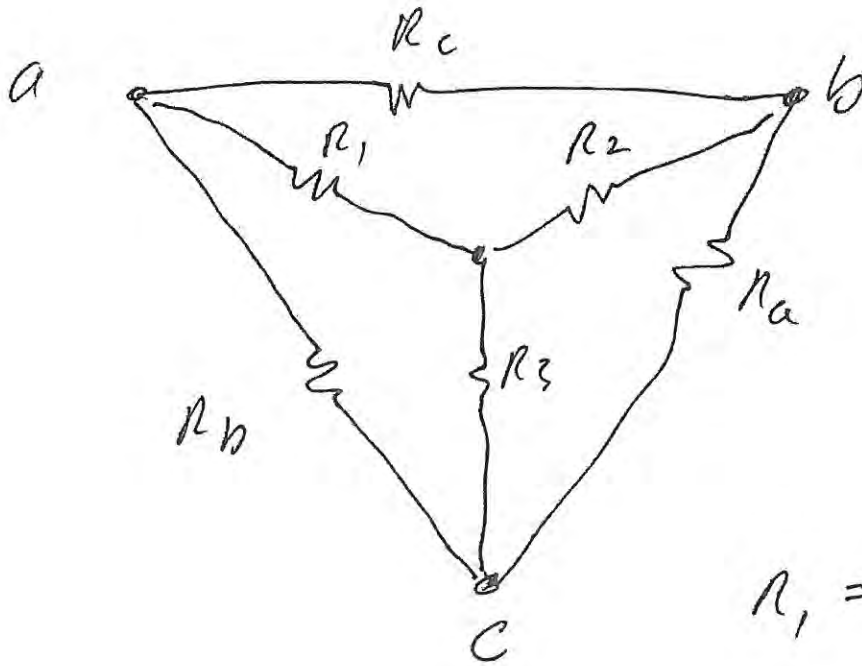

$$R_1 = \frac{R_b R_c}{R_5}$$


$$R_2 = \frac{R_a R_c}{R_5}$$

$$R_3 = \frac{R_a R_b}{R_5}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
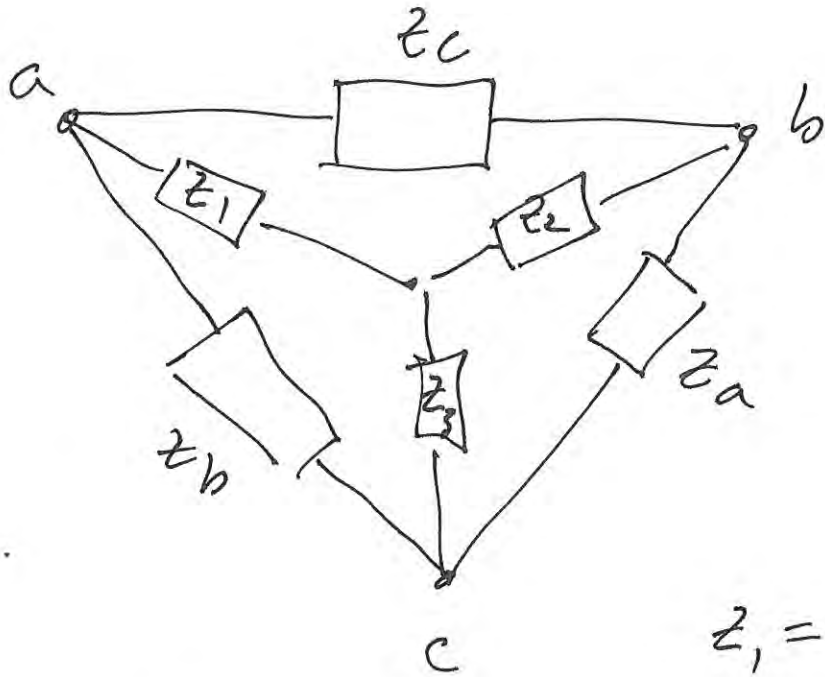
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



$$z_a = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_1}$$

$$z_b = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_2}$$




$$z_c = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_3}$$

$$z_1 = \frac{z_b z_c}{z_a + z_b + z_c}$$

$$z_2 = \frac{z_a z_c}{z_a + z_b + z_c}$$

$$z_3 = \frac{z_a z_b}{z_a + z_b + z_c}$$

EXAMPLE 9.8 $\Delta \rightarrow Y$

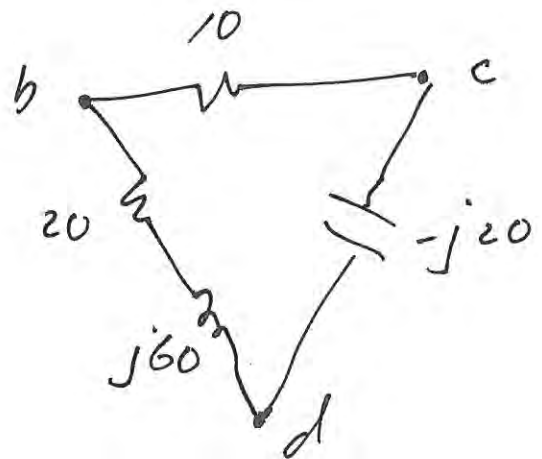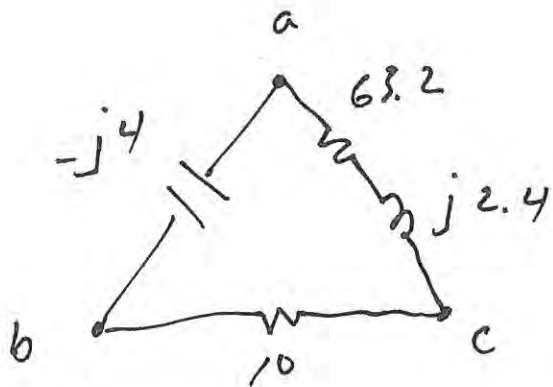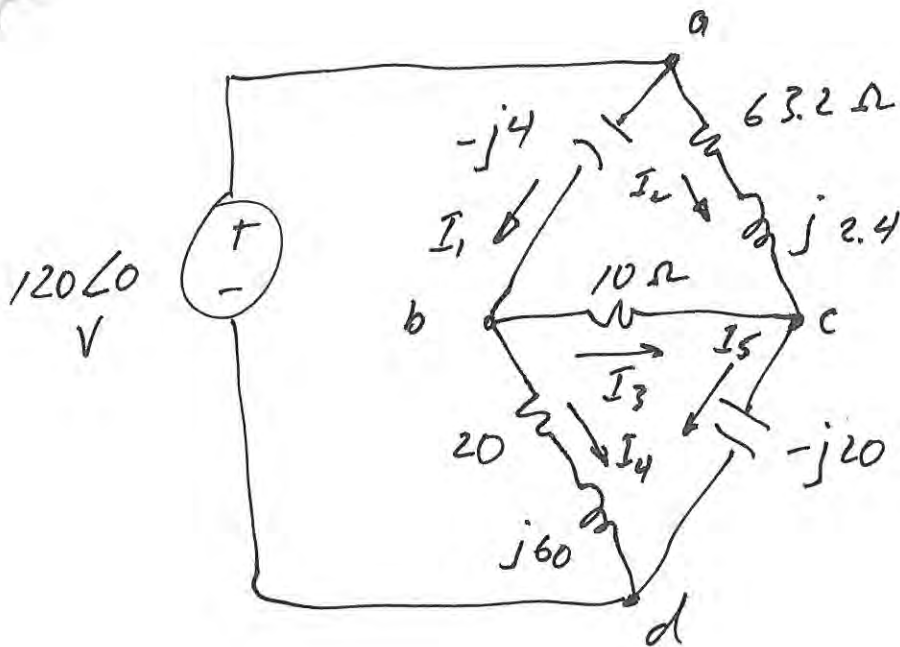


WHICH Δ TO TRANSFORM?

$$\text{LOOP: } R_T = -j4 + 63.2 + j2.4 + 10$$

$$= 73.2 - j1.6$$

$$R_T = 10 - j20 + j60 + 20$$

$$= 30 + j40$$

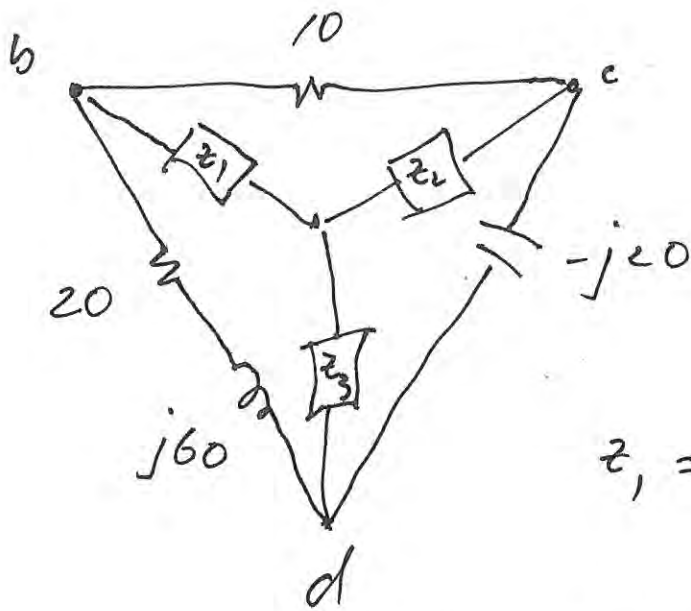

$$z_1 = \frac{(10)(20+j60)}{R_T} = \frac{200(1+j3)}{30+j40}$$

$$z_2 = \frac{(10)(-j20)}{R_T} = \frac{-j200}{30+j40}$$

$$z_3 = \frac{(20+j60)(-j20)}{R_T} = \frac{400(3-j1)}{30+j40}$$

HOW TO CALCULATE - LEAVE IN RECT
OR CONVERT TO POLAR?

$$z_1 = \frac{200(1+j3)}{10(3+j4)} \frac{(3-j4)}{(3-j4)} = \frac{200(3-j4+j9+12)}{10(9+16)}$$


$$z_1 = \frac{200}{250}(15+j5) = 12+j4$$

$$z_2 = \frac{-200(j)(3-j4)}{10(3+j4)(3-j4)} = \frac{-200(4+j3)}{10(25)}$$

$$= -\frac{16}{5} - j\frac{12}{5} = -3.2 - j2.4$$

$$z_3 = \frac{400(3-j1)(3-j4)}{10(3+j4)(3-j4)} = \frac{400(9-j12-j3-4)}{10(25)}$$

$$= \frac{400}{250}(5-j15) = 8 - j24$$

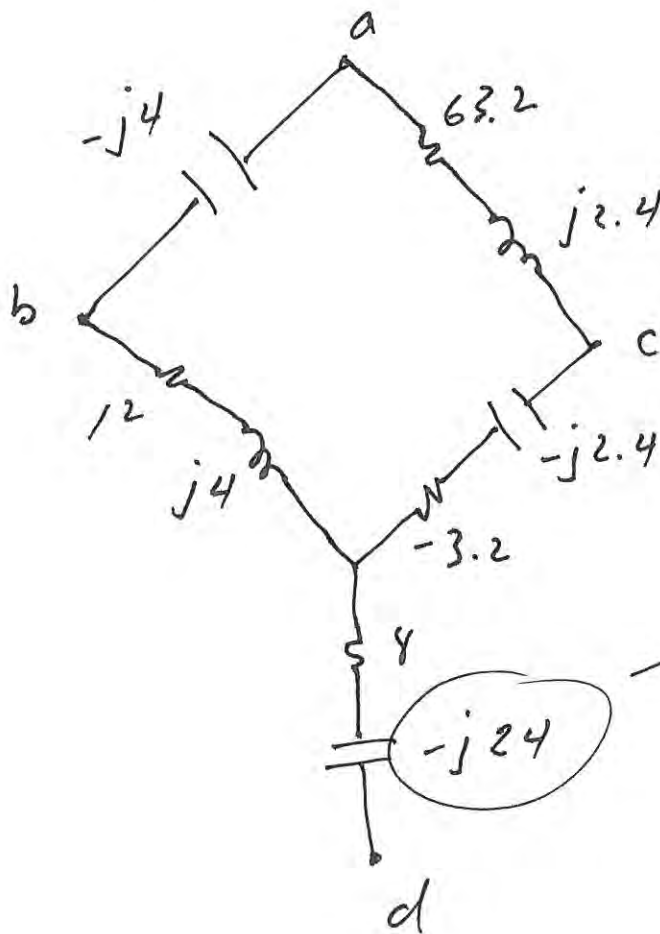


note typo in fig 9.22

✓ ASSESSMENT PROBLEM

Objective 3—Know how to use circuit analysis techniques to solve a circuit in the frequency domain



9.9 Use a Δ -to-Y transformation to find the current I in the circuit shown.

Answer: $I = 4 \angle 28.07^\circ$ A.

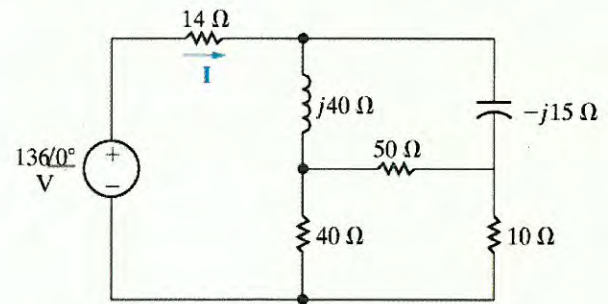

NOTE: Also try Chapter [Problem 9.42](#).


EXAMPLE 9.9 SOURCE TRANSFORMATIONS

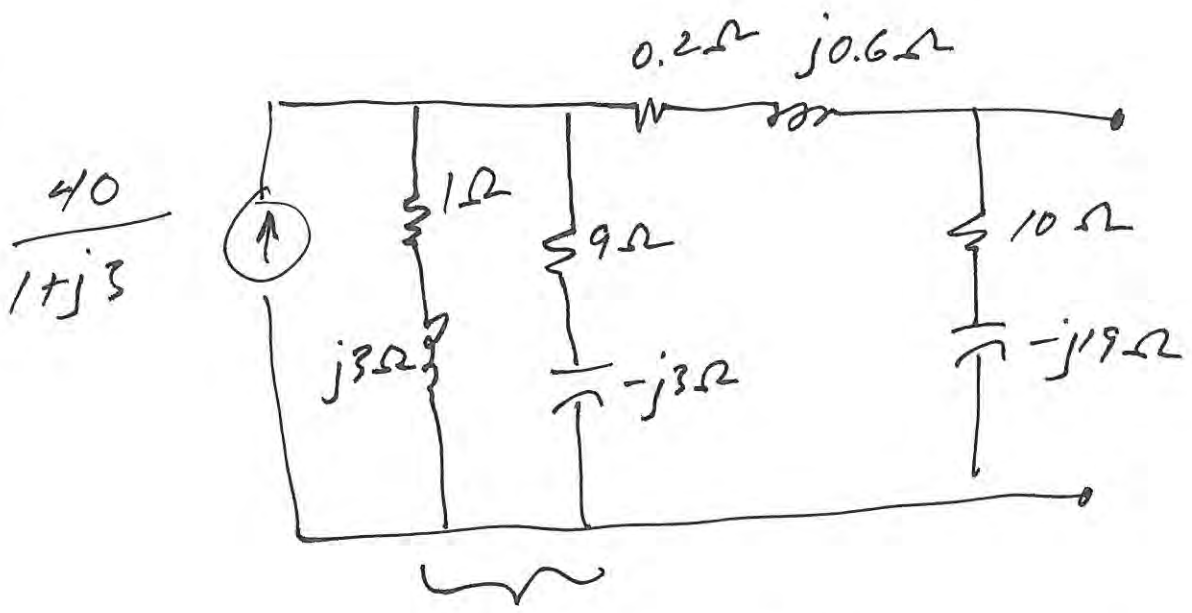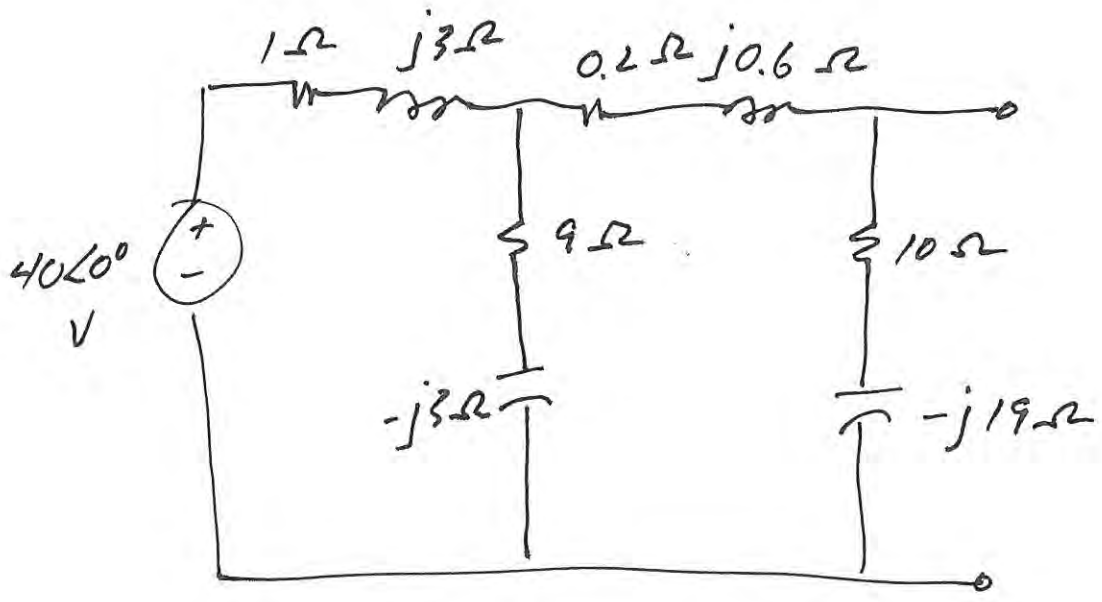

$$Z_{EQ} = (1 + j3) \parallel (9 - j3)$$

$$= \frac{(1 + j3)(9 - j3)}{1 + j3 + 9 - j3} = \frac{18 + j24}{10}$$


$$Z_{EQ} = 1.8 + j2.4$$

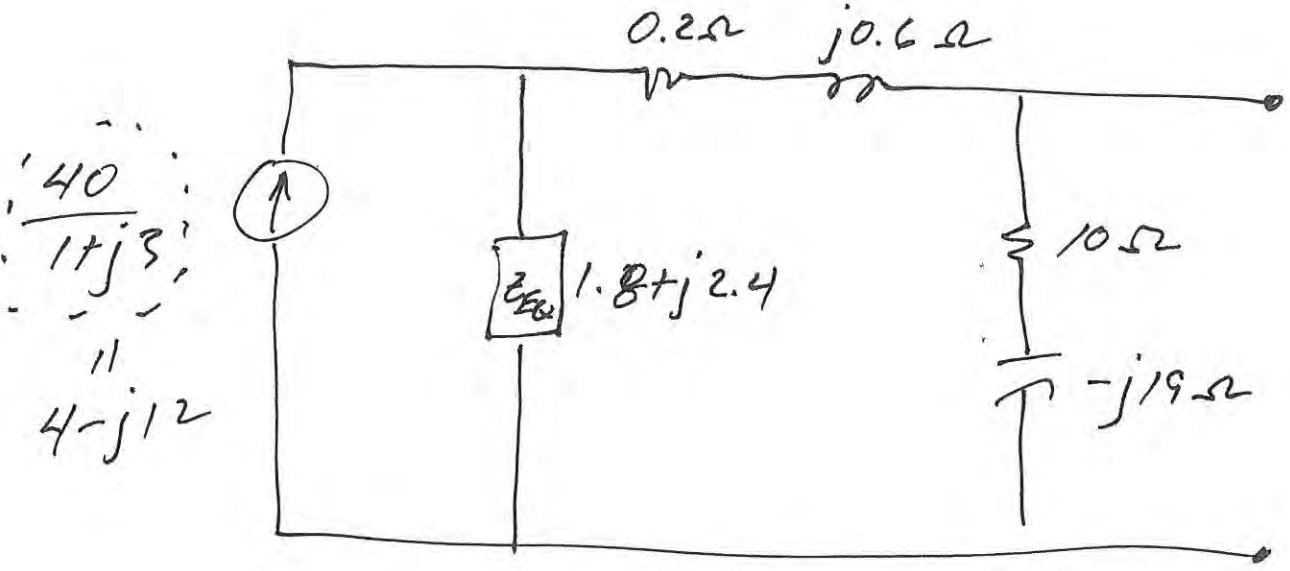

$$\frac{40}{1+j3}$$

||


$$4-j12$$

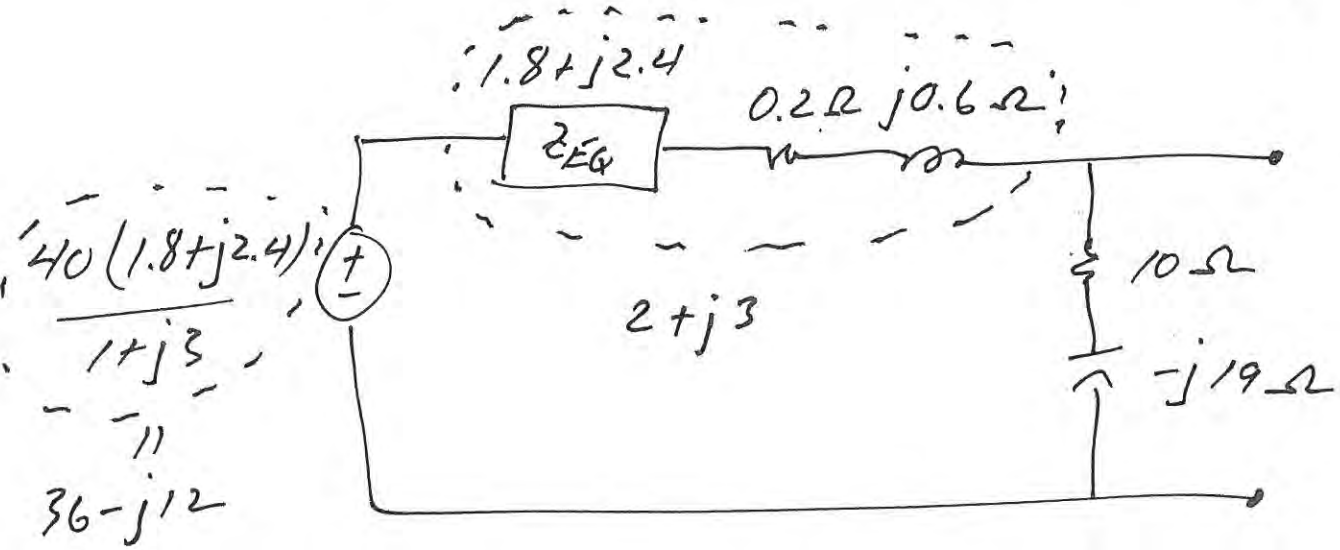

$$\frac{40(1.8+j2.4)}{1+j3}$$

||

$$36-j12$$

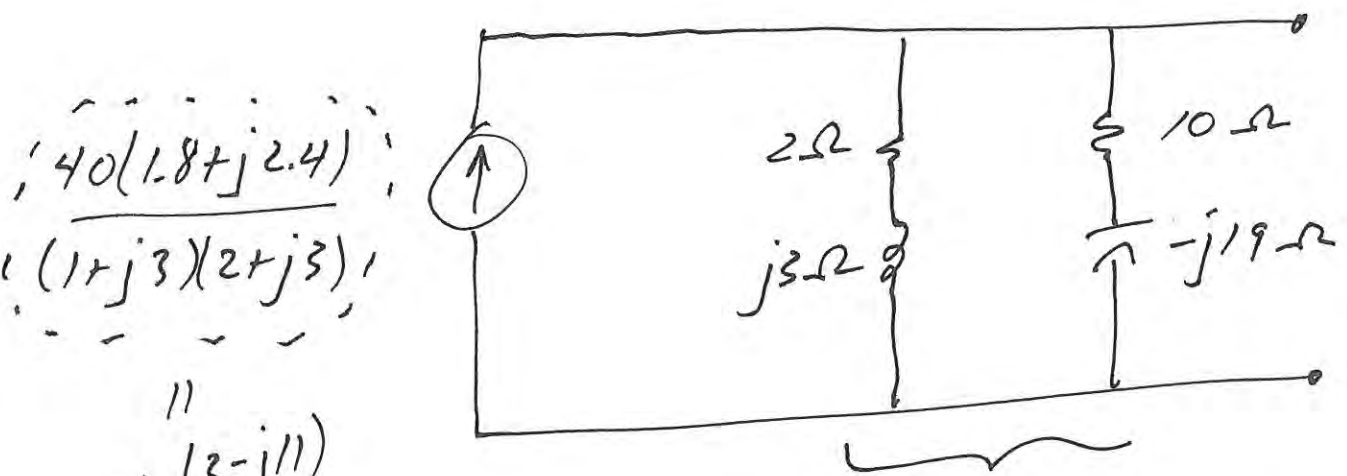

$$\frac{40(1.8+j2.4)}{(1+j3)(2+j3)}$$

||


$$12(3-j11)$$

13

$$Z_{EQ} = \frac{(2+j3)(10-j19)}{2+j3+10-j19}$$

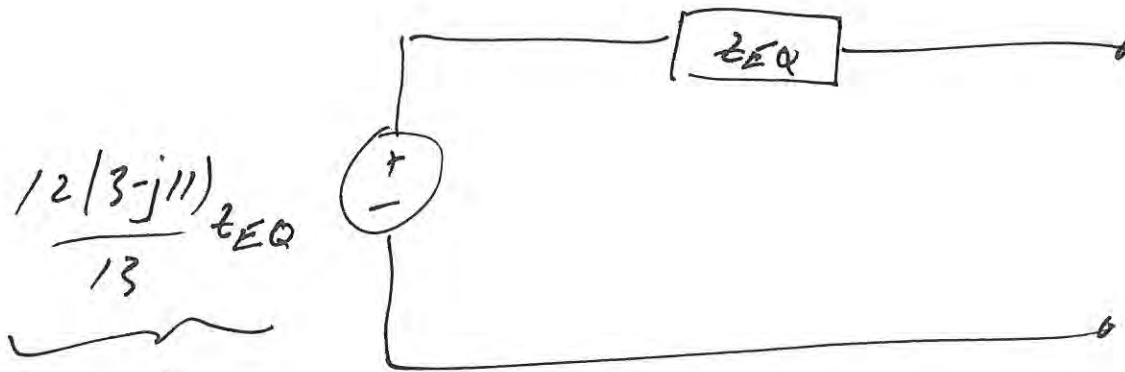
(7)

$$z_{EQ} = \frac{263 + j284}{100} = 2.63 + j2.84 \Omega$$



$$\frac{12(3-j11)}{13} z_{EQ}$$
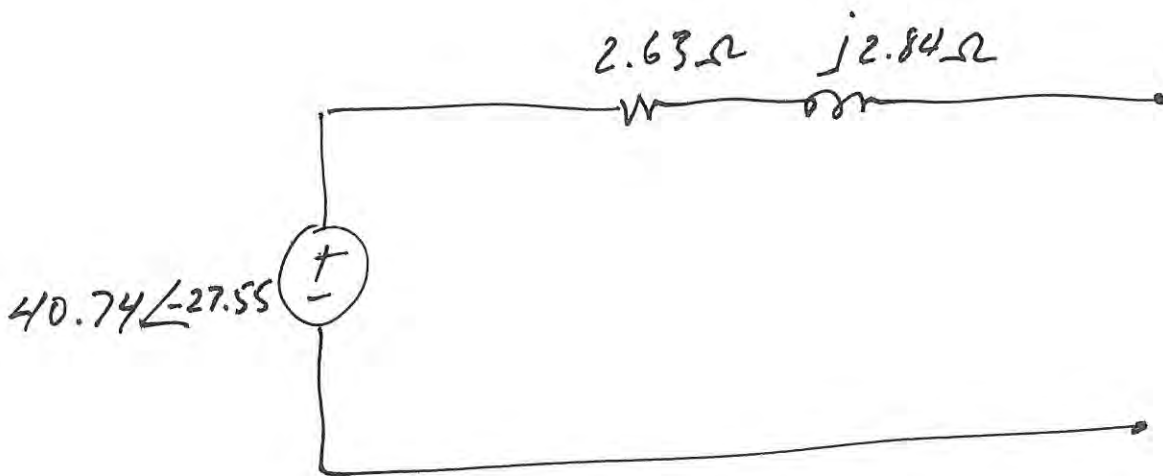
$$V = \frac{12(3-j11)}{13} \left(\frac{263 + j284}{100} \right) = 36.12 - j18.84 \Omega$$



$$40.74 \angle -27.55^\circ$$


MY TIME DOMAIN CKT CHOSE

$$j3\Omega = j\omega L\Omega$$

$$\text{WITH } \omega = 5,000 \text{ RAD/S}$$


$$\Rightarrow j3\Omega = j(5,000)(0.6\text{mH})$$


FINAL TIME DOMAIN EQ CKT IS

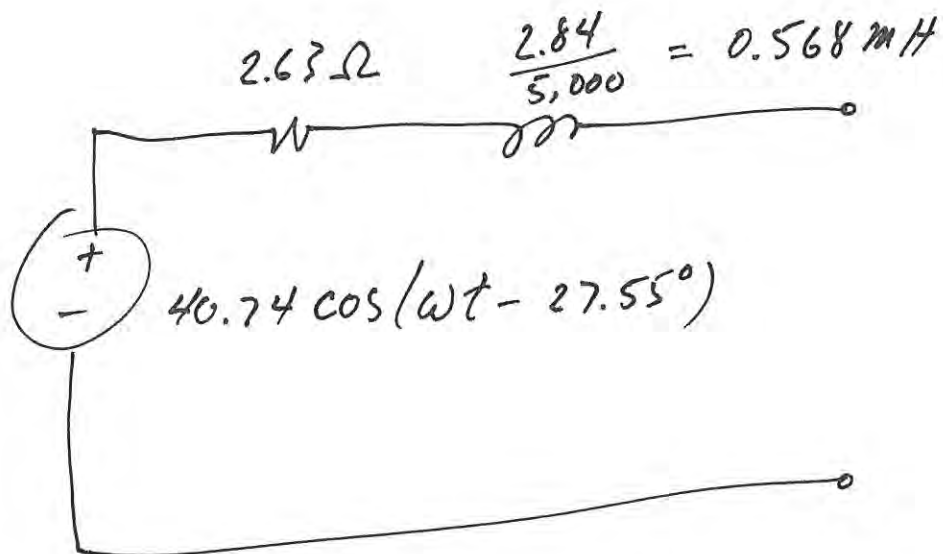

IS THIS VALID FOR ARBITRARY
FREQUENCY, ω ?

Example 9.9

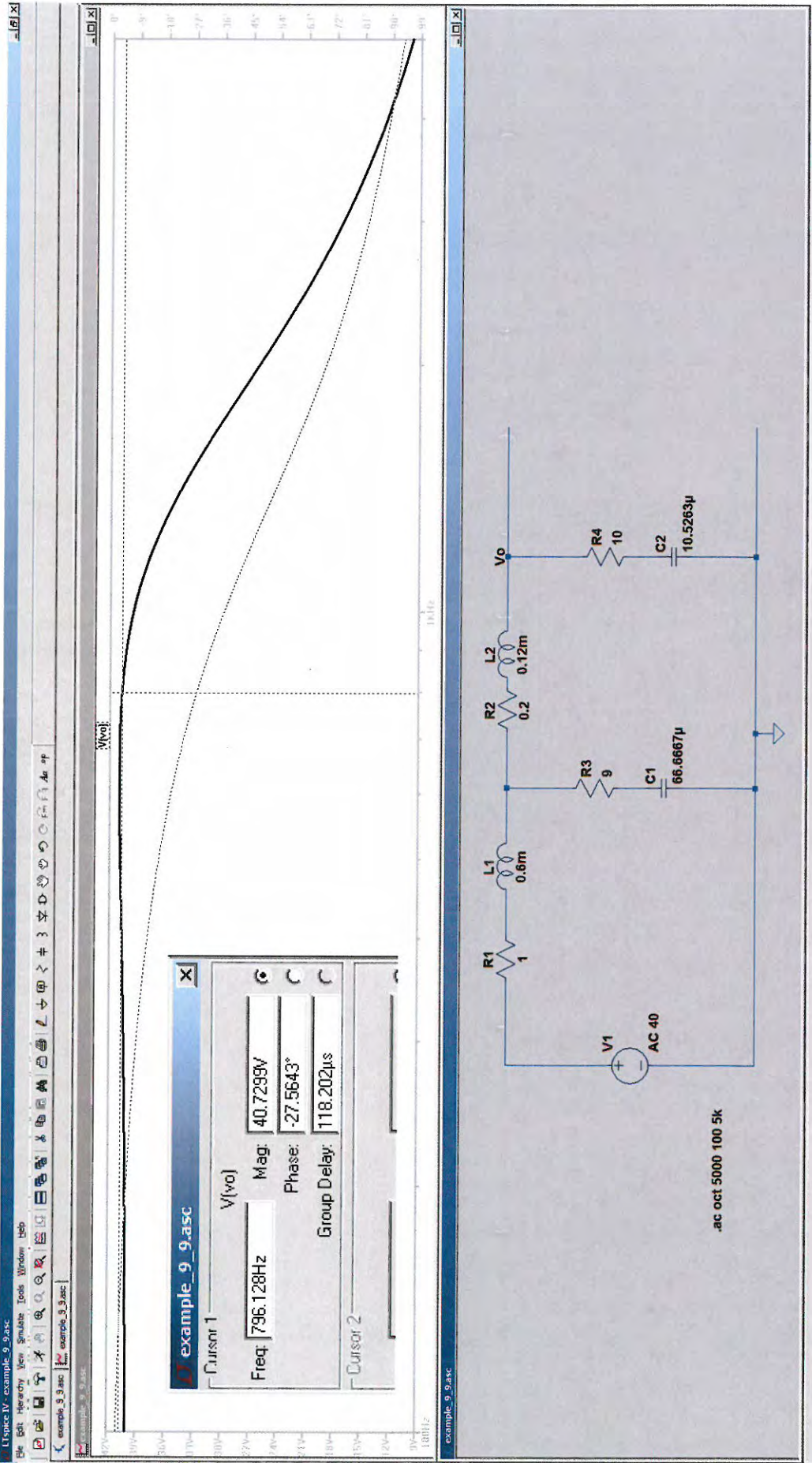

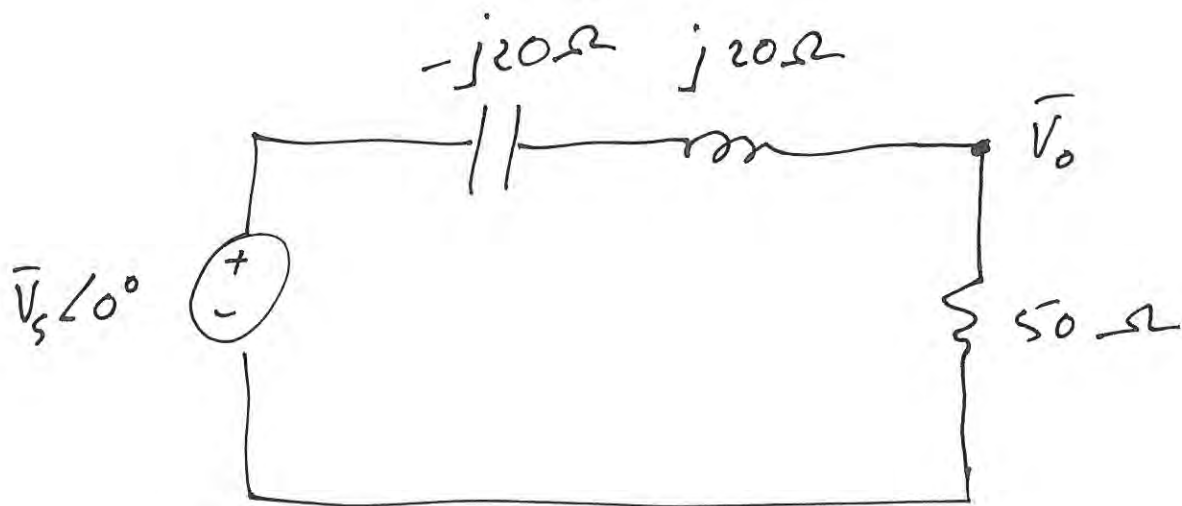




VOLTAGE DIVISION:


$$\bar{V}_o = \frac{\bar{V}_s (50)}{-j20 + j20 + 50} = \bar{V}_s$$

$$\bar{V}_o = \bar{V}_s$$

GENERAL SOLUTION ?

EXAMPLE 9.10 THEVENIN EQ IN FREQ DOMAIN

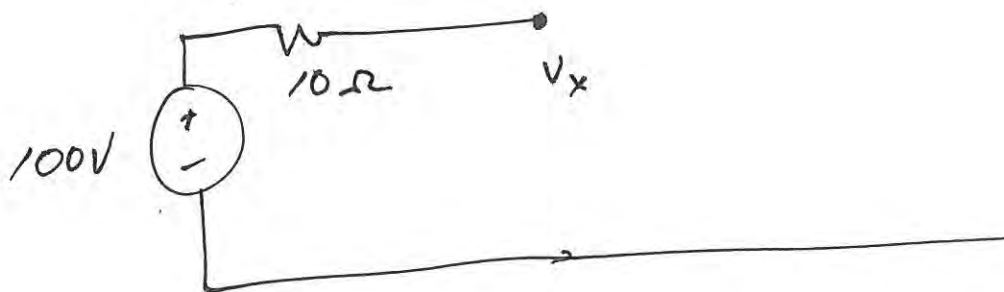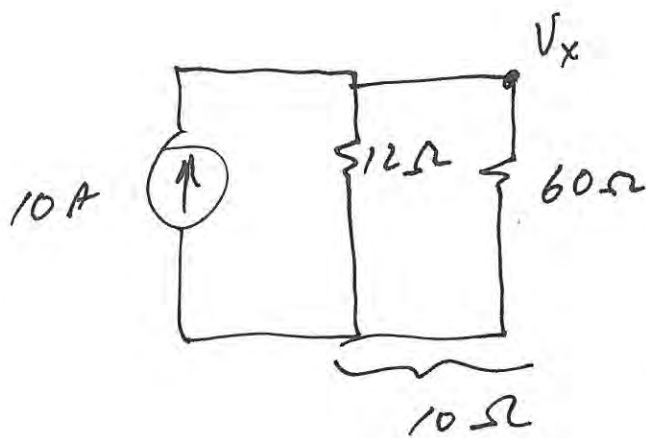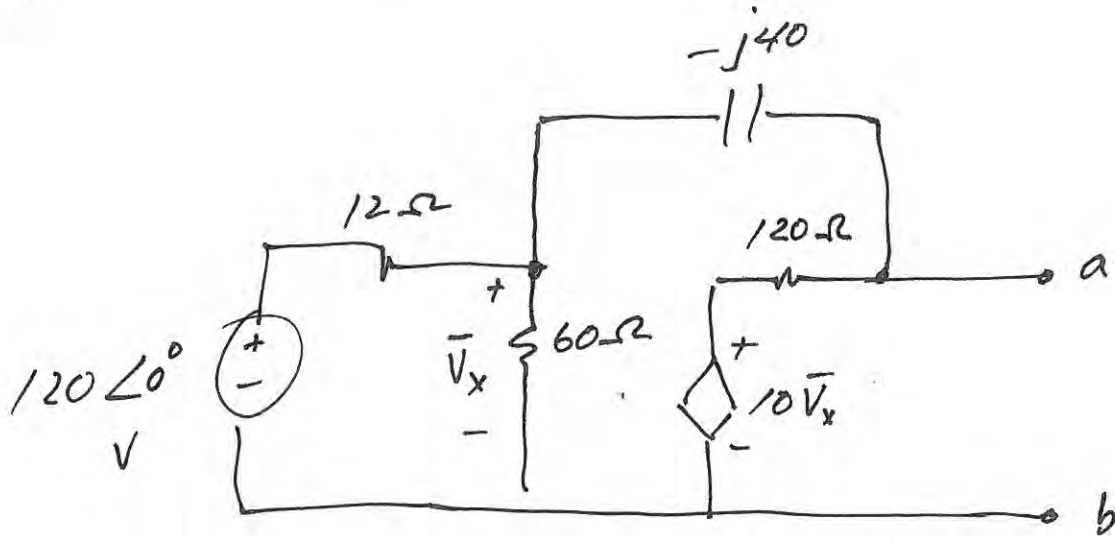

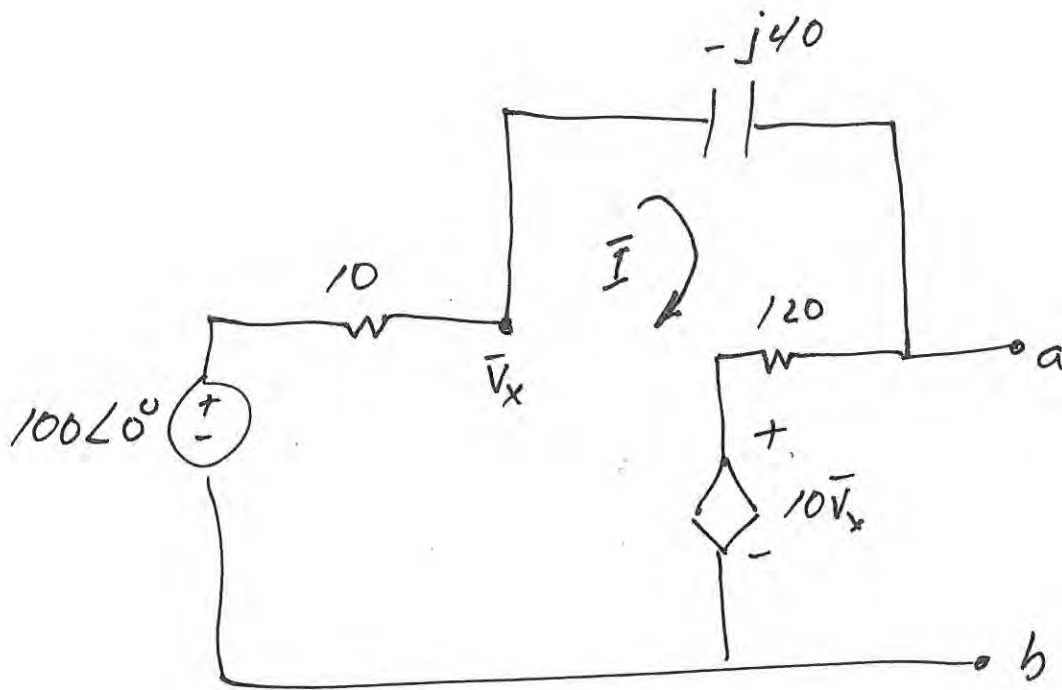

MESH EQ

$$100 - 10\bar{I} - (-j40)\bar{I} - 120\bar{I} - 10\bar{V}_x = 0$$

$$\text{BUS: } 100 - 10\bar{I} = \bar{V}_x$$

$$100 - 10\bar{I} + j40\bar{I} - 120\bar{I} - 10(100 - 10\bar{I}) = 0$$

$$100 - 1,000 + \bar{I}(-10 + j40 - 120 + 100) = 0$$

$$-900 + \bar{I}(-30 + j40) = 0$$

$$\bar{I} = \frac{-900}{30 - j40}$$

$$\bar{V}_{ab} = \bar{V}_{TH} = 10\bar{V}_x + 120\bar{I}$$

$$\bar{V}_{TH} = 10(100 - 10\bar{I}) + 120\bar{I}$$


$$= 1,000 + 20\bar{I}$$

$$= 1,000 + 20\left(\frac{-900}{30 - j40}\right)$$

$$= 1,000 - \frac{1,800}{3 - j4}$$

$$= \frac{1,000(3 - j4) - 1,800}{3 - j4} = \frac{400(3 - j10)}{3 - j4}$$
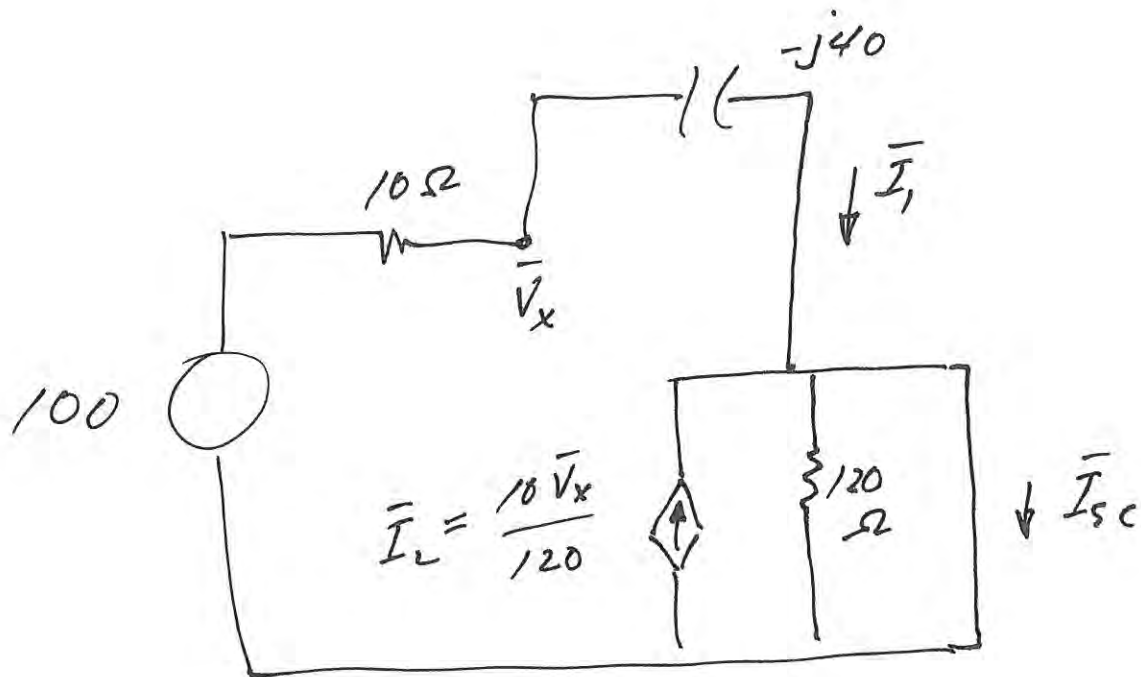
$$\bar{V}_{TH} = \frac{400(3 - j10)}{3 - j4}$$



TWO COMPONENTS OF $\bar{I}_{sc} = \bar{I}_1 + \bar{I}_L$

$$\bar{I}_{sc} = \bar{I}_1 + \frac{10\bar{V}_x}{120} \quad \text{BUT } 100 - 10\bar{I}_1 = \bar{V}_x$$

$$\text{AND } \bar{I}_1 = \frac{100}{10 - j40}$$

$$\bar{I}_{sc} = \bar{I}_1 + \frac{10}{120} (100 - 10\bar{I}_1)$$

$$= \frac{100}{12} + \frac{2\bar{I}_1}{12}$$

$$\bar{I}_{sc} = \frac{100}{12} \left(1 + \frac{2}{10 - j40} \right)$$

$$= \frac{100}{12} \left(1 + \frac{1}{5 - j20} \right) = \frac{100}{12} \left(\frac{5 - j20 + 1}{5 - j20} \right)$$


$$\bar{I}_{sc} = \frac{20}{6} \left(\frac{3-j10}{1-j4} \right)$$

$$Z_{TH} = \frac{\bar{V}_{TH}}{\bar{I}_{sc}} = \frac{400(3-j10)}{(3-j4)} \cdot \frac{6(1-j4)}{20(3-j10)}$$


$$= \frac{20.6(1-j4)(3+j4)}{(3-j4)(3+j4)}$$

$$= \frac{20.6}{25} (1-j4)(3+j4)$$
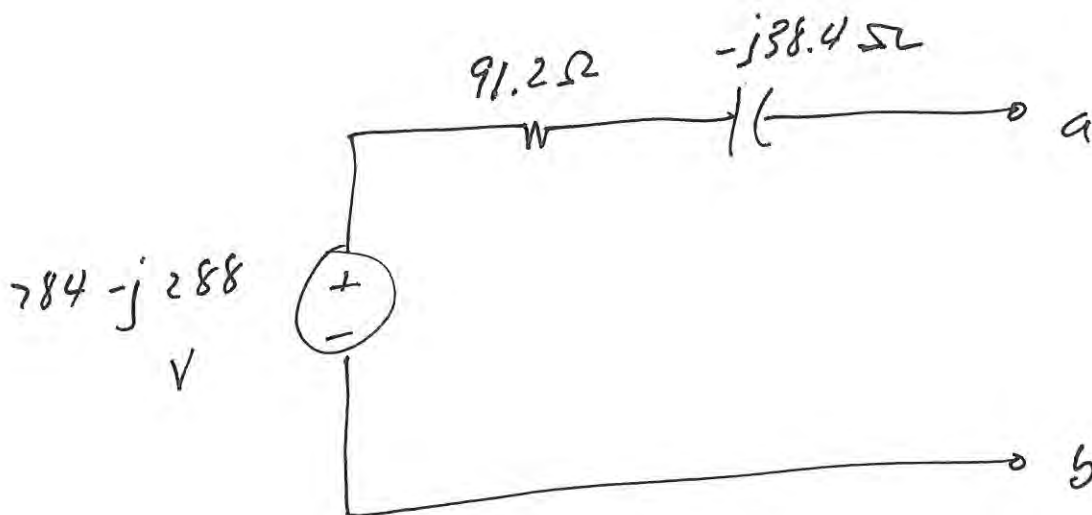
$$Z_{TH} = \frac{120}{25} (19-j8) = 91.2 - j38.4 \Omega$$



ALTERNATE
USING TEST SOURCE

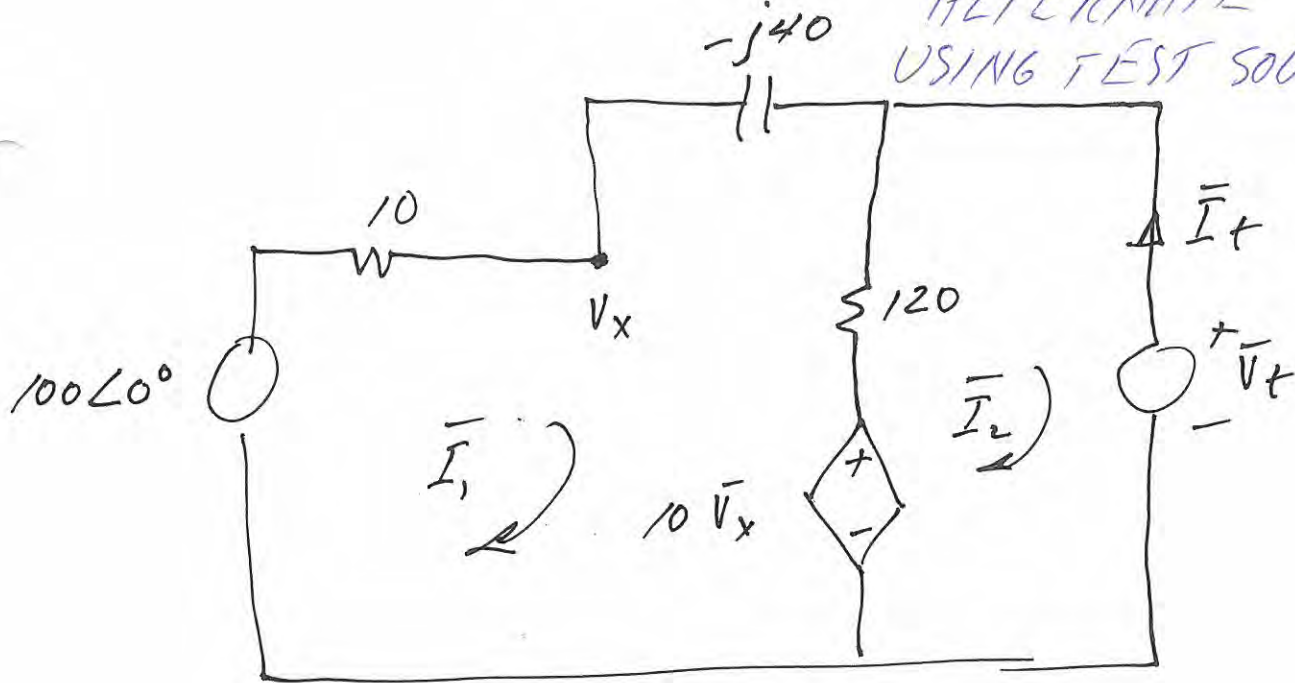

$$100 - 10\bar{I}_1 - (-j40)\bar{I}_1 - 120(\bar{I}_1 - \bar{I}_2) - 10\bar{V}_x = 0$$

$$10\bar{V}_x - 120(\bar{I}_2 - \bar{I}_1) - V_t = 0$$

$$\text{BUT } 100 - 10\bar{I}_1 = \bar{V}_x$$

$$100 - 10\bar{I}_1 + j40\bar{I}_1 - 120(\bar{I}_1 - \bar{I}_2) - 10(100 - 10\bar{I}_1) = 0$$

$$10(100 - 10\bar{I}_1) - 120(\bar{I}_2 - \bar{I}_1) - V_t = 0$$

$$\bar{I}_t = \frac{\text{DET} \begin{vmatrix} (-30 + j40) & 900 \\ 20 & V_t - 1000 \end{vmatrix}}{\text{DET} \begin{vmatrix} (-30 + j40) & -120 \\ 20 & 120 \end{vmatrix}}$$

$$D = 120(-30 + j40) + 120(20)$$

$$= 120(-30 + j40 + 20)$$

$$= 120(-10 + j40) = 1,200(-1 + j4)$$

$$N = (-30 + j40)(V_t - 1,000) - 18,000$$

$$\bar{I}_t = \frac{(-30 + j40)(V_t - 1,000) - 18,000}{1,200(-1 + j4)}$$

$$\bar{I}_t = 1,200(-1 + j4) + 18,000$$

$$= (-30 + j40)(V_t - 1,000)$$

$$\bar{I}_1 (-10 + j40 - 120 + 100) + \bar{I}_2 (120) = 1,000 - 100$$

$$\bar{I}_1 (-100 + 120) + \bar{I}_2 (-120) = V_t - 1,000$$

$$\bar{I}_2 = -\bar{I}_1$$

$$\bar{I}_1 (-30 + j40) + \bar{I}_1 (-120) = 900$$

$$\bar{I}_1 (20) + \bar{I}_1 (120) = V_t - 1,000$$

$$\bar{I}_t \frac{1,200(-1+j4)}{-30+j40} + \frac{18,000}{-30+j40} = V_t - 1,000$$

$$V_t = \frac{120(-1+j4)}{-3+j4} \bar{I}_t + \frac{1,800}{-3+j4} + 1,000$$

$$R_{th} = \frac{120(-1+j4)}{-3+j4} = \frac{120(1-j4)(3+j4)}{(3-j4)(3+j4)}$$

$$= \frac{120(1-j4)(3+j4)}{25}$$

$$= \frac{120(3+j4-j12+16)}{25}$$

$$= \frac{120(19-j8)}{25}$$

$$= 91.2 - j38.4 \Omega$$

$$V_{TH} = \frac{1,800}{-3+j4} + 1,000$$

$$= \frac{1,800 + 1,000(-3+j4)}{-3+j4}$$

$$= \frac{-1,200 + j4000}{-3+j4} = \frac{1,200 - j4000}{3-j4}$$

$$= \frac{100(12-j40)(3+j4)}{(3-j4)(3+j4)}$$

$$= \frac{4}{25} \frac{100(12-j40)(3+j4)}{25}$$

$$= 4(36 + j48 - j120 + 160)$$

$$= 4(196 - j72)$$

$$V_{TH} = 784 - j288$$


ASSESSMENT PROBLEMS

Objective 3—Know how to use circuit analysis techniques to solve a circuit in the frequency domain

9.10 Find the steady-state expression for $v_o(t)$ in the circuit shown by using the technique of source transformations. The sinusoidal voltage sources are

$$v_1 = 240 \cos(4000t + 53.13^\circ) \text{ V},$$


$$v_2 = 96 \sin 4000t \text{ V}.$$

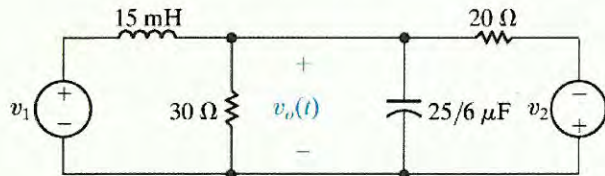

Answer: $48 \cos(4000t + 36.87^\circ) \text{ V}$

NOTE: Also try Chapter Problems 9.44, 9.45, and 9.48.

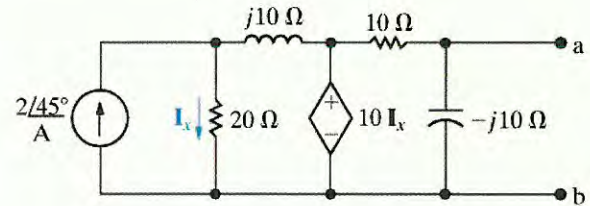9.11 Find the Thévenin equivalent with respect to terminals a,b in the circuit shown.



Answer: $V_{Th} = V_{ab} = 10 \angle 45^\circ \text{ V};$
 $Z_{Th} = 5 - j5 \Omega.$


ASSESSMENT PROBLEM

Objective 3—Know how to use circuit analysis techniques to solve a circuit in the frequency domain

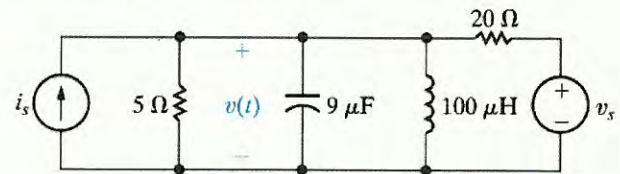9.12 Use the node-voltage method to find the steady-state expression for $v(t)$ in the circuit shown. The sinusoidal sources are $i_s = 10 \cos \omega t$ A and $v_s = 100 \sin \omega t$ V, where $\omega = 50$ krad/s.


Answer: $v(t) = 31.62 \cos(50,000t - 71.57^\circ)$ V.

NOTE: Also try Chapter Problems 9.54 and 9.58.




SIMPLIFICATIONS

①

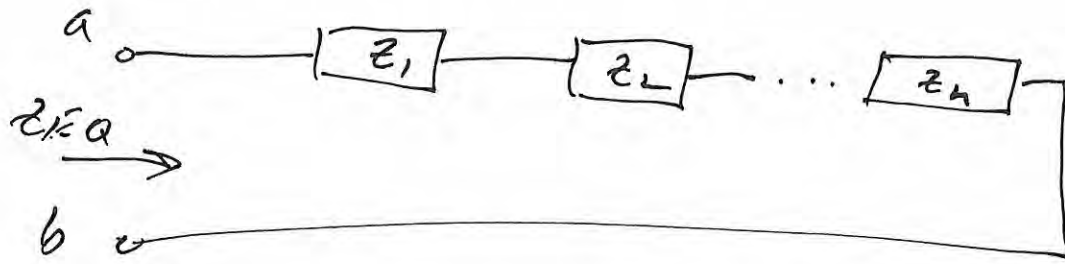

$$z_{EQ} = z_1 + z_2 + \dots + z_n$$

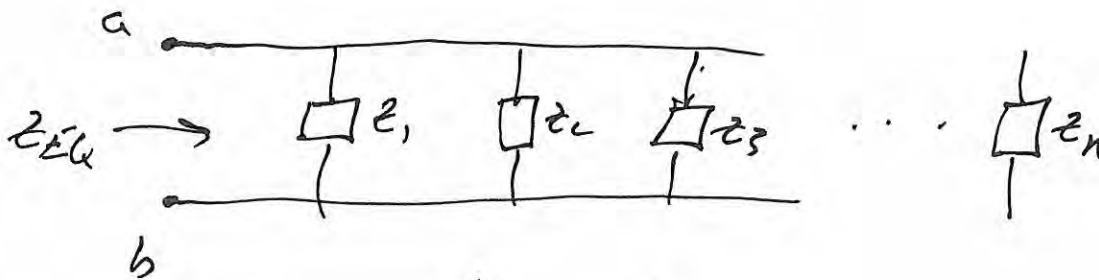

$$z_{EQ}^{-1} = \frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n}$$

SPECIAL CASE $n=2$: $z_{EQ} = \frac{z_1 z_2}{z_1 + z_2}$

OLIVIER
HEAVISIDE

EASIER WAY? YES - DEFINE ADMITTANCE

$$Y \equiv \frac{1}{z} = G + jB \quad (\text{SIEMENS})$$

$$[Y] = \sigma$$

$$\Rightarrow Y_{EQ} = Y_1 + Y_2 + \dots + Y_n$$

ERNST WERNER

$G \equiv$ CONDUCTANCE

VON SIEMENS


$B \equiv$ SUSCEPTANCE

SIEMENS

FOR CAPACITOR $Y = j\omega C$

FOR INDUCTOR $Y = 1/j\omega L$


EXAMPLE 9.7

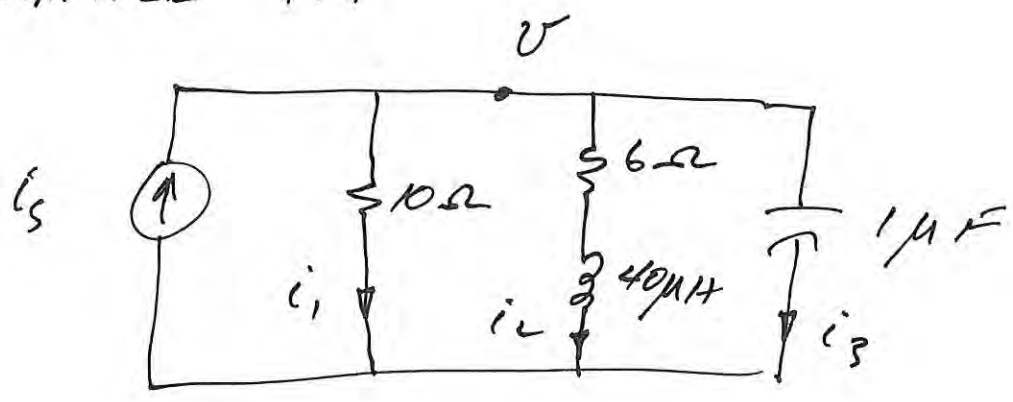

$i_s(t) = 8 \cos(200,000t) \text{ A}$

FIND:
 i_1, i_2, i_3, v

$\bar{I}_s = 8 \angle 0^\circ \text{ A}$

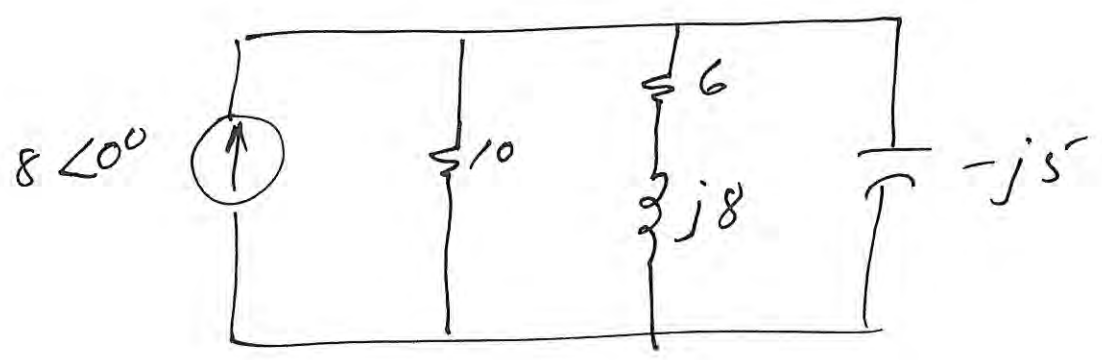

$$Y_1 = 0.10$$

$$Y_2 = \frac{1}{6+j8} = \frac{6-j8}{100} = 0.06 - j0.08$$

$$Y_3 = j0.2$$

$$Y_{EQ} = Y_1 + Y_2 + Y_3 = 0.16 + j0.12$$

$$= 0.20 \angle 36.87^\circ$$

$$Z_{EQ} = 5 \angle -36.87^\circ$$

$$\bar{V} = \bar{I}_S Z_{EQ} = 40 \angle -36.87^\circ$$

$$\bar{I}_1 = \frac{\bar{V}}{Z_1} = \frac{40}{10} \angle -36.87^\circ$$

$$\bar{I}_2 = \frac{\bar{V}}{Z_2} = \frac{40 \angle -36.87^\circ}{6+j8}$$

$$= \frac{40 \angle -36.87^\circ}{10 \angle 53.13^\circ} = 4 \angle -90^\circ$$

$$\bar{I}_3 = \bar{V} Y_3 = (40 \angle -36.87^\circ) (0.2 \angle 90^\circ)$$

$$= 8 \angle 53.13^\circ$$