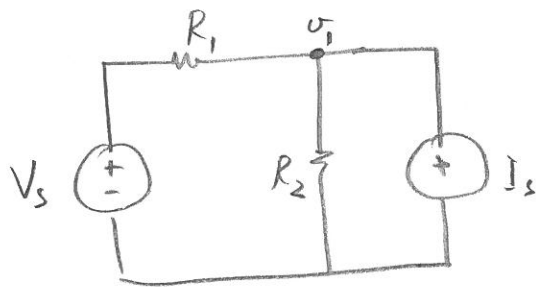


## EXAMPLE

WE WILL ANALYZE THE SAME CIRCUIT  
USING THE FOLLOWING METHODS:


- 1) NODAL ANALYSIS
- 2) MESH ANALYSIS
- 3) SOURCE TRANSFORMATION — THEVENIZING
- 4) SOURCE TRANSFORMATION — NORTONIZING
- 5) SUPERPOSITION

CONSIDER THE FOLLOWING CIRCUIT



WE WILL SOLVE FOR VOLTAGE  $v_1$  USING ALL  
THE ABOVE METHODS

## NODAL ANALYSIS

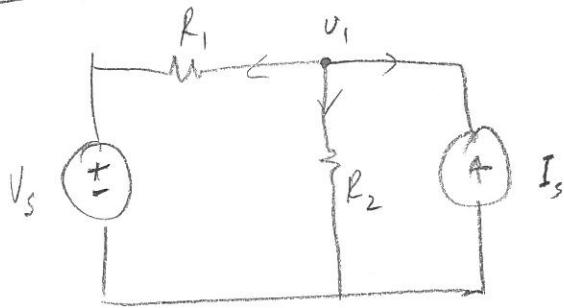


AT THE NODE: 
$$\frac{v_1 - V_s}{R_1} + \frac{v_1}{R_2} - I_s = 0.$$

$$\Rightarrow v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = I_s + \frac{V_s}{R_1}$$

$$\Rightarrow v_1 = \left( \frac{R_1 R_2}{R_1 + R_2} \right) \left( I_s + \frac{V_s}{R_1} \right)$$

# LOOP ANALYSIS

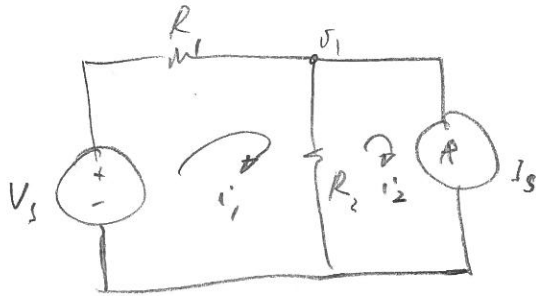

$$i_2 = -I_s$$

$$\text{Loop: } -V_s + R_1 i_1 + R_2 (i_1 - i_2) = 0.$$

$$\Rightarrow i_1 (R_1 + R_2) = V_s + R_2 i_2$$

$$\Rightarrow i_1 = \frac{1}{R_1 + R_2} (V_s + R_2 i_2)$$

$$i_1 = \frac{1}{R_1 + R_2} (V_s - R_2 I_s)$$

$$v_1 = V_s - R_1 i_1$$

$$\Rightarrow v_1 = V_s - \frac{R_1}{R_1 + R_2} (V_s - R_2 I_s)$$

$$= V_s \left( 1 - \frac{R_1}{R_1 + R_2} \right) + \frac{R_1 R_2}{R_1 + R_2} I_s.$$

$$= \frac{R_2}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} I_s$$

$$= \frac{R_1 R_2}{R_1 + R_2} \left( I_s + \frac{V_s}{R_1} \right)$$


$$\text{or } v_1 = R_2 (i_1 - i_2)$$
$$= R_2 i_1 + R_2 I_s.$$

$$= \frac{R_2}{R_1 + R_2} (V_s - R_2 I_s) + R_2 I_s.$$

$$= \frac{R_1 R_2}{R_1 + R_2} \left( \frac{V_s}{R_1} - \frac{R_2 I_s}{R_1} + \frac{(R_1 + R_2)}{R_1} I_s \right)$$

$$= \frac{R_1 R_2}{R_1 + R_2} \left( \frac{V_s}{R_1} + I_s \right)$$

## THEVENINZE

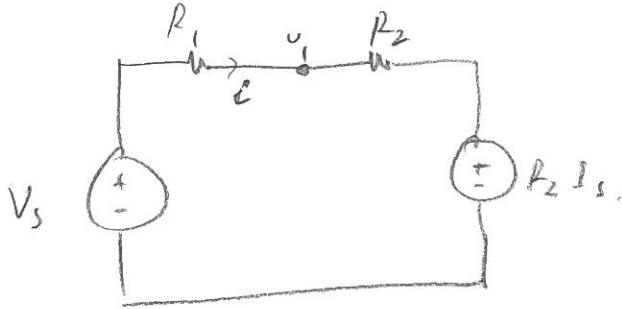

$$-V_S + (R_1 + R_2) i + R_2 I_S = 0.$$

$$\Rightarrow i = \frac{(V_S - R_2 I_S)}{R_1 + R_2}.$$

$$\Rightarrow u_1 = V_S - R_1 i$$


$$= V_S - \frac{R_1}{R_1 + R_2} (V_S - R_2 I_S)$$

$$= V_S \left( 1 - \frac{R_1}{R_1 + R_2} \right) + \frac{R_1 R_2}{R_1 + R_2} I_S.$$

$$= \frac{R_2}{R_1 + R_2} V_S + \frac{R_1 R_2}{R_1 + R_2} I_S.$$

$$u_1 = \frac{R_1 R_2}{R_1 + R_2} \left( I_S + \frac{V_S}{R_1} \right)$$


NOTION 32 E

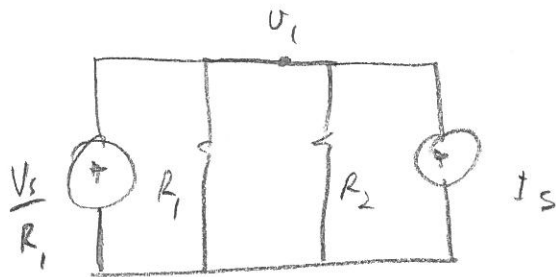


$$U_L = \left( \frac{V_s}{R_1} + I_s \right) (R_1 \parallel R_2)$$

$$= \left( \frac{V_s}{R_1} + I_s \right) \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

SUPERPOSITION

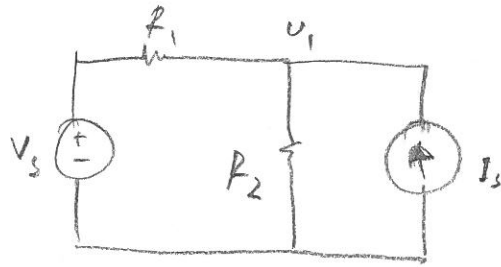


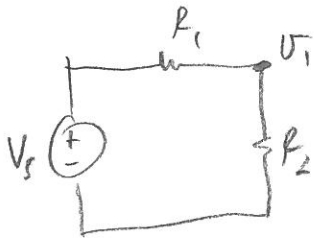$v_1, v_s$  ( $v_1$  due to  $v_s$  alone)



$$v_1 = \frac{R_2}{R_1 + R_2} V_s$$

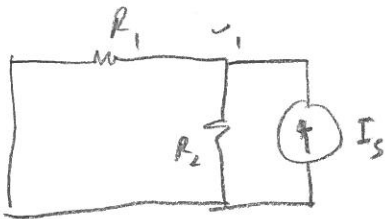$v_1, I_s$  ( $v_1$  due to  $I_s$  alone)





$$v_1 = (R_1 \parallel R_2) I_s$$

$$\begin{aligned} \Rightarrow v_1 &= v_{1, v_s} + v_{1, I_s} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} I_s \\ &= \frac{R_1 R_2}{R_1 + R_2} \left( \frac{V_s}{R_1} + I_s \right) \end{aligned}$$



---

# POWER

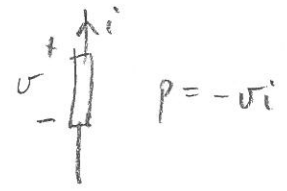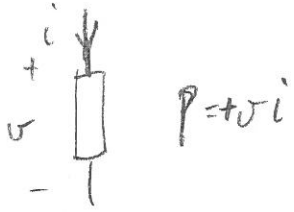


## RESISTOR

## V<sub>SOURCE</sub>

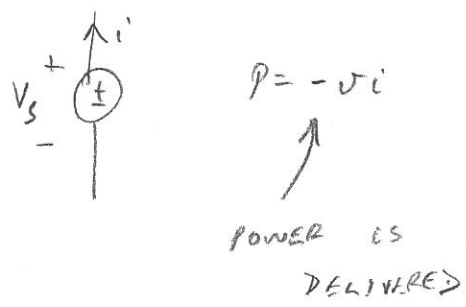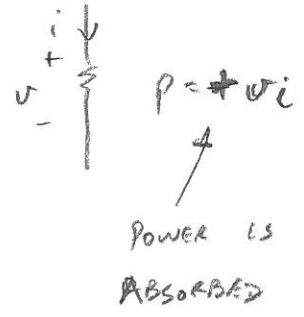

EXAMPLE

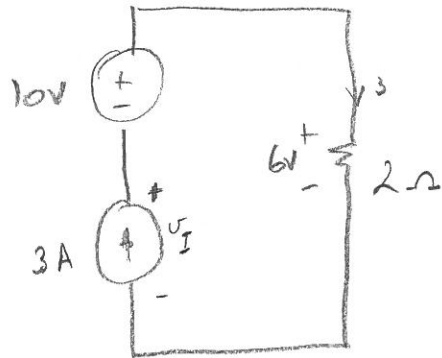

$$-V_I - 10 + 6 = 0$$

$$V_I = -4$$

$$\therefore p = -vi$$

$$= -(-4)3$$

$$= +12 \text{ W}$$

$\nearrow$   
+ve  $\Rightarrow$  power is absorbed