
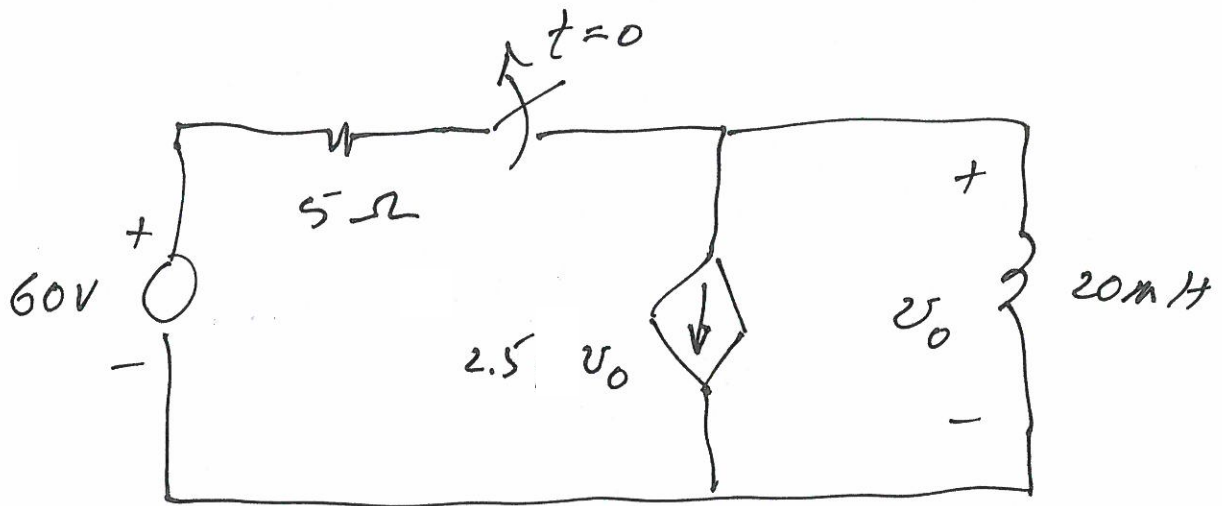



1)

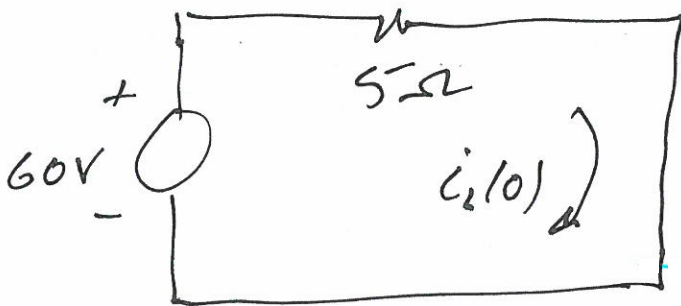

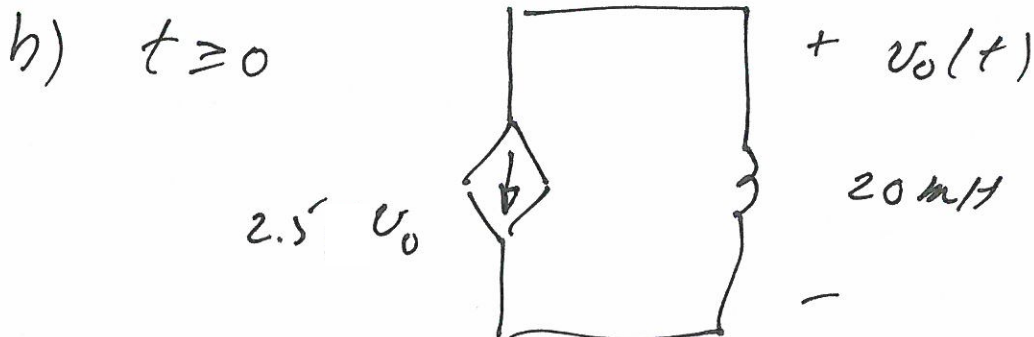- a) $t < 0$ INDUCTOR IS A WIRE $\Rightarrow v_0(0^-) = 0$
 \Rightarrow DEP SOURCE IS ZERO CURRENT




$$i_L(0) = \frac{60\text{V}}{5\Omega} = 12\text{A} //$$



NO INDPA SOURCE $\Rightarrow i_L(\infty) = 0 //$

THEVENIN EQ SEEN BY INDUCTOR


c)

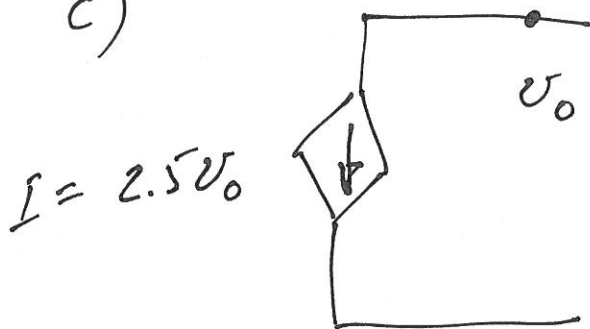

$$I = 2.5v_0$$

$$v_0 = \frac{1}{2.5} I$$

$$\Rightarrow R_{TH} = \frac{1}{2.5}$$

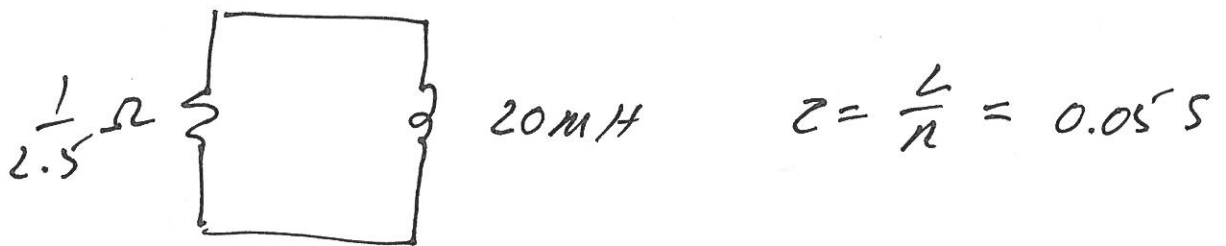

$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] e^{-t/\tau}$$

d)

$$i_L(t) = 12 e^{-20t} \text{ A}; t \geq 0 //$$



$$v_0(t) = L \frac{di_L(t)}{dt}$$

e)

$$= 20\text{mH} (-20)(12) e^{-20t}$$

$$v_0(t) = -4.8 e^{-20t}; t \geq 0^+$$

F)

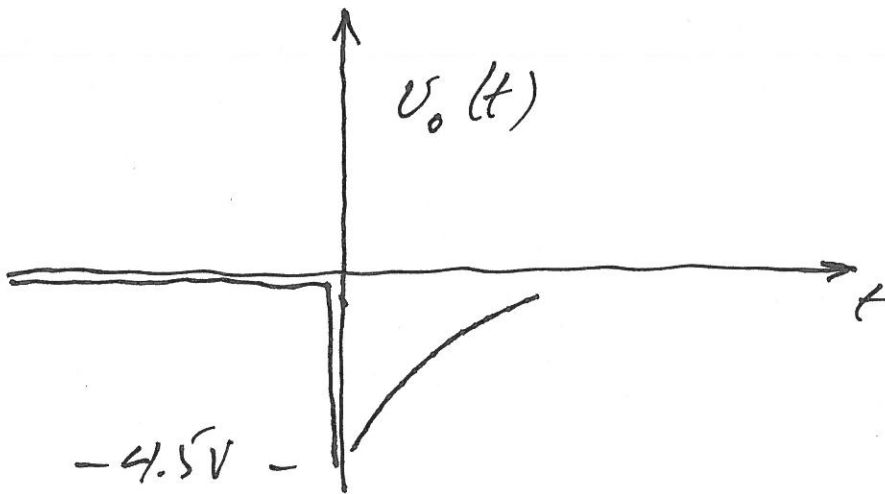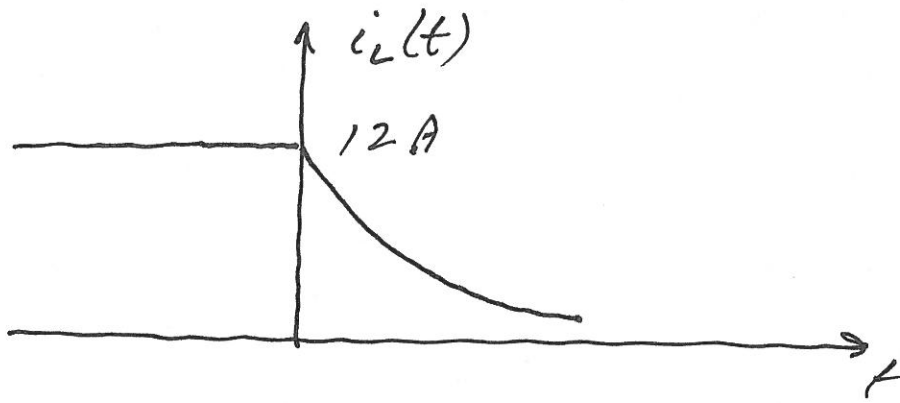

2)

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

1ST INITIAL COND: $v(0) = V_0$ (VOLTAGE ON CAP.)

$$\boxed{A_1 + A_2 = V_0}$$

2ND INITIAL COND: KCL

$$i_c + i_L + i_R = 0$$

$$(1) \quad c \left. \frac{dv}{dt} \right|_{t=0} + i_L(0) + \frac{v(0)}{R} = 0$$

$= I_0$ (CURRENT IN INDUCTOR)

$$\text{BUT } v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\frac{dv(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$(2) \quad \left. \frac{dv(t)}{dt} \right|_{t=0} = A_1 s_1 + A_2 s_2$$

$$(1), (2): \quad c(A_1 s_1 + A_2 s_2) + I_0 + \frac{v(0)}{R} = 0$$

$$\boxed{A_1 s_1 + A_2 s_2 = \frac{-(I_0 + V_0/R)}{c}}$$

3)

$$3x + j2y - jx + 5y = 18 + j5$$

$$11) 3x + 5y = 18$$

$$(2) 2y - x = 5 \rightarrow x = 2y - 5$$


$$11) \text{ ; } (2) : 3(2y - 5) + 5y = 18 \rightarrow 6y - 15 + 5y = 18$$

$$11y = 33 \rightarrow y = 3 //$$

$$\text{Faktor } (2) : x = 2 \cdot 3 - 5 \rightarrow x = 1 //$$

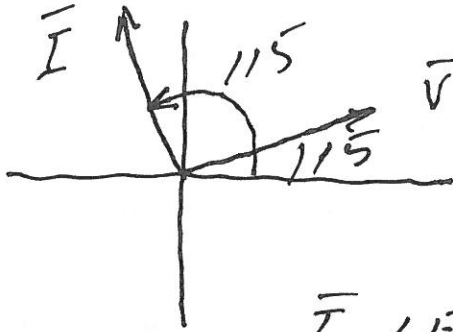4)

$$\bar{V} = 20 \angle 15^\circ \quad \bar{I} = 2 \angle 105^\circ$$



\bar{I} LEADS \bar{V} BY 90°

0° CAPACITOR

$$5) \quad z = 4 \angle -30^\circ$$

$$z = 4 \cos(-30^\circ)$$


$$+ 4 \sin(-30^\circ)$$

$$z = 3.46 - j2$$

b) CAPACITIVE

c) REACTANCE = -2Ω



d) CURRENT WILL LEAD VOLTAGE BY 30°

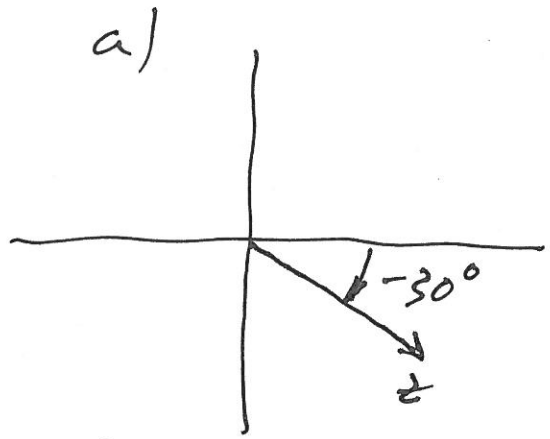

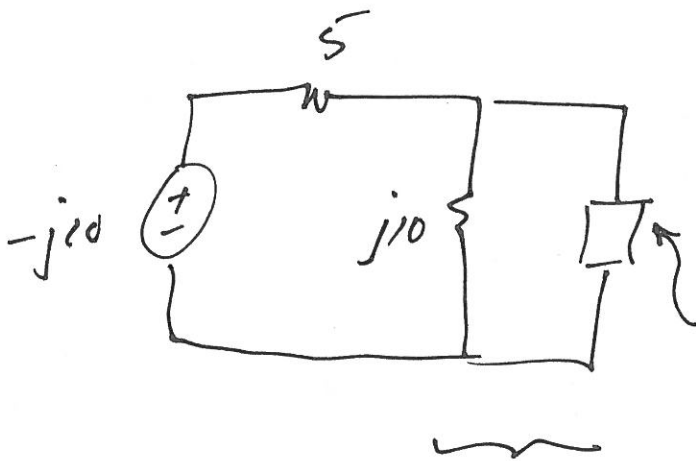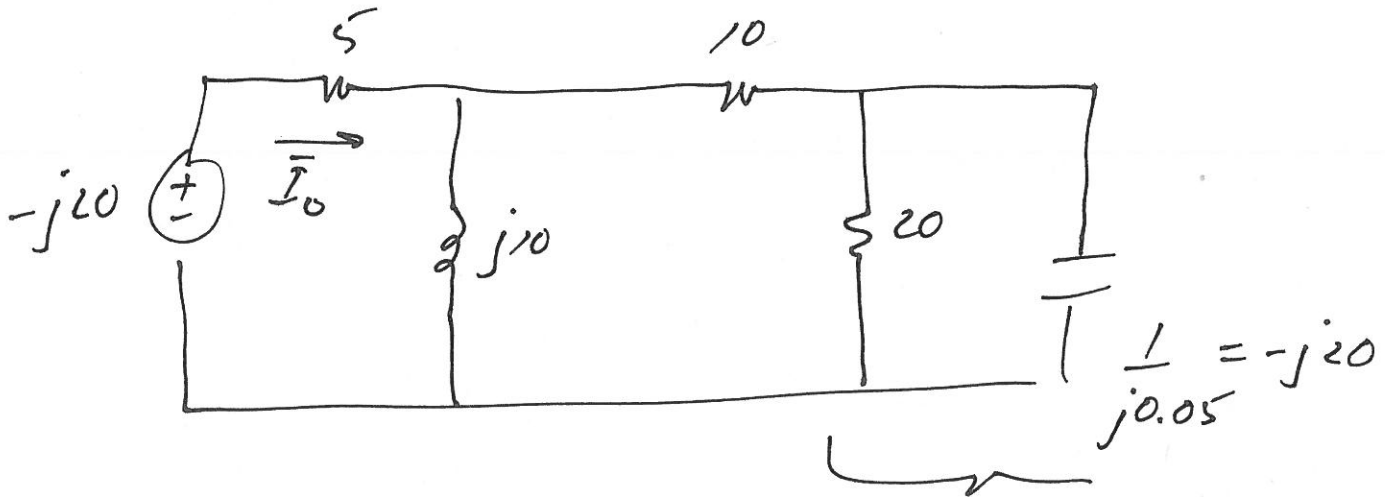6)

$$v_g(t) = 20 \sin(4,000t) = 20 \cos(4,000t - 90^\circ)$$

$$\bar{V}_g = 20 \angle -90^\circ = -j20$$




$$\frac{20(-j20)}{20 - j20} = \frac{-j20}{1-j}$$

$$= \frac{-j20}{1-j} \left(\frac{1+j}{1+j} \right) = 10 - j10$$

$$10 - j10 + 10 = 20 - j10$$
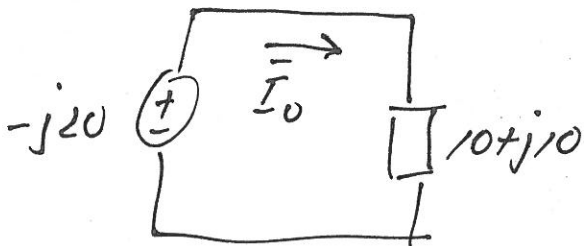
$$\frac{j10(20 - j10)}{j10 + 20 - j10} = 5 + j10$$




$$\bar{I}_0 = \frac{-j20}{10 + j10} \left(\frac{10 - j10}{10 - j10} \right)$$

$$= -1 - j = \sqrt{2} \angle -135^\circ$$

$$i_0(t) = \sqrt{2} \cos(4,000t - 135^\circ)$$

7)

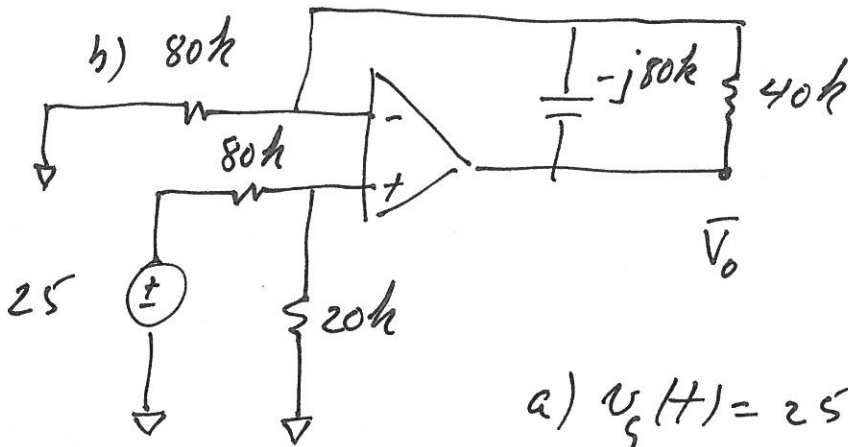

a) $v_s(t) = 25 \cos(50,000t) \text{ V}$

$\bar{V}_s = 25 \angle 0^\circ = 25$

c)
$$\frac{\bar{V}_n}{80k} + \frac{\bar{V}_n - \bar{V}_o}{-j80k} + \frac{\bar{V}_n - \bar{V}_o}{40k} = 0 \quad (1)$$

$$\frac{V_p - 25}{80k} + \frac{\bar{V}_p}{20k} = 0 \quad (2)$$

$$\bar{V}_n + j(\bar{V}_n - \bar{V}_o) + 2(\bar{V}_n - \bar{V}_o) = 0 \quad (1')$$

$$\bar{V}_p - 25 + 4\bar{V}_p = 0 \Rightarrow \bar{V}_p = 5 \text{ V} \quad (2')$$

d) $\bar{V}_n = \bar{V}_p = 5 \text{ V}$

(1'') $5 + j(5 - \bar{V}_o) + 2(5 - \bar{V}_o) = 0$

$5 + j5 + 10 - j\bar{V}_o - 2\bar{V}_o = 0$

$15 + j5 = \bar{V}_o(2 + j)$

$$\bar{V}_o = \frac{15 + j5}{2 + j}$$

②

$$\bar{V}_0 = \frac{15+j5}{2+j} \left(\frac{2-j}{2-j} \right) = \frac{5(3+j)(2-j)}{5}$$


$$= 6 - 3j + 2j + 1 = 7 - j$$

$$\bar{V}_0 = \sqrt{50} \angle -8.13^\circ$$

e) $v_0(t) = \sqrt{50} \cos(50,000t - 8.13^\circ) \text{ V}$

f) THE TWO RESISTORS AT THE NO-INVERTING TERMINAL CONSTITUTE A VOLTAGE DIVIDER

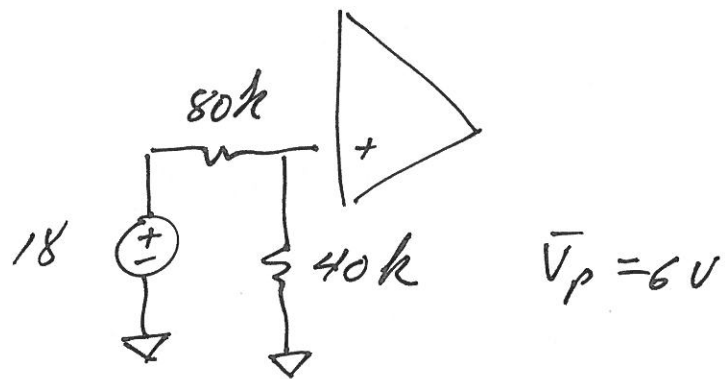g) THIS CIRCUIT AMPLIFIES THE INPUT AND SHIFTS THE PHASE



$$v_0(t) = \frac{6}{5} \sqrt{50} \cos(50,000t - 8.13^\circ) \text{ V}$$