

ECE222

Quiz 1

For the circuit below find an expression for the inductor current $i_1, t \geq 0$. (Show all your work).

