

# ECE222

## Quiz 2

The switch in the circuit shown below has been closed for a long time before opening at  $t = 0$ . Find  $v_o(t)$ ,  $t \geq 0^+$ . (Show all your work).

