

# ECE222

## Quiz 3

The switch in the circuit shown below has been in the left position for a long time before moving to the right position at  $t = 0$ . Find  $i_L(t)$ ,  $t \geq 0$ . (Show all your work).

