

ECE 222

Voltage (inductor):	$v = L \frac{di}{dt}$
Current over time:	$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$
Current (capacitor):	$i = C \frac{dv}{dt}$
Voltage over time:	$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$
Energy:	$W(t) = \frac{1}{2} C v^2(t) = \frac{1}{2} L i^2(t)$
Capacitance (Series):	$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$
Capacitance (Parallel):	$C_{eq} = C_1 + C_2$
Capacitance:	$C = \frac{\epsilon A}{d}$
Dielectric Constant:	$\epsilon = 8.85 \times 10^{-12} F/m$
Stored Charge:	$q = Cv$
Inductance (Series):	$L_{eq} = L_1 + L_2$
Inductance (Parallel):	$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$
General Transient Solution:	$x(t) = x_f + [x_0 - x_f] e^{-t/\tau}$
• For RC network:	
	$x(t) = v_C(t)$, the capacitor voltage
	$\Rightarrow x_0 = v_C(0)$ (initial voltage value) and
	$x_f = v_C(\infty)$ (final voltage value)
	Time constant: $\tau = RC$
	The initial condition response only is given by: $v_C(t) = v_C(0) e^{-t/\tau}$
• For RL network:	
	$x(t) = i_L(t)$, the inductor current
	$\Rightarrow x_0 = i_L(0)$ (initial current value) and
	$x_f = i_L(\infty)$ (final current value)
	Time constant: $\tau = \frac{L}{R}$
	The initial condition response only is given by: $i_L(t) = i_L(0) e^{-t/\tau}$