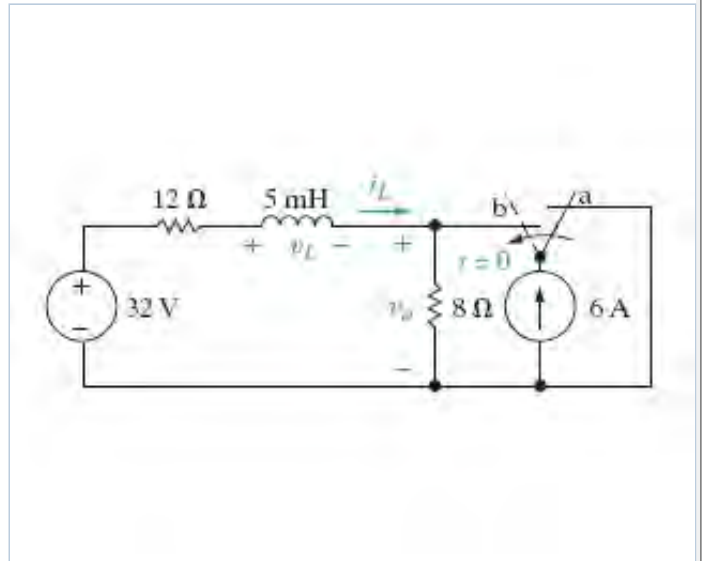


Problem 7.36 PSpice|Multisim

The switch in the circuit shown in has been in position a for a long time before moving to position b at $t = 0$.



Part A

Choose the correct numerical expression for $i_L(t)$ for $t \geq 0$.

ANSWER:

- $i_L(t) = -0.8 + 2.4e^{-25t}$ A, where t is in milliseconds
- $i_L(t) = 2.4 - 0.8e^{-25t}$ A, where t is in milliseconds
- $i_L(t) = 2.8 + 0.4e^{-4t}$ A, where t is in milliseconds
- $i_L(t) = -0.8 + 2.4e^{-4t}$ A, where t is in milliseconds

Part B

Choose the correct numerical expression for $v_o(t)$ for $t \geq 0$.

ANSWER:

- $v_o(t) = 19.2 + 41.6e^{25t}$ V, where t is in milliseconds
- $v_o(t) = 41.6 - 19.2e^{-25t}$ V, where t is in milliseconds
- $v_o(t) = 19.2 - 41.6e^{-4t}$ V, where t is in milliseconds
- $v_o(t) = 41.6 + 19.2e^{-4t}$ V, where t is in milliseconds

Part C

Find the numerical value of $v_L(0^+)$.

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$v_L(0^+) = \text{[input box]}$$

Part D

Find the numerical value of $v_o(0^+)$.


Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$v_o(0^+) = \text{[input box]}$$

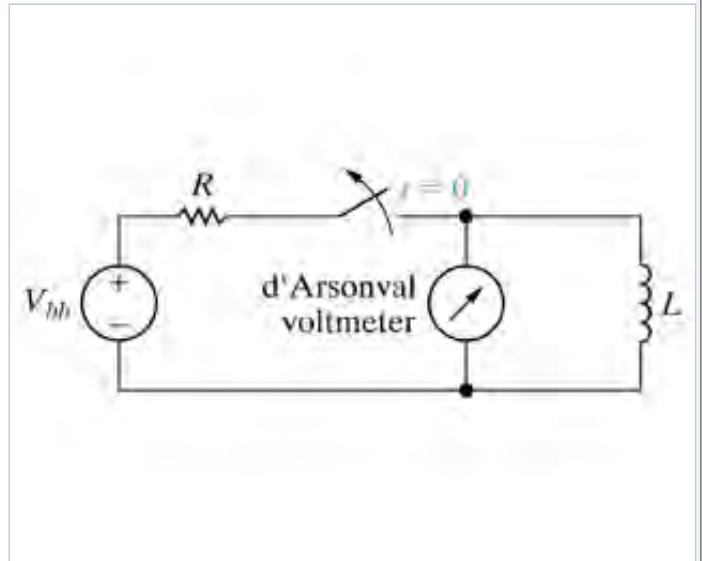Problem 7.42


The switch in the circuit in has been closed for a long time. A student abruptly opens the switch and reports to her instructor that when the switch opened, an electric arc with noticeable persistence was established across the switch, and at the same time the voltmeter placed across the coil was damaged.



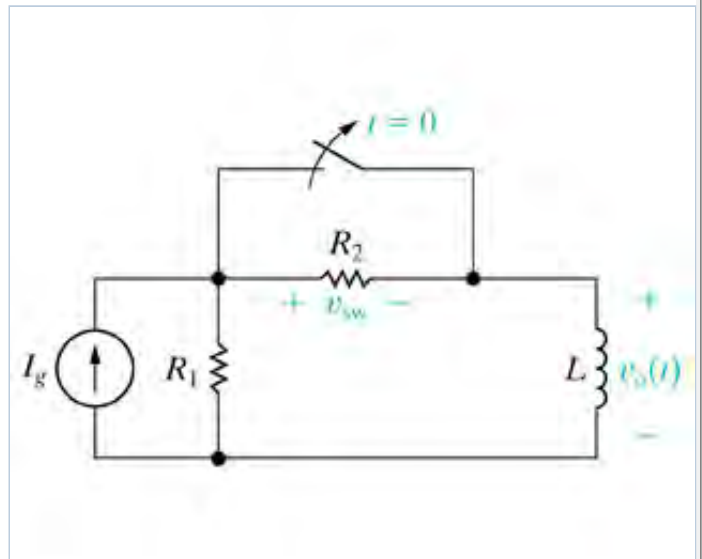Part A

On the basis of your analysis of the circuit in , can you explain to the student why this happened?

Drag the terms on the left to the appropriate blanks on the right to complete the sentences.



ANSWER:

Reset

Help

small

large


also appears

doesn't appear

Opening the inductive circuit causes a very voltage to be induced across the inductor L . This voltage across the switch, causing the switch to arc over. At the same time, the voltage across L damages the meter movement.

Problem 7.44 PSpice|Multisim

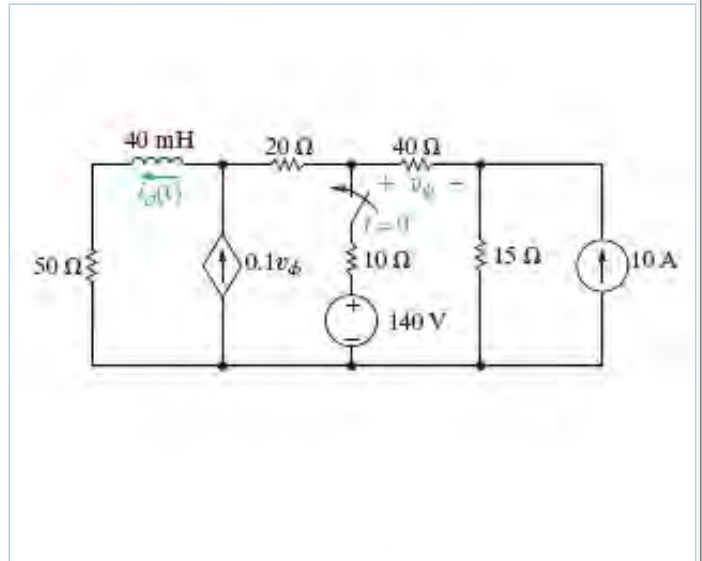The switch in the circuit in has been open a long time before closing at $t = 0$.



Part A

Find $i_o(t)$ for $t \geq 0$.


Express your answer in terms of t , where t is in milliseconds.

ANSWER:

$i_o(t) =$ A

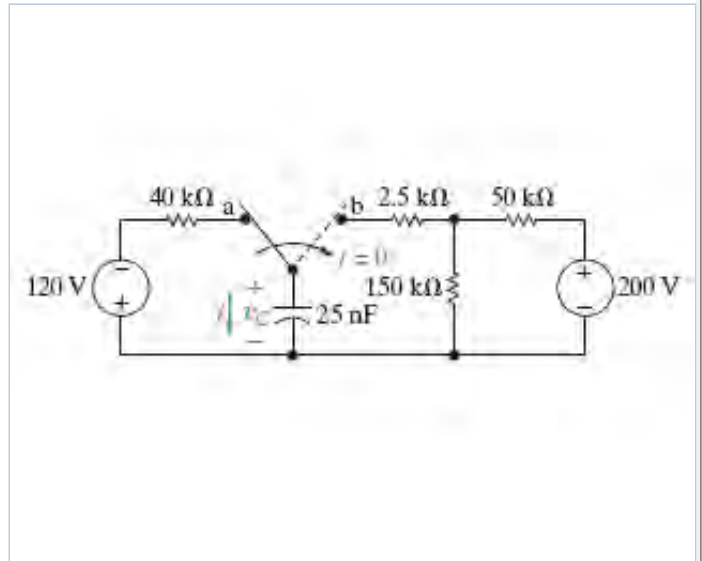Problem 7.51

Assume that the switch in the circuit in has been in position a for a long time and that at $t = 0$ it is moved to position b.



Part A

Find $v_C(0^+)$.

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$v_C(0^+) = \text{[input box]}$$

Part B

Find $v_C(\infty)$.

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$v_C(\infty) = \text{[input box]}$$

Part C

Find τ for $t > 0$.

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$\tau = \text{[input box]}$$

Part D

Find $i(0^+)$.

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$i(0^+) = \text{[input box]}$$

Part E

Choose the correct expression for $v_C(t), t \geq 0$.

ANSWER:

- $v_C(t) = 150 + 270e^{1000t}$ V, where t is in seconds
- $v_C(t) = 15 + 27e^{-t}$ V, where t is in second
- $v_C(t) = 150 - 270e^{-1000t}$ V, where t is in seconds
- $v_C(t) = 15 - 27e^{-t}$ V, where t is in seconds

Part F

Find $i(t), t \geq 0^+$.


Express your answer in terms of t , where t is in milliseconds.

ANSWER:

$$i(t) = \text{[input box]} \text{ mA}$$

Problem 7.61 PSpice|Multisim

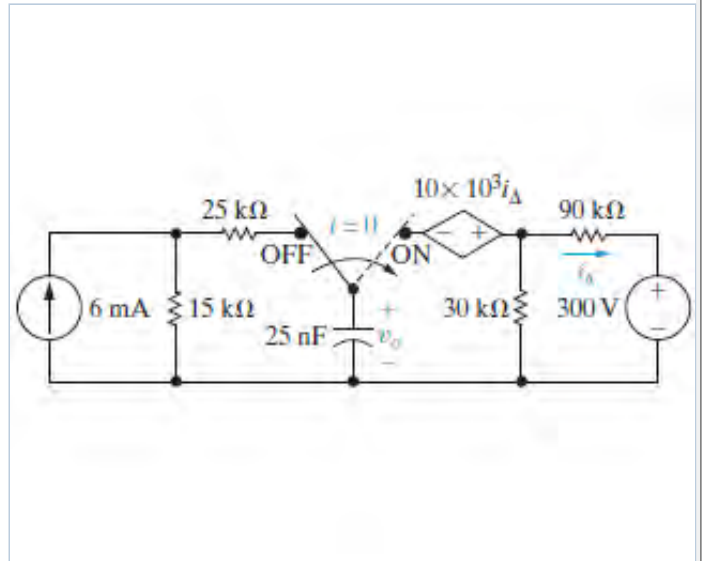The switch in the circuit shown in has been in the OFF position for a long time. At $t = 0$, the switch moves instantaneously to the ON position.



Part A

Find $v_o(t)$ for $t \geq 0$.


Express your answer in terms of t , where t is in milliseconds.

ANSWER:

$v_o(t) =$ V

Problem 7.69 PSpice|Multisim

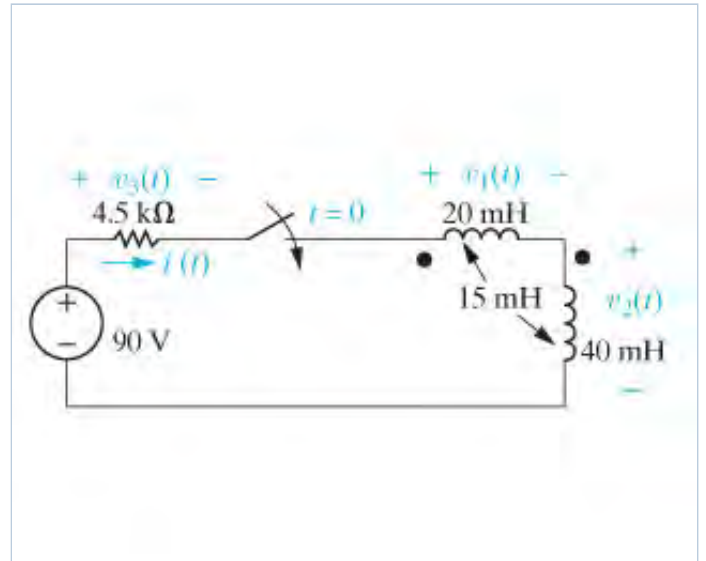There is no energy stored in the circuit in at the time the switch is closed.



Part A

Find $i(t)$ for $t \geq 0$.

Express your answer in terms of t , where t is in microseconds.

ANSWER:

$$i(t) = \text{[input box]} \text{ mA}$$

Part B

Find $v_1(t)$ for $t \geq 0^+$.

Express your answer in terms of t , where t is in microseconds.

ANSWER:

$$v_1(t) = \text{[input box]} \text{ V}$$

Part C

Find $v_2(t)$ for $t \geq 0^+$.

Express your answer in terms of t , where t is in microseconds.

ANSWER:

$$v_2(t) = \text{[input box]} \text{ V}$$

Part D

Find $v_3(t)$ for $t \geq 0^+$.

Express your answer in terms of t , where t is in microseconds.

ANSWER:


$v_3(t) =$ V

Part E

This question will be shown after you complete previous question(s).


Instructors: [View all hidden parts](#)

7.36

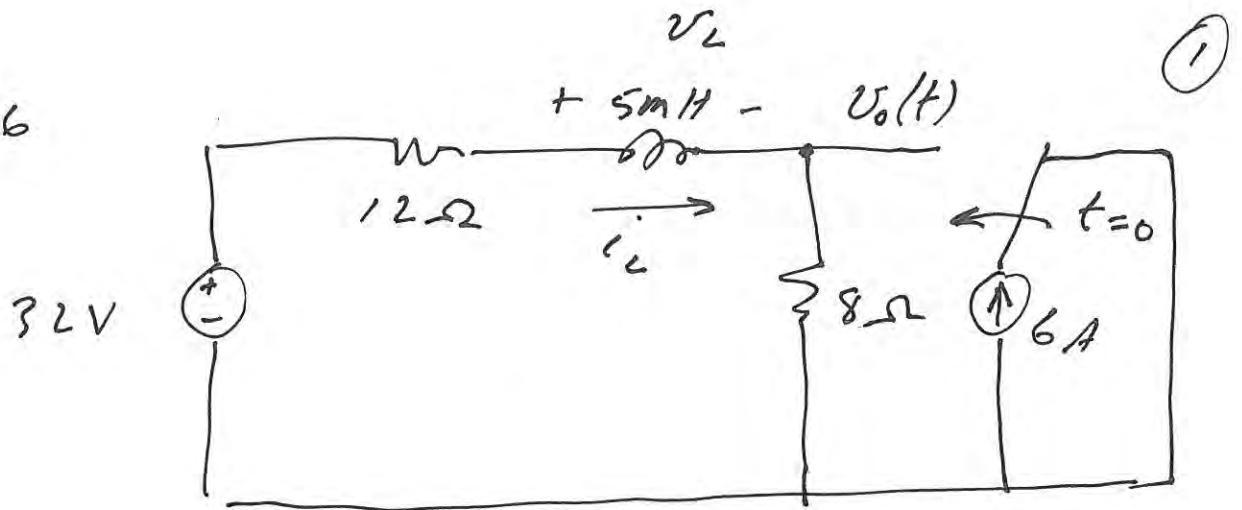

a) FIND $i_L(t)$ & $v_o(t)$



b) FIND $v_L(0^+)$ & $v_o(0^+)$

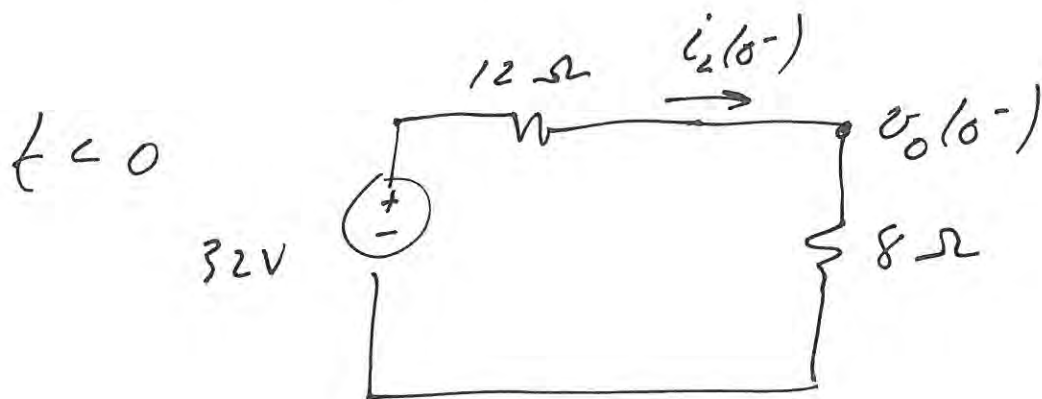

$$i_L(0^-) = \frac{32\text{ V}}{20\ \Omega} = 1.6\text{ A} = i_L(0^+)$$


$$v_o(0^-) = 1.6\text{ A} \times 8\ \Omega = 12.8\text{ V}$$

7.36, CONT'D.

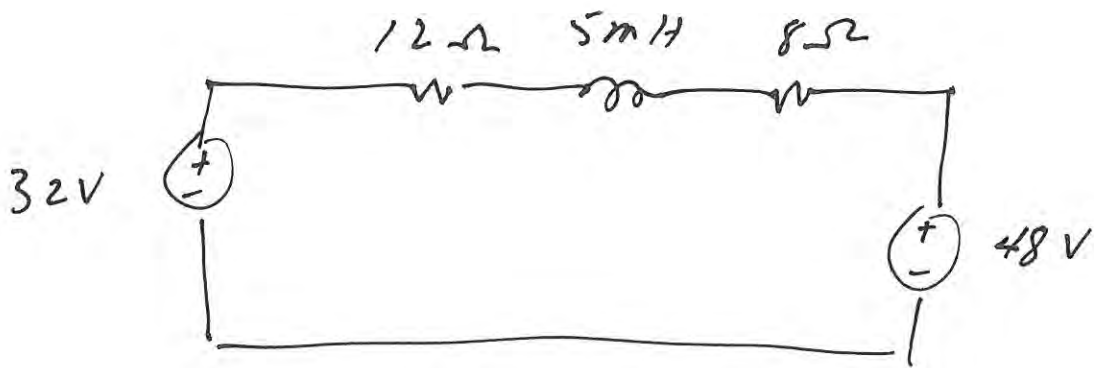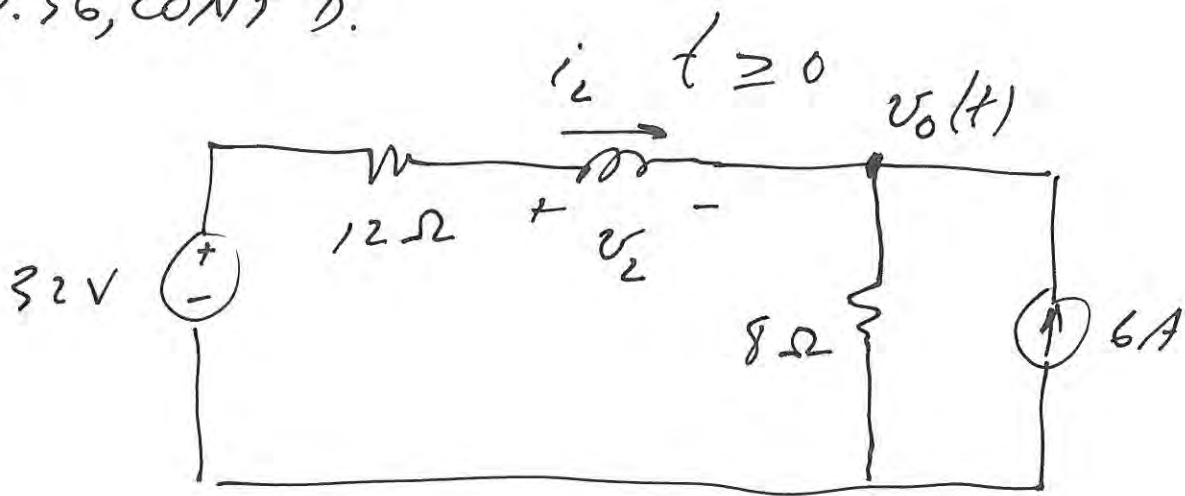

$$\tau = L/R = 5\text{mH} / 20\Omega = 0.25\text{ms}$$

$$1/\tau = 4000\text{ s}^{-1}$$

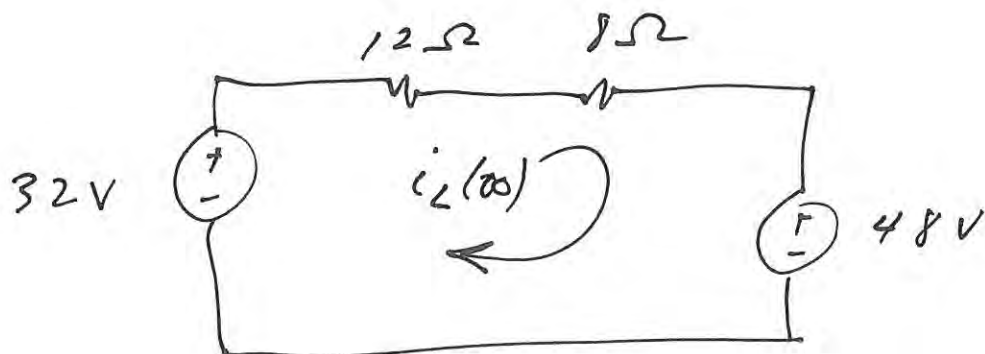

MESH: $32 - 20i_2(\infty) - 48 = 0$

$$\Rightarrow i_2(\infty) = \frac{(32 - 48)\text{V}}{20\Omega} = -0.8\text{A}$$

7.36, CONT'D.

$$i_2(t) = i_2(\infty) + [i_2(0) - i_2(\infty)] e^{-t/\tau}$$

$$= -0.8 + (1.6 + 0.8) e^{-4,000t}$$

$$i_2(t) = -0.8 + 2.4 e^{-4,000t} \text{ A ; } t \geq 0$$

$$v_2(t) = L \frac{d}{dt} i_2(t)$$

$$= 5 \text{ mH} (24) (-4000) e^{-4,000t} \text{ V}$$

$$v_2(t) = -48 e^{-4,000t} \text{ V ; } t \geq 0^+$$

NODAL FOR $v_0(t)$ (SEE TOP PAGE 2)

$$-i_2(t) + \frac{v_0(t)}{8\Omega} - 6\text{A} = 0$$



$$v_0(t) = [i_2(t) + 6\text{A}] 8\Omega$$

$$= (5.2 + 2.4 e^{-4,000t}) 8$$

$$v_0(t) = 41.6 + 19.2 e^{-4,000t} \text{ V ; } t \geq 0^+$$

$$v_0(0^+) = 60.8 \text{ V}$$

7.42

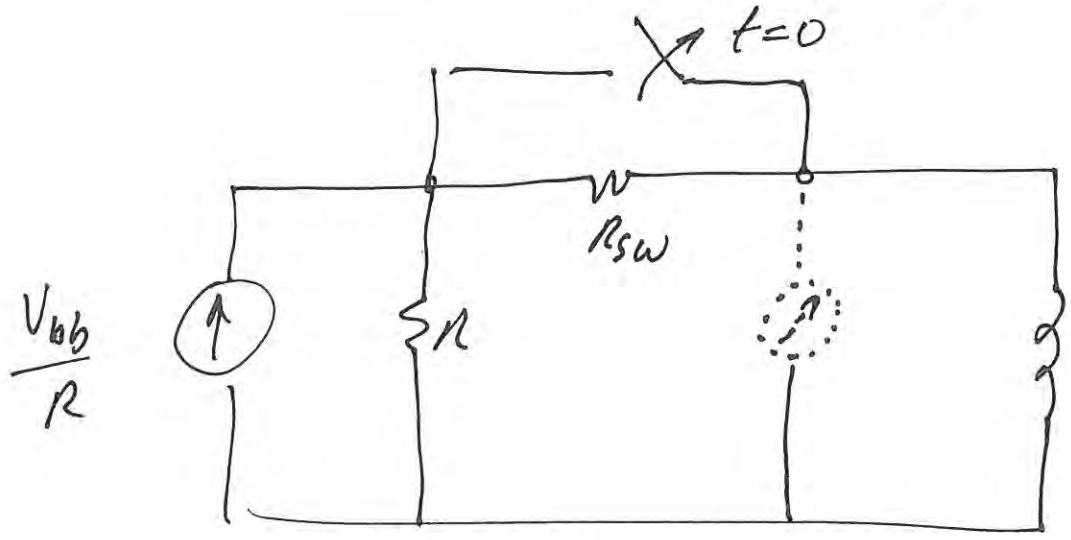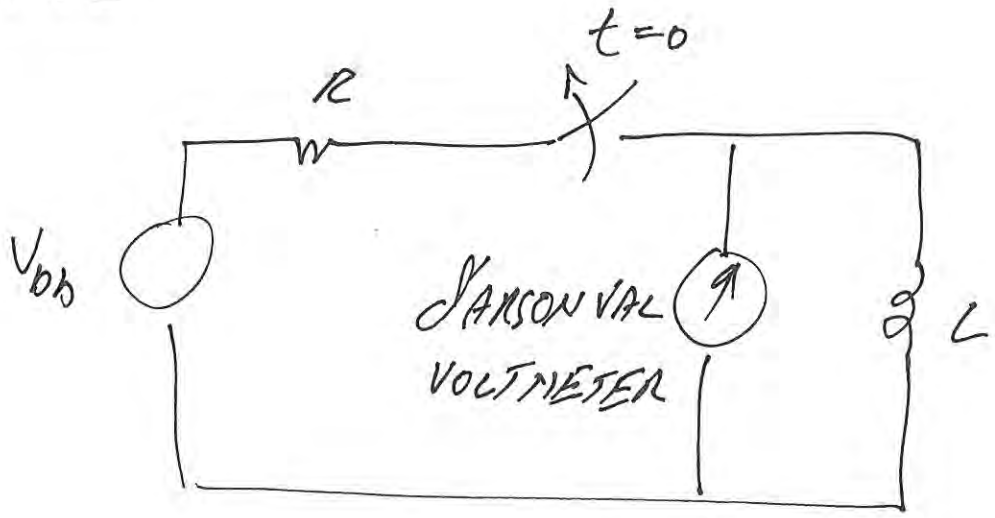

R_{sw} VERY LARGE

PRIOR TO SWITCH, INDUCTOR IS A SHORT

$$i_L(0) = \frac{V_{bb}}{R}$$


THROWING SWITCH CAUSES ABRUPT CHANGE IN CURRENT

$$v_L(t) = L \frac{di_L(t)}{dt} \text{ IS VERY LARGE}$$



7.42, CONT'D.

VERY LARGE, ABRUPT VOLTAGE CAUSES
ARC AT SWITCH & DAMAGES METER.

7.44

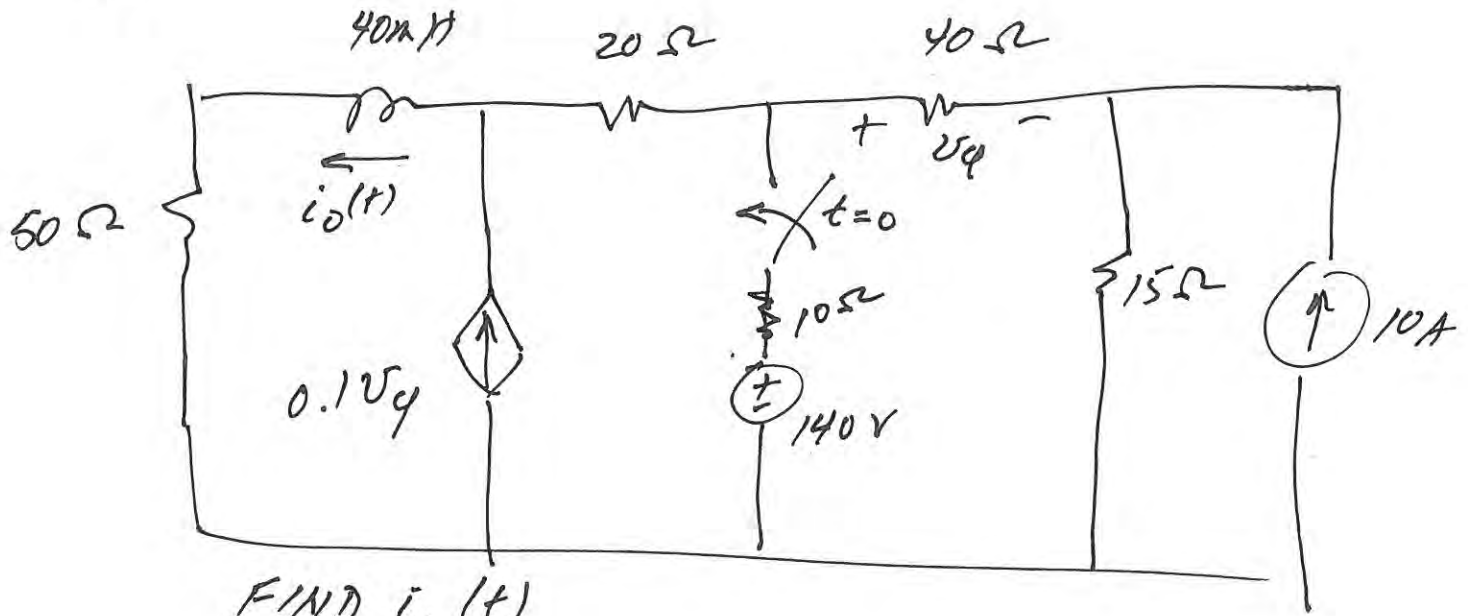

$t < 0$

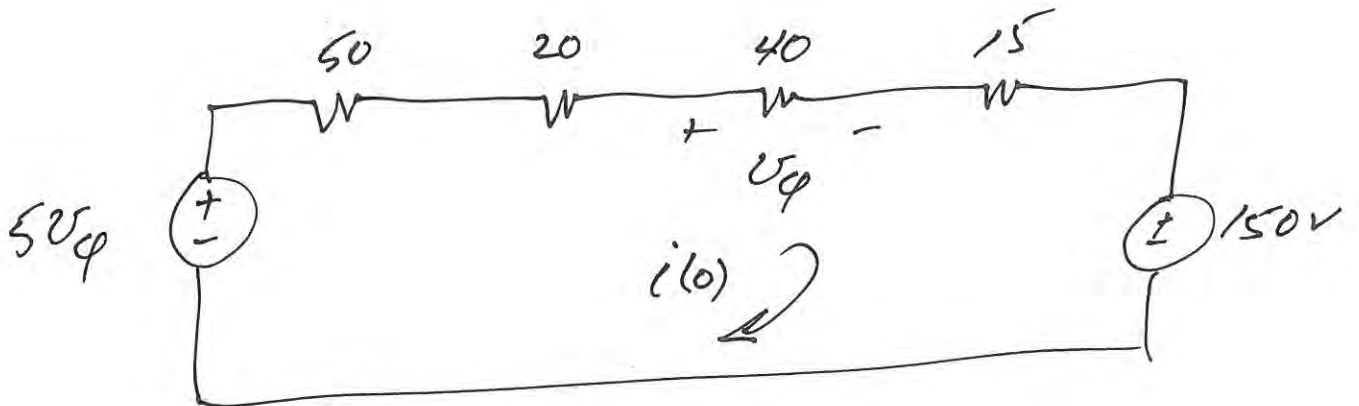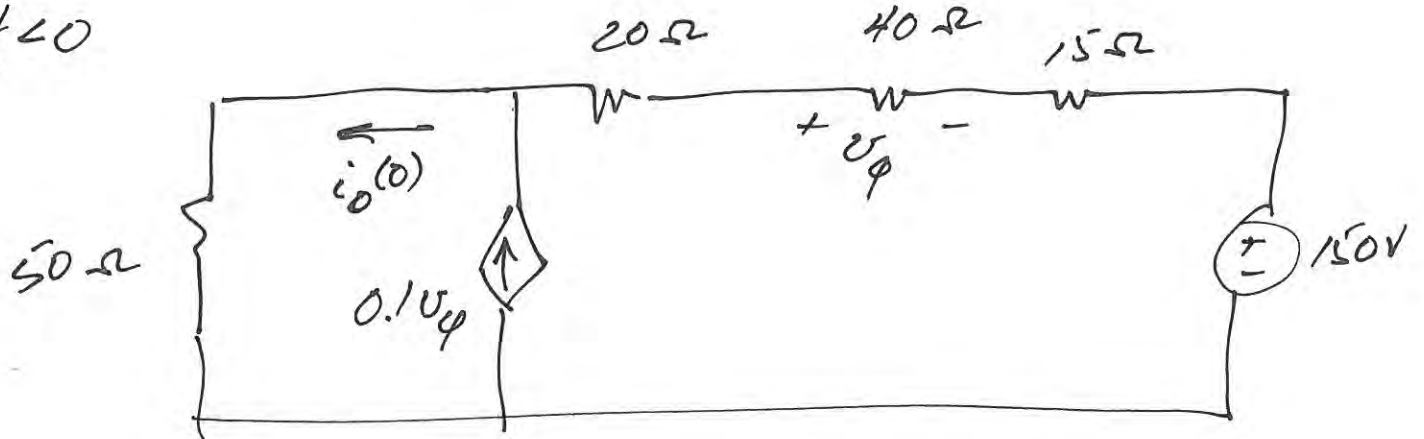

7.44, (CONT'D)

(2)

mesh analysis


$$5v_\phi - (50 + 20 + 40 + 15)i(0) - 150V = 0$$

$$\text{But } v_\phi = 40 i(0)$$

$$200 i(0) - 125 i(0) = 150V$$

$$75 i(0) = 150V$$

$$i(0) = \frac{150V}{75\Omega} = 2A$$

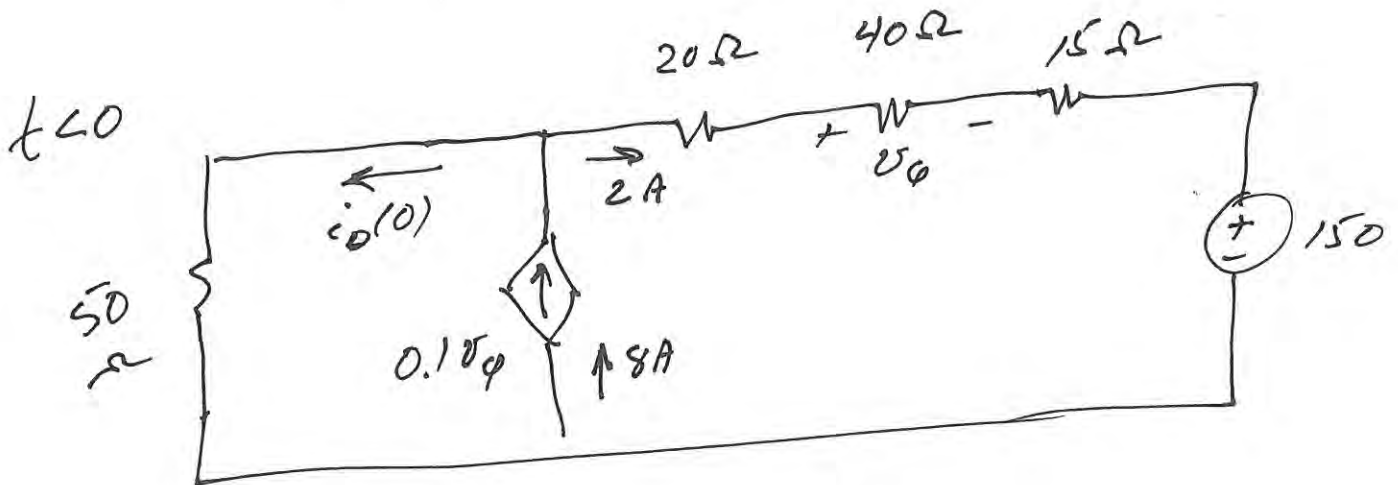


$$v_\phi = 80V$$


$$\Rightarrow i_o(0) = 6A$$

7.44, CONT'D. $t \geq 0$

(3)

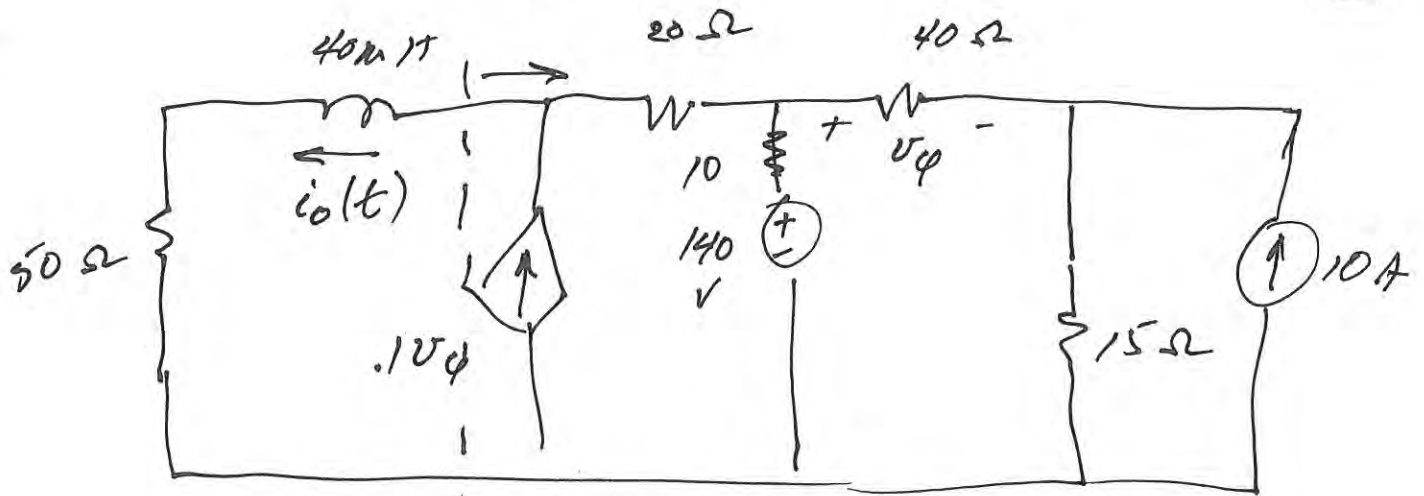

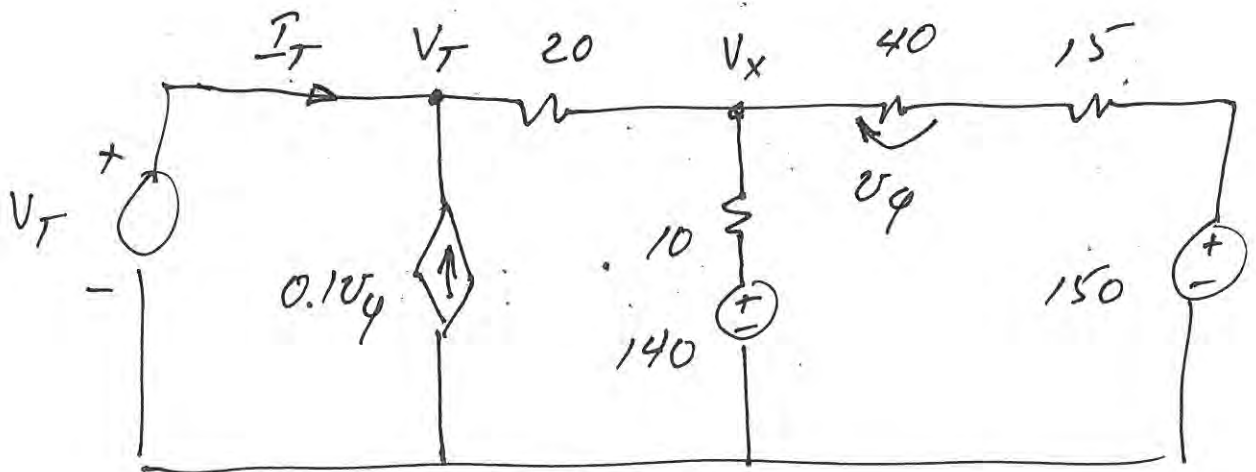DETERMINE THEVENIN EQ TO RIGHT OF INDUCTOR & 50 Ω RESISTOR: APPLY TEST SOURCE



NODAL ANALYSIS

$$\textcircled{1} \quad \frac{V_T - V_x}{20} - I_T - 0.1V_q = 0$$

$$\textcircled{2} \quad \frac{V_x - 150}{55} + \frac{V_x - 140}{10} + \frac{V_x - V_T}{20} = 0$$

7.44, CONT'D.

(4)

VOLTAGE DIV FOR v_g :

$$(3) \quad v_g = (v_x - 150) \left(\frac{40}{55} \right)$$

COMBINE EQ'S (1) & (3):

$$\frac{v_T - v_x}{20} - I_T - 0.1 \left(v_x - 150 \right) \left(\frac{40}{55} \right) = 0$$

∴

$$(4) \quad 135 v_x - 55 v_T + 1,100 I_T = 12,000$$


REWRITE EQ (2) AS:

$$(5) \quad 185 v_x - 55 v_T = 18,400$$

ELIMINATE v_x BETWEEN EQ'S (4) & (5):

$$v_T = 96 + 74 I_T$$

↑ ↑
 v_{TH} R_{TH}

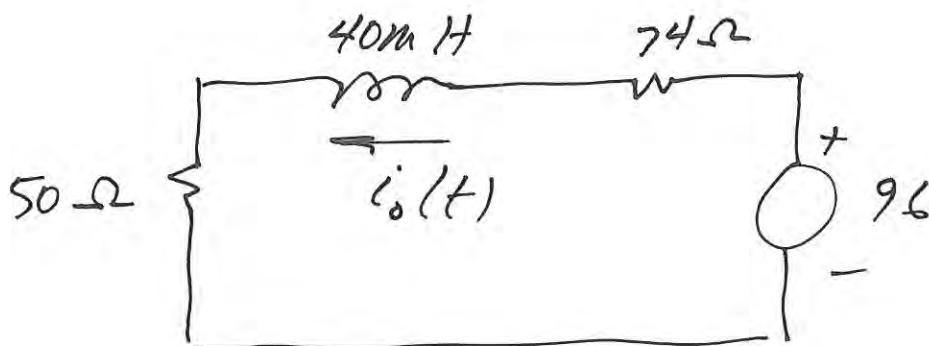

7.44, CONT'D.

(5)

$$i_o(\infty) = \frac{96\text{V}}{124\ \Omega} = 0.774\text{A}$$

$$\tau = L/R = 40\text{mH}/124\ \Omega$$

$$= 0.3226\text{ms}$$


$$1/\tau = 3,100\ \text{s}^{-1}$$

$$\begin{aligned} i_o(t) &= i_o(\infty) + [i_o(0) - i_o(\infty)]e^{-t/\tau} \\ &= 0.774 + (6 - 0.774)e^{-3,100t} \end{aligned}$$


$$\boxed{i_o(t) = 0.774 + 5.226e^{-3,100t}\ \text{A}, t \geq 0}$$

7.51


(1)

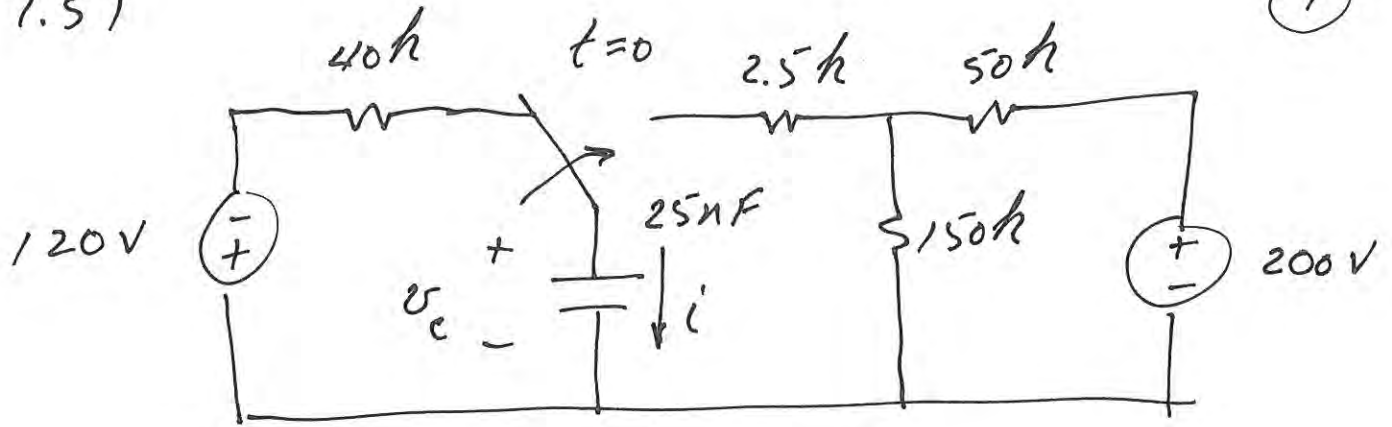

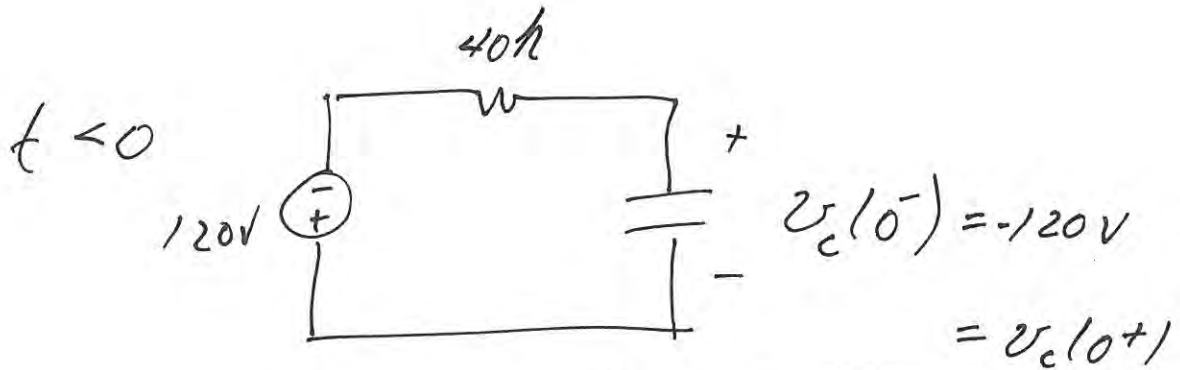- a) $v_c(0^+)$ b) $v_c(\infty)$ c) τ
 d) $i(0^+)$ e) $v_c(t); t \geq 0$ f) $i(t); t \geq 0^+$






a) $v_c(0^+) = 720V$

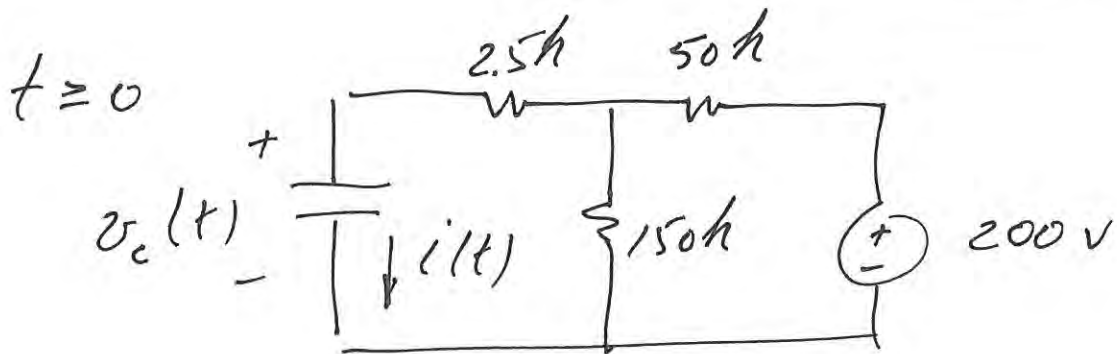

7.51, CONT'D.

(2)

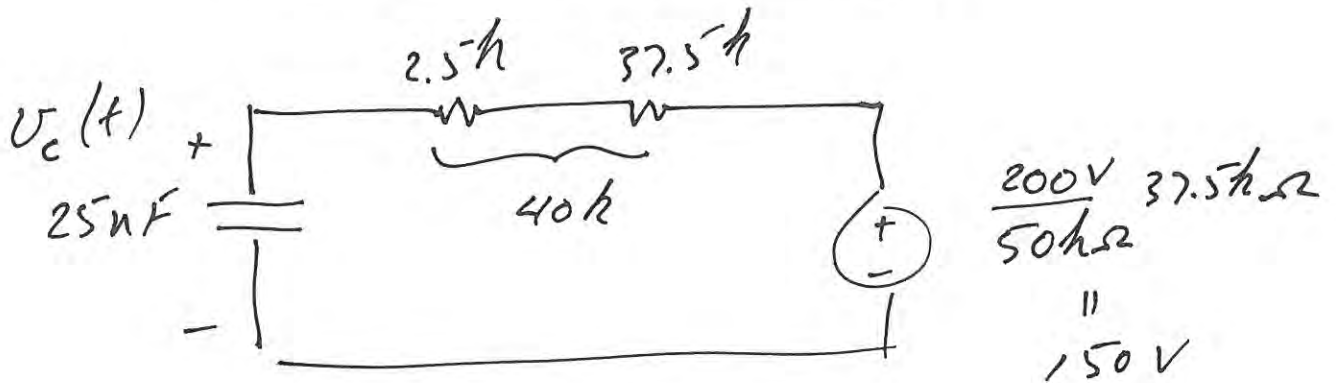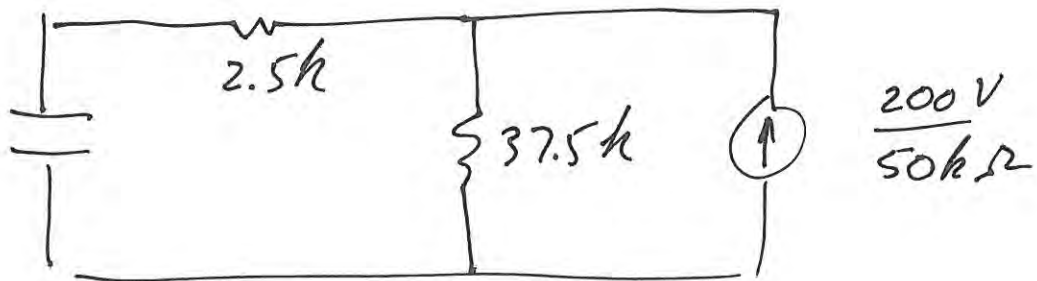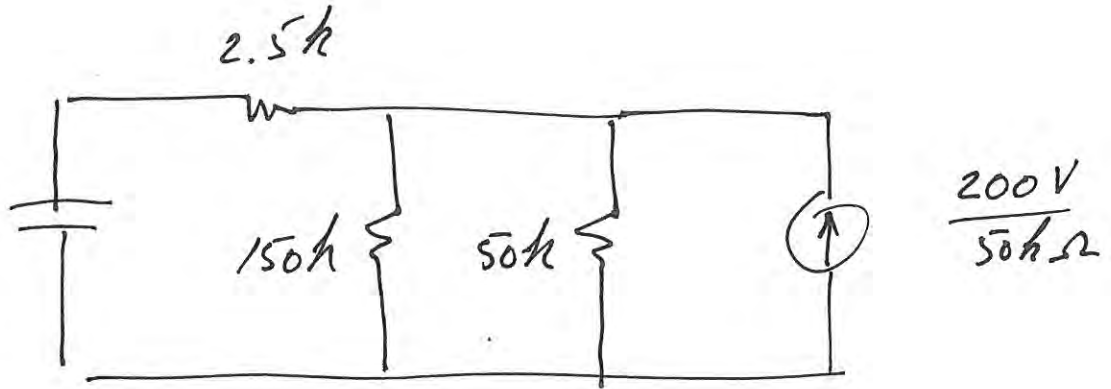

b) $V_c(\infty) = 150V$


c) $\tau = RC = (40k\Omega)(25nF) = 1\mu s$

$1/\tau = 1,000 s^{-1}$ **c) $\tau = 1\mu s$**

7.51, CONT'D.

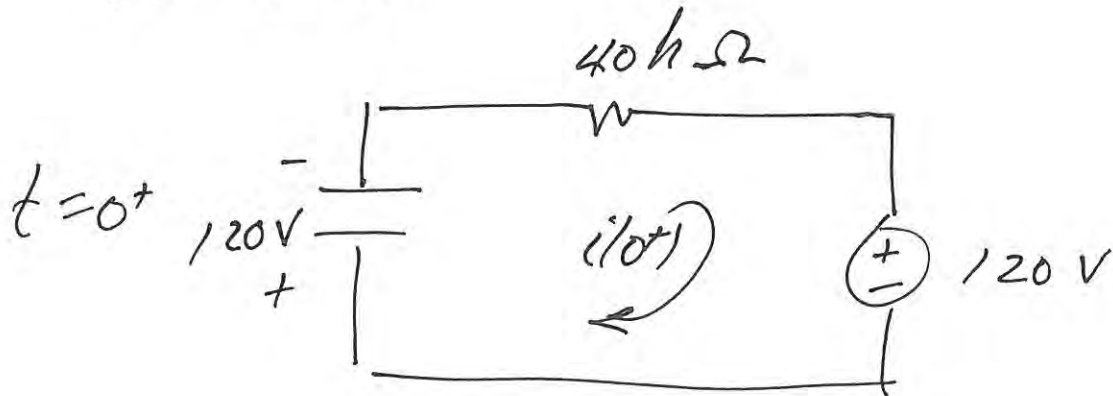(3)

TO GET $i(0^+)$ CONSIDER MESH EQ
AT $t=0^+$



$$-120V - 40k\Omega i(0^+) - 120V = 0$$

$$i(0^+) = \frac{+270V}{40k\Omega}$$

$$d) i(0^+) = 6.75mA$$

$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)]e^{-t/\tau}$$
$$= 150V + (-120 - 150)e^{-1,000t}$$


$$e) v_c(t) = 150 - 270e^{-1,000t}; t \geq 0$$

$$i(t) = C \frac{dv_c(t)}{dt} = (25 \times 10^{-9}) (-270) (-1000) e^{-1,000t}$$


$$i(t) = 6.75e^{-1,000t} mA; t \geq 0^+$$

7.61


①

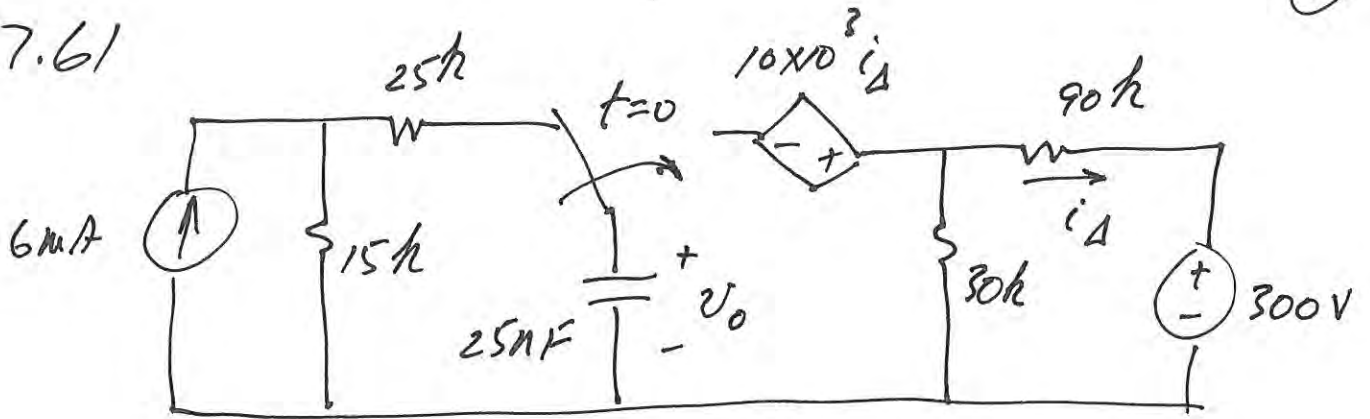

FIND $v_0(t)$; $t \geq 0$

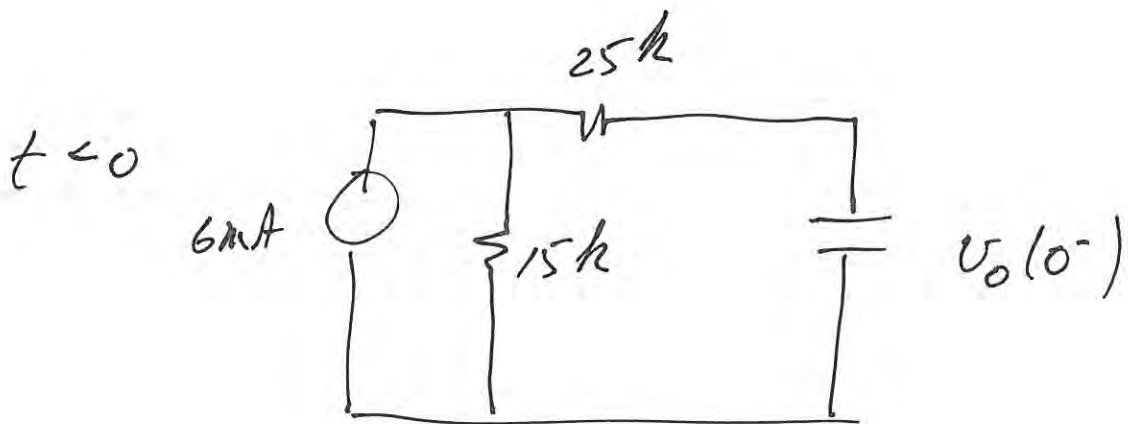

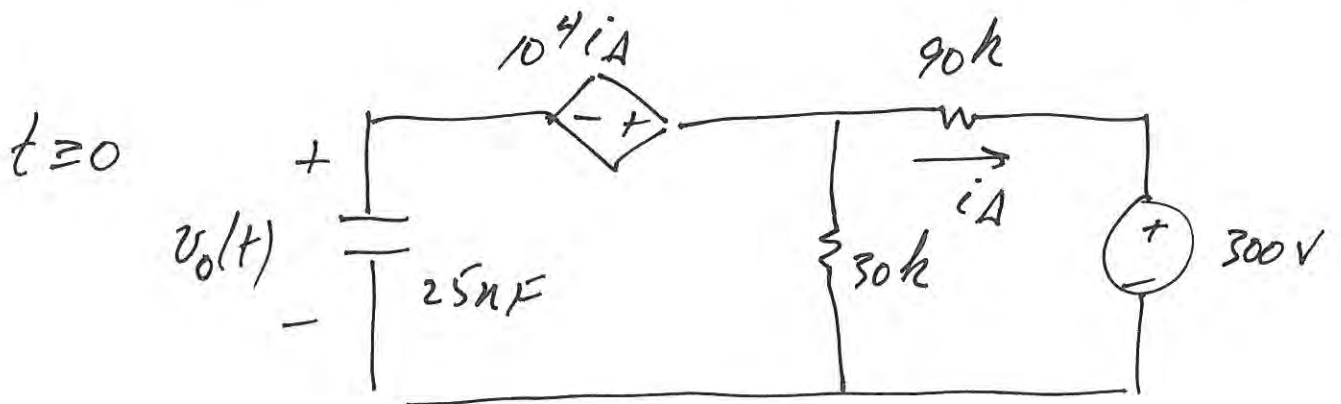
$$v_0(0^-) = (6\text{mA})(15\text{k}\Omega) = 90\text{V} = v_0(0^+)$$



7.61, CONT'D.

(2)

THEVENIN EQ "SEEN" BY CAP

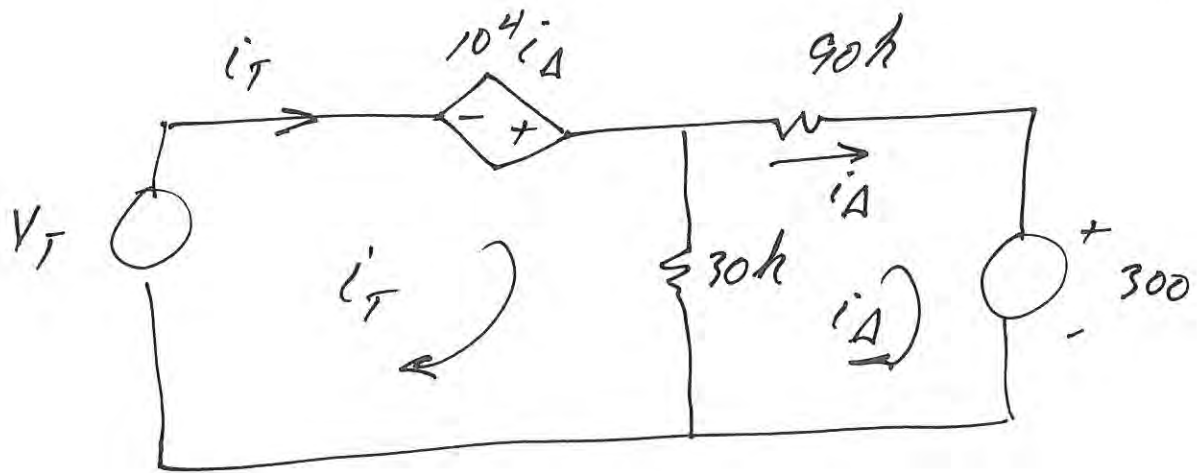

MESH EQ'S: ① $V_T + 10^4 i_A - 30k\Omega (i_T - i_A) = 0$

② $-90k\Omega i_A - 300V - 30k\Omega (i_A - i_T) = 0$

ELIMINATE i_A

FROM EQ ①: $V_T - 30k i_T + i_A (10^4 + 30k)$

③ $i_A = \frac{30k\Omega i_T - V_T}{40k\Omega}$

FROM EQ ②: $i_A (-90k\Omega - 30k\Omega) - 300 + 30k\Omega i_T$

④

EQ'S ③ & ④:

= 0

$-120k\Omega \left(\frac{30k\Omega i_T - V_T}{40k\Omega} \right) - 300V + 30k\Omega i_T = 0$


(2)

7.61, CONT'D.

$$-3(30k\Omega i_T - v_T) - 300V + 30k\Omega i_T = 0$$

$$v_T = 100V + 20k\Omega i_T$$
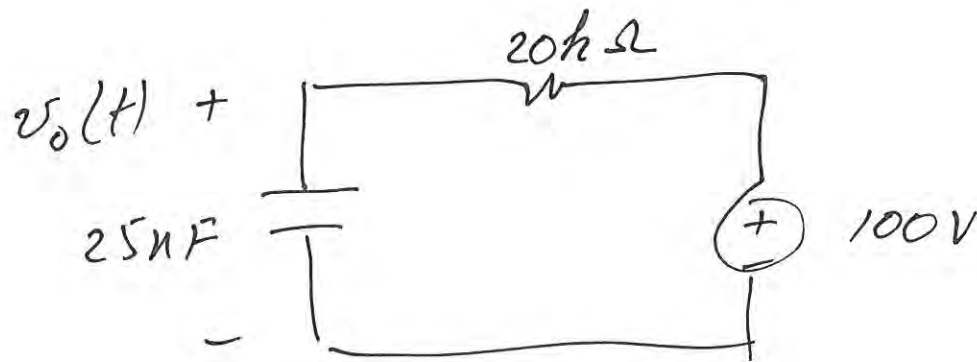
$$\begin{array}{cc} \uparrow & \uparrow \\ v_{T1} & R_{T1} \end{array}$$



$$v_o(\infty) = 100V, \tau_c = (25nF)(20k\Omega) = 0.5ms$$


$$v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau_c}$$

$$v_o(t) = 100 - 10e^{-2,000t} \text{ V}; t \geq 0$$

7.61, CONT'D.

ALTERNATE THEVENIN

(1)

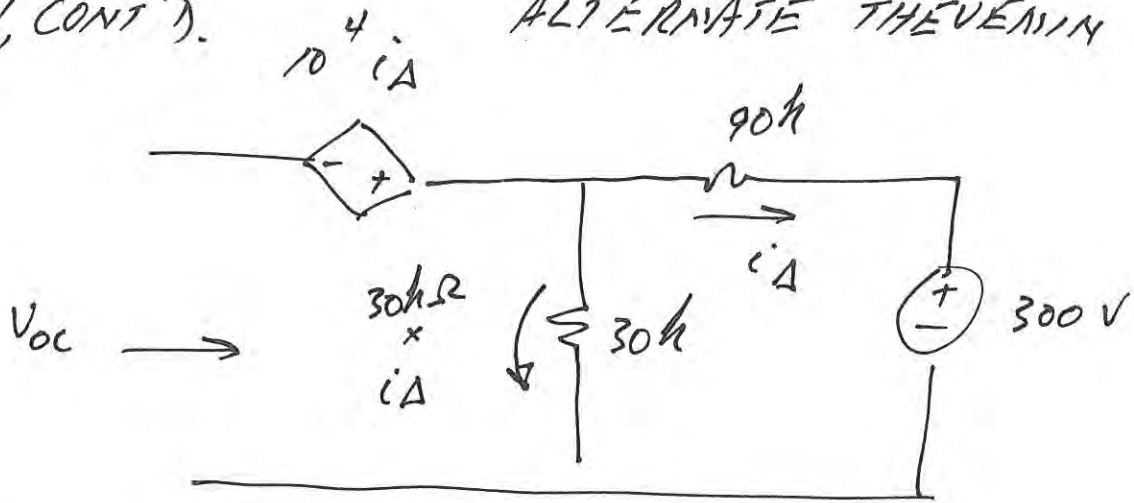

MESH:

$$V_{OC} + 10^4 i_{\Delta} + 30k i_{\Delta} = 0$$

$$V_{OC} = -40k\Omega i_{\Delta} \quad (1)$$

MESH $-90k i_{\Delta} - 300V - 30k i_{\Delta} = 0$

$$-120k i_{\Delta} = 300V$$


$$i_{\Delta} = \frac{-300V}{120k\Omega} = \underline{\underline{-2.5mA}} \quad (2)$$

(1), (2): $V_{OC} = (-40k\Omega)(-2.5mA) = 100V$

$$\underline{\underline{V_{TH} = 100V}}$$

7.61, CONT'D.

(2)

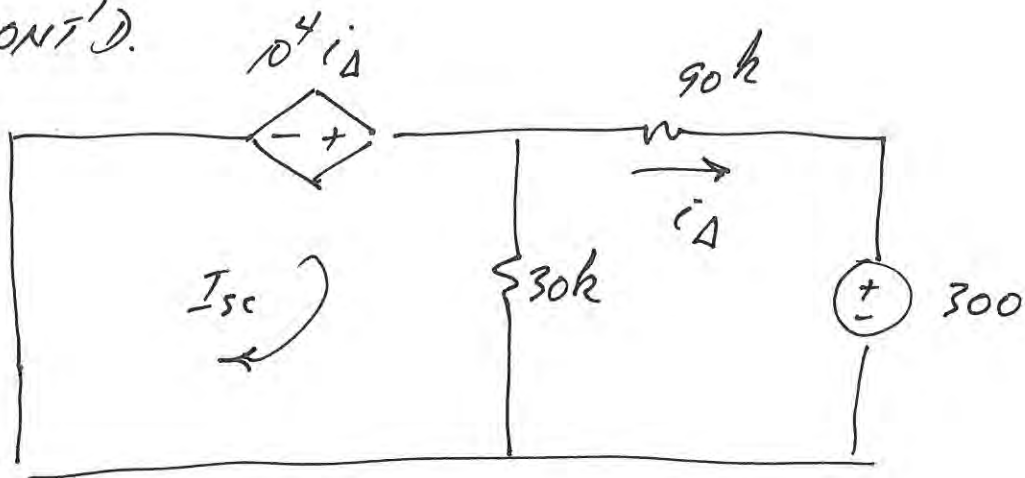

MESH EQ'S

$$10^4 i_D - (I_{sc} - i_D) 30k = 0 \quad (1)$$

$$-90ki_D - 300 - (i_D - I_{sc}) 30k = 0 \quad (2)$$

$$(1) \rightarrow 40ki_D = 30kI_{sc} \rightarrow i_D = \frac{3}{4} I_{sc} \quad (3)$$

$$(2) \rightarrow -120ki_D + 30kI_{sc} = 300$$


$$(2), (3) \rightarrow -120k\left(\frac{3}{4}\right)I_{sc} + 30kI_{sc} = 300$$

$$-60kI_{sc} = 300 \rightarrow \underline{\underline{I_{sc} = -5mA}}$$

$$R_{TH} = \frac{V_{TH}}{-I_{sc}} = 20k\Omega$$

(NOTE SENSE OF I_{sc} & V_{TH} IN SAME DIRECTION)
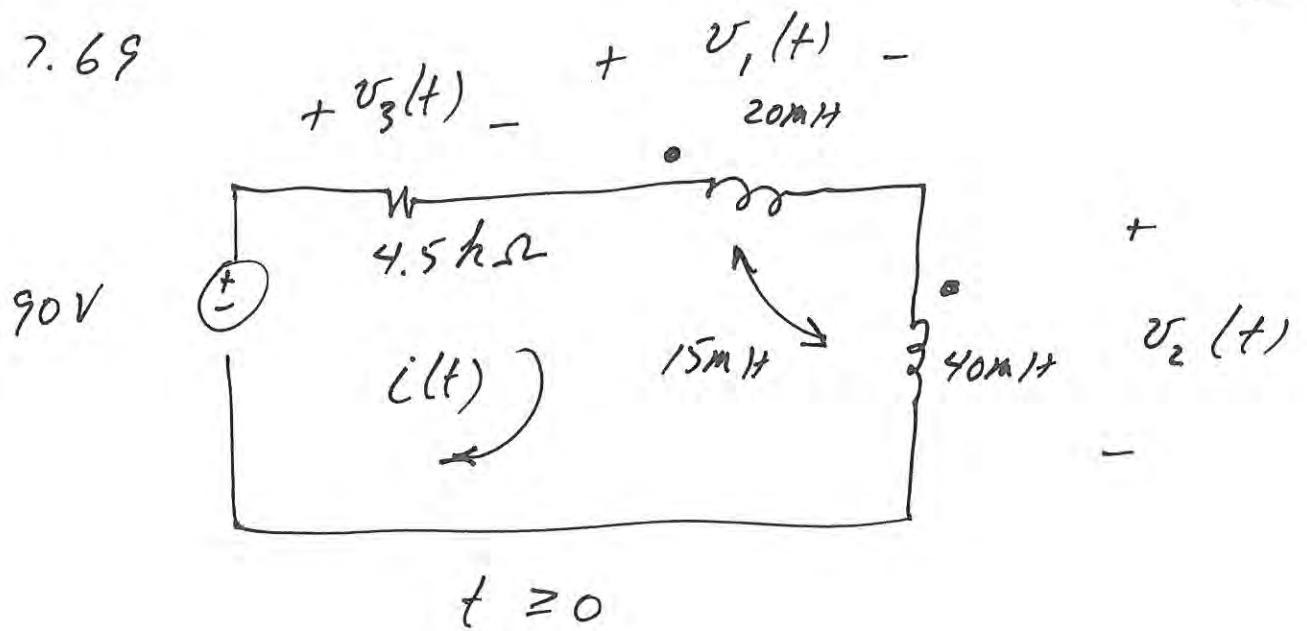
$$\underline{\underline{R_{TH} = 20k\Omega}}$$



$$i(0) = 0$$

$$i(\infty) = 90V / 4.5k\Omega = 0.02A = 20mA$$

$$L_{eq} = L_1 + L_2 + L_3 = 20mH + 40mH + 30mH = 0.090H$$

$$\tau = L_{eq} / R = 0.090 / 4.5k = 20\mu s$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$a) i(t) = 20(1 - e^{-50,000t}) mA; t \geq 0$$

7.69, CONT'D.

$$\begin{aligned}
v_1(t) &= L_1 \frac{di(t)}{dt} + R_1 \frac{di(t)}{dt} \\
&= (0.02 + 0.015) \frac{d}{dt} [20(1 - e^{-50,000t}) \text{ mA}] \\
&= (0.02 + 0.015)(-20 \text{ mA})(-50,000) e^{-50,000t}
\end{aligned}$$

$$\boxed{b) \ v_1(t) = 35 e^{-50,000t}; \ t \geq 0^+} \quad \text{VOLTS}$$

$$\begin{aligned}
v_2(t) &= L_2 \frac{di(t)}{dt} + R_2 \frac{di(t)}{dt} \\
&= (0.04 + 0.015)(-20 \text{ mA})(-50,000) e^{-50,000t}
\end{aligned}$$

$$\boxed{c) \ v_2(t) = 55 e^{-50,000t}; \ t \geq 0^+} \quad \text{VOLTS}$$

$$d) \ v_3(t) = 4.5 \text{ k}\Omega \times i(t)$$

$$\boxed{v_3(t) = 90(1 - e^{-50,000t}) \text{ V}; \ t \geq 0}$$

7.69, CONT'D.

DO ANSWERS FOR b), c), & d)

MAKE SENSE?

MESH EQ:

$$90 \stackrel{?}{=} v_1(t) + v_2(t) + v_3(t)$$

$$\begin{aligned} \text{R.H.S.} &= 35e^{-50,000t} + 55e^{-50,000t} \\ &\quad + 90(1 - e^{-50,000t}) \\ &= 90 = \text{L.H.S.} \end{aligned}$$

YES, ANSWERS MAKE SENSE