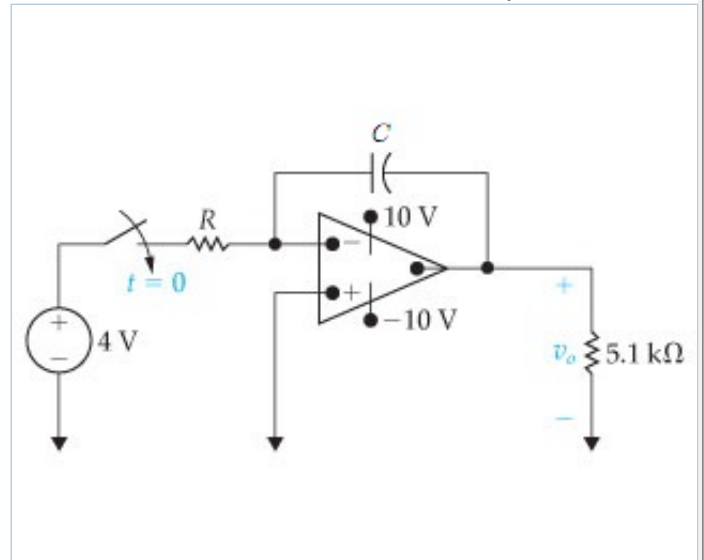


Problem 7.90 PSpice|Multisim

The energy stored in the capacitor in the circuit is zero at the instant the switch is closed. The ideal operational amplifier reaches saturation in 18 ms .



Part A


What is the numerical value of R in kilo-ohms, if $C = 310 \text{ nF}$?

ANSWER:

$R =$ $\text{k}\Omega$

Problem 8.2 PSpice|Multisim

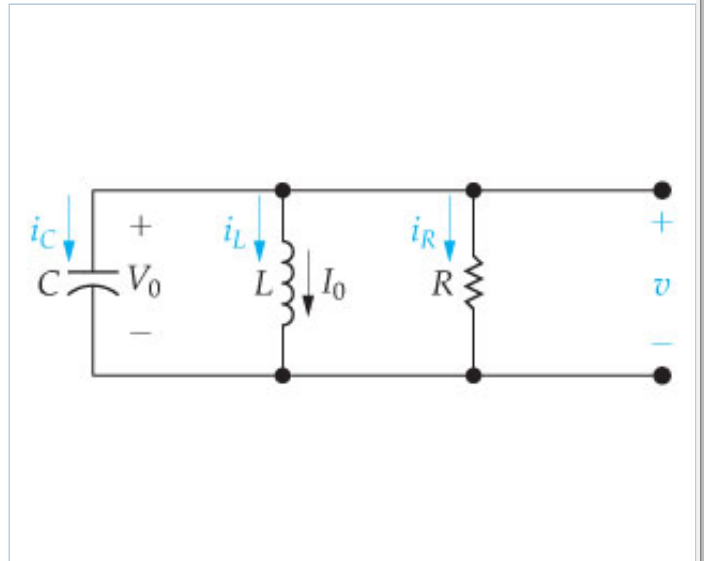The circuit elements in the circuit in are $R = 100 \Omega$, $C = 5 \mu\text{F}$, and $L = 200 \text{ mH}$. The initial inductor current is -0.3 A , and the initial capacitor voltage is 25 V .



Part A


Find the expression for $v(t)$ for $t \geq 0$.

ANSWER:

- $70,000te^{-1000t} + 50e^{-1000t} \text{ V}$
- $35,000te^{-1000t} - 50e^{-1000t} \text{ V}$
- $70,000te^{-1000t} + 25e^{-1000t} \text{ V}$
- $70,000te^{-1000t} - 50e^{-1000t} \text{ V}$
- $35,000te^{-1000t} + 25e^{-1000t} \text{ V}$
- $35,000te^{-1000t} + 50e^{-1000t} \text{ V}$
- $70,000te^{-1000t} - 25e^{-1000t} \text{ V}$
- $35,000te^{-1000t} - 25e^{-1000t} \text{ V}$

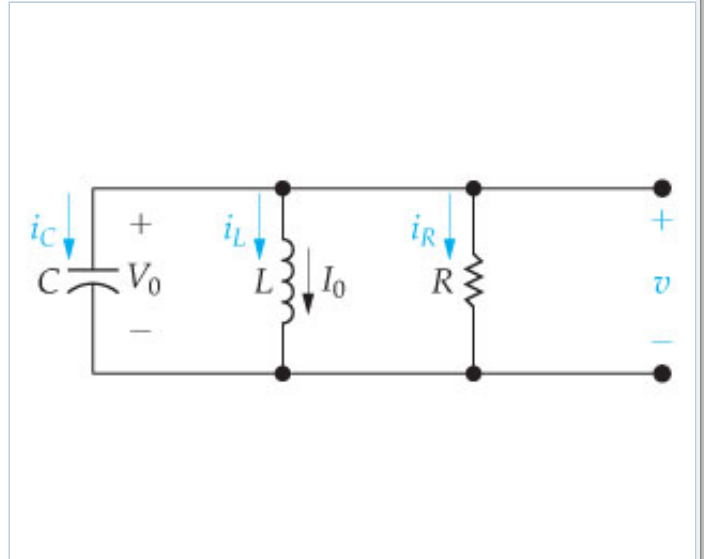Problem 8.7

The voltage response for the circuit in is known to be $v(t) = D_1 t e^{-80t} + D_2 e^{-80t}$, $t \geq 0$, where t is in seconds. The initial current in the inductor (I_0) is -25 mA , and the initial voltage on the capacitor (V_0) is 5 V . The resistor has a value of 50Ω .



Part A

Find the value of L .

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$L =$

Part B

Find the value of C .

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$C =$

Part C

Find the value of D_1 .

Express your answer using three significant figures.

ANSWER:

$D_1 =$ V/s

Part D

Find the value of D_2 .

Express your answer using three significant figures.

ANSWER:

$$D_2 = \text{[input box]} \text{ V}$$

Part E

Find $i_C(t)$ for $t \geq 0^+$.


Express your answer in terms of t , where t is in milliseconds.

ANSWER:

$$i_C = \text{[input box]} \text{ mA}$$

Problem 8.24 PSpice|Multisim

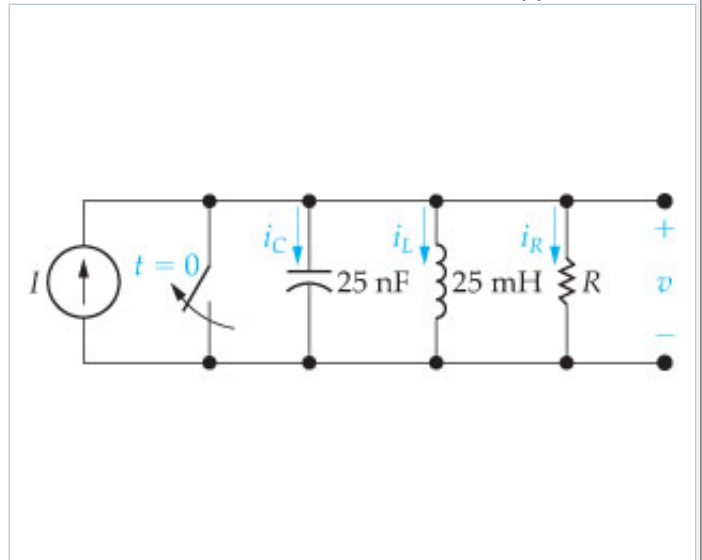The initial energy stored in the circuit in the figure is zero. At $t = 0$, a dc current source of 24 mA is applied to the circuit. The value of the resistor is $400\ \Omega$.



Part A

Find $v(t)$ for $t \geq 0$;

ANSWER:

- $32(e^{-20,000t} + e^{-40,000t})\ \text{V}$
- $16(e^{-20,000t} - e^{-80,000t})\ \text{V}$
- $16(e^{-20,000t} - e^{-40,000t})\ \text{V}$
- $32(e^{-20,000t} - e^{-80,000t})\ \text{V}$
- $16(e^{-20,000t} + e^{-80,000t})\ \text{V}$
- $16(e^{-20,000t} + e^{-40,000t})\ \text{V}$
- $32(e^{-20,000t} + e^{-80,000t})\ \text{V}$
- $32(e^{-20,000t} - e^{-40,000t})\ \text{V}$

Part B

Find $i_R(t)$ for $t \geq 0$;

ANSWER:

- $40(e^{-20,000t} - 2e^{-80,000t}) \text{ mA}$
- $40(e^{-20,000t} + 2e^{-80,000t}) \text{ mA}$
- $20(e^{-20,000t} - e^{-80,000t}) \text{ mA}$
- $20(e^{-20,000t} - 2e^{-80,000t}) \text{ mA}$
- $20(e^{-20,000t} + 2e^{-80,000t}) \text{ mA}$
- $20(e^{-20,000t} + e^{-80,000t}) \text{ mA}$
- $40(e^{-20,000t} - e^{-80,000t}) \text{ mA}$
- $40(e^{-20,000t} + e^{-80,000t}) \text{ mA}$

Part C


Find $i_C(t)$ for $t \geq 0$;

ANSWER:

- $-8e^{-20,000t} + 32e^{-80,000t} \text{ mA}$
- $-8e^{-20,000t} - 32e^{-80,000t} \text{ mA}$
- $-8e^{-20,000t} + 16e^{-80,000t} \text{ mA}$
- $-4e^{-20,000t} - 32e^{-80,000t} \text{ mA}$
- $-4e^{-20,000t} + 16e^{-80,000t} \text{ mA}$
- $-8e^{-20,000t} - 16e^{-80,000t} \text{ mA}$
- $-4e^{-20,000t} + 32e^{-80,000t} \text{ mA}$
- $-4e^{-20,000t} - 16e^{-80,000t} \text{ mA}$

Problem 8.31 PSpice|Multisim

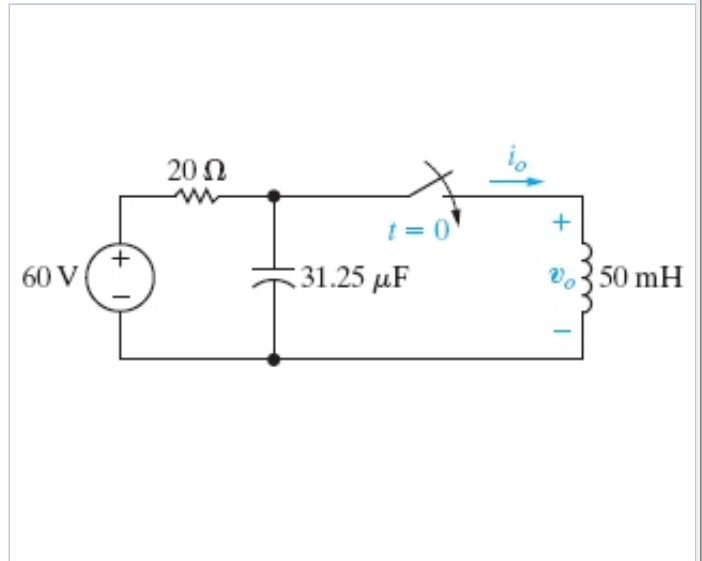The switch in the circuit in has been open for a long time before closing at $t = 0$.



Part A

Find $i_o(t)$ for $t \geq 0$.

ANSWER:


- $3 - 1200te^{-800t} + 6e^{-800t}$ A
- $3 - 1200te^{-800t} - 6e^{-800t}$ A
- $6 - 1200te^{-800t} - 3e^{-800t}$ A
- $3 - 1200te^{-800t} + 3e^{-800t}$ A
- $6 - 1200te^{-800t} + 6e^{-800t}$ A
- $3 - 1200te^{-800t} - 3e^{-800t}$ A
- $6 - 1200te^{-800t} + 3e^{-800t}$ A
- $6 - 1200te^{-800t} - 6e^{-800t}$ A

Problem 8.39

The current in the circuit in the following figure is known to be

$$i = B_1 e^{-2000t} \cos 1500t + B_2 e^{-2000t} \sin 1500t, t \geq 0.$$

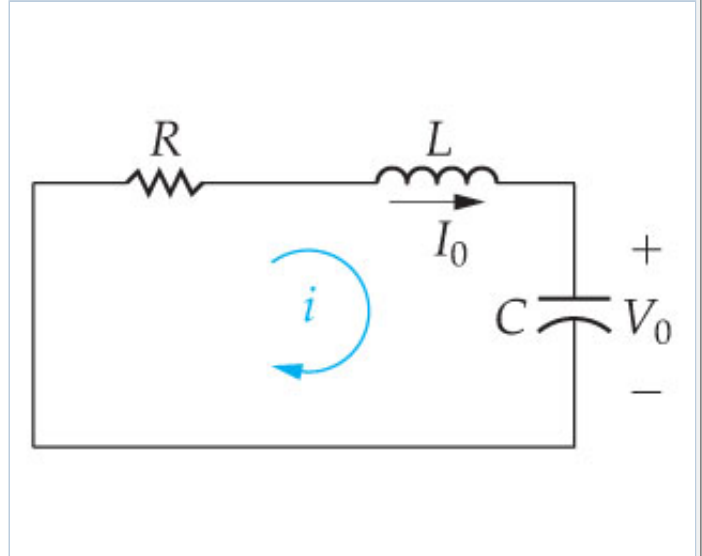The capacitor has a value of 80 nF ; the initial value of the current is 6 mA ; and the initial voltage on the capacitor is -21 V .



Part A

Find the value of R .

Express your answer with the appropriate units.

ANSWER:

$R =$

Part B

Find the value of L .

Express your answer with the appropriate units.

ANSWER:

$L =$

Part C

Find the value of B_1 .

Express your answer with the appropriate units.

ANSWER:

$$B_1 = \text{[input box]}$$

Part D

Find the value of B_2 .

Express your answer with the appropriate units.

ANSWER:

$$B_2 = \text{[input box]}$$



7.90 NODAL EQ AT NEG TERMINAL

$$\frac{v_n - 4V}{R} + C \frac{d}{dt}(v_n - v_o) = 0$$

POS TERM @ GROUND, $v_p = 0$

$$\text{BUT } v_n = v_p \Rightarrow \frac{-4V}{R} - C \frac{dv_o(t)}{dt} = 0$$

$$\frac{dv_o}{dt} = -\frac{4}{RC}$$

$$v_o(t) = \int_0^t \left(-\frac{4}{RC}\right) dx + v_o(0) \quad \begin{array}{l} \text{BY} \\ \text{INITIAL} \\ \text{COND} \end{array}$$


$$v_o(t) = -\frac{4}{RC} x \Big|_0^t$$

$$v_o(t) = -\frac{4t}{RC}$$

SATURATION (-10V) REACHED AT $t = 18 \text{ms}$

$$\frac{-4(0.018)}{R(310 \text{ nF})} = -10 \Rightarrow R = 23.226 \text{ k}\Omega //$$

8.2

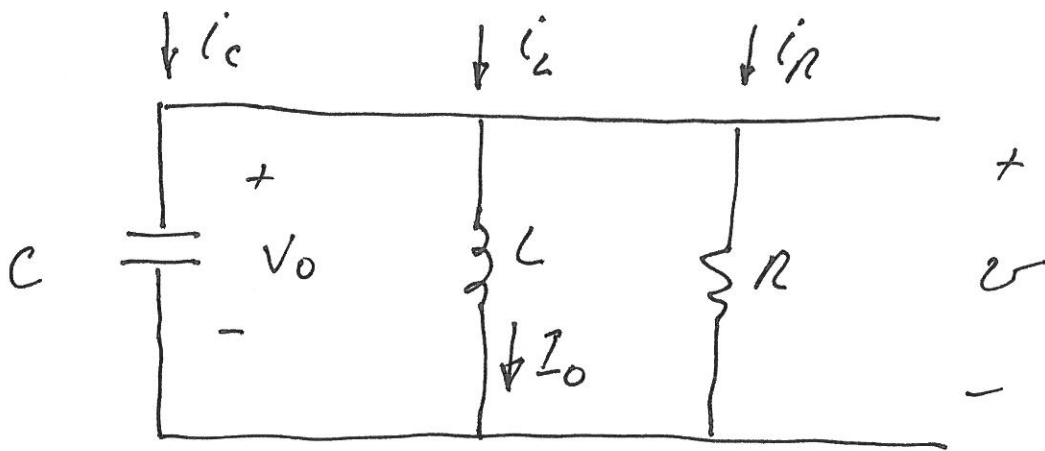

$$R = 100 \Omega$$

$$I_0 = -0.3 \text{ A}$$

$$L = 200 \text{ mH}$$

$$V_0 = 25 \text{ V}$$

$$C = 5 \mu\text{F}$$

FIND $v(t)$; $t \geq 0$

$$\left. \begin{aligned} \alpha &= \frac{1}{2RC} = 1,000 \text{ NP/S} \\ \omega_0 &= \frac{1}{\sqrt{LC}} = 1,000 \text{ RAD/S} \end{aligned} \right\} \Rightarrow \text{CRITICAL DAMPING}$$

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$v(0) = D_2 = V_0 \quad (1)$$

$$i_c(0^+) = C \frac{dv(t)}{dt} \Big|_{t=0^+}$$

$$= C \frac{d}{dt} [D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}] \Big|_{t=0^+}$$

8.2, CONT'D.

(2)

$$i_c(t^+) = c \left[\lambda_1 e^{-\alpha t} - \alpha \lambda_2 t e^{-\alpha t} - \alpha \lambda_2 e^{-\alpha t} \right] \Big|_{t=0^+}$$

$$i_c(t^+) = c (\lambda_1 - \alpha \lambda_2) \quad (2)$$

APPLY KCL AT NODE FOR $t=0^+$:

$$i_c(t^+) + i_2(t^+) + i_R(t^+) = 0$$

$$i_c(t^+) + I_0 + V_0/R = 0$$

$$i_c(t^+) = -I_0 - V_0/R \quad (3)$$

COMBINE EQ'S (1), (2), & (3):



$$c(\lambda_1 - \alpha \lambda_2) = -I_0 - V_0/R$$

$$\lambda_1 = \alpha \lambda_2 - \frac{1}{c} (I_0 + V_0/R)$$

$$\lambda_1 = 35,000 \text{ V/S}$$

$$v(t) = 35,000 t e^{-1,000 t} + 25 e^{-1,000 t}; \quad t \geq 0$$

Problem 8.2 (10th edition)

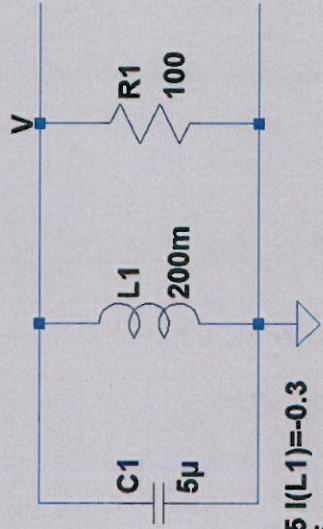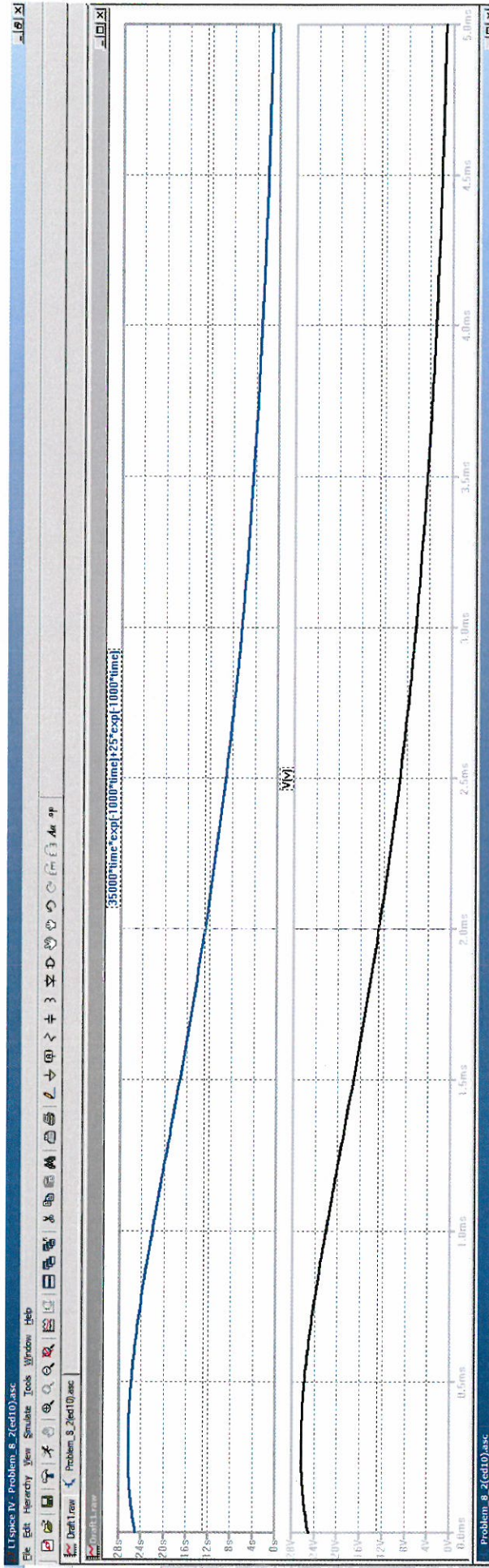

```
.ic V(V)=25 I(L1)=-0.3
.tran 0.005
```

Note units of seconds on ordinate of top plot.

①

8.7 $v(t) = D_1 + e^{-80t} + D_2 e^{-80t}; t \geq 0$

$$I_0 = -25 \text{ mA}, V_0 = 5 \text{ V}, R = 50 \Omega$$

a) L ? CRITICAL DAMPING // RLC

$$\alpha = \frac{1}{2RC} = \omega_0 = \frac{1}{\sqrt{LC}}$$

IN SOLN, $s_{1,2} = -\alpha = -80$

$$\frac{1}{2RC} = 80 \Rightarrow C = \frac{1}{2R \times 80} = 125 \mu\text{F}$$

$$\omega_0^2 = \alpha^2 = \frac{1}{LC} \Rightarrow L = \frac{1}{(80)^2 C}$$

$$L = 1.25 \text{ H} //$$

b) C ? FROM PART a, $C = 125 \mu\text{F} //$

c) $D_2 = v(0^+) = V_0 \Rightarrow D_2 = 5 \text{ V} //$

$$\frac{i_c(0)}{C} = D_1 - \alpha D_2 \rightarrow D_1 = \frac{i_c(0)}{C} + \alpha D_2$$

KCL AT TOP NODE:

$$\frac{v(0)}{R} + I_0 + i_c(0) = 0$$

$$i_c(0) = -I_0 - \frac{v(0)}{R}$$

(2)

$$i_c(0) = 25 \text{ mA} - \frac{D_2}{50}$$

$$= 25 \text{ mA} - \frac{5}{50} = -75 \text{ mA}$$

$$D_1 = \frac{-75 \text{ mA}}{125 \mu\text{F}} + 80 D_2 = -200 \text{ V/s} //$$

d) D_2 ? FROM PART c, $D_2 = 5 \text{ V} //$

e) $i_c(t)$; $t \geq 0^+$?

$$i_c(t) = C \frac{dv}{dt}$$

$$= C \frac{d}{dt} (D_1 t e^{-80t} + D_2 e^{-80t})$$

$$= C (D_1 e^{-80t} - 80 D_1 t e^{-80t} - 80 D_2 e^{-80t})$$

$$= C (D_1 - 80 D_2 - 80 D_1 t) e^{-80t}$$


$$= (2t - 0.075) e^{-80t} \text{ A}; t \text{ IN SEC}$$

$$= (0.002t - 0.075) e^{-0.08t} \text{ A}; t \text{ IN MS}$$

$$i_c(t) = \underline{\underline{(2t - 75) e^{-0.08t} \text{ mA}, t \text{ IN MS}}}$$

8.24

①

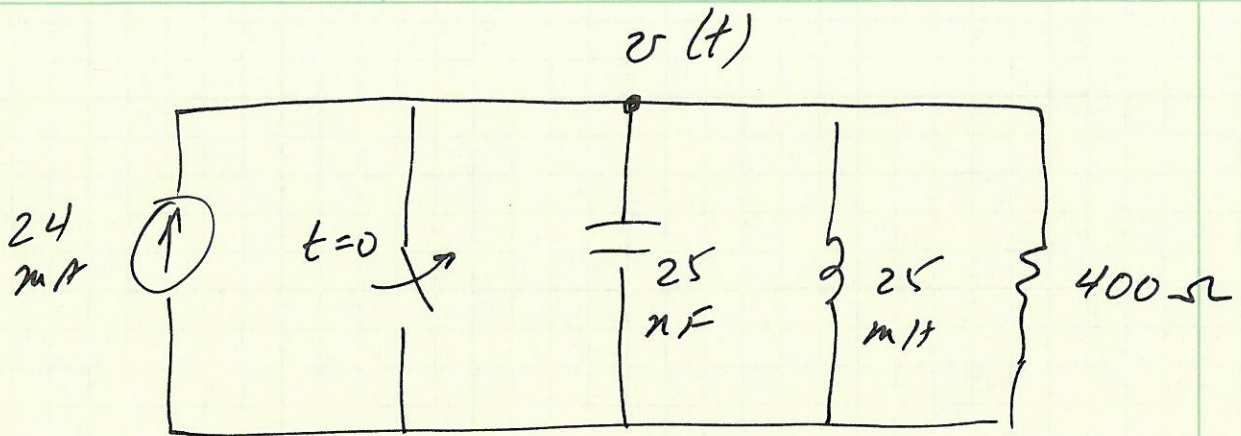

NO INITIAL ENERGY IN CIRCUIT

$$\alpha = \frac{1}{2RC}$$

$$= 50,000/\text{s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$= 40,000 \text{ RAD/S}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -20,000/\text{s}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -80,000/\text{s}$$

UNDERDAMPED \Rightarrow RESPONSE OF FORM

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{INITIAL CONDITION: } v(0) = 0 \Rightarrow A_1 + A_2 = 0$$

INITIAL CONDITION:

$$C \left. \frac{dv}{dt} \right|_{t=0^+} = i_c(0^+) = C(A_1 s_1 + A_2 s_2)$$

KCL AT UPPER NODE (AT $t=0^+$):

$$-24 \text{ mA} + i_c(0^+) + i_L(0^+) + \frac{v(0^+)}{4R} = 0$$

INDUCTOR
CURRENT
CANNOT CHANGE
INSTANTANEOUSLY

FROM NO INITIAL
ENERGY, $v(0^+) = 0$

$$\Rightarrow i_L(0^+) = 0$$

$$\circ \circ \quad i_c(0^+) = 24 \text{ mA}$$

$$24 \text{ mA} = C(A_1 S_1 + A_2 S_2)$$

$$\text{BUT } A_2 = -A_1$$

$$\frac{24 \text{ mA}}{25 \text{ nF}} = -20,000 A_1 + 80,000 A_1 = +60,000 A_1$$

$$A_1 = \frac{24 \text{ mA}}{(25 \text{ nF})(+60,000)} = +16 \text{ V}$$

$$v(t) = +16 e^{-20,000t} - 16 e^{-80,000t} \text{ V}; t \geq 0$$

FOR t IN μs ,

$$a) \quad v(t) = +16 (e^{-20t} - e^{-80t}) \text{ V}; t \geq 0$$

$$b) i_R(t) = \frac{v(t)}{R} = +40(e^{-20t} - e^{-80t}) \text{ mA}; t \geq 0$$

t IN ms

$$c) i_c(t) = C \frac{dv}{dt}$$

$$= 25 \text{ nF} \frac{d}{dt} \left[+16(e^{-20,000t} - e^{-80,000t}) \right]$$

$$= 25 \text{ nF} \left[+16(20,000) e^{-20,000t} \right.$$

$$\left. - 16(80,000) e^{-80,000t} \right]$$

$$= (-8 e^{-20,000t} + 32 e^{-80,000t}) \text{ mA}; t \geq 0$$

CHECK FOR $t=0$:


$$i_c(0) = 24 \text{ mA} \checkmark$$


Problem 8.24 (10th edition)

LTspice IV - Problem_8_24.asc

File Edit Hierarchy View Simulate Tools Window Help


Problem_8_24.asc Problem_8_24.asc

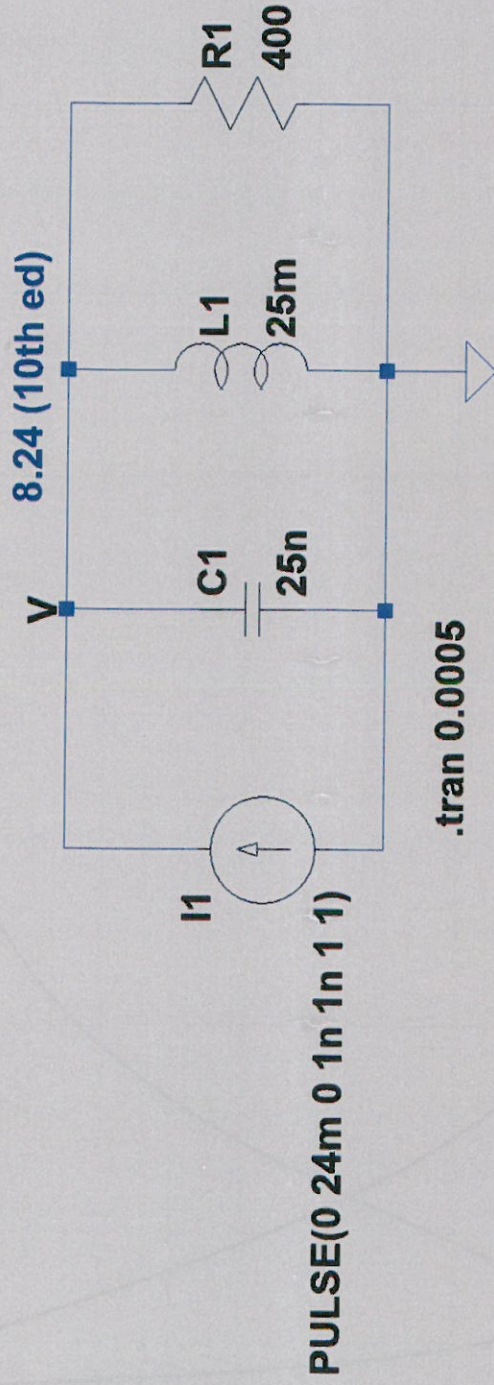



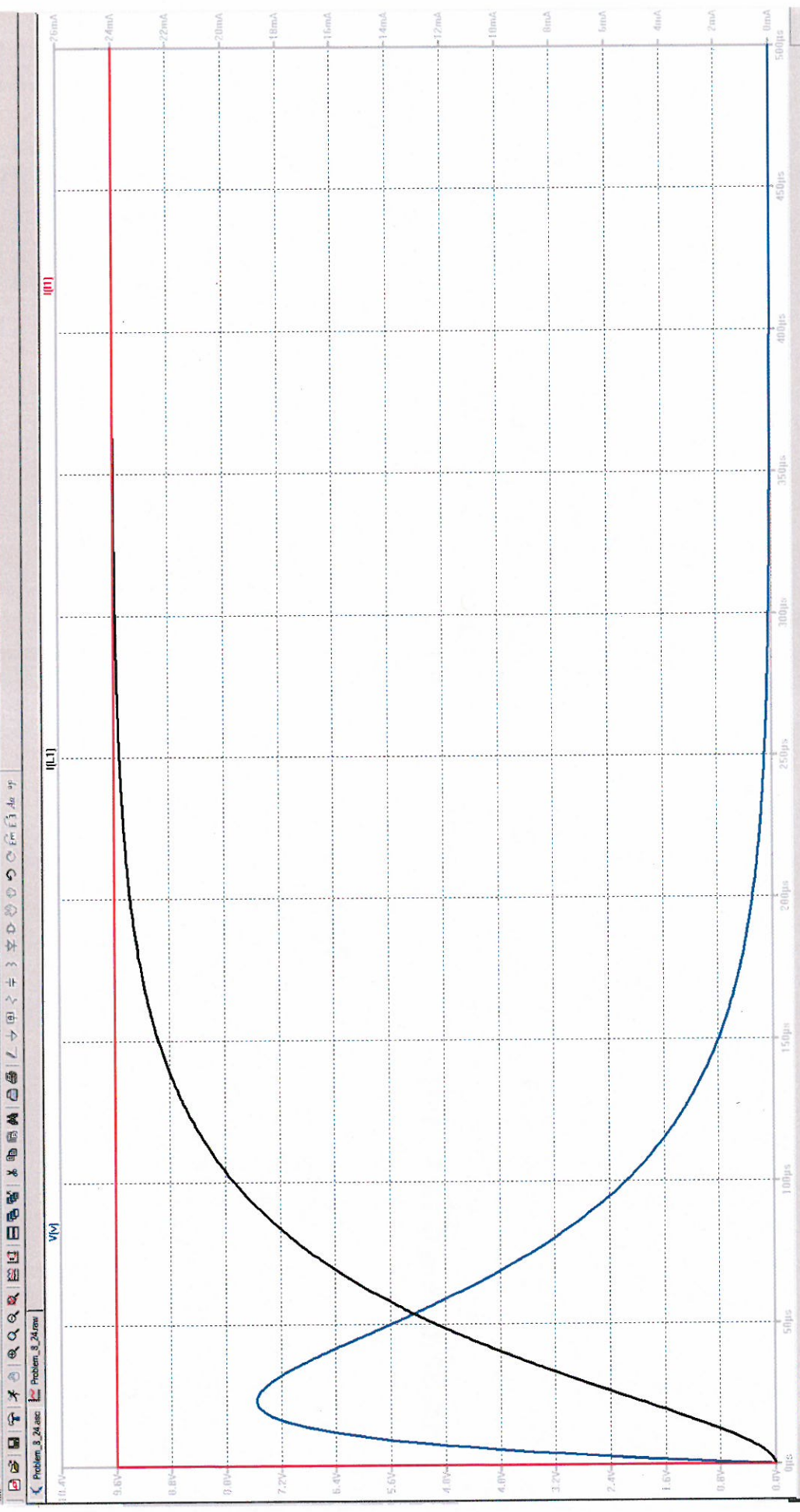


8.31

(1)

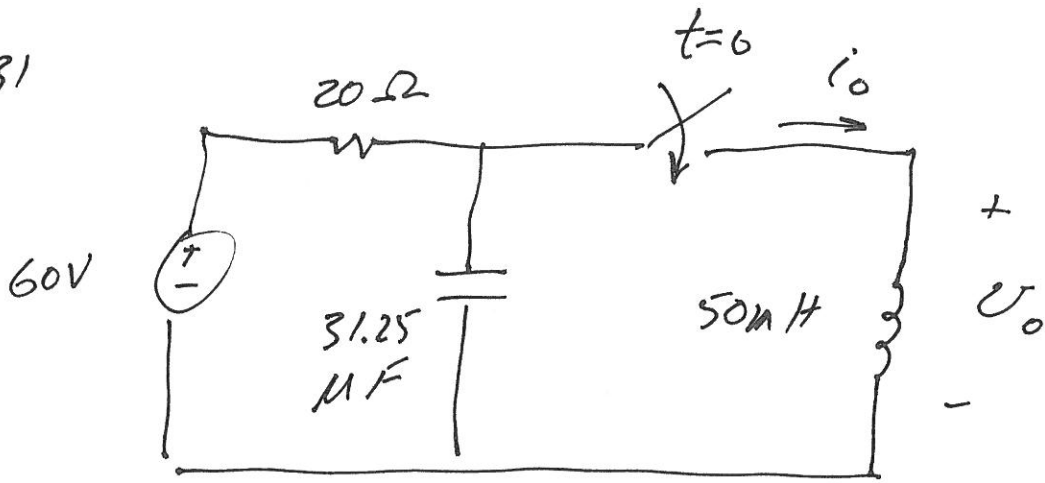

FIND $i_0(t)$

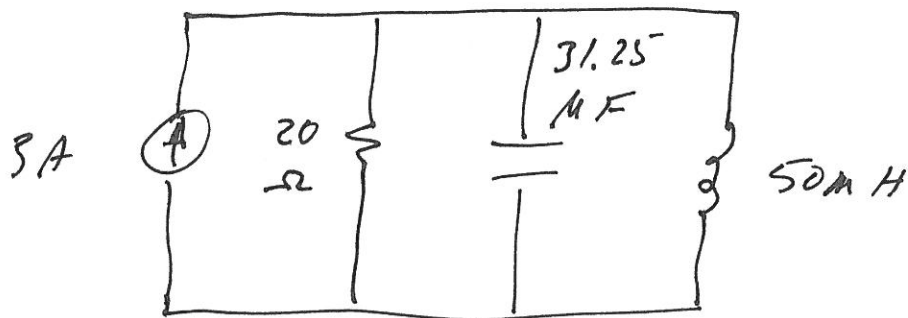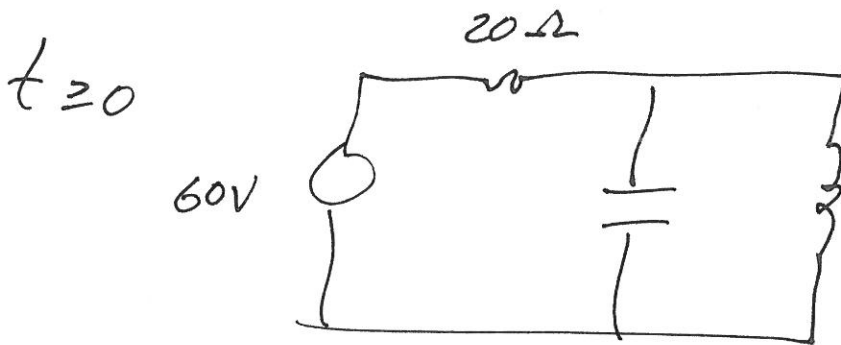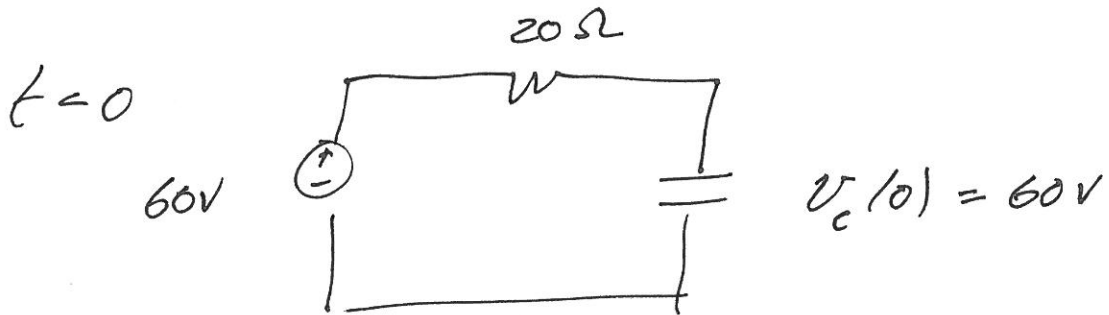

(2)

8.31, CONT'D.

PARALLEL RLC

$$s_i = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 800 \text{ RAD/S}$$

$$\alpha = \frac{1}{2RC} = 800 \text{ NP/S}$$

 \Rightarrow CRITICAL DAMPING

$$i_o(t) = I_F + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$I_F = 3 \text{ A}$$

$$v_o(0) = L \left. \frac{di_o(t)}{dt} \right|_{t=0}$$

$$= L \left. \frac{d}{dt} (I_F + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}) \right|_{t=0}$$

$$= L (-\alpha D_1 t e^{-\alpha t} + D_1 e^{-\alpha t} - \alpha D_2 e^{-\alpha t}) \Big|_{t=0}$$

$$v_o(0) = L (D_1 - \alpha D_2) = 60 \text{ V}$$


$$i_o(0) = 0 = I_F + D_2 \Rightarrow D_2 = -3 \text{ A}$$

$$D_1 = \frac{60 \text{ V}}{L} + \alpha D_2 = -1,200 \text{ A/S}$$

$$i_o(t) = 3 - 1,200 t e^{-800 t} - 3 e^{-800 t}; t \geq 0$$

8.39

①

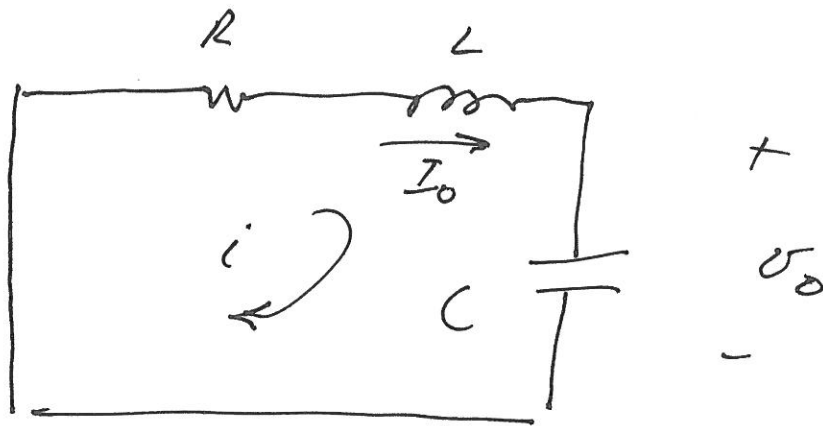

$$\text{GIVEN: } i(t) = B_1 e^{-2,000t} \cos 1,500t + B_2 e^{-2,000t} \sin 1,500t$$

THIS IS A NATURAL RESPONSE

$$C = 80 \text{ nF} \quad I_0 = 7.5 \text{ mA}$$

$$U_0(0) = -30 \text{ V}$$

$$\text{FIND: } R, L, B_1, B_2$$

SERIES RLC WITH UNDERDAMPED RESPONSE

$$\alpha = \frac{R}{2L} = 2,000 \text{ Np/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 1,500 \text{ rad/s}$$

$$\omega_0^2 - \alpha^2 = (1,500)^2$$

8.39, CONT'D.

(2)

$$\omega_0^2 = (1500)^2 + (2000)^2 = \frac{1}{LC}$$

$$L = \frac{1}{C[(1500)^2 + (2000)^2]}$$

$$\boxed{L = 2H}$$

$$\frac{R}{2L} = 2,000 \Rightarrow R = 2(2,000)L$$

$$\boxed{R = 8k\Omega}$$

$$i(0) = I_0 = B_1$$

$$\boxed{B_1 = 7.5mA}$$

MESH EQ AT $t=0$:

$$-I_0 R - L \left. \frac{di}{dt} \right|_{t=0} - V_0 = 0$$

NEED $\left. \frac{di}{dt} \right|_{t=0}$

$$\frac{di}{dt} = \frac{d}{dt} \left[e^{-2,000t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \right]$$

8.39, CONT'D.

(3)

$$\frac{di}{dt} = -2,000 e^{-2,000t} (B_1 \cos \omega t + B_2 \sin \omega t) + e^{-2,000t} (-B_1 \omega \sin \omega t + B_2 \omega \cos \omega t)$$

$$\left. \frac{di}{dt} \right|_{t=0} = -2,000 B_1 + \omega B_2$$

$$\text{NOW } L \left. \frac{di}{dt} \right|_{t=0} = -I_0 R - V_0$$

$$B_2 = \frac{-I_0 R - V_0}{L} + 2,000 B_1 = 0$$

1,500

$$\boxed{B_2 = 0}$$