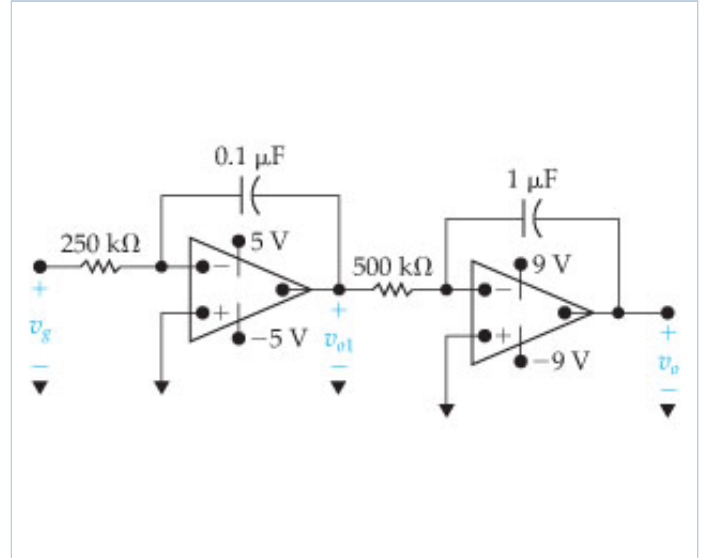


Problem 8.60 PSpice|Multisim

No energy is stored in the circuit shown in the figure when the input voltage v_g jumps instantaneously from 0 to 25 mV. The initial values of voltage are $v_{o1}(0) = 5$ V and $v_o(0) = 8$ V.



Part A

Find the equation for $v_o(t)$ for $0 \leq t \leq t_{\text{sat}}$

Express your answer in terms of t , where t is in seconds.

ANSWER:

$$v_o = \text{[input box]} \text{ V}$$

Part B

How long does the circuit take to reach saturation?

Express your answer with the appropriate units.

ANSWER:

$$t = \text{[input box]}$$

Problem 9.3

Consider the sinusoidal voltage
 $v(t) = 35 \cos(400\pi t + 60^\circ)$ V.

Part A

What is the maximum amplitude of the voltage?

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$v_{\max} =$

Part B

What is the frequency in hertz?

Express your answer using three significant figures.

ANSWER:

$f =$ Hz

Part C

What is the frequency in radians per second?

Express your answer using three significant figures.

ANSWER:

$\omega =$ rad/s

Part D

What is the phase angle in radians?

Express your answer using three significant figures.

ANSWER:

$\theta =$ rad

Part E

What is the phase angle in degrees?

Express your answer using three significant figures.

ANSWER:

$$\theta = \text{[input box]}^\circ$$

Part F

What is the period?

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$T = \text{[input box]}$$

Part G

What is the first time after $t = 0$ that $v = 0$ V?

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$t = \text{[input box]}$$

Part H

The sinusoidal function is shifted $5/6$ ms to the right along the time axis. What is the expression for $v(t)$?

ANSWER:

- $35 \cos(400\pi t + 2\pi/3)$ V
- $35 \sin(400\pi t + 2\pi/3)$ V
- $35 \cos(400\pi t)$ V
- $35 \sin(400\pi t)$ V

Part I

What is the minimum value of milliseconds that the function must be shifted to the left if the expression for $v(t)$ is $35 \sin(400\pi t)$ V?

Express your answer using three significant figures.

ANSWER:

$t =$

ms




Problem 9.7

Part A

Find the rms value of the half-wave rectified sinusoidal voltage shown in the figure.

Express your answer in terms of V_m .

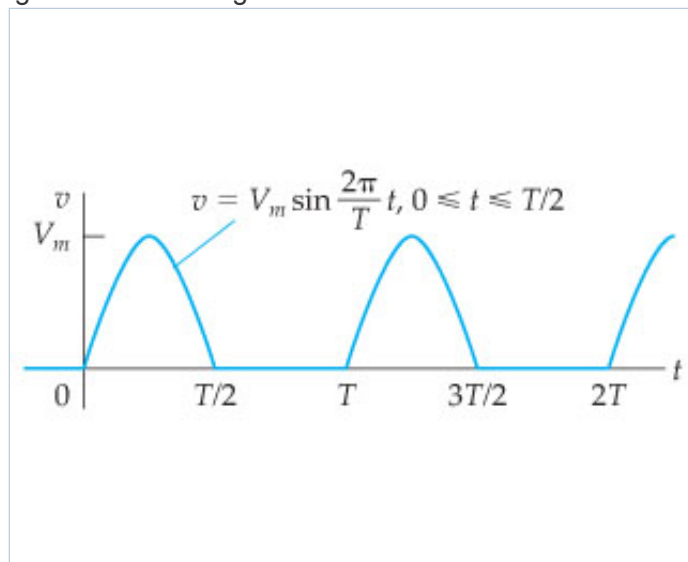

ANSWER:

$V_{\text{rms}} =$ V

Problem 9.11

Select the correct expression for combination the following sinusoidal functions into a single trigonometric expression:

Part A

$$y = 30 \cos(200t - 160^\circ) + 15 \cos(200t + 70^\circ).$$

ANSWER:

- $y = -23.4 \cos(200t - 171^\circ)$
 - $y = 23.4 \cos(200t + 171^\circ)$
 - $y = 0$
 - $y = -23.4 \cos(200t + 171^\circ)$
 - $y = 23.4 \cos(200t - 171^\circ)$
-

Part B

$$y = 90 \sin(50t - 20^\circ) + 60 \cos(50t - 70^\circ).$$

ANSWER:

- $y = 0$
 - $y = -141.3 \cos(50t + 94.2^\circ)$
 - $y = 141.3 \cos(50t - 94.2^\circ)$
 - $y = -141.3 \cos(50t - 94.2^\circ)$
 - $y = 141.3 \cos(50t + 94.2^\circ)$
-

Part C

$$y = 50 \cos(5000t - 60^\circ) + 25 \sin(5000t + 110^\circ) - 75 \cos(5000t - 30^\circ).$$

ANSWER:

- $y = 0$
 - $y = 16.7 \cos(5000t - 171^\circ)$
 - $y = -16.7 \cos(5000t - 171^\circ)$
 - $y = 16.7 \cos(5000t + 171^\circ)$
 - $y = -16.7 \cos(5000t + 171^\circ)$
-

Part D

$$y = 10 \cos(\omega t + 30^\circ) + 10 \sin \omega t + 10 \cos(\omega t + 150^\circ).$$

ANSWER:


- $y = -10 \cos(\omega t + 153^\circ)$
- $y = 10 \cos(\omega t - 153^\circ)$
- $y = 0$
- $y = -10 \cos(\omega t - 153^\circ)$
- $y = 10 \cos(\omega t + 153^\circ)$

Problem 9.14

The expressions for the steady-state voltage and current at the terminals of the circuit seen in the figure are

$$v_g = 310 \cos(5000\pi t + 75^\circ) \text{ V},$$
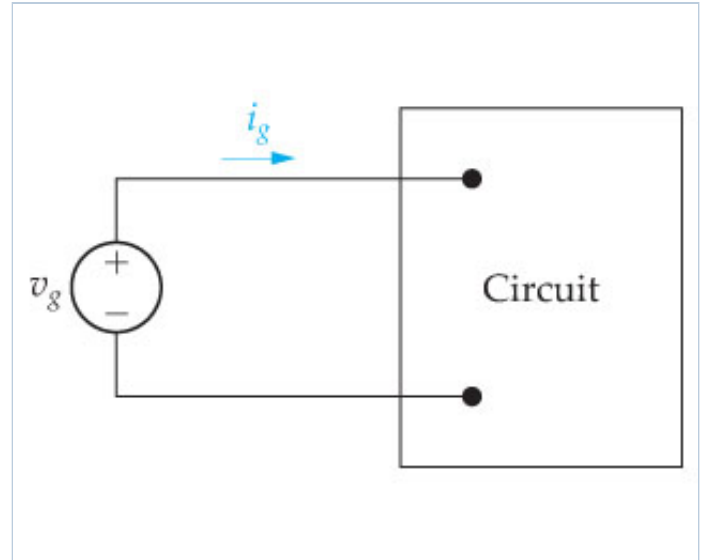
$$i_g = 4 \sin(5000\pi t + 106^\circ) \text{ A}$$



Part A

What is the impedance seen by the source?

Enter your answer using polar notation. Express argument in degrees.

ANSWER:

$$Z = \text{[input box]} \Omega$$

Part B


By how many microseconds is the current out of phase with the voltage?

Express your answer with the appropriate units.

ANSWER:

$$t = \text{[input box]}$$

8.60

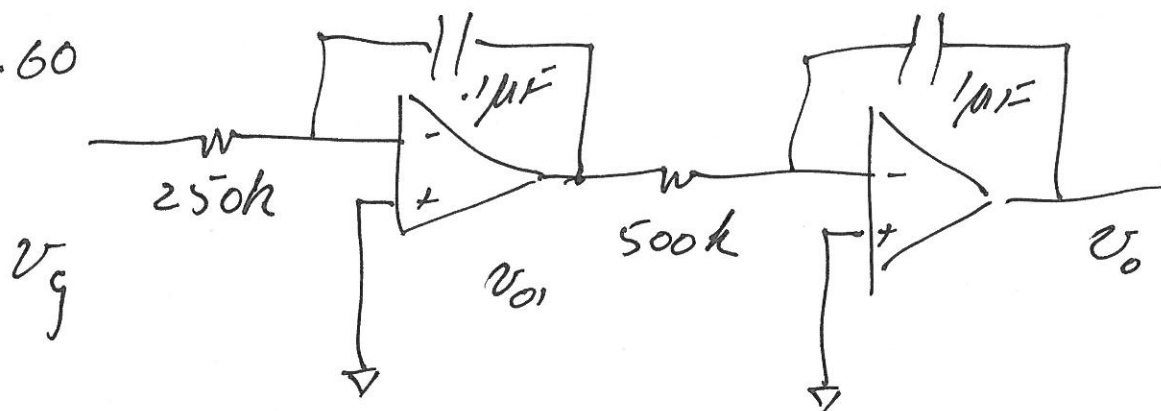

$$v_g = \begin{cases} 0; & t < 0 \\ 25\text{mV}; & t > 0 \end{cases} \quad \begin{aligned} v_{o1}(0) &= 5\text{V} \\ v_o(0) &= 8\text{V} \end{aligned}$$

1ST STAGE NODAL $\frac{v_n - v_g}{250k} + 0.1\mu\text{F} \frac{d}{dt}(v_n - v_{o1}) = 0$

$$v_p = v_n = 0$$

$$\Rightarrow \frac{dv_{o1}}{dt} = -\frac{v_g}{250k\Omega \times 0.1\mu\text{F}} = -40v_g \quad (1)$$

SIMILARLY, $\frac{dv_o}{dt} = \frac{-v_{o1}}{500k\Omega \times 0.1\mu\text{F}} = -2v_{o1} \quad (2)$

DIFFERENTIATE EQ (2) : $\frac{d^2v_o}{dt^2} = -2 \frac{dv_{o1}}{dt} \quad (3)$

SUB EQ (1) INTO EQ (3) :


$$\frac{d^2v_o}{dt^2} = 80v_g(t) = 2 \quad \text{FOR } t > 0$$

INTEGRATE: $\frac{dv_o}{dt} = 2t + K_1,$

INTEGRATE: $v_o(t) = t^2 + K_1 t + K_2$

APPLY INITIAL COND: $v_o(0) = 8 \Rightarrow K_2 = 8V$

TO GET K_1 , INSPECT 2ND STAGE AT $t=0$

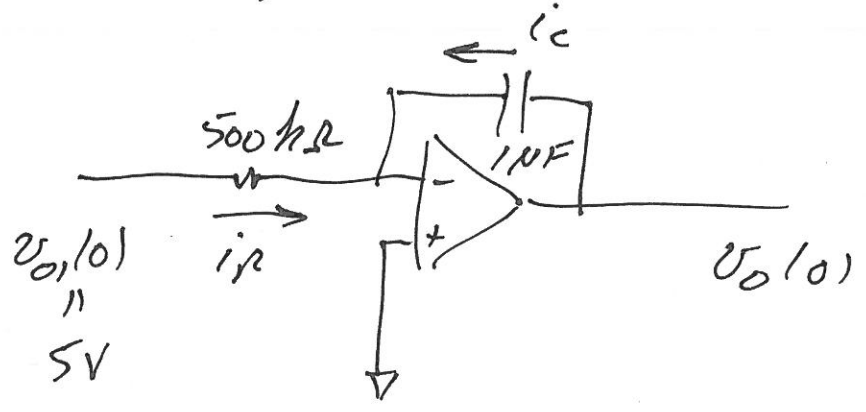

KCL AT NEG TERMINAL

$$\frac{v_o(0)}{R} + C \frac{dv_o(t)}{dt} \Big|_{t=0} = 0$$

$$\Rightarrow \frac{dv_o(t)}{dt} \Big|_{t=0} = -\frac{v_o(0)}{RC} = -10V/S$$

BUT $\frac{dv_o(t)}{dt} = 2t + K_1 \Rightarrow K_1 = -10V/S$

$$\therefore v_o(t) = t^2 - 10t + 8V$$

(3)

2ND STAGE SATURATES WHEN $v_o(t) = \pm 9V \equiv 1$

THIS IS WHEN $t^2 - 10t + 8 = 1$

$$t^2 - 10t + 8 - 1 = 0$$

$$t = \frac{+10 \pm \sqrt{10^2 - 4(8-1)}}{2}$$

$$t = 5 \pm \sqrt{25 - 8 + 1}$$

EARLIEST SOL'N IS $5 - \sqrt{25 - 8 + 1} = 2.17 \text{ SEC}$

$$\text{CHECK } v_o(2.17) = -9V$$

CHECK 1ST STAGE AT THIS TIME

$$\text{FROM EQ (2)(1), } v_{o1}(t) = -4025 t + K_3$$

$$\text{INITIAL CONDITION: } v_{o1}(0) = 5V = K_3$$

$$v_{o1}(t) = -t + 5$$

$$v_{o1}(2.17) = 2.83V - \text{OK}$$

9.3

①

$$v(t) = 25 \cos(400\pi t + 60^\circ) \text{ V}$$

a) MAX AMPLITUDE IS WHEN $\cos(\dots) = 1$

$$\boxed{v(t)_{\text{max}} = 25 \text{ V}}$$

b) FREQ IN Hz? $400\pi = \omega = 2\pi f$

$$400\pi = 2\pi f \rightarrow f = \frac{400\pi}{2\pi}$$

$$\boxed{f = 200 \text{ Hz}}$$

c) FREQ IN RAD/S?

$$\text{FROM PART b, } \boxed{\omega = 400\pi \text{ RAD/S}}$$

d) PHASE ANGLE IN RAD?

$$\phi = 60^\circ \times \frac{\pi \text{ RAD}}{180^\circ}$$

$$\boxed{\phi = \pi/3 \text{ RAD}}$$

e) PHASE ANGLE IN DEG?

$$\text{FROM PART d, } \boxed{\phi = 60^\circ}$$

9.3, CONT'D.

(2)

f) PERIOD IN ms ?

$$T = \frac{1}{f} = \frac{1}{200\text{Hz}} = 0.005\text{S}$$

$$\boxed{T = 5\text{ms}}$$

g) FIRST TIME AFTER $t=0$ THAT $v(t)=0$?

$v(t)=0$ WHEN ARG OF COSINE = $\pi/2$

$$400\pi t + 60^\circ \left(\frac{\pi}{180^\circ} \right) = \frac{\pi}{2}$$

$$400\pi t = \frac{\pi}{2} - \frac{\pi}{3} = \frac{(3-2)\pi}{6}$$

$$t = \frac{\pi}{6} \frac{1}{400\pi} = \frac{1}{2,400}\text{S}$$

$$\boxed{t = 4.17 \times 10^{-4}\text{S} = 0.417\text{ms}}$$

h) SHIFT $v(t)$ $\frac{5}{6}$ ms TO RIGHT. WHAT IS EXPRESSION FOR $v(t)$?

$$\text{SHIFT} = \frac{5}{6}\text{ms} \quad \text{---} \quad \frac{5\mu\text{ms}}{5\mu\text{s}}$$

$$\text{FRACTION OF PERIOD} = \frac{5/6\text{ms}}{5\text{ms}} = \frac{1}{6}$$

$$\text{EXPRESSED IN DEGREES: } \frac{1}{6} 360 = 60^\circ$$

9.3, CONT'D.

SHIFT IS 60° , BUT DO WE ADD TO OR SUBTRACT FROM EXISTING 60° PHASE?

FOR ANSWER CONSIDER PART (g). IF WE SUBTRACT 60° FROM EXISTING 60° , THE $v(t)$ REACHES 0V AT

$$400\pi t = \frac{\pi}{2} \rightarrow t = \frac{\pi}{2} \frac{1}{400\pi} = \frac{1}{800} \text{ s}$$

$$\text{OR } t = 1.25 \text{ ms}$$

THIS IS $5/6$ ms LATER THAN TIME IN PART (g)

$$\circ \circ \quad \boxed{v(t) = 25 \cos(400\pi t) \text{ V}}$$

i) WHAT IS MIN TIME MS FOR SHIFT TO LEFT YIELDING

$$v(t) = 25 \cos(400\pi t) ?$$

$$\text{WANT } 25 \cos(400\pi t + 60^\circ + \phi)$$

$$= 25 \cos(400\pi t)$$

9.3, CONT'D.

SHIFT TO LEFT BY ADDING PHASE

MAKE COS LOOK LIKE SIN - SHIFT LEFT
BY $\frac{3\pi}{2} = 270^\circ$

$$60^\circ + \phi = 270^\circ$$

$$\phi = 210^\circ$$


$$\text{FRACTION OF PERIOD} = \frac{210^\circ}{360^\circ}$$

$$\text{PERIOD} = 5 \text{ ms (PART F)}$$

$$\text{LEFT-SHIFT IN ms} = \frac{210}{360} 5 \text{ ms}$$

$$\boxed{\text{SHIFT} = 2.92 \text{ ms}}$$

9.7

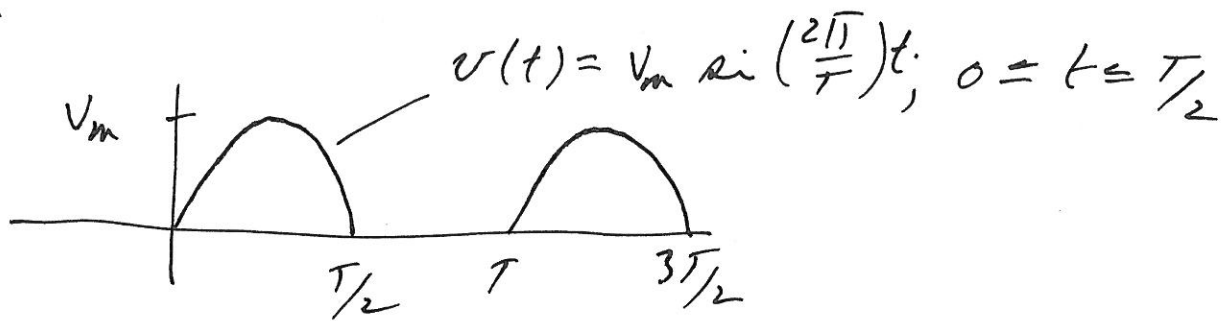~~9.8~~

$$\text{RMS VOLTAGE} = \left[\frac{1}{T} \int_0^{T/2} \left(V_m \sin\left(\frac{2\pi}{T}t\right) \right)^2 dt \right]^{1/2}$$

C.O.V. : LET $x = \frac{2\pi}{T}t; dx = \frac{2\pi}{T} dt$

$$= \left[\frac{1}{T} \int_0^{\pi} \left(V_m \sin x \right)^2 \frac{T}{2\pi} dx \right]^{1/2}$$

$$= \left[\frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 x dx \right]^{1/2}$$

$$= \left[\frac{V_m^2}{2\pi} \int_0^{\pi} \frac{1}{2} (1 - \cos 2x) dx \right]^{1/2}$$

$$= \left[\frac{V_m^2}{4\pi} x \Big|_0^{\pi} \right]^{1/2}$$


$$\text{RMS VOLTAGE} = V_m/2$$

9.11

①

- a) $y = 30 \cos(200t - 160^\circ) + 15 \cos(200t + 70^\circ)$
- b) $y = 90 \sin(150t - 20^\circ) + 60 \cos(200t - 70^\circ)$
- c) $y = 50 \cos(5000t - 60^\circ) + 25 \sin(5000t + 110^\circ) - 75 \cos(15000t - 30^\circ)$
- d) $y = 10 \cos(\omega t + 30^\circ) + 10 \sin(\omega t) + 10 \cos(\omega t + 150^\circ)$

//

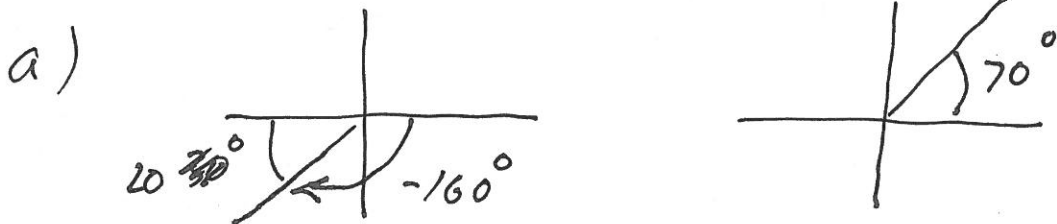

$$\begin{aligned}
 & 30 \angle -160^\circ + 15 \angle 70^\circ \\
 &= -30 \angle 20^\circ + 15 \angle 70^\circ \\
 &= (-30 \cos 20^\circ + 15 \cos 70^\circ) + j(-30 \sin 20^\circ + 15 \sin 70^\circ) \\
 &= -23.06 + j 3.83 \\
 &= 23.38 \angle -9.44^\circ = 23.38 \angle 170.56
 \end{aligned}$$

$$y = 23.38 \cos(200t + 170.56)$$

b) $90 \sin(150t - 20^\circ) + 60 \cos(200t - 70^\circ)$

DIFFERENT FREQUENCIES

CANNOT COMBINE

9.11 a) ELABORATION

$$30 \angle -160 + 15 \angle 70$$

$$= 30 \cos(-160) + j 30 \sin(-160)$$

$$+ 15 \cos(70) + j 15 \sin(70)$$


$$= [30 \cos(160) + 15 \cos(70)]$$

$$+ j [-30 \sin(160) + 15 \sin(70)]$$

$$= -23.38 + j 3.83$$

$$= 23.38 \angle -9.44^\circ$$

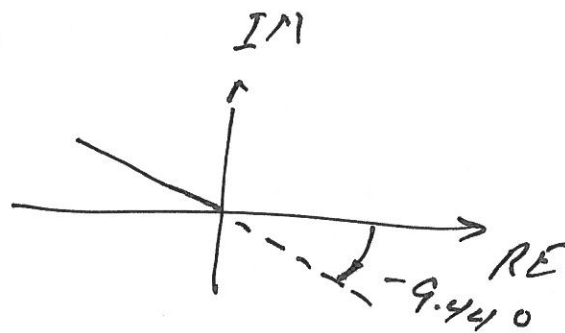THIS AS CALCULATED BY $\tan^{-1}(3.83/23.38)$



RESULT ACTUALLY
IN 2ND QUADRANT

⇒ MUST ADD 180°
TO ANSWER

$$y = 23.38 \cos(200t + 170.56^\circ)$$

9.11, CONT'D.

(2)

ASSUME TYPO IN TEXT - SHOULD BE

$$\begin{aligned}y &= 90 \operatorname{Re}(50t - 20^\circ) + 60 \operatorname{Re}(50t - 70^\circ) \\&= 90 \operatorname{Re}(50t - 20^\circ - 90^\circ) + 60 \operatorname{Re}(50t - 70^\circ) \\&= 90 \angle -110 + 60 \angle -70 \\&= -90 \angle 70^\circ + 60 \angle -70 \\&= -90 \cos 70^\circ - 90 \operatorname{Im} 70^\circ \\&\quad + 60 \cos(-70) + j \operatorname{Im}(-70) \\&= (-90 \cos 70 + 60 \cos 70) + j(-90 \operatorname{Im} 70 - 60 \operatorname{Im} 70) \\&= -10.26 - j 140.95 \\&= 141.33 \angle 85.84 = 141.33 \angle -94.16\end{aligned}$$

$$\boxed{y(t) = 141.33 \cos(50t - 94.16)}$$

$$\begin{aligned}c) \quad y &= 50 \cos(\omega t - 60^\circ) + 25 \operatorname{Re}(\omega t + 110^\circ) \\&\quad - 75 \cos(\omega t - 30^\circ) \\&= 50 \cos(\omega t - 60^\circ) + 25 \cos(\omega t + 110^\circ - 90^\circ) \\&\quad - 75 \cos(\omega t - 30^\circ)\end{aligned}$$

(3)

9.11, CONT'D.

$$\begin{aligned}
 y &= 50 \angle -60^\circ + 25 \angle 20^\circ - 75 \angle -30^\circ \\
 &= 50 \cos(-60) + 25 \cos(20) - 75 \cos(-30) \\
 &\quad + j(50 \sin(-60) + 25 \sin(20) - 75 \sin(-30)) \\
 &= -16.46 + j 2.75 \\
 &= \cancel{16.69} \quad 16.69 \angle -9.48^\circ
 \end{aligned}$$

$$\boxed{
 \begin{aligned}
 y &= 16.69 \cos(5000t - 9.48^\circ) \\
 16.69 &= 16.69 \cos(5000t + 170.52^\circ)
 \end{aligned}
 }$$

$$\begin{aligned}
 d) \quad y &= 10 \cos(\omega t + 30^\circ) + 10 \sin(\omega t) \\
 &\quad + 10 \cos(\omega t + 150^\circ) \\
 &= 10 \cos(\omega t + 30^\circ) + 10 \cos(\omega t - 90^\circ) \\
 &\quad + 10 \cos(\omega t + 150^\circ) \\
 &= 10 \angle 30^\circ + 10 \angle -90^\circ + 10 \angle 150^\circ \\
 &= (10 \cos(30) + 10 \cos(-90) + 10 \cos(150)) \\
 &\quad + j(10 \sin(30) + 10 \sin(-90) + 10 \sin(150))
 \end{aligned}$$

9.11, CONT'D.

(2)


$$y = 0 + j0$$

$$\boxed{y = 0}$$

9.14

~~9.12~~

v_g

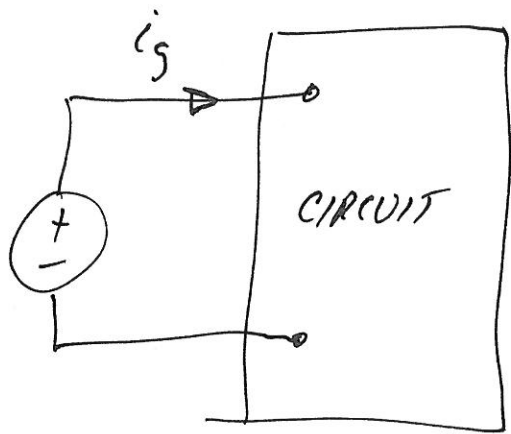

$$v_g = 300 \cos(5,000\pi t + 78^\circ) \text{ V}$$

$$i_g = 6 \sin(5,000\pi t + 123^\circ) \text{ A}$$

$$i_g = 6 \cos(5,000\pi t + 123^\circ - 90^\circ) \text{ A}$$

$$= 6 \cos(5,000\pi t + 33^\circ) \text{ A}$$

$$\mathcal{P}\{v_g\} = \bar{V}_g = 300 e^{j78^\circ}$$

$$\mathcal{P}\{i_g\} = \bar{I}_g = 6 e^{j33^\circ}$$

$$\bar{V}_g = z \bar{I}_g \rightarrow z = \frac{\bar{V}_g}{\bar{I}_g}$$

$$z = \frac{300 e^{j78^\circ}}{6 e^{j33^\circ}} = 50 e^{j45^\circ}$$

9.14

(2)

~~9.12~~, CONT'D.

$$a) z = 50e^{j45^\circ}$$

$$b) v_g = V_m \cos(\omega t + \phi)$$

$$\omega = 5,000\pi = 2\pi f = \frac{2\pi}{T}$$

$$\Rightarrow T = \frac{2\pi}{5,000\pi} = 4 \times 10^{-4} \text{ s}$$

$$= 400 \mu\text{s}$$

PHASE DELAY BETWEEN VOLTAGE
& CURRENT IS 45° . THIS IS

$$\frac{45^\circ}{360^\circ} = \frac{1}{8} \text{ OF A PERIOD OR}$$

$$\frac{1}{8} 400 \mu\text{s} = 50 \mu\text{s}$$