


Problem 9.16 PSpice|Multisim

A $25\ \Omega$ resistor and a $10\ \text{mH}$ inductor are connected in parallel. This parallel combination is also in parallel with the series combination of a $30\ \Omega$ resistor and a $10\ \mu\text{F}$ capacitor. These three parallel branches are driven by a sinusoidal current source whose current is $225 \sin(2500t + 60^\circ)\ \text{A}$.

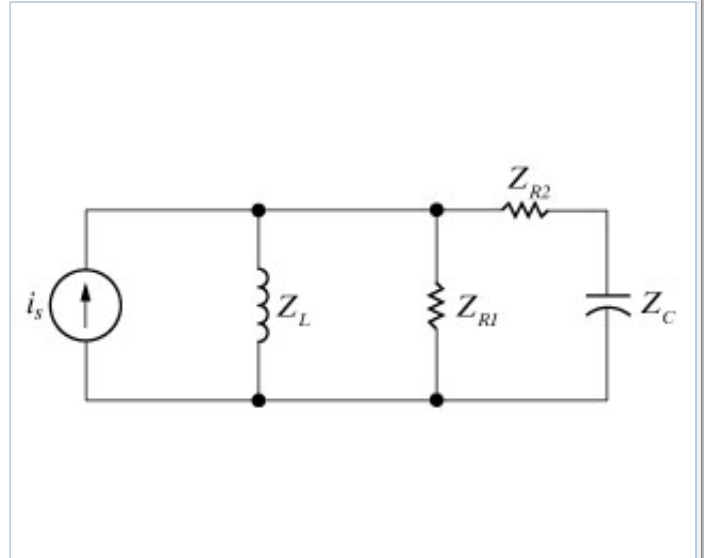Part A

Determine the impedances in .

Express your answers in complex form using three significant figures separated by commas.



ANSWER:

$Z_L, Z_{R1}, Z_{R2}, Z_C =$ $\Omega, \Omega, \Omega, \Omega$

Part B

Reference the voltage across the current source as a rise in the direction of the source current, and find the phasor voltage.

Enter your answer using polar notation. Express argument in degrees.

ANSWER:

$V_o =$ V

Part C

Choose the correct steady-state expression for $v(t)$.


ANSWER:

- $-5.22 \sin(2500t + 3930^\circ) \text{V}$
- $-5.22 \cos(2500t + 3930^\circ) \text{V}$
- $3930 \cos(2500t - 5.22^\circ) \text{V}$
- $3930 \sin(2500t - 5.22^\circ) \text{V}$



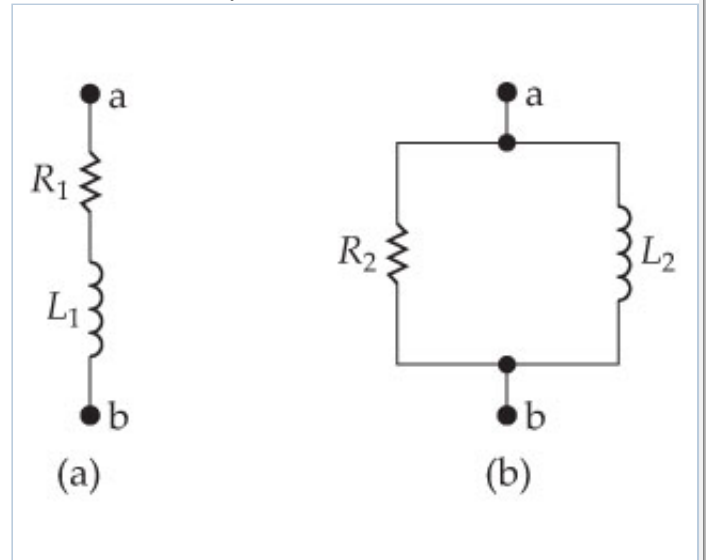Problem 9.18

At a given frequency ω , the circuits in the figures (a) and (b) have the same impedance between the terminals a,b.



Part A

Find R_1 .

Express your answer in terms of the variables ω , L_2 and R_2 .

ANSWER:

$$R_1 =$$

Part B

Find L_1 .

Express your answer in terms of the variables ω , L_2 and R_2 .

ANSWER:

$$L_1 =$$

Part C

Find the value of resistance that when connected in series will have the same impedance at 4.8 krad/s as that of a $6 \text{ k}\Omega$ resistor connected in parallel with a 1.4 H inductor.

Express your answer to four significant figures and include the appropriate units.

ANSWER:

$R_1 =$

Part D

Find the value of inductance that when connected in series will have the same impedance at 4.8 krad/s as that of a $6 \text{ k}\Omega$ resistor connected in parallel with a 1.4 H inductor.

Express your answer with the appropriate units.

ANSWER:


$L_1 =$

Problem 9.24 PSpice|Multisim

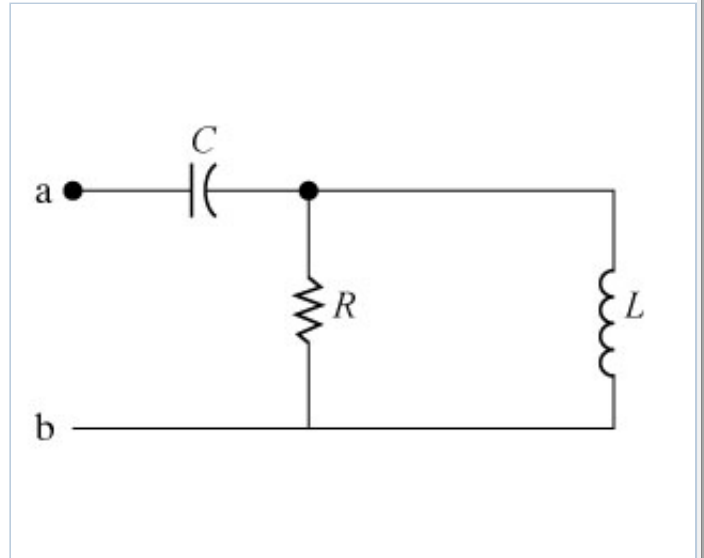Part A

For the circuit shown in , find the frequency at which the impedance Z_{ab} is purely resistive. Suppose $R = 400 \ \Omega$, $L = 400 \ \text{mH}$, and $C = 50 \ \mu\text{F}$.

Express your answer using three significant figures.



ANSWER:

$$\omega = \text{[input box]} \text{ rad/s}$$

Part B

Find the value of Z_{ab} at the frequency of Part A.


Express your answer to two significant figures and include the appropriate units.

ANSWER:

$$Z_{ab} = \text{[input box]}$$

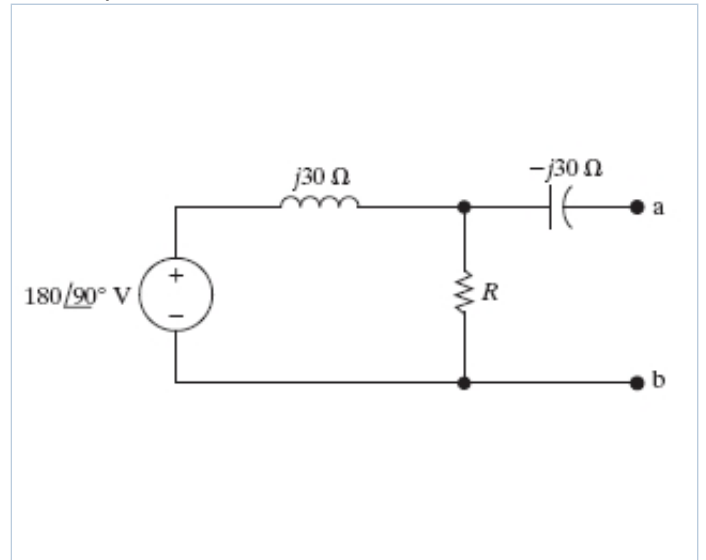Problem 9.44

Use source transformations to find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in . Suppose that $R = 13 \ \Omega$.



Part A

Find the value of Z_N .

Express your answer in complex form using three significant figures.

ANSWER:

$$Z_N = \text{[input box]} \ \Omega$$

Part B

Find the value of I_N .


Express your answer in complex form using three significant figures.

ANSWER:

$$I_N = \text{[input box]} \ \text{A}$$

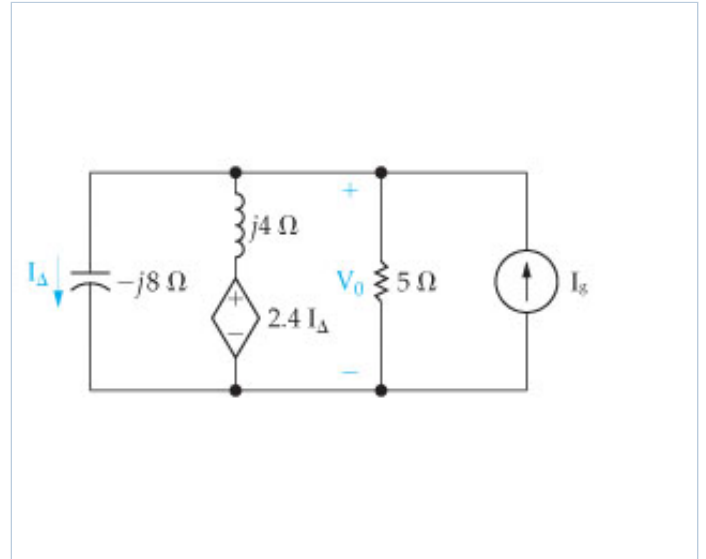Problem 9.58

Use the node-voltage method to find the phasor voltage \mathbf{V}_o in the circuit shown in the figure when $I_g = 12 + 12j\text{A}$.



Part A

Express the voltage in polar form.

Enter your answer using polar notation. Express argument in degrees.

ANSWER:

$$\mathbf{V}_o = \text{[input box]} \text{ V}$$

Part B

Express the voltage in rectangular form.


Express your answer in complex form.

ANSWER:

$$\mathbf{V}_o = \text{[input box]} \text{ V}$$

9.16

(1)

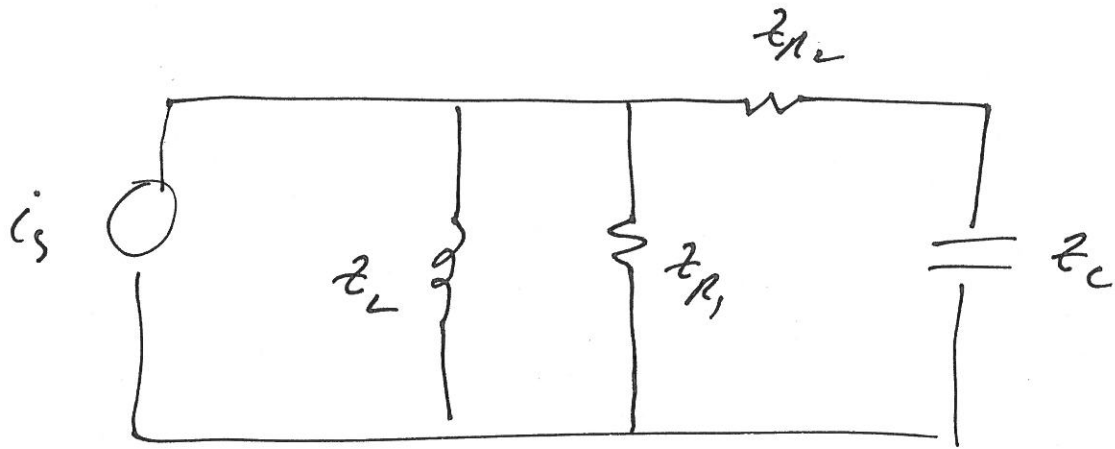

$$L = 10 \text{ mH}; R_1 = 25 \Omega; R_2 = 30 \Omega; C = 10 \mu\text{F}$$

$$i_s = 225 \sin(2500t + 60^\circ) \text{ A}$$

$\omega \nearrow$

$$a) Z_L = j\omega L = j25.0 \Omega$$

$$Z_{R_1} = 25 \Omega$$

$$Z_{R_2} = 30 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{40}{j} = -j40 \Omega$$

$$b) i_s = 225 \sin(2500t + 60^\circ) \\ = 225 \cos(2500t + 60^\circ - 90^\circ)$$

$$I_s = 225 \angle -30^\circ$$

$$Z_{eq} = [25 \parallel (30 - j40)] \parallel j25$$

(2)

$$25 \parallel (30 - j40) = \frac{25(30 - j40)}{25 + 30 - j40} = \frac{25(30 - j40)}{55 - j40}$$

$$Z_{eq} = \frac{\left[\frac{25(30 - j40)}{55 - j40} \right] \times j25}{\left[\frac{25(30 - j40)}{55 - j40} \right] + j25}$$

$$= \frac{25(30 - j40)(j25)}{25(30 - j40) + j25(55 - j40)}$$

$$= \frac{j25(30 - j40)}{30 + 40 + j55 - j40} = \frac{j25(30 - j40)}{70 + j15}$$

$$= \frac{j5(30 - j40)}{14 + j3} \cdot \frac{(14 - j3)}{(14 - j3)}$$

$$= j5 \frac{(30 - j40)(14 - j3)}{196 + 9} = j5 \frac{(30 - j40)(14 - j3)}{205}$$

$$= j \frac{(30 \times 14 - j3 \times 30 - j14 \times 40 - 40 \times 3)}{41}$$

$$= \frac{650 + j300}{41} = 17.461 \angle 24.775^\circ$$

3


$$V_s = I_s Z_{eq}$$

$$= 225 \angle -30^\circ (17.461 \angle 24.775^\circ)$$

$$b) \quad V_s = 3,928.67 \angle -5.2257^\circ$$

$$c) \quad v(t) = 3,930 \cos(2500t - 5.22^\circ) \text{ V}$$

9.18

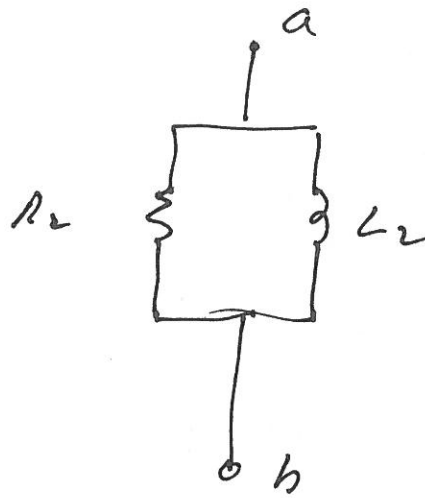

$$z_L = R_1 + j\omega L_1$$

$$z_R = \frac{R_2(j\omega L_2)}{R_2 + j\omega L_2}$$

SET $z_L = z_R$ & SOLVE FOR R_1 ,

STRATEGY: FIND $\text{RE}\{z_R\} = R_1$,

$$z_R = \frac{j\omega L_2 R_2}{R_2 + j\omega L_2} \left(\frac{R_2 - j\omega L_2}{R_2 - j\omega L_2} \right)$$

$$= \frac{\omega^2 R_2 L_2^2}{R_2^2 + (\omega L_2)^2} + \frac{j\omega R_2^2 L_2}{R_2^2 + (\omega L_2)^2}$$

$$a) \quad R_1 = \frac{\omega^2 R_2 L_2^2}{R_2^2 + (\omega L_2)^2}$$

9.18, CONT'D.

(2)

b) SET $\text{IM}\{z_L\} = \text{IM}\{z_A\}$:

$$j\omega L_1 = \frac{j\omega R_2^2 L_2}{R_2^2 + (\omega L_2)^2}$$

$$L_1 = \frac{R_2^2 L_2}{R_2^2 + (\omega L_2)^2}$$

NOW FOR $\omega = 3,800 \text{ RAD/S}$


$$R_2 = 5.5 \text{ k}\Omega$$

$$L_2 = 1.35 \text{ H}$$

c) FROM PART a), $R_1 = 2,559 \Omega$

d) FROM PART b), $L_1 = 0.7219 \text{ H}$

9.24

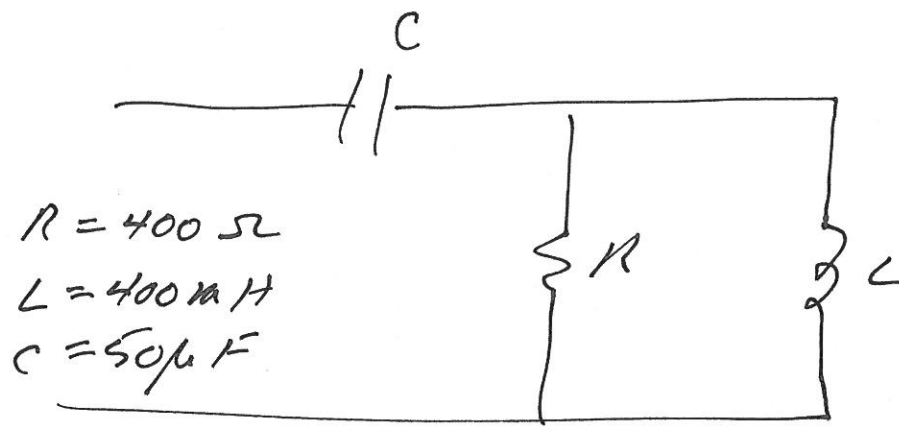

$$\begin{aligned}
 z_{eq} &= \frac{1}{j\omega C} + \frac{R \cdot j\omega L}{R + j\omega L} \\
 &= -\frac{j}{\omega C} + \frac{j\omega R L (R - j\omega L)}{R + j\omega L (R - j\omega L)} \\
 &= -\frac{j}{\omega C} + \frac{j\omega R^2 L}{R^2 + (\omega L)^2} + \frac{\omega^2 R L^2}{R^2 + (\omega L)^2}
 \end{aligned}$$

b) ? ω FOR WHICH z_{eq} PURELY REAL?

$$\Rightarrow \text{Im}\{z_{eq}\} = 0$$

$$-\frac{j}{\omega C} + \frac{j\omega R^2 L}{R^2 + (\omega L)^2} = 0$$

$$\frac{\omega R^2 L}{R^2 + (\omega L)^2} = \frac{1}{\omega C}$$

$$\omega^2 R^2 L C = R^2 + (\omega L)^2$$

$$\omega^2(R^2LC - L^2) = R^2$$

$$\omega = \frac{R}{\sqrt{R^2LC - L^2}}$$

USING SPECIFIED VALUES, $\omega = 229.4157 \text{ RAD/S}$


$$b) \text{ NOW } R_0 \{ z_{eq} \} = \frac{\omega^2 RL^2}{R^2 + (\omega L)^2}$$


AT THIS FREQUENCY (PART a),

$$R_0 \{ z_{eq} \} = z_{eq} = 20 \Omega$$

(PURELY RESISTIVE)


Problem 9.24

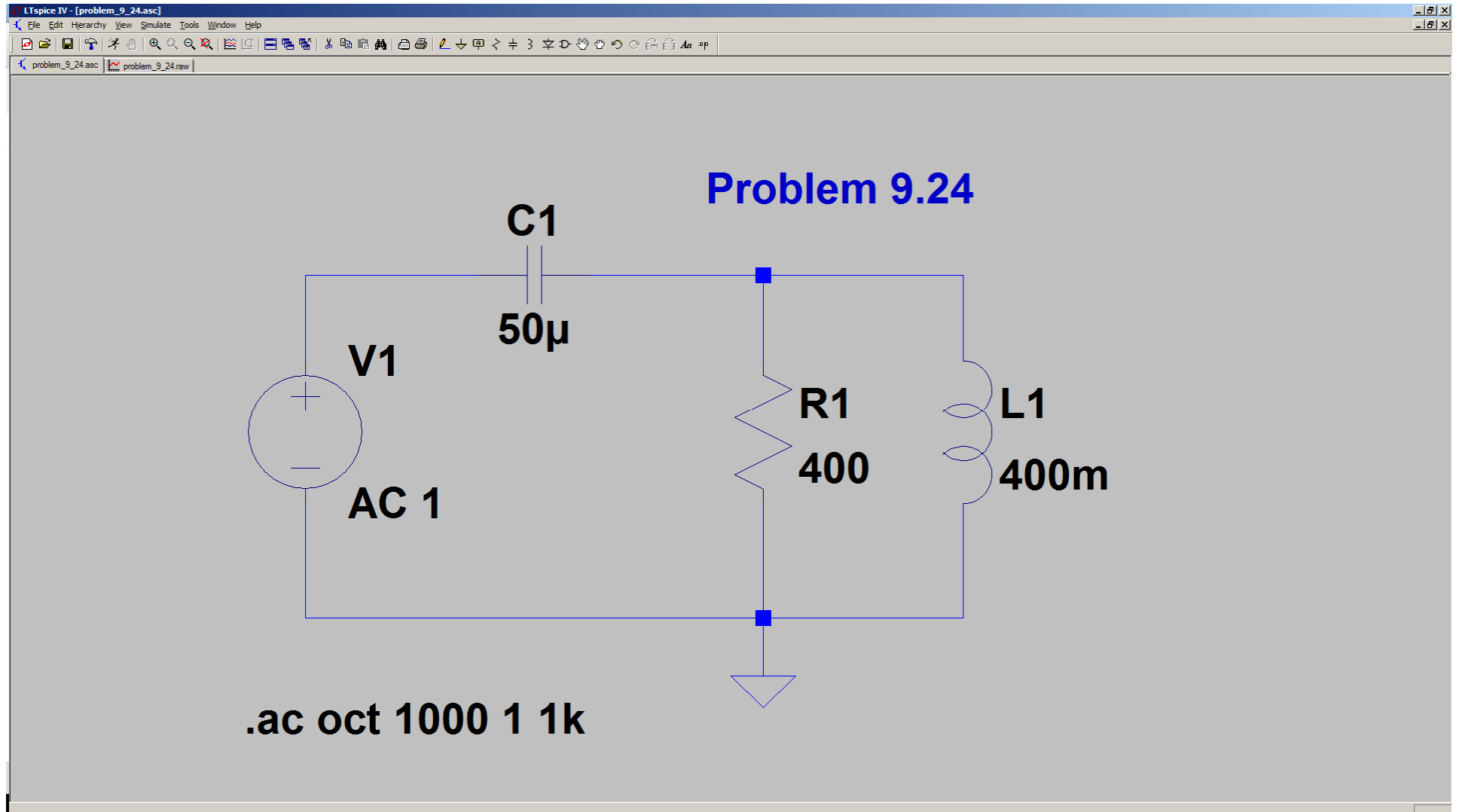

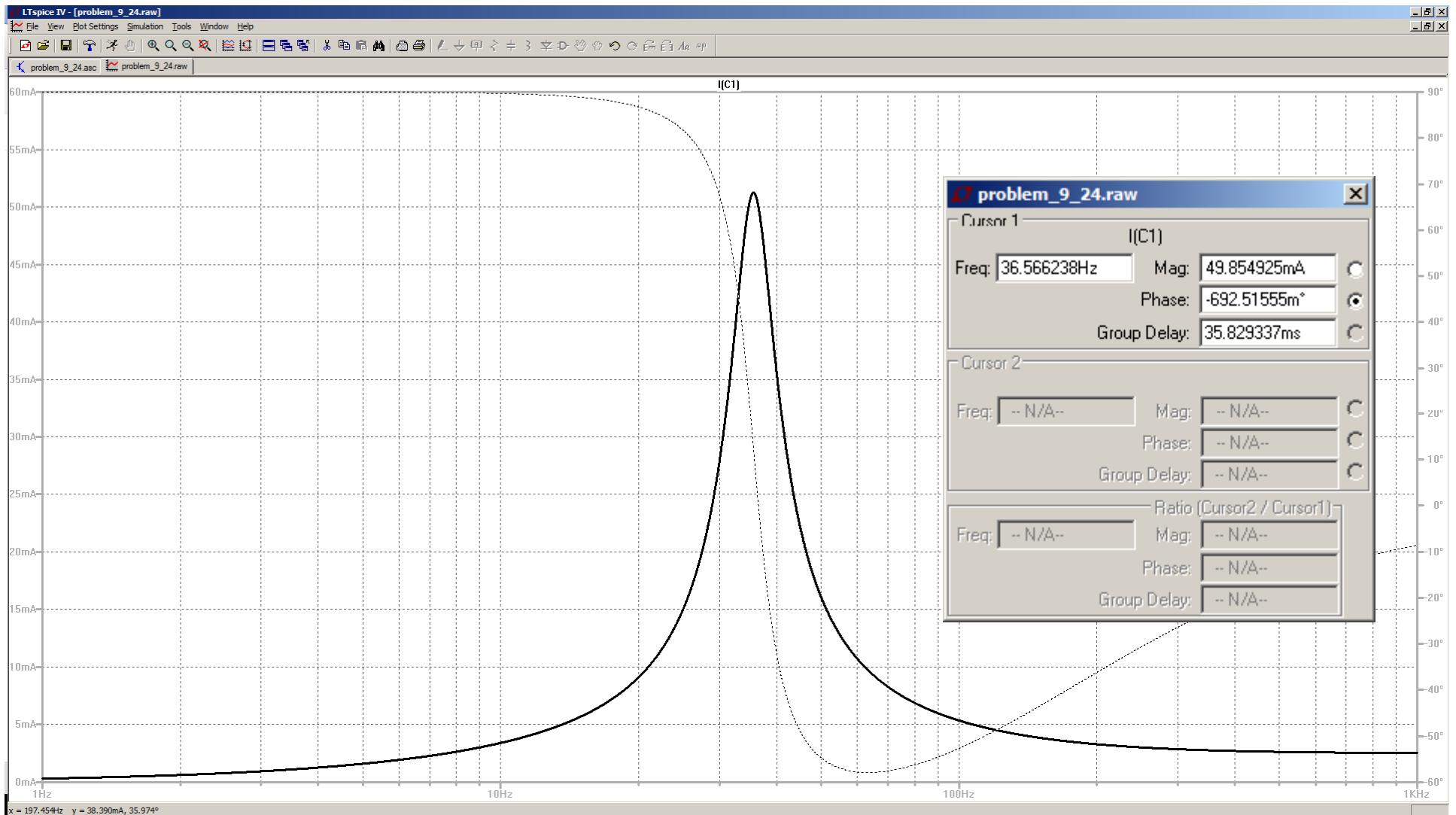


Zero phase at 36.566 HZ or 229 rad/s

9.44

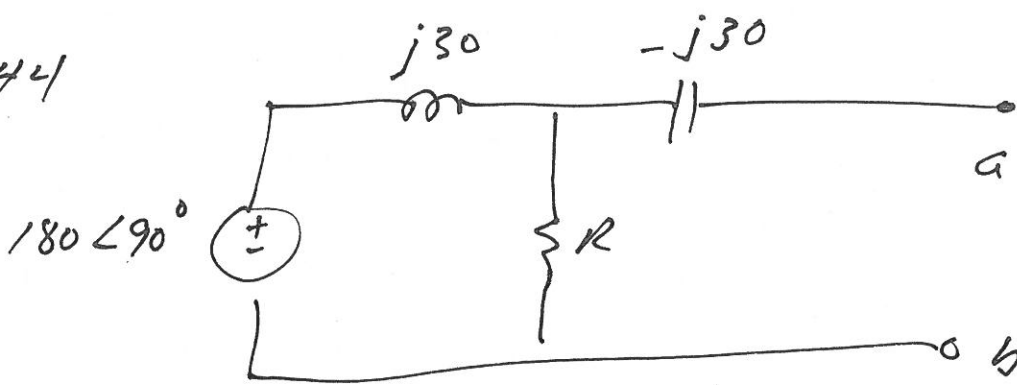

WANT: NORTON EQUIV

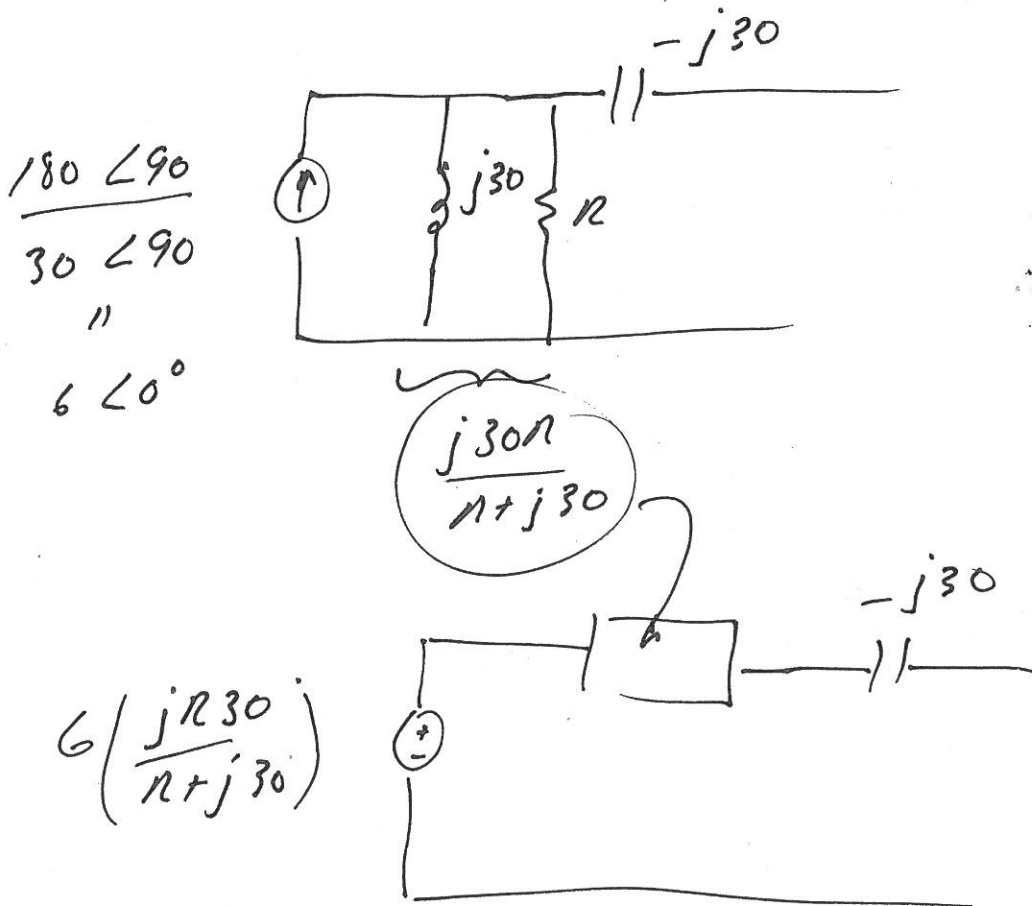


$$Z_{EQ} = \frac{jR30}{R+j30} - j30 = \frac{jR30 - j30(R+j30)}{R+j30}$$

$$Z_{EQ} = \frac{900}{R+j30}$$

9.44, CONT'D.

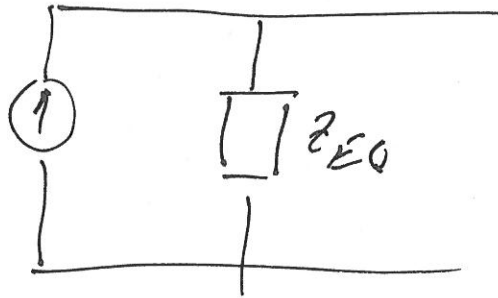(2)


$$6 \left(\frac{j1130}{11+j30} \right) \left(\frac{11+j30}{900} \right)$$



||

$$\frac{j11}{5}$$
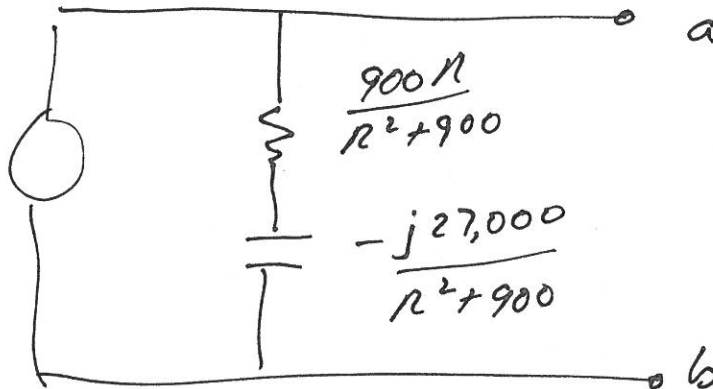
$$z_{EQ} = \frac{900}{11+j30} \left(\frac{11-j30}{11-j30} \right) = \frac{90011 - j27,000}{11^2 + 900}$$




$$\frac{j11}{5}$$

||

$$\frac{11}{5} \angle 90^\circ$$

9.58

(1)

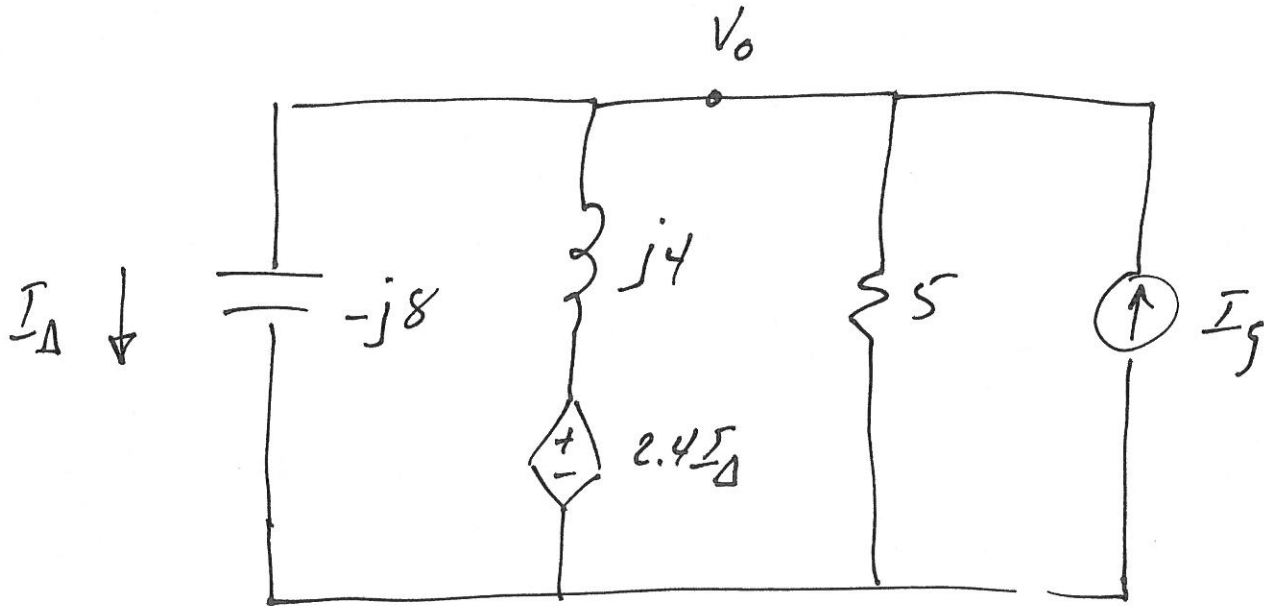

$$I_\gamma = 12 + j12$$

NODAL FOR V_0 :

$$\frac{V_0 - 2.4 I_\Delta}{j4} + \frac{V_0}{5}$$

$$- (12 + j12) + I_\Delta = 0$$

BUT $I_\Delta = V_0 / -j8$

$$\frac{V_0 - 2.4 \left(\frac{V_0}{-j8} \right)}{j4} + \frac{V_0}{5} - (12 + j12) - \frac{V_0}{j8} = 0$$

(2)

$$\frac{V_0 + \frac{0.3V_0}{j}}{j4} + \frac{V_0}{5} - 12 - j12 + j\frac{V_0}{8} = 0$$

$$V_0 - j0.3V_0 + \frac{V_0}{5}(j4) - (12 + j12)(j4) + j\frac{V_0}{8}(j4) = 0$$

$$V_0(1 - j0.3 - 0.5 + j0.8) = (12 + j12)j4$$

$$V_0(0.5 + j0.5) = 48(-1 + j)$$

$$V_0 = \frac{96(-1 + j)}{(1 + j)} \frac{(1 - j)}{(1 - j)}$$

$$= \frac{96(-1 + j + j + 1)}{2} = j96$$

$$V_0 = 96 \angle 90^\circ$$

OR

$$V_0 = j96$$