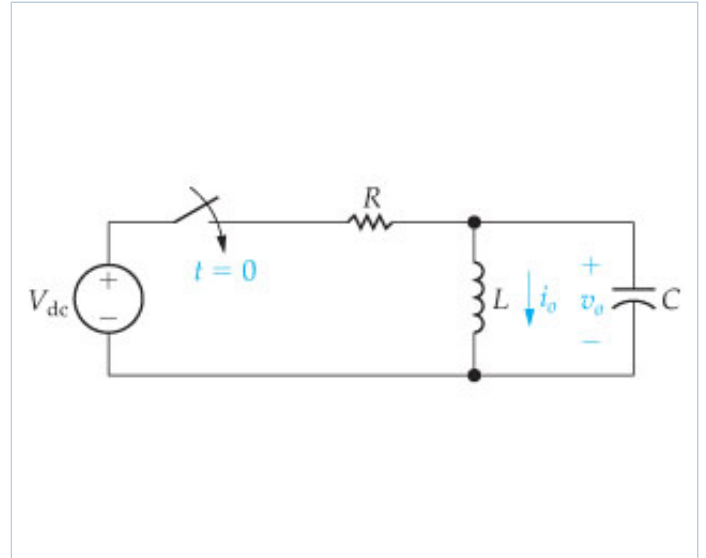


## Problem 12.30

The switch in the circuit in the figure has been open for a long time. At  $t = 0$ , the switch closes.



### Part A

Derive the integrodifferential equation that governs the behavior of the voltage  $v_o$  for  $t \geq 0$ .

ANSWER:

- $v_o + \frac{L}{R} \int_0^t v_o d\tau + RC \frac{dv_o}{dt} = V_{dc}$
- $v_o + \frac{R}{C} \int_0^t v_o d\tau + RL \frac{dv_o}{dt} = V_{dc}$
- $v_o - \frac{R}{L} \int_0^t v_o d\tau - RC \frac{dv_o}{dt} = V_{dc}$
- $v_o + \frac{R}{L} \int_0^t v_o d\tau + RC \frac{dv_o}{dt} + V_{dc} = 0$
- $v_o + \frac{R}{L} \int_0^t v_o d\tau + RC \frac{dv_o}{dt} = V_{dc}$
- $\frac{R}{L} \int_0^t v_o d\tau + RC \frac{dv_o}{dt} = V_{dc}$

### Part B

Find  $V_o(s)$ .

Express your answer in terms of  $V_{dc}$ ,  $s$ ,  $R$ ,  $L$ , and  $C$ .

ANSWER:

$V_o(s) =$

### Part C

Find  $I_o(s)$ .


Express your answer in terms of  $V_{dc}$ ,  $s$ ,  $R$ ,  $L$ , and  $C$ .

ANSWER:

$I_o(s) =$

## Problem 12.34 PSpice|Multisim

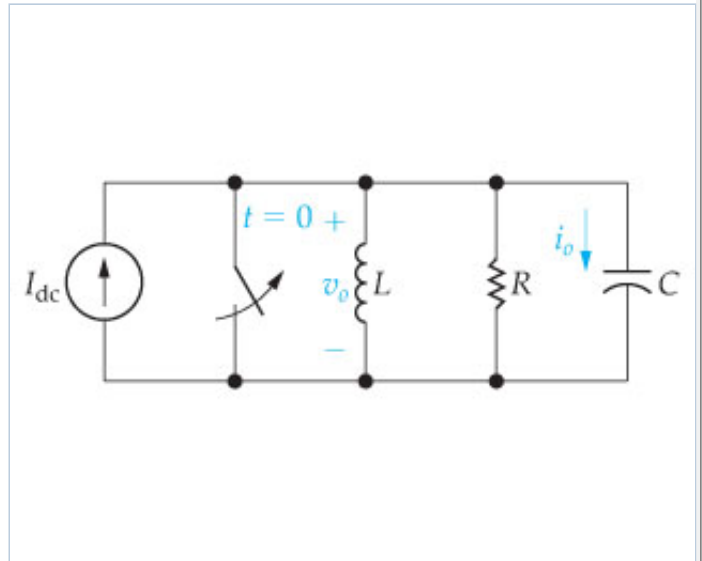The circuit parameters in the circuit shown in have the following values:  $R = 20 \Omega$ ,  $L = 50 \text{ mH}$ ,  $C = 20 \mu\text{F}$ , and  $I_{\text{dc}} = 87 \text{ mA}$ . There is no energy stored in the circuit at the time the switch is opened.



### Part A

Select the correct expression for  $v_o(t)$  for  $t \geq 0$ , where  $t$  is in seconds.

ANSWER:

- $v_o(t) = (11.6e^{500t} + 11.6e^{2000t})u(t) \text{ V}$
- $v_o(t) = (2.9e^{-500t} - 2.9e^{-2000t})u(t) \text{ V}$
- $v_o(t) = (11.6e^{500t} + 2.9e^{2000t})u(t) \text{ V}$
- $v_o(t) = (2.9e^{500t} - 2.9e^{2000t})u(t) \text{ V}$
- $v_o(t) = (2.9e^{-500t} - 11.6e^{-2000t})u(t) \text{ V}$
- $v_o(t) = (2.9e^{500t} - 11.6e^{2000t})u(t) \text{ V}$
- $v_o(t) = (2.9e^{-500t} + 2.9e^{-2000t})u(t) \text{ V}$
- $v_o(t) = (11.6e^{-500t} + 2.9e^{-2000t})u(t) \text{ V}$

### Part B

Select the correct expression for  $i_o(t)$  for  $t \geq 0$ , where  $t$  is in seconds.

ANSWER:

- $i_o(t) = (-29e^{-500t} - 116e^{-2000t})u(t)$  mA
- $i_o(t) = (29e^{500t} + 116e^{2000t})u(t)$  mA
- $i_o(t) = (116e^{-500t} - 29e^{-2000t})u(t)$  mA
- $i_o(t) = (-29e^{500t} - 116e^{2000t})u(t)$  mA
- $i_o(t) = (-29e^{-500t} + 116e^{-2000t})u(t)$  mA
- $i_o(t) = (-116e^{-500t} - 29e^{-2000t})u(t)$  mA
- $i_o(t) = (-116e^{500t} - 29e^{2000t})u(t)$  mA
- $i_o(t) = (116e^{500t} - 29e^{2000t})u(t)$  mA

### Part C


Does your solution for  $i_o(t)$  make sense when  $t = 0$ ?

ANSWER:

- No, it doesn't. The initial current through the capacitor  $i_o(0) = 87$  mA is equal to the source current, the initial inductor current is zero, therefore the current through the resistor is zero, which is unreasonable.
- Yes, it does. The initial current through the capacitor  $i_o(0) = 87$  mA is equal to the source current, the initial inductor current is zero, the initial resistor current is zero because the initial capacitor voltage is zero.
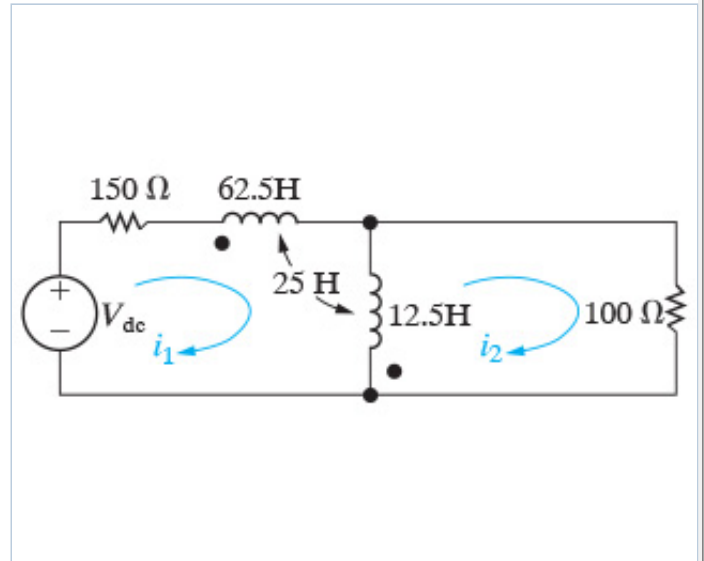
## Problem 12.39

Consider the circuit shown in . Suppose that  $V_{dc} = 625u(t)$  V. Assume that the initial energy stored in the circuit is zero.



### Part A

Select the correct expression for  $i_1(t)$  where  $t$  is in seconds and the parameters are rounded to three significant figures.

ANSWER:

- $i_1(t) = (2.50 + 1.67e^{-4t} + 4.17e^{-24t})u(t)$  A
- $i_1(t) = (2.50 + 4.17e^{-4t} - 1.67e^{-24t})u(t)$  A
- $i_1(t) = (4.17 + 2.50e^{-4t} - 1.67e^{-24t})u(t)$  A
- $i_1(t) = (2.50 - 1.67e^{-4t} - 4.17e^{-24t})u(t)$  A
- $i_1(t) = (4.17 + 2.50e^{-4t} + 1.67e^{-24t})u(t)$  A
- $i_1(t) = (2.50 - 4.17e^{-4t} + 1.67e^{-24t})u(t)$  A
- $i_1(t) = (4.17 - 1.67e^{-4t} + 2.50e^{-24t})u(t)$  A
- $i_1(t) = (4.17 - 2.50e^{-4t} - 1.67e^{-24t})u(t)$  A

### Part B

Select the correct expression for  $i_2(t)$  where  $t$  is in seconds and the parameters are rounded to three significant figures.

ANSWER:

- $i_2(t) = (1.25e^{-24t} + 1.25e^{-4t})u(t)$  A
- $i_2(t) = (1.25e^{-24t} - 1.25e^{-4t})u(t)$  A
- $i_2(t) = (2.50e^{-24t} + 1.25e^{-4t})u(t)$  A
- $i_2(t) = (1.25e^{-24t} + 2.50e^{-4t})u(t)$  A
- $i_2(t) = (2.50e^{-24t} - 2.50e^{-4t})u(t)$  A
- $i_2(t) = (2.50e^{-24t} + 2.50e^{-4t})u(t)$  A
- $i_2(t) = (2.50e^{-24t} - 1.25e^{-4t})u(t)$  A
- $i_2(t) = (1.25e^{-24t} - 2.50e^{-4t})u(t)$  A

### Part C

Find  $i_1(\infty)$ .

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$i_1(\infty) = \text{[input field]}$$

### Part D

Find  $i_2(\infty)$ .

Express your answer to three significant figures and include the appropriate units.

ANSWER:

$$i_2(\infty) = \text{[input field]}$$

### Part E

Do the solutions for  $i_1$  and  $i_2$  make sense?

ANSWER:


- No, they don't. At  $t = \infty$  the current through the resistor is zero, therefore the voltage at 12.5 H is zero, which is unreasonable, because the current through the inductor is not zero.
- Yes, they do. Since  $i_1$  is dc current, at  $t = \infty$  there is no voltage on the 12.5 H inductor, it corresponds to  $i_2 = 0$ .  $i_1(0) = 0$ ,  $i_2(0) = 0$  satisfy the condition of no initial energy stored in the circuit.

## Problem 12.46

In the circuit shown in the figure, the dc current source is replaced with a sinusoidal source that delivers a current of  $1.2 \cos t$  A. The circuit components are  $R = 1 \Omega$ ,  $C = 625 \text{ mF}$ , and  $L = 1.6 \text{ H}$ .
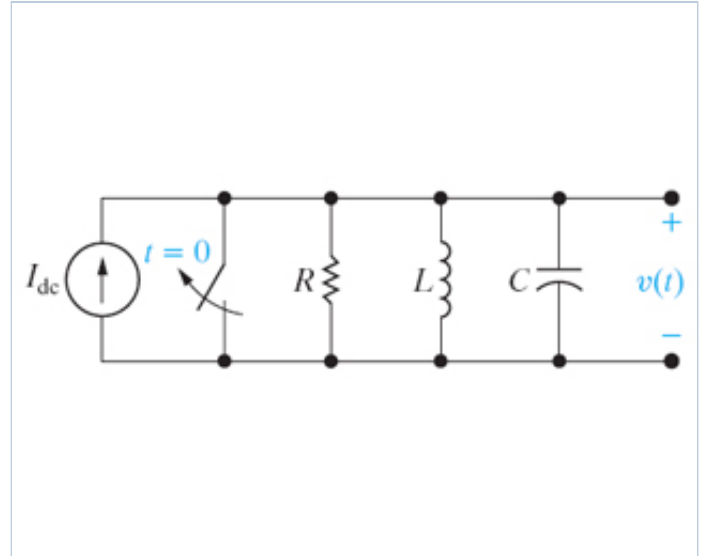
### Part A

Use the initial-value theorem to find the initial value of  $v$ .



ANSWER:

$v(0^+) =$   V

### Part B

Can the final-value theorem be used to find the steady-state value of  $v$ ?

ANSWER:

- yes  
 no

## Problem 12.52

### Part A

Can the initial- and final-value theorems be applied to  $F(s) = \frac{320}{s^2(s+8)}$ ?

ANSWER:

- only the final-value theorem can be applied
- only the initial-value theorem can be applied
- both theorems can be applied
- none of these theorems can be applied

### Part B

Apply the initial-value theorem to  $F(s) = \frac{320}{s^2(s+8)}$  to find the initial value of  $f(t)$ .

Express your answer using three significant figures.

ANSWER:

$f(0^+) =$

### Part C

Can the initial- and final-value theorems be applied to  $F(s) = \frac{95(s+3)}{s(s+7)^2}$ ?

ANSWER:

- only the initial-value theorem can be applied
- only the final-value theorem can be applied
- both theorems can be applied
- none of these theorems can be applied

### Part D

Apply the final-value theorem to  $F(s) = \frac{95(s+3)}{s(s+7)^2}$  to find the final value of  $f(t)$ .

Express your answer using three significant figures.

ANSWER:



$$f(\infty) = \text{[input box]}$$

### Part E

Apply the initial-value theorem to  $F(s) = \frac{95(s+3)}{s(s+7)^2}$  to find the initial value of  $f(t)$ .

Express your answer using three significant figures.

ANSWER:

$$f(0^+) = \text{[input box]}$$

### Part F

Can the initial- and final-value theorems be applied to  $F(s) = \frac{60(s+5)}{(s+1)^2(s^2+6s+25)}$ ?

ANSWER:

- only the initial-value theorem can be applied
- only the final-value theorem can be applied
- both theorems can be applied
- none of these theorems can be applied

### Part G

Apply the final-value theorem to  $F(s) = \frac{60(s+5)}{(s+1)^2(s^2+6s+25)}$  to find the final value of  $f(t)$ .

Express your answer using three significant figures.

ANSWER:

$$f(\infty) = \text{[input box]}$$

### Part H

Apply the initial-value theorem to  $F(s) = \frac{60(s+5)}{(s+1)^2(s^2+6s+25)}$  to find the initial value of  $f(t)$ .

Express your answer using three significant figures.

ANSWER:

$$f(0^+) = \text{[input box]}$$

### Part I

Can the initial- and final-value theorems be applied to  $F(s) = \frac{25(s+4)^2}{s^2(s+5)^2}$ ?

ANSWER:

- only the initial-value theorem can be applied
- only the final-value theorem can be applied
- both theorems can be applied
- none of these theorems can be applied

### Part J

Apply the initial-value theorem to  $F(s) = \frac{25(s+4)^2}{s^2(s+5)^2}$  to find the initial value of  $f(t)$ .

**Express your answer using three significant figures.**

ANSWER:


$$f(0^+) = \text{[input box]}$$

## Problem 12.54
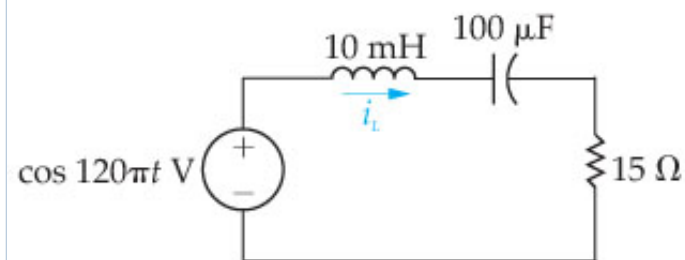
### Part A

Use phasor circuit analysis techniques from Chapter 9 in the textbook to determine the steady-state expression for the inductor current in the figure.

Express your answer in terms of  $t$ , where  $t$  is in seconds. Enter the phase angle in radians.




ANSWER:

$$i_{L-ss}(t) = \text{[input box]} \text{ mA}$$

12.30

(1)

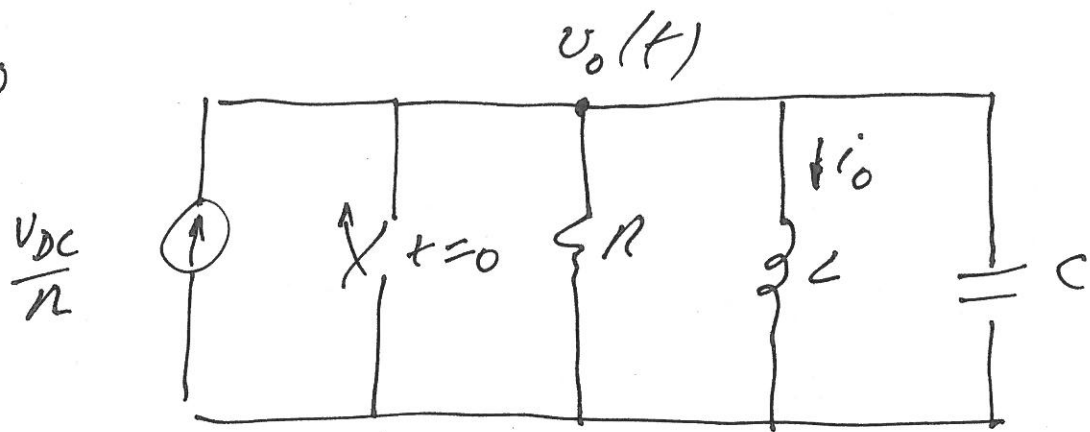

$$\text{KCL: } \frac{v_o(t)}{R} + \frac{1}{L} \int_0^t v_o(x) dx + C \frac{d}{dt} v_o(t) - \frac{V_{DC}}{R} = 0$$

$$a) \quad v_o(t) + \frac{R}{L} \int_0^t v_o(x) dx + RC \frac{d}{dt} v_o(t) = V_{DC}$$

S-DOMAIN: (NO PRIOR ENERGY)

$$\frac{V_o(s)}{R} + \frac{V_o(s)}{Ls} + Cs V_o(s) - \frac{V_{DC}/R}{s} = 0$$

NOTE UNIT STEP

$$V_o(s) \left( \frac{1}{R} + \frac{1}{Ls} + Cs \right) = \frac{V_{DC}/R}{s}$$

$$V_o(s) = \frac{V_{DC}}{s(RCs + R/Ls + 1)}$$

$$V_o(s) = \frac{s V_{DC}/RC}{s(s^2 + s/RC + 1/LC)}$$

$$b) \quad V_o(s) = \frac{V_{DC}/RC}{s^2 + s/RC + 1/LC}$$


(2)

$$I_0(s) = \frac{V_0(s)}{Ls}$$

c) 
$$I_0(s) = \frac{V_{DC}/RLC}{s(s^2 + s/\tau_c + 1/\tau_c^2)}$$

12.34

①

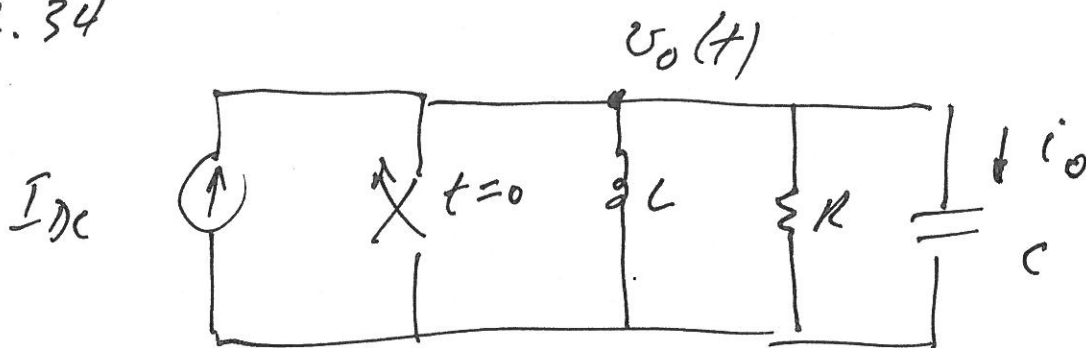

$$I_{DC} = 87 \text{ mA}; R = 20 \Omega; L = 50 \text{ mH}$$

$$C = 20 \mu\text{F}$$

SAME PROBLEM AS 12.30, EXCEPT

$V_{DC}/R$  REPLACED BY  $I_{DC}$

$$V_o(s) = \frac{I_{DC}/C}{s^2 + s/RC + 1/LC} = \frac{4,350}{s^2 + 2,500s + 10^6}$$

ROOTS OF DENOMINATOR

$$s_i = \frac{-2,500 \pm \sqrt{(2,500)^2 - 4 \times 10^6}}{2}$$

$$= -500, -2,000$$

$$V_o(s) = \frac{4,350}{(s+500)(s+2,500)} = \frac{K_1}{s+500} + \frac{K_2}{s+2,000}$$

$$\frac{4,350}{s+2,000} \Big|_{s=-500} = K_1 = 2.90$$

$$\frac{4,350}{s+500} \Big|_{s=-2,000} = K_2 = -2.90$$

$$V_o(s) = \frac{2.9}{s+500} - \frac{2.9}{s+2,000}$$

a)  $v_o(t) = 2.9(e^{-500t} - e^{-2,000t})u(t) \text{ V}$

$$I_o(s) = \frac{V_o(s)}{1/s} = s V_o(s)$$

$$I_o(s) = \frac{875}{(s+500)(s+2,000)} = \frac{K_1}{s+500} + \frac{K_2}{s+2,000}$$

$$\frac{875}{s+2,000} \Big|_{s=-500} = K_1 = -29$$

$$\frac{875}{s+500} \Big|_{s=-2,000} = K_2 = 116$$

b)  $i_o(t) = (-29e^{-500t} + 116e^{-2,000t})u(t) \text{ mA}$

3

c) DOES  $i_o(0) = 116 - 29 = 87 \text{ mA}$

MAKE SENSE?

CONSIDER KCL AT  $t=0$

$$-I_{DC} + i_L(0) + i_R(0) + i_o(0) = 0$$

BUT  $i_R(0) = \frac{v_o(0)}{R}$ ,  $\because v_o(0) = 0 \Rightarrow i_R(0) = 0$

MOREOVER,  $i_L(0) = 0$

$$\Rightarrow -I_{DC} + i_o(0) = 0$$

$$i_o(0) = I_{DC} = 87 \text{ mA} \quad \checkmark$$



12.39

①

$$V - 150I_1 - 4,5I_1 - 5L_2(I_1 - I_2)$$

$$- 5M(I_2 - I_1) + 5M I_1 = 0$$

$$\textcircled{1} \quad I_1(150 + 5L_2 + 5L_2 - 25M) + I_2(5M - 5L_2) = V$$

$$- 5L_2(I_2 - I_1) - 100 I_2 - 5M I_1 = 0$$

$$\textcircled{2} \quad I_1(5M - 5L_2) + I_2(5L_2 + 100) = 0$$

$$\textcircled{2'} \quad I_2 = \frac{I_1(5L_2 - 5M)}{5L_2 + 100}$$

USE  $\textcircled{1}$  &  $\textcircled{2'}$ :

$$I_1 \left[ (150 + 5L_2 + 5L_2 - 25M) + \frac{(5M - 5L_2)(5L_2 - 5M)}{5L_2 + 100} \right] = V$$

$$I_1 \left[ (150 + 5L_2 + 5L_2 - 25M)(5L_2 + 100) - (5L_2 - 5M)^2 \right]$$

$$= V(5L_2 + 100)$$

12.39, CONT'D

(2)

TERM IN SQUARE BRACKETS ONLY:

$$\begin{aligned}
 [\dots] &= 150sL_2 + 15,000 + s^2L_2L_2 + 100sL_2 \\
 &\quad + \cancel{s^2L_2^2} + 100sL_2 - \cancel{25L_2L_2} - 200sL_2 \\
 &\quad - \cancel{s^2L_2^2} + \cancel{25L_2L_2} - s^2L_2^2 \\
 &= s^2(L_2L_2 - L_2^2) + s(250L_2 + 100L_2 - 200L_2) \\
 &\qquad\qquad\qquad + 15,000
 \end{aligned}$$

$$\begin{aligned}
 \text{NOW } \bar{I}_1 &= \frac{V(s)(sL_2 + 100)}{s^2(L_2L_2 - L_2^2) + s(250L_2 + 100L_2 - 200L_2) + 15,000} \\
 &= \frac{V(s)(s + 100/L_2)}{s^2(L_2 - L_2^2/L_2) + s(250 + 100L_2/L_2 - 200L_2/L_2) + 15,000/L_2}
 \end{aligned}$$

$$\bar{I}_1 = \frac{V(s)(s+8)}{s^2(12.5) + s(350) + 1,200}$$

$$= \frac{V(s)/12.5 (s+8)}{s^2 + 28s + 96}$$

$$\text{ROOTS ARE } \frac{-28 \pm \sqrt{(28)^2 - 4 \times 96}}{2} = -4, -24$$

12.39, (CONT'D).

(3)

$$\text{NOW } v(t) = 625u(t) \rightarrow V(s) = \frac{625}{s}$$

$$\bar{I}(s) = \frac{625}{s} \cdot \frac{1}{12.5} \cdot \frac{(s+8)}{(s+4)(s+24)}$$

$$= \frac{50(s+8)}{s(s+4)(s+24)} = \frac{K_1}{s} + \frac{K_2}{s+4} + \frac{K_3}{s+24}$$

$$\left. \frac{50(s+8)}{(s+4)(s+24)} \right|_{s=0} = K_1 = \frac{50(8)}{(4)(24)} = \underline{\underline{4.1667}} = K_1$$

$$\left. \frac{50(s+8)}{s(s+24)} \right|_{s=-4} = K_2 = \frac{50(8-4)}{(-4)(24-4)} = \underline{\underline{-2.5}} = K_2$$

$$\left. \frac{50(s+8)}{s(s+4)} \right|_{s=-24} = K_3 = \frac{50(8-24)}{(-24)(4-24)} = \underline{\underline{-1.6667}} = K_3$$

$$\bar{I}(s) = \frac{4.1667}{s} - \frac{2.5}{s+4} - \frac{1.6667}{s+24}$$

$$i(t) = (4.1667 - 2.5e^{-4t} - 1.6667e^{-24t})u(t)$$

A

12.39, CONT'D.

(4)

EQ. (2')

$$I_2(s) = \frac{I_1 s (L_2 - M)}{sL_2 + 100} = \frac{I_1 s (1 - M/L_2)}{s + 100/L_2}$$

$$I_2(s) = \frac{50(s+8)}{(s+4)(s+24)} \frac{(s)(-1)}{(s+8)}$$

$$= \frac{-50}{(s+4)(s+24)} = \frac{K_1}{s+4} + \frac{K_2}{s+24}$$

$$\frac{-50}{(s+24)} \Big|_{s=-4} = K_1 = \frac{-50}{24-4} = \underline{\underline{-2.5 = K_1}}$$

$$\frac{-50}{(s+4)} \Big|_{s=-24} = K_2 = \frac{-50}{4-24} = \underline{\underline{2.5 = K_2}}$$

$$I_2(s) = \frac{-2.5}{s+4} + \frac{2.5}{s+24}$$

$$i_2(t) = (2.5e^{-24t} - 2.5e^{-4t})u(t) \text{ A}$$


12.39, CONT'D.

(5)

$$i_1(t) \xrightarrow{t \rightarrow \infty} 4.1667 \text{ A}$$

$$i_2(t) \xrightarrow{t \rightarrow \infty} 0 \text{ A}$$


THIS MAKE SENSE AS CKT BECOMES

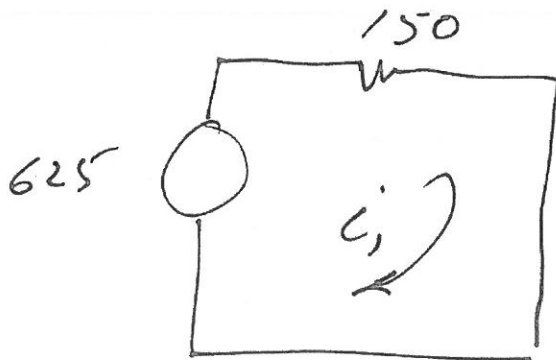

$$i_1 \rightarrow \frac{625}{150} = 4.1667 \text{ A}$$

12.46

①

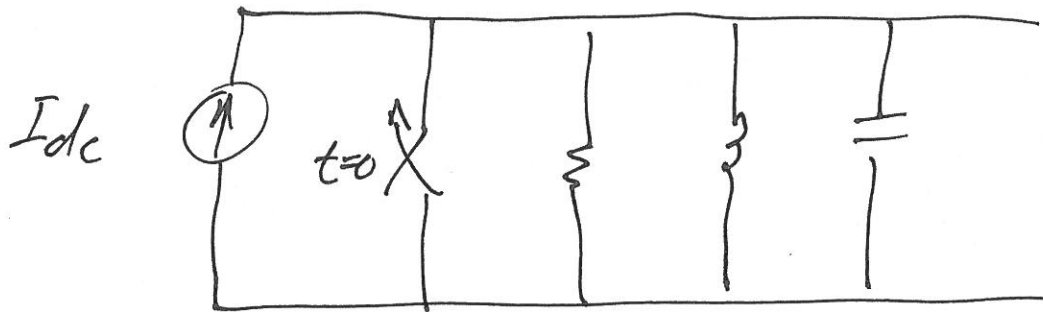

$$I_{dc} = 1.2 \cos t \text{ A}$$

$$R = 1 \Omega, C = 625 \text{ mF}, L = 1.6 \text{ H}$$

SAME GENERAL SOL'N AS 12.26

$$V(s) = \frac{s/C}{s^2 + s/Rc + 1/Lc} = \frac{1.25}{(s^2 + 1)}$$

$$V(s) = \frac{1.92 s^2}{(s^2 + 1.6s + 1)(s^2 + 1)}$$

INITIAL VALUE THM:  $v(0^+) = \lim_{s \rightarrow \infty} sF(s)$

$$\lim_{s \rightarrow \infty} \frac{1.92 s^3}{(s^2 + 1.6s + 1)(s^2 + 1)} = \underline{\underline{0}} = \underline{\underline{v(0^+)}}$$

AGREES WITH WHAT WE KNOW ABOUT  
INSTANTANEOUS VOLTAGE CHANGE  
FOR A CAPACITOR

12.46

(2)


FINAL VALUE THM:  $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0^+} sF(s)$

IFF POLES LIE IN LHP (WITH  
EXCEPTION OF SIMPLE POLE AT  $s=0$ )

POLES ARE  $\frac{-1.6 \pm \sqrt{(0.6)^2 - 4}}{2}$

$$= \frac{-1.6 \pm j1.2}{2} = -0.8 \pm j0.6$$

AND AS  $\pm j$

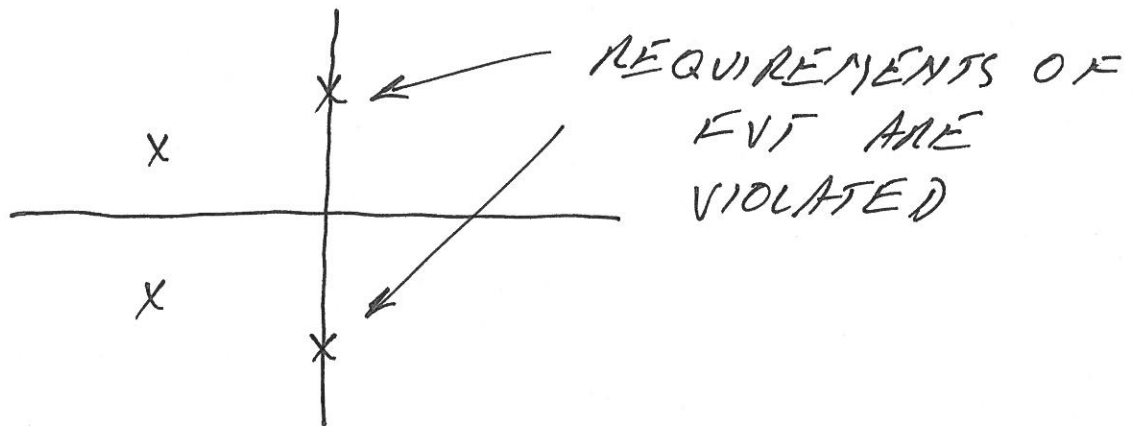

12.52

$$a) F(s) = \frac{320}{s^2(s+8)}$$

FVT CANNOT BE APPLIED (DOUBLE POLE AT ORIGIN)

$$b) \text{IVT: } f(0^+) = \lim_{s \rightarrow \infty} \frac{s \cdot 320}{s^2(s+8)} = 0$$

$$c) F(s) = \frac{95(s+3)}{s(s+7)^2} \quad \text{IVT, FVT OK}$$

$$d) \text{FVT: } f(\infty) = \lim_{s \rightarrow 0} \frac{95(s+3)}{(s+7)^2} = \frac{95 \times 3}{49} = 5.82$$

$$e) \text{IVT: } f(0^+) = \lim_{s \rightarrow \infty} \frac{95(s+3)}{(s+7)^2} = 0$$

$$f) F(s) = \frac{60(s+5)}{(s+1)^2(s^2+6s+25)} \quad \text{IVT, FVT OK}$$

$$g) \text{FVT: } f(\infty) = \lim_{s \rightarrow 0} \frac{s \cdot 60(s+5)}{(s+1)^2(s^2+6s+25)} = 0$$


$$h) \text{IVT: } f(0^+) = \lim_{s \rightarrow \infty} \frac{s \cdot 60(s+5)}{(s+1)^2(s^2+6s+25)} = 0$$

$$i) F(s) = \frac{25(s+4)^2}{s^2(s+5)^2} \quad \text{ONLY IVT}$$

$$j) \text{IVT: } f(0^+) = \lim_{s \rightarrow \infty} \frac{25(s+4)^2}{s(s+5)^2} = 0$$



12.54

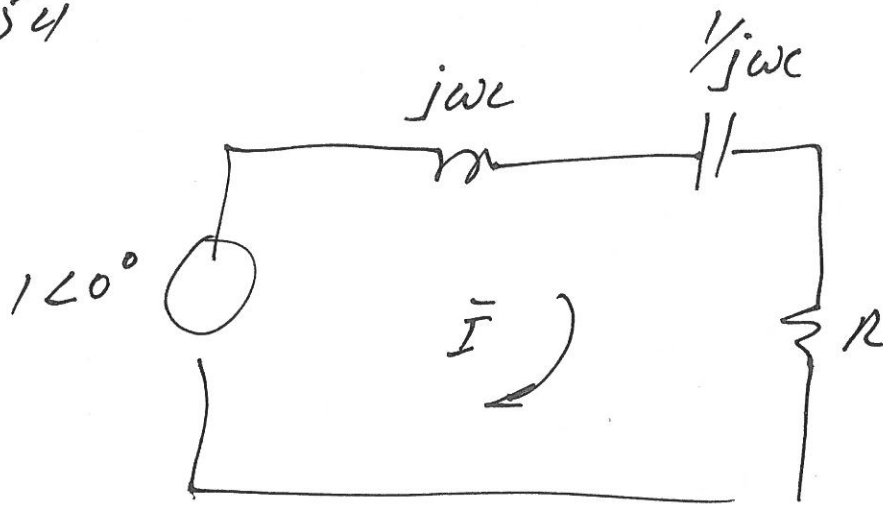

$$1 = \bar{I} (j\omega L + 1/j\omega C + R)$$

$$\bar{I} = \frac{1}{j\omega L + 1/j\omega C + R} = \frac{j\omega}{-\omega^2 L + \frac{1}{C} + j\omega R}$$

$$\bar{I} = \frac{j\omega/L}{(\frac{1}{LC} - \omega^2) + j\omega R/L}$$

$$= \frac{\omega/L \angle 90^\circ}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\omega R/L)^2}} \angle \theta$$

$$\theta = \text{TAN}^{-1} \left( \frac{\omega R/L}{\frac{1}{LC} - \omega^2} \right)$$

$$\bar{I} = 36.69 \angle 90^\circ - 33.39^\circ \text{ mA}$$

$$i_L(t) = i(t) = 36.69 \cos(120\pi t - 0.988) \text{ mA}$$

IN RADIANS ↗