
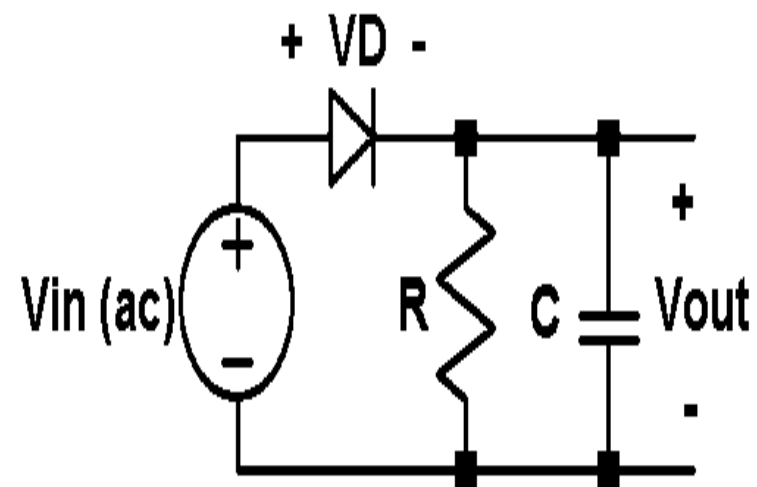


# Lab1: Rectifier Circuits

## a) Half Wave Rectifier with RC filter

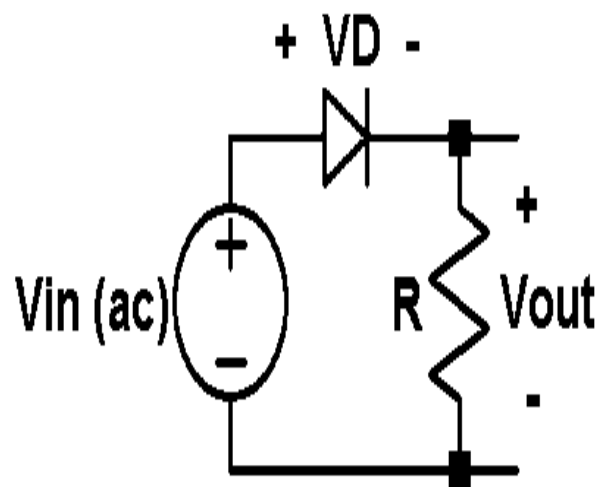

- For this experiment consider diode to be a switch.
- For ideal diode

$V_d > 0$ , the switch is closed and diode conducts like a short circuit

$V_d < 0$ , the switch is open and diode does not conduct, just like an open circuit.

- Practical diode:

$V_d > V_{on} = 0.7V$  (Silicon). After this voltage diode start conducting.

- Expected waveform without capacitor in the circuit
- Diode conducts in only positive half cycle and hence voltage appears at load resistance.

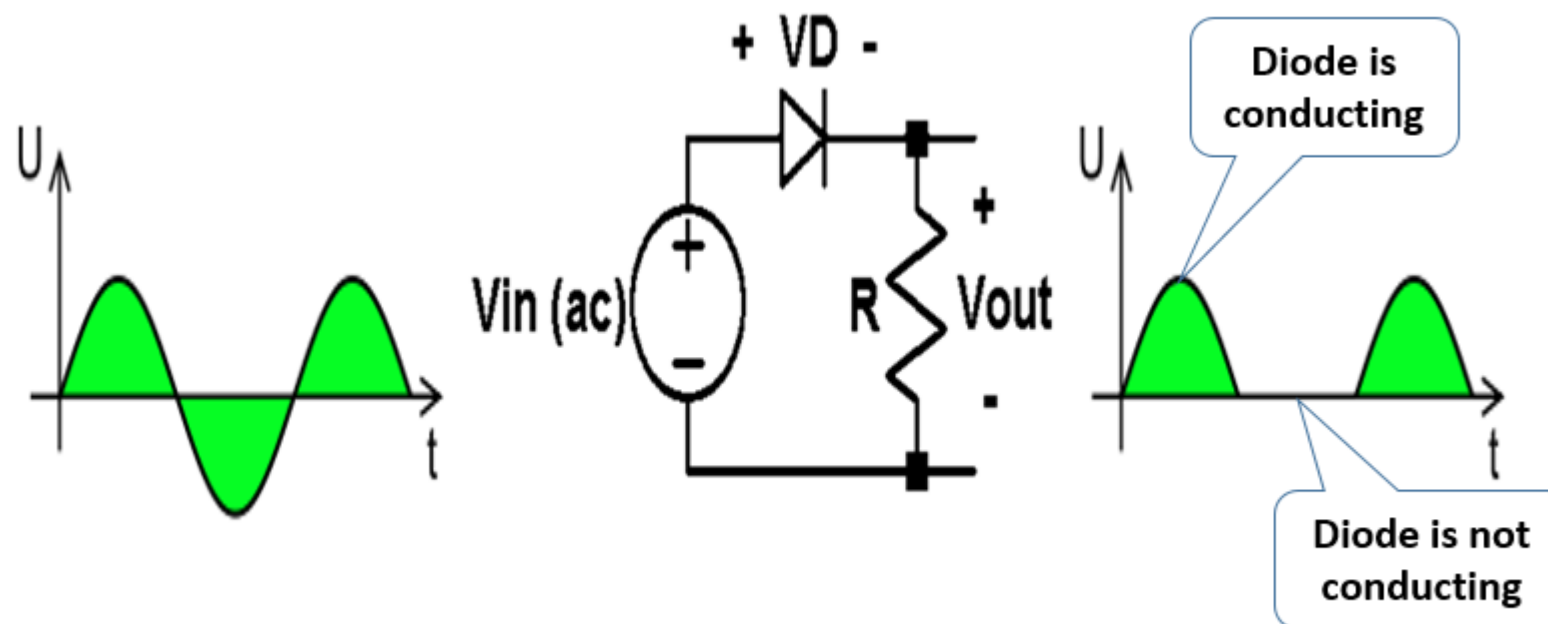


Fig. 1 Half wave rectifier

[Figure is taken from lab1 doc ECE-222]

- Adding capacitor to the previous circuit gives smoothing effect. It blocks DC and hence we get DC at load resistance.
- As value of capacitance increases, DC content will increase.
- Amount of AC present in DC is defined as ripple voltage, represented by  $\Delta V$ .
- Less ripple voltage is good,  $\Delta V/V_p = T/RC$  [2]

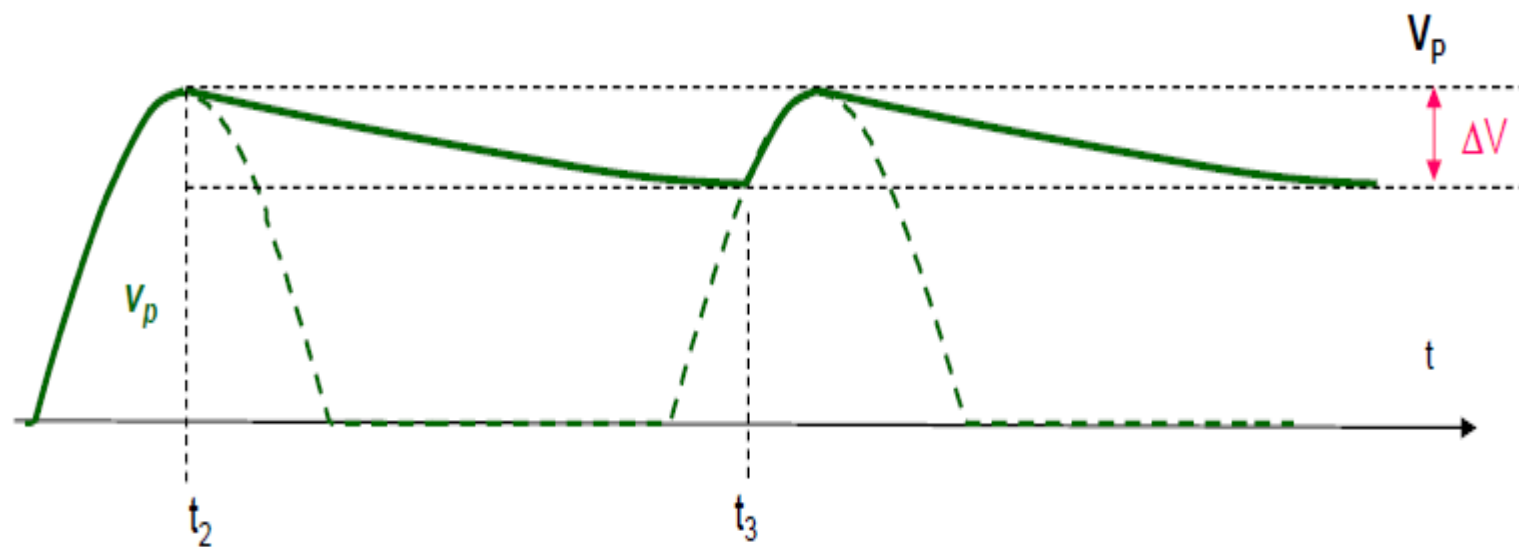


Fig. 2 Capacitor effect in Half-wave rectifier [2]

## b) Full Wave Rectifier using Centered-Tapped Transformer

- Inductance is directly proportional to square of turns.

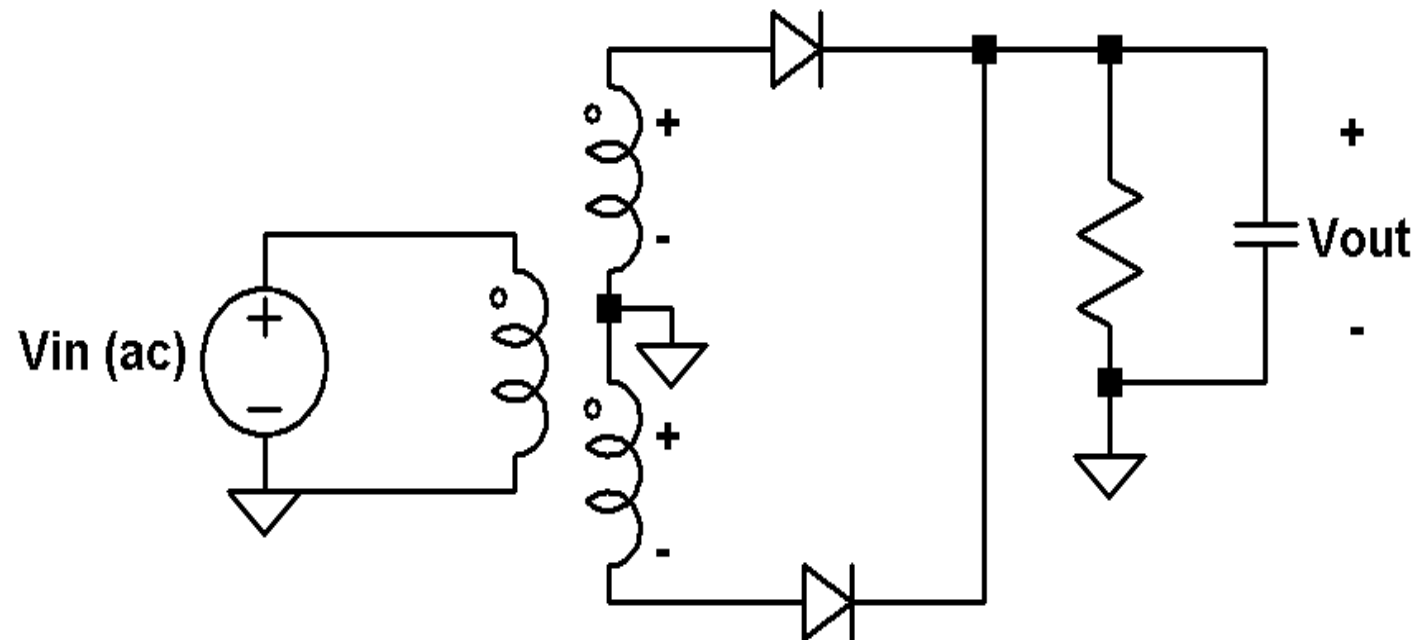


Fig. 3 Full wave Rectifier

[Figure is taken from lab1 doc ECE-222]

- In this experiment
  - Primary winding has  $N_1$  turns.
  - Secondary Winding has  $N_1/2$  turns each.
- For getting 10V at the output side, 20 V peak-to-peak is applied on the primary side.

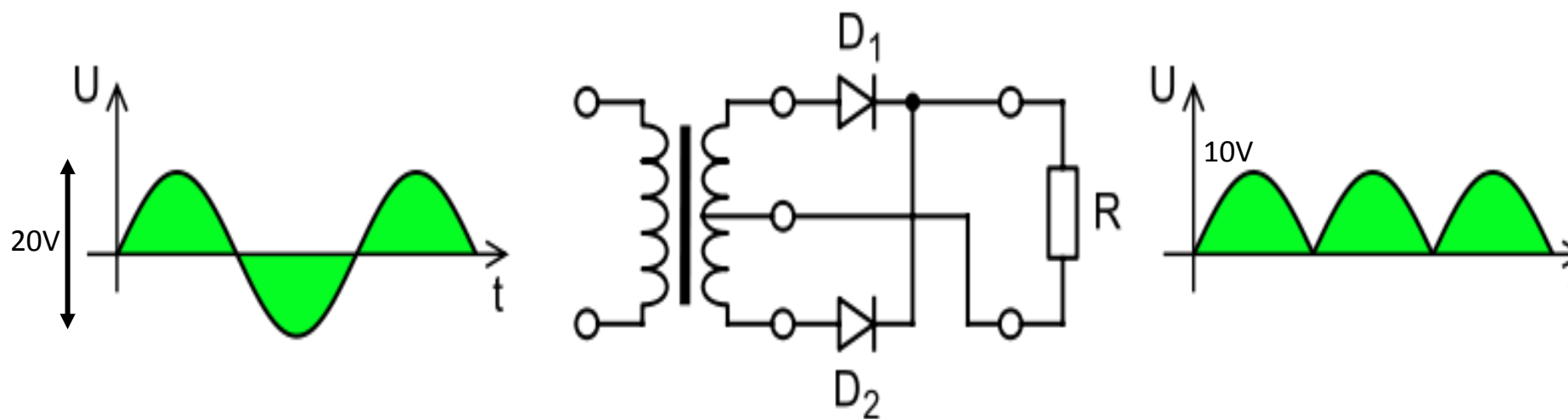


Fig. 4 Full wave rectifier [3]

1. <http://en.wikipedia.org/wiki/Rectifier>
2. <http://didattica.uniroma2.it/assets/uploads/corsi/141016/Laboratory Half wave rectifier with capacitive filter.pdf>
3. <http://engineering.electrical-equipment.org/electrical-distribution/centre-tapped-transformer.html>
4. <http://www-inst.eecs.berkeley.edu/~ee40/fa03/lecture/lecture13.pdf>