


SOLUTION

## ECE222

## Quiz 7

To get full credit, show all your work.

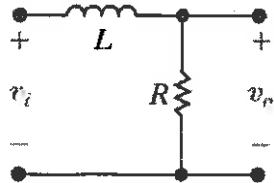- a) Find the transfer function:  $H(s) = \frac{V_o}{V_i}$  for the following circuit.



VOLTAGE DIVIDER RULE  $\Rightarrow$

$$H(s) = \frac{R}{sL + R}$$

$$\text{or } H(s) = \frac{1}{1 + \frac{sL}{R}}$$

- b) State the locations of all the poles and zeros. Including any non-finite locations.

$$\text{POLE AT } s = -\frac{R}{L}$$

$$\text{ZERO AT INFINITY } s = \infty$$

- c) Assuming values of  $L = 10mH$  and  $R = 10\Omega$  and an input signal  $v_i(t) = 10\cos(1000t + 25^\circ)$  determine the steady state output  $v_o(t)$ .

$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{R/L}} \quad \frac{R}{L} = \frac{10}{10 \times 10^{-3}} = 1000 \quad \omega = 1000$$

$$\Rightarrow H(j\omega) \Big|_{\omega=1000} = \frac{1}{1 + j \frac{1000}{1000}} = \frac{1}{1+j}$$

$$\left| H(j\omega) \right|_{\omega=1000} = \left| \frac{1}{1+j} \frac{1-j}{1-j} \right| = \left| \frac{1-j}{1+j} \right| = \left| \frac{\frac{1}{2} - \frac{1}{2}j}{1+j} \right| = \sqrt{\left(\frac{1}{2}\right)^2 + \left(-\frac{1}{2}\right)^2} = \frac{1}{\sqrt{2}} = 0.707$$

$$\angle H(j\omega) \Big|_{\omega=1000} = \text{atan} \left( \frac{-\frac{1}{2}}{\frac{1}{2}} \right) = \text{atan}(-1) = -45^\circ$$

$$\Rightarrow v_o(t) = 10 \times 0.707 \cos(1000t + 25^\circ - 45^\circ)$$

$$v_o(t) = 7.07 \cos(1000t - 20^\circ)$$