

PROBLEMS


Section 11.3 Instantaneous Power and Average Power

P 11.3-1 An *RLC* circuit is shown in Figure P 11.3-1. Find the instantaneous power delivered to the inductor when $i_s = 1 \cos \omega t$ A and $\omega = 6283$ rad/s.



Figure P 11.3-1

Solution:

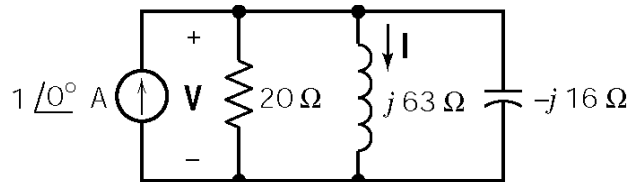

$$1 \angle 0^\circ = \frac{\mathbf{V}}{20} + \frac{\mathbf{V}}{j63} + \frac{\mathbf{V}}{-j16} \Rightarrow \mathbf{V} = 14.6 \angle -43^\circ \text{ V}$$

$$\mathbf{I} = \frac{\mathbf{V}}{j63} = 0.23 \angle -133^\circ \text{ A}$$

$$\begin{aligned} p(t) &= i(t)v(t) = 0.23 \cos(2\pi \cdot 10^3 t - 133^\circ) \times 14.6 \cos(2\pi \cdot 10^3 t - 43^\circ) \\ &= 3.36 \cos(2\pi \cdot 10^3 t - 133^\circ) \cos(2\pi \cdot 10^3 t - 43^\circ) \\ &= 1.68 (\cos(90^\circ) + \cos(4\pi \cdot 10^3 t - 176^\circ)) \\ &= 1.68 \cos(4\pi \cdot 10^3 t - 176^\circ) \end{aligned}$$

P 11.3-8

- (a) Find the average power delivered by the source to the circuit shown in Figure P 11.3-8.
 (b) Find the power absorbed by resistor R_1 .

Answer: (a) 30 W
 (b) 20 W

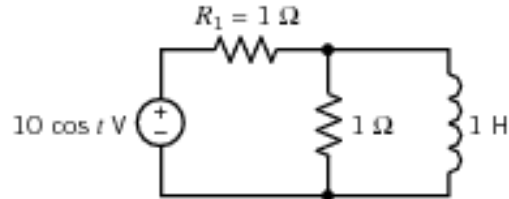
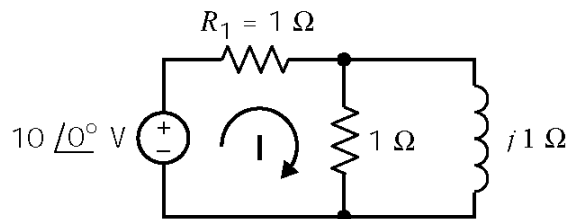


Figure P 11.3-8

Solution:

The equivalent impedance of the parallel resistor and inductor is $\mathbf{Z} = \frac{(1)(j)}{1+j} = \frac{1}{2}(1+j) \Omega$. Then

$$\mathbf{I} = \frac{10 \angle 0^\circ}{1 + \frac{1}{2}(1+j)} = \frac{20}{3+j} = \frac{20}{\sqrt{10}} \angle -18.4^\circ \text{ A}$$

$$(a) P_{\text{source}} = \frac{|\mathbf{I}||\mathbf{V}|}{2} \cos \theta = \frac{(10) \left(\frac{20}{\sqrt{10}} \right)}{2} \cos(-18.4^\circ) = 30.0 \text{ W}$$

$$(b) P_{R_1} = \frac{|\mathbf{I}|^2 R_1}{2} = \frac{\left(\frac{20}{\sqrt{10}} \right)^2 (1)}{2} = 20 \text{ W}$$

P 11.3-2 Find the average power absorbed by the 0.6-k Ω resistor and the average power supplied by the current source for the circuit of Figure P 11.3-2.


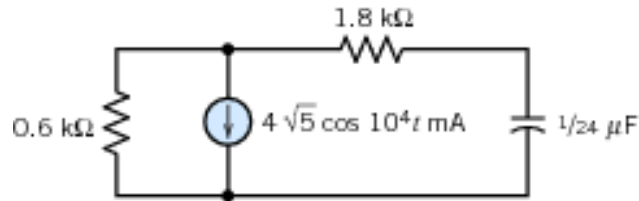


Figure P 11.3-2

Solution:

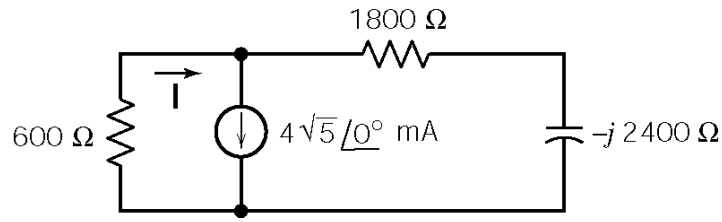

Current division:

$$\mathbf{I} = 4\sqrt{5} \left[\frac{1800 - j2400}{1800 - j2400 + 600} \right]$$

$$= 5\sqrt{\frac{5}{2}} \angle -8.1^\circ \text{ mA}$$

$$P_{600\Omega} = \frac{|\mathbf{I}|^2 600}{2} = 300(25) \left(\frac{5}{2} \right) = 1.875 \times 10^4 \mu\text{W} = 18.75 \text{ mW}$$

$$P_{\text{source}} = \frac{|\mathbf{V}||\mathbf{I}|\cos\theta}{2} = \frac{1}{2}(600) \left(5\sqrt{\frac{5}{2}} \right) (4\sqrt{5}) \cos(-8.1^\circ) = 2.1 \times 10^4 \mu\text{W} = 21 \text{ mW}$$