

ECE241
HW #4
SOLUTION

Problems from "Introduction to Electric Circuits", Svoboda and Dorf, 9th ed. Pages 204-213.

- 1) P 5.2-2
- 2) P 5.2-7
- 3) P 5.3-7
- 4) P 5.4-3
- 5) P 5.5-3
- 6) P 5.6-3

SOLUTION:

P 5.2-2 Consider the circuit of Figure P 5.2-2. Find i_a by simplifying the circuit (using source transformations) to a single-loop circuit so that you need to write only one KVL equation to find i_a .


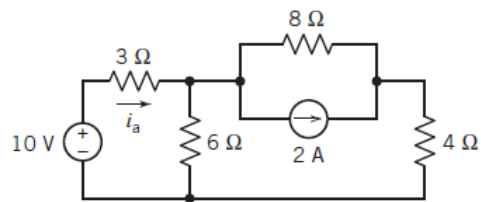
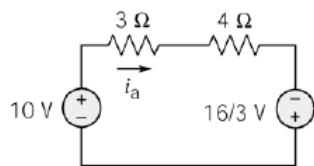
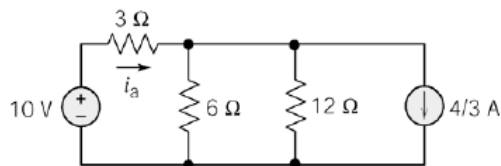
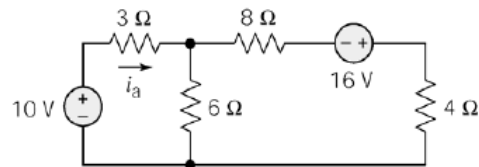


Figure P 5.2-2

Solution:

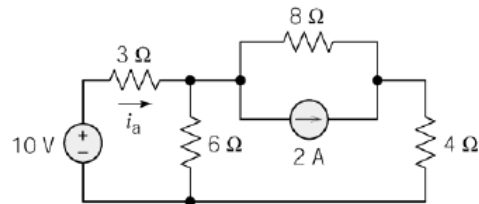

Finally, apply KVL:
$$-10 + 3i_a + 4i_a - \frac{16}{3} = 0 \quad \therefore \underline{i_a = 2.19 \text{ A}}$$

P5.2-7


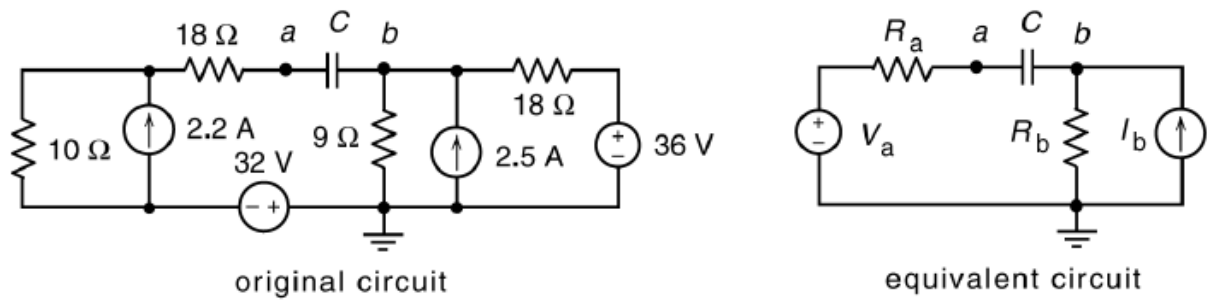



Figure P5.2-7

The equivalent circuit in Figure P5.2-7 is obtained from the original circuit using source transformations and equivalent resistances. (The lower case letters a and b identify the nodes of the capacitor in both the original and equivalent circuits.) Determine the values of R_a , V_a , R_b and I_b in the equivalent circuit.


Solution

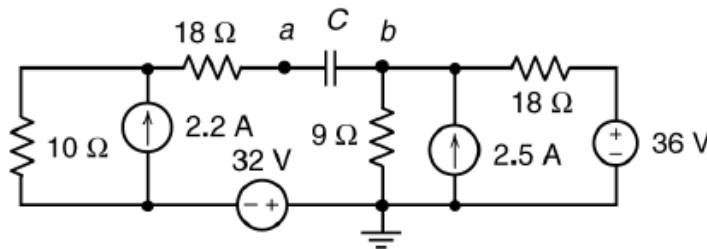

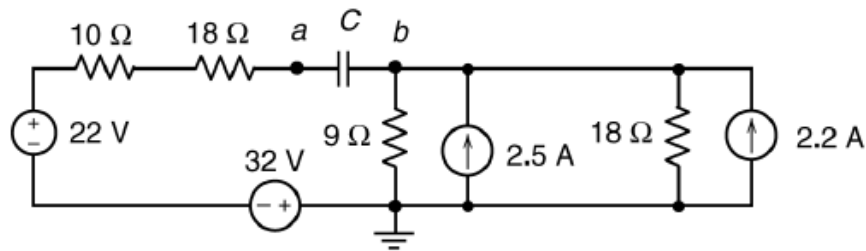Performing a source transformation at each end of the circuit yields



Thenx

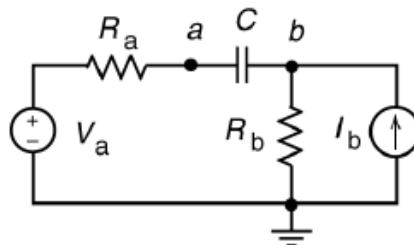

where

$$V_a = 2.2(10) - 32 = -10 \text{ V}, \quad R_a = 18 + 10 = 28 \text{ } \Omega, \quad R_b = 18 \parallel 9 = 6 \text{ } \Omega \quad \text{and} \quad I_b = 2.5 + \frac{36}{18} = 4.5 \text{ A}$$


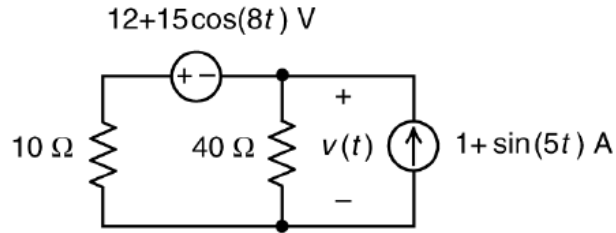


Figure P5.3-7

P5.3-7 Determine $v(t)$, the voltage across the $40\ \Omega$ resistor in the circuit in Figure P5.3-7.

Solution:

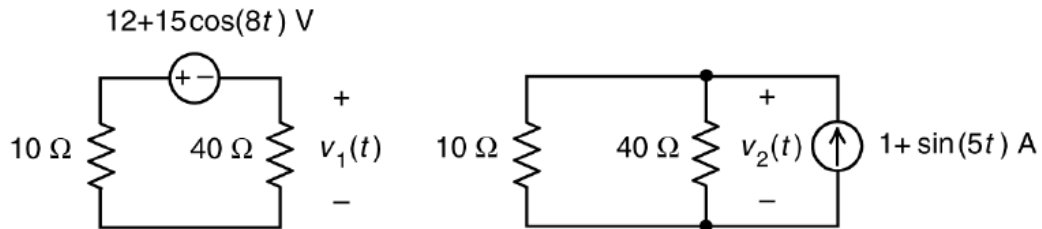We'll use superposition. Let $v_1(t)$ be the part of $v(t)$ due to the voltage source acting alone. Similarly, let $v_2(t)$ be the part of $v(t)$ due to the current source acting alone. We can use these circuits to calculate $v_1(t)$ and $v_2(t)$.



Using voltage division we calculate

$$v_1(t) = -\frac{40}{10+40}(12+15\cos(8t)) = -9.6-12\cos(8t)$$

Using equivalent resistance we first determine $10\parallel 40 = 8\ \Omega$ and then calculate

$$v_2(t) = 8(1+\sin(5t)) = 8+8\sin(5t)$$

Using superposition $v(t) = v_1(t) + v_2(t) = -1.6 + 8\sin(5t) - 12\cos(8t)$ V

P 5.4-3 The circuit shown in Figure P 5.4-3b is the Thévenin equivalent circuit of the circuit shown in Figure P 5.4-3a. Find the value of the open-circuit voltage, v_{oc} , and Thévenin resistance, R_t .

Answer: $v_{oc} = 2 \text{ V}$ and $R_t = 4 \text{ } \Omega$


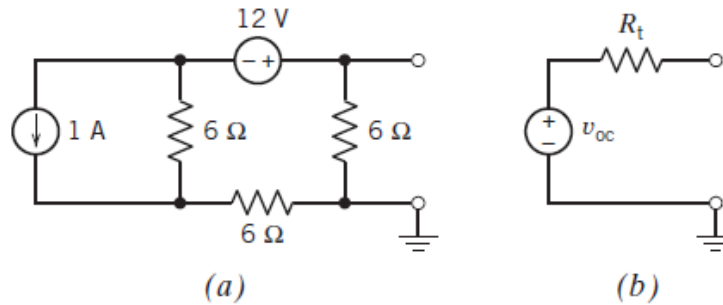



Figure P 5.4-3

Solution:

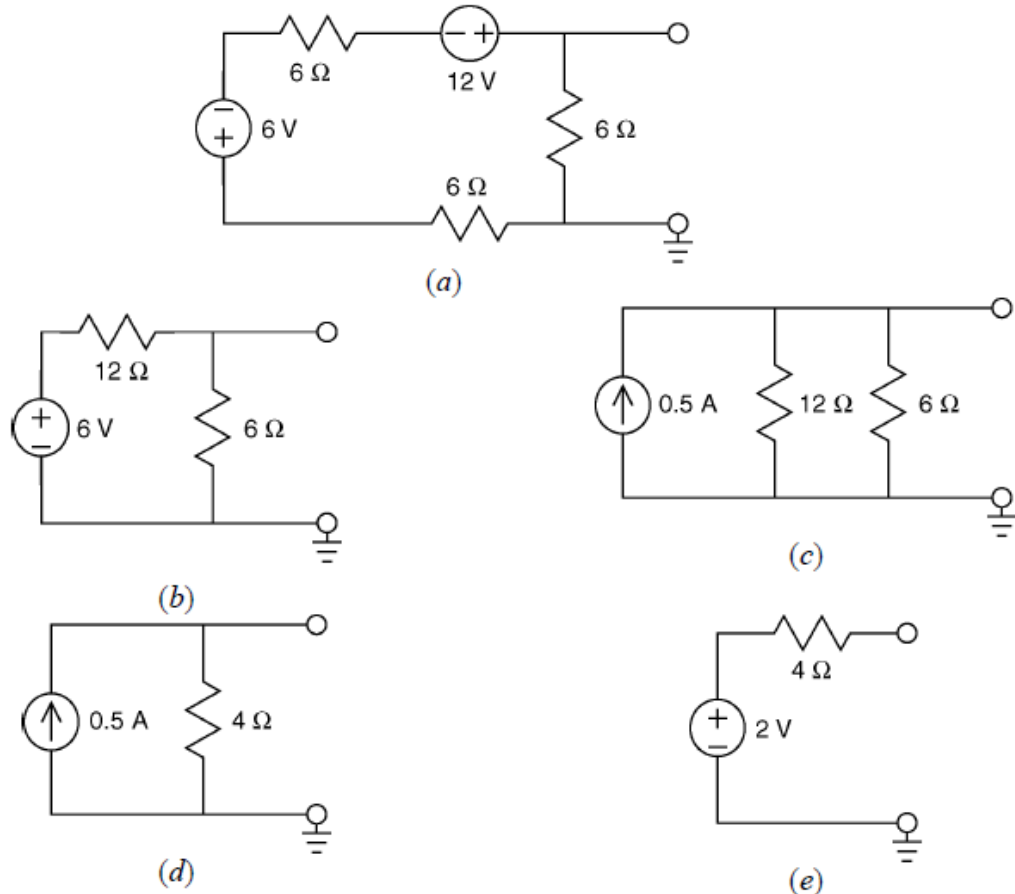
The circuit from Figure P5.4-3a can be reduced to its Thévenin equivalent circuit in five steps:



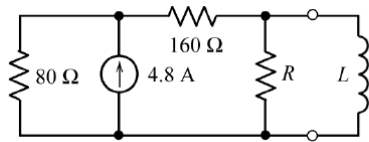Comparing (e) to Figure P5.4-3b shows that the Thévenin resistance is $R_t = 4 \text{ } \Omega$ and the open circuit voltage, $v_{oc} = 2 \text{ V}$.



(a)

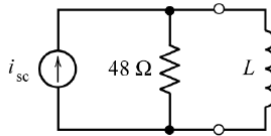

(b)

Figure P5.5-3

P5.5-3 The circuit shown in Figure P5.5-3a can be reduced to the circuit shown in Figure P5.5-3b using source transformations and equivalent resistances. Determine the values of the source current i_{sc} and the resistance R .

Solution:



$$48 = R_t = R \parallel (80 + 160) = \frac{240R}{R + 240} \Rightarrow R = 60 \Omega$$

$$i_{sc} = \frac{80}{80 + 160}(4.8) = 1.6 \text{ A}$$

P 5.6-3 For the circuit in Figure P 5.6-3, prove that for R_s variable and R_L fixed, the power dissipated in R_L is maximum when $R_s = 0$.


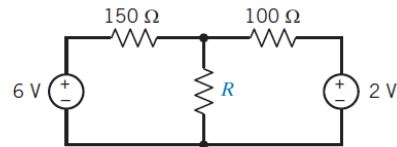
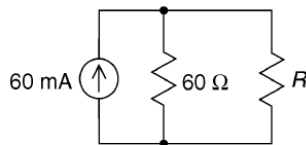


Figure P 5.6-3

Solution:

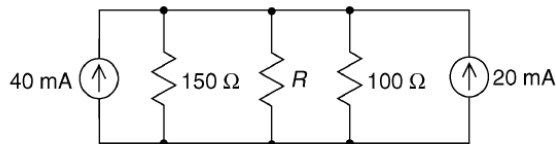Reduce the circuit using source transformations:



Then (a) maximum power will be dissipated in resistor R when: $R = R_t = 60 \Omega$ and (b) the value of that maximum power is

$$P_{\max} = i_R^2(R) = (0.03)^2(60) = \underline{54 \text{ mW}}$$