

ECE241
HW #5
SOLUTION

Problems from “Introduction to Electric Circuits”, Svoboda and Dorf, 9th ed. Pages 305-319.

- 1) P 7.2-7
 - 2) P 7.4-5
 - 3) P 7.5-19
 - 4) P 7.7-5
 - 5) P 7.8-6
 - 6) P 7.8-7
-

SOLUTIONS:

P 7.2-7 The voltage across a 40- μ F capacitor is 25 V at $t_0 = 0$. If the current through the capacitor as a function of time is given by $i(t) = 6e^{-6t}$ mA for $t < 0$, find $v(t)$ for $t > 0$.

Answer: $v(t) = 50 - 25e^{-6t}$ V

Solution:

$$\begin{aligned} v(t) &= v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau = 25 + 2.5 \times 10^4 \int_0^t (6 \times 10^{-3}) e^{-6\tau} d\tau \\ &= 25 + 150 \int_0^t e^{-6\tau} d\tau \\ &= 25 + 150 \left[-\frac{1}{6} e^{-6\tau} \right]_0^t = \underline{50 - 25e^{-6t}} \text{ V} \end{aligned}$$

P7.4-5 Determine the value of the capacitance C in the circuit shown in Figure P 7.4-5, given that $C_{eq} = 8 \text{ F}$.

Answer: $C = 20 \text{ F}$


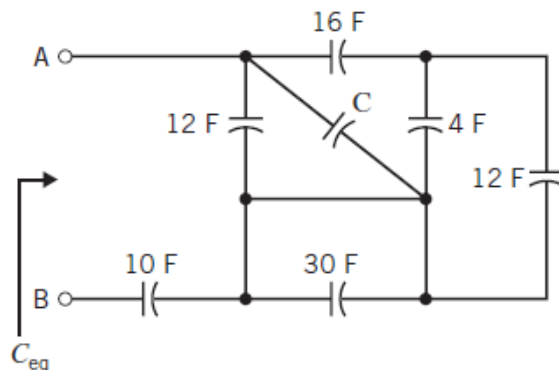


Figure P 7.4-5

Solution: The 16 F capacitor is in series with a parallel combination of 4 F and 12 F capacitors. The capacitance of the equivalent capacitor is

$$\frac{16(4+12)}{16+(4+12)} = 8 \text{ F}$$

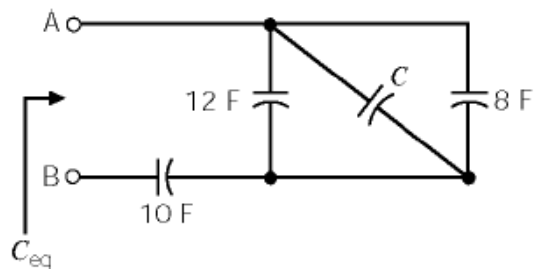The 30 F capacitor is in parallel with a short circuit, which is equivalent to a short circuit. After making these simplifications, we have



Then

$$8 = C_{eq} = \frac{10(12+C+8)}{10+(12+C+8)} \Rightarrow C = 20 \text{ F}$$

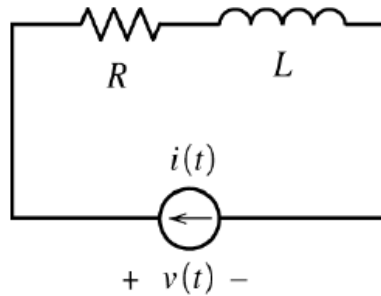


Figure P7.5-19

P7.5-19 . The input to the circuit shown in Figure P7.5-19 is the current

$$i(t) = 5 + 2e^{-7t} \text{ A for } t > 0$$

The output is the voltage: $v(t) = 75 - 82e^{-7t} \text{ V for } t > 0$

Determine the values of the resistance and inductance.

Solution:

$$\begin{aligned} v(t) = 75 - 82e^{-7t} &= R(5 + 2e^{-7t}) + L \frac{d}{dt}(5 + 2e^{-7t}) \\ &= R(5 + 2e^{-7t}) + L((-7)2e^{-7t}) = 5R + (2R - 14L)e^{-7t} \end{aligned}$$

Equating coefficients gives $75 = 5R \Rightarrow R = 15 \Omega$ and

and $-82 = 2R - 14L = 30 - 14L \Rightarrow L = \frac{82 + 30}{14} = 8 \text{ H}$

P 7.7-5 Determine the value of the inductance L in the circuit shown in Figure P 7.7-5, given that $L_{eq} = 18$ H.

Answer: $L = 20$ H


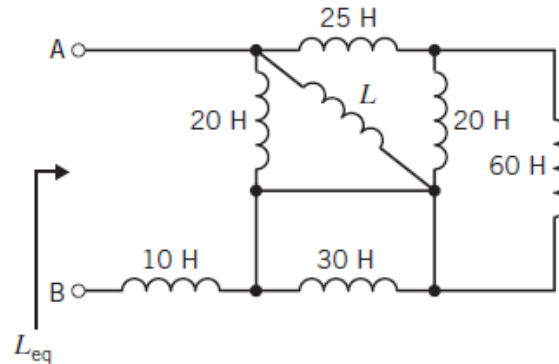


Figure P 7.7-5

Solution: The 25 H inductor is in series with a parallel combination of 20 H and 60 H inductors. The inductance of the equivalent inductor is

$$25 + \frac{60 \times 20}{60 + 20} = 40 \text{ H}$$

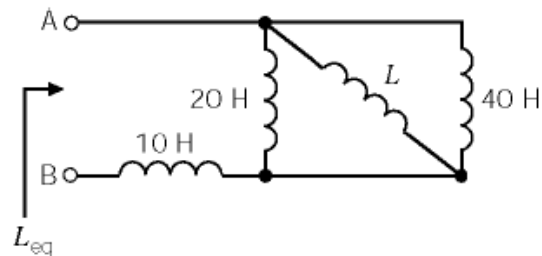The 30 H inductor is in parallel with a short circuit, which is equivalent to a short circuit. After making these simplifications, we have



Then

$$18 = L_{eq} = 10 + \frac{1}{\frac{1}{20} + \frac{1}{L} + \frac{1}{40}} \Rightarrow \frac{1}{20} + \frac{1}{L} + \frac{1}{40} = \frac{1}{8} \Rightarrow L = 20 \text{ H}$$


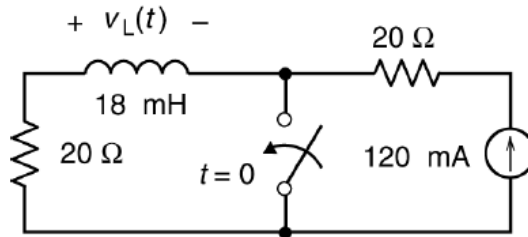


Figure P7.8-6

P7.8-6. The switch in the circuit shown in Figure P7.8-6 has been open for a long time before it closes at time $t = 0$. Determine the values of $v_L(0^-)$, the voltage across the inductor immediately before the switch closes and $v_L(0^+)$, the voltage across the inductor immediately after the switch closes.

Solution:

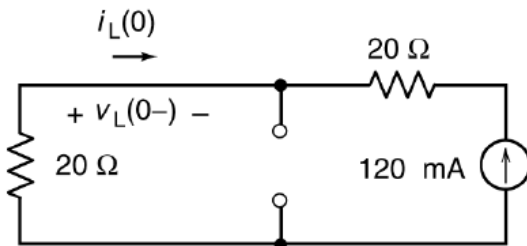The circuit is at steady state immediately before the switch closes. We have




The inductor acts like a short circuit so

$$v_L(0^-) = 0.$$

The inductor current is the negative of the current source current:

$$i_L(0) = -120 \text{ mA}$$

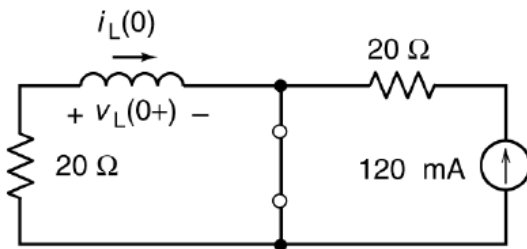The inductor current does not change instantaneously so $i_L(0^+) = i_L(0^-) \triangleq i_L(0)$. Immediately after the switch closes we have:



Applying KVL to the left mesh gives:

$$v_L(0^+) + 20i_L(0) = 0$$

$$v_L(0^+) + 20(-0.12) = 0$$

$$v_L(0^+) = 2.4$$


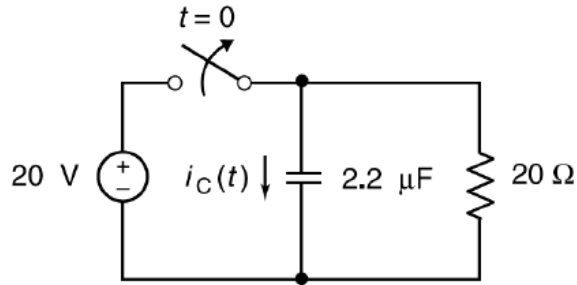


Figure P7.8-7

P7.8-7. The switch in the circuit shown in Figure P7.8-7 has been closed for a long time before it opens at time $t = 0$. Determine the values of $i_C(0^-)$, the current in the capacitor immediately before the switch opens and $i_C(0^+)$, the current in the capacitor immediately after the switch opens.

Solution:

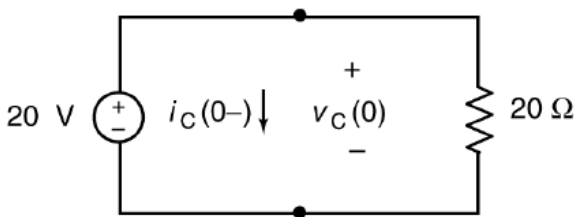The circuit is at steady state immediately before the switch opens. We have




The capacitor acts like an open circuit so $i_C(0^-) = 0$.

The capacitor voltage is equal to the voltage source voltage:

$$v_C(0) = 20 \text{ V}$$

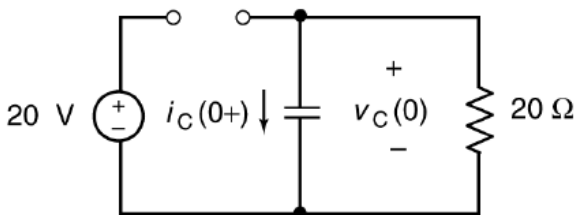The capacitor does not change instantaneously so $v_C(0^+) = v_C(0^-) \triangleq v_C(0)$. Immediately after the switch opens we have:



Applying KCL at the top node of the capacitor, we see that:

$$i_C(0^+) + \frac{v_C(0)}{20} = 0$$

$$i_C(0^+) = -\frac{v_C(0)}{20} = -1 \text{ A}$$