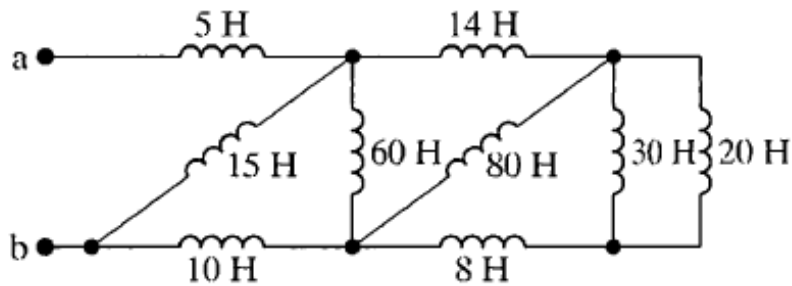


6.20 Assume that the initial energy stored in the inductors of Fig. P6.20 is zero. Find the equivalent inductance with respect to the terminals a,b.

PSPIICE
MULTISIM

Figure P6.20



Solution:

$$P\ 6.20\quad 30\parallel 20 = 12\text{ H}$$

$$80\parallel(8 + 12) = 16\text{ H}$$


$$60\parallel(14 + 16) = 20\text{ H}$$

$$15\parallel(20 + 10) = 20\text{ H}$$

$$L_{ab} = 5 + 10 = 15\text{ H}$$

6.21 Assume that the initial energy stored in the inductors of Fig. P6.21 is zero. Find the equivalent inductance with respect to the terminals a,b.

Figure P6.21

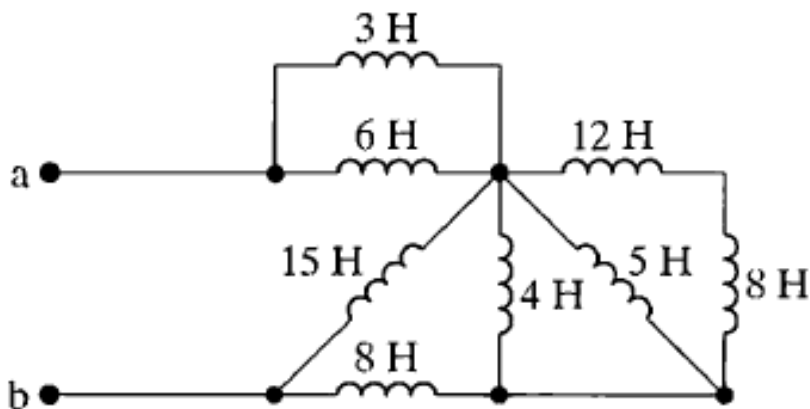

Solution:

$$P\ 6.21 \quad 5 \parallel (12 + 8) = 4\ H$$

$$4 \parallel 4 = 2\ H$$


$$15 \parallel (8 + 2) = 6\ H$$

$$3 \parallel 6 = 2\ H$$

$$6 + 2 = 8\ H$$

6.26 Find the equivalent capacitance with respect to the terminals a,b for the circuit shown in Fig. P6.26.


Figure P6.26

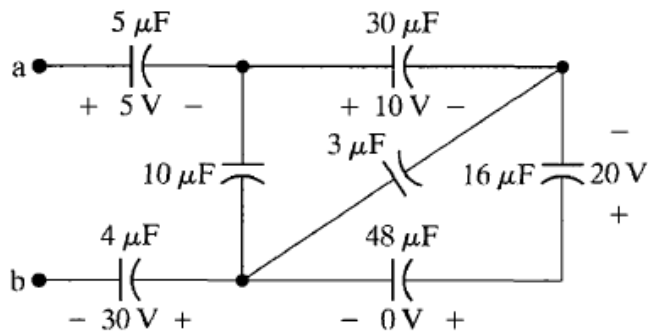

Solution:


$$P\ 6.26 \quad \frac{1}{C_1} = \frac{1}{48} + \frac{1}{16} = \frac{1}{12}; \quad C_1 = 12\ \mu\text{F}$$

$$C_2 = 3 + 12 = 15\ \mu\text{F}$$

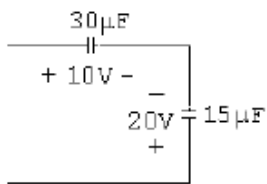


$$\frac{1}{C_3} = \frac{1}{30} + \frac{1}{15} = \frac{1}{10}; \quad C_3 = 10\ \mu\text{F}$$

$$C_4 = 10 + 10 = 20\ \mu\text{F}$$

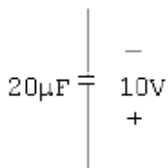

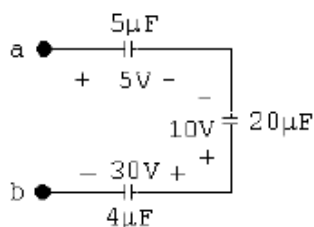
$$\frac{1}{C_5} = \frac{1}{5} + \frac{1}{20} + \frac{1}{4} = \frac{1}{2}; \quad C_5 = 2\ \mu\text{F}$$



Equivalent capacitance is $2\ \mu\text{F}$ with an initial voltage drop of $+25\ \text{V}$.


6.27 Find the equivalent capacitance with respect to the terminals a,b for the circuit shown in Fig. P6.27.

Figure P6.27

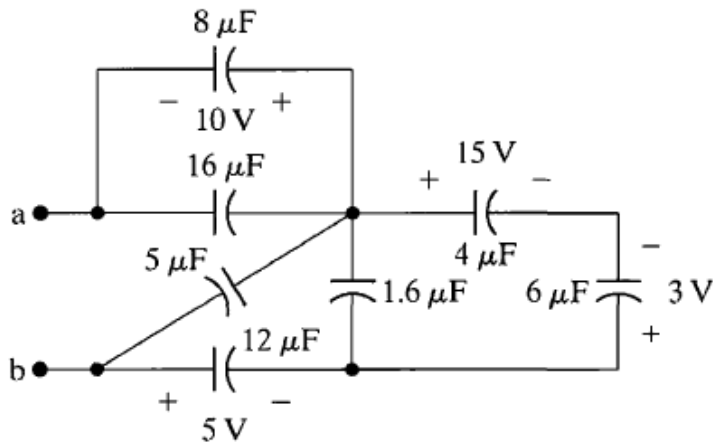

Solution:
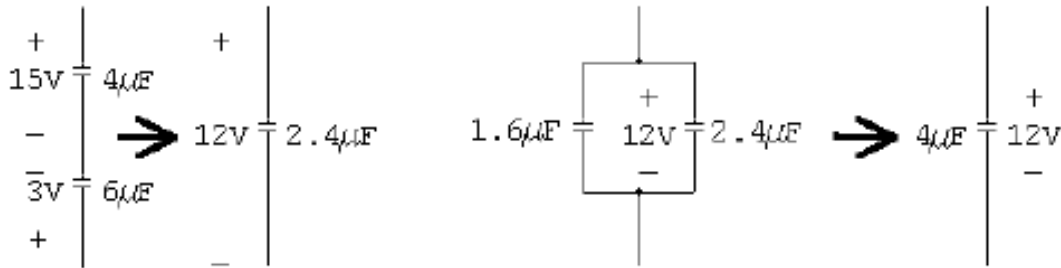
$$\text{P 6.27} \quad \frac{1}{4} + \frac{1}{6} = \frac{5}{12} \quad \therefore C_{\text{eq}} = 2.4 \mu\text{F}$$



$$\frac{1}{4} + \frac{1}{12} = \frac{4}{12} \quad \therefore C_{\text{eq}} = 3 \mu\text{F}$$