

Section 4-2 Node Voltage Analysis of Circuits with Current Sources

P 4.2-1 The node voltages in the circuit of Figure P 4.2-1 are

$$v_1 = -4 \text{ V and } v_2 = 2 \text{ V.}$$

Determine i , the current of the current source.

Answer: $i = 1.5 \text{ A}$

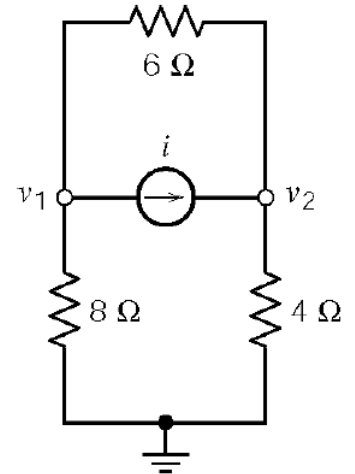


Figure P 4.2-1

Solution:

KCL at node 1:
$$0 = \frac{v_1}{8} + \frac{v_1 - v_2}{6} + i = \frac{-4}{8} + \frac{-4 - 2}{6} + i = -1.5 + i \Rightarrow i = 1.5 \text{ A}$$

P 4.2-2 Determine the node voltages for the circuit of Figure P 4.2-2.

Answer: $v_1 = 2 \text{ V}$, $v_2 = 30 \text{ V}$, and $v_3 = 24 \text{ V}$

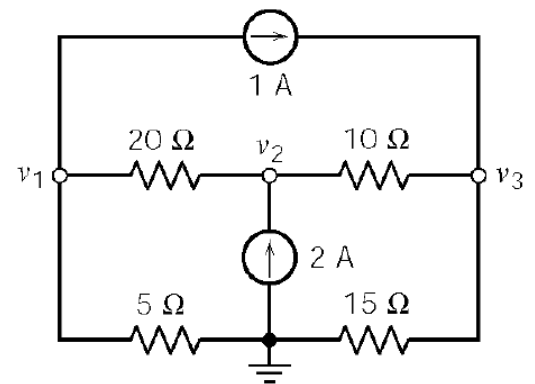


Figure P 4.2-2

Solution:

KCL at node 1:
$$\frac{v_1 - v_2}{20} + \frac{v_1}{5} + 1 = 0 \Rightarrow 5v_1 - v_2 = -20$$

KCL at node 2:
$$\frac{v_1 - v_2}{20} + 2 = \frac{v_2 - v_3}{10} \Rightarrow -v_1 + 3v_2 - 2v_3 = 40$$

KCL at node 3:
$$\frac{v_2 - v_3}{10} + 1 = \frac{v_3}{15} \Rightarrow -3v_2 + 5v_3 = 30$$

Solving gives $v_1 = 2 \text{ V}$, $v_2 = 30 \text{ V}$ and $v_3 = 24 \text{ V}$.

Section 4-3 Node Voltage Analysis of Circuits with Current and Voltage Sources


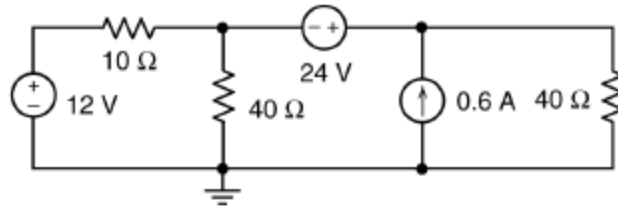



Figure P4.3-3

P4.3-3. Determine the values of the power supplied by each of the sources in the circuit shown in Figure P4.3-3.

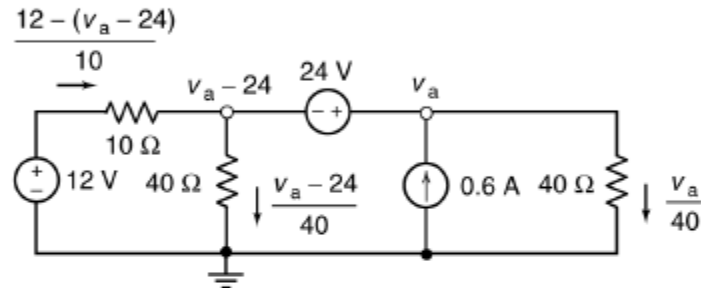Solution: First, label the node voltages. Next, express the resistor currents in terms of the node voltages.



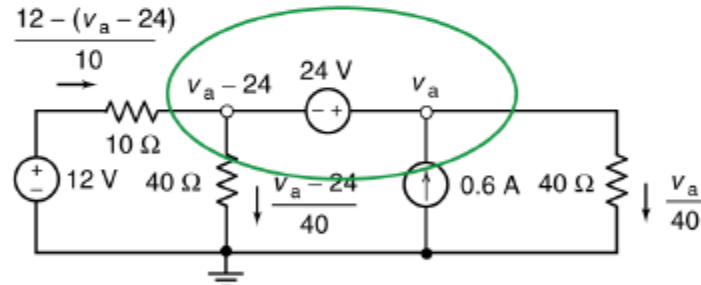Identify the supernode corresponding to the 24 V source



Apply KCL to the supernode to get

$$\frac{12 - (v_a - 24)}{10} + 0.6 = \frac{v_a - 24}{40} + \frac{v_a}{40} \Rightarrow 196 = 6v_a \Rightarrow v_a = 32 \text{ V}$$

The 12 V source supplies $12 \left(\frac{12 - (v_a - 24)}{10} \right) = 12 \left(\frac{12 - (32 - 24)}{10} \right) = 4.8 \text{ W}$

The 24 V source supplies $24 \left(-0.6 + \frac{v_a}{40} \right) = 24 \left(-0.6 + \frac{32}{40} \right) = 4.8 \text{ W}$

The current source supplies $0.6v_a = 0.6(32) = 19.2 \text{ W}$



Section 4-4 Node Voltage Analysis with Dependent Sources

P 4.4-3 Determine the node voltage v_b for the circuit of Figure P 4.4-3.

Answer: $v_b = 1.5$ V


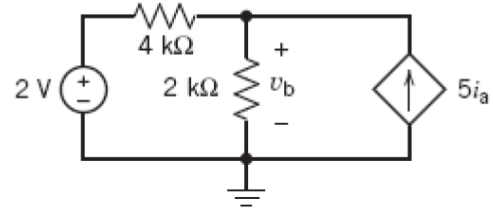


Figure P 4.4-3

Solution:

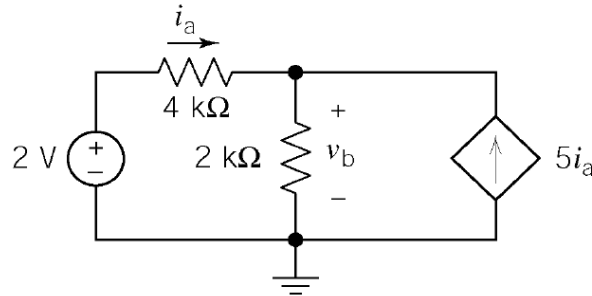

First express the controlling current in terms of the node voltages:

$$i_a = \frac{2 - v_b}{4000}$$

Write and solve a node equation:

$$-\frac{2 - v_b}{4000} + \frac{v_b}{2000} - 5\left(\frac{2 - v_b}{4000}\right) = 0 \Rightarrow \underline{v_b = 1.5 \text{ V}}$$

Section 4-5 Mesh Current Analysis with Independent Voltage Sources

P 4.5-1 Determine the mesh currents, i_1 , i_2 , and i_3 , for the circuit shown in Figure P 4.5-1.

Answers: $i_1 = 3$ A, $i_2 = 2$ A, and $i_3 = 4$ A

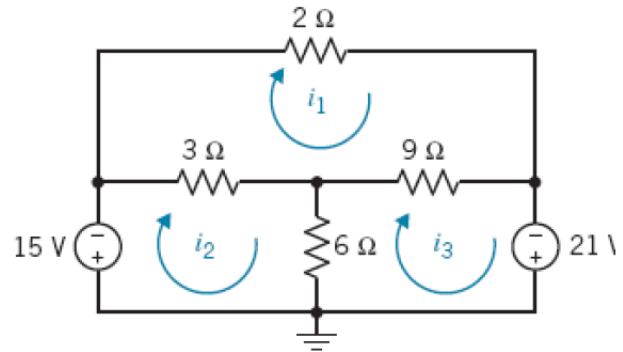


Figure P 4.5-1

Solution:

The mesh equations are

$$2i_1 + 9(i_1 - i_3) + 3(i_1 - i_2) = 0$$

$$15 - 3(i_1 - i_2) + 6(i_2 - i_3) = 0$$

$$-6(i_2 - i_3) - 9(i_1 - i_3) - 21 = 0$$

or

$$14i_1 - 3i_2 - 9i_3 = 0$$

$$-3i_1 + 9i_2 - 6i_3 = -15$$

$$-9i_1 - 6i_2 + 15i_3 = 21$$

so

$$i_1 = 3 \text{ A}, \quad i_2 = 2 \text{ A} \text{ and } i_3 = 4 \text{ A.}$$

Section 4-6 Mesh Current Analysis with Voltage and Current Sources

P 4.6-2 Find v_c for the circuit shown in Figure P 4.6-2.

Answer: $v_c = 15$ V

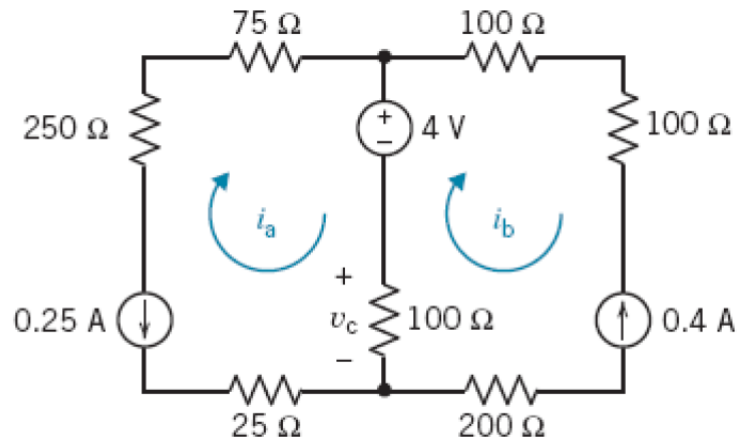


Figure P 4.6-2

Solution:

Mesh currents:

$$\text{mesh a: } i_a = -0.25 \text{ A}$$

$$\text{mesh b: } i_b = -0.4 \text{ A}$$

Ohm's Law:

$$v_c = 100(i_a - i_b) = 100(0.15) = \underline{15 \text{ V}}$$

P 4.6-4 Find v_c for the circuit shown in Figure P 4.6-4.

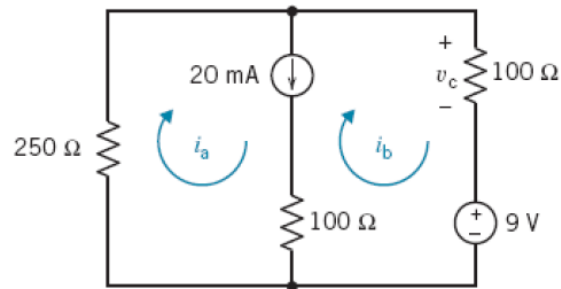


Figure P 4.6-4

Solution:

Express the current source current in terms of the mesh currents:


$$i_b = i_a - 0.02$$

Apply KVL to the supermesh:

$$250 i_a + 100 (i_a - 0.02) + 9 = 0$$

$$\therefore i_a = -0.02 \text{ A} = -20 \text{ mA}$$

$$v_c = 100(i_a - 0.02) = \underline{-4 \text{ V}}$$

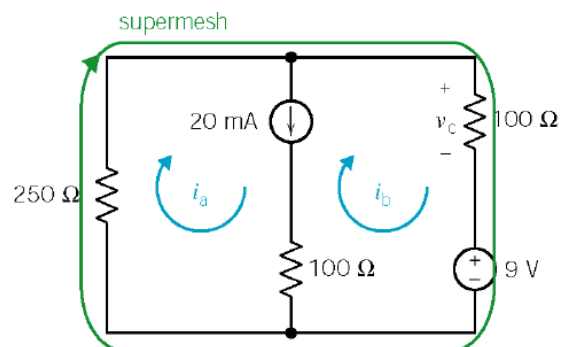

Section 4-7 Mesh Current Analysis with Dependent Sources

P 4.7-1 Find v_2 for the circuit shown in Figure P 4.7-1.

Answer: $v_2 = 10 \text{ V}$

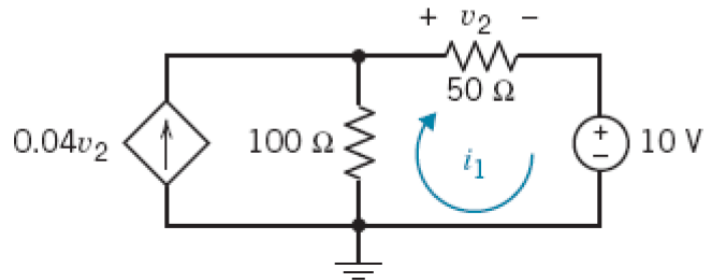


Figure P 4.7-1

Solution:

Express the controlling voltage of the dependent source as a function of the mesh current

$$v_2 = 50 i_1$$

Apply KVL to the right mesh:

$$-100 (0.04(50i_1) - i_1) + 50i_1 + 10 = 0 \Rightarrow i_1 = 0.2 \text{ A}$$

$$v_2 = 50 i_1 = 10 \text{ V}$$

P 4.7-7 The currents i_1 , i_2 and i_3 are the mesh currents of the circuit shown in Figure P 4.7-7. Determine the values of i_1 , i_2 , and i_3 .

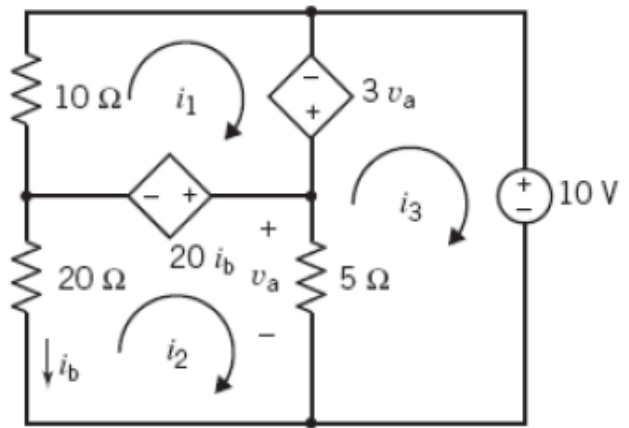


Figure P 4.7-7

Solution:

Express v_a and i_b , the controlling voltage and current of the dependent sources, in terms of the mesh currents

$$v_a = 5(i_2 - i_3) \quad \text{and} \quad i_b = -i_2$$

Next express $20 i_b$ and $3 v_a$, the controlled voltages of the dependent sources, in terms of the mesh currents

$$20 i_b = -20 i_2 \quad \text{and} \quad 3 v_a = 15(i_2 - i_3)$$

Apply KVL to the meshes

$$-15(i_2 - i_3) + (-20 i_2) + 10 i_1 = 0$$

$$-(-20 i_2) + 5(i_2 - i_3) + 20 i_2 = 0$$

$$10 - 5(i_2 - i_3) + 15(i_2 - i_3) = 0$$

These equations can be written in matrix form

$$\begin{bmatrix} 10 & -35 & 15 \\ 0 & 45 & -5 \\ 0 & 10 & -10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -10 \end{bmatrix}$$

Solving, e.g. using MATLAB, gives

$$i_1 = -1.25 \text{ A}, \quad i_2 = +0.125 \text{ A}, \quad \text{and} \quad i_3 = +1.125 \text{ A}$$