

# ECE446/546 Project 1

## Deliverables:

- All Bode plots should be obtained using the Matlab 'margin' command.
- All Matlab code used needs to be included in an Appendix
- The loop bandwidth for all three designs should be the same
- Step load change referred to below is 0.1A to 5A to 0.1A
- Step input voltage change referred to below is 28V to 30V to 28V

### Design 0: Open loop converter

- a) Loop gain (compensator gain in unity)
- b) Open loop output impedance
- c) Open loop audio-susceptibility
- d) Pecs response to step load change
- e) Pecs response to step input voltage change

### Design 1: Passive Droop Control

- a) Pecs schematic
- b) Steps in obtaining your compensator design values
- c) Loop gain Bode plot
- d) Closed loop output impedance (together with open loop response on same plot)
- e) Closed loop audio-susceptibility (together with open loop response on same plot)
- f) Pecs response to step load change
- g) Pecs response to step input voltage change

### Design 2: Active Droop Control

- a) Pecs schematic
- b) Steps in obtaining your compensator design values
- c) Loop gain Bode plot. Show the three loop gains on the same figure
- d) Closed loop output impedance (together with open loop response on same plot)
- e) Closed loop audio-susceptibility (together with open loop response on same plot)
- f) Pecs response to step load change
- g) Pecs response to step input voltage change

### Design 3: Single Loop Control

- a) Pecs schematic
- b) Steps in obtaining your compensator design values
- c) Loop gain Bode plot.
- d) Closed loop output impedance (together with open loop response on same plot)
- e) Closed loop audio-susceptibility (together with open loop response on same plot)
- f) Pecs response to step load change
- g) Pecs response to step input voltage change