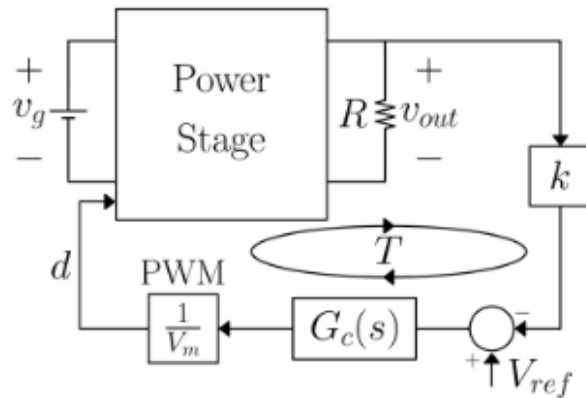


## D4 Regulator Classical Control Design

Regulator configuration:



Block diagram of the voltage regulator system with a feedback loop  $T(s)$  consisting of the D4 converter power stage characterized by its control to output transfer function  $G_{vd} = \hat{v}_{out} / \hat{d}$ , resistive divider gain  $k$ , compensator transfer function  $G_c(s)$ , and PWM gain  $F_M = 1/V_M$ .

Use the SSA (state space averaging) model to determine the control to output transfer function.

### State Space Averaging (SSA) Model:

The large signal model is given by:

$$\dot{x} = Ax + Bu$$

$$y = Cx + Eu$$

where

$$A = DA_1 + D'A_2$$

$$B = DB_1 + D'B_2$$

$$C = DC_1 + D'C_2$$

$$E = DE_1 + D'E_2$$

$$x = \begin{bmatrix} i_1 \\ i_2 \\ v_1 \\ v_2 \end{bmatrix}$$

$$u = v_g$$

$X$  is the steady state vector and  $U$  is  $V_g$ , the DC value of the input voltage.

$$X = -A^{-1}BU$$

For the transient simulations we will use the small-signal SSA model:

$$\dot{\hat{x}} = A\hat{x} + B\hat{u} + B_d\hat{d}$$

$$\hat{y} = C\hat{x} + E\hat{u} + E_d\hat{d}$$

where matrices A, B, C and E were previously defined and where

$$B_d = (A_1 - A_2)X + (B_1 - B_2)U$$

$$E_d = (C_1 - C_2)X + (E_1 - E_2)U$$

→

$$G_{vd}(s) = C(sI - A)^{-1}B_d + E_d$$

Using this model results in the small-signal control to output transfer function,  $G_{vd}(s)$

**Factoring the control to output transfer function:**

$$G(s) = \frac{\hat{v}_g}{\hat{d}}(s) = \frac{V_g \left[ L_1 C_1 s^2 + D(1-D) \frac{L_1}{R} s + 1 \right]}{C_1 C_2 L_1 L_2 s^4 + L_1 C_1 \frac{L_2}{R} s^3 + \left[ (1-D)^2 C_2 L_1 + L_2 C_2 + L_1 C_1 \right] s^2 + \left[ (1-D) \frac{L_1}{R} + \frac{L_2}{R} \right] s + 1}$$

GIVEN  $k \left( = \frac{1}{5} \right)$  ;  $\frac{1}{V_m} = \frac{1}{0.6} = F_m$

APPROXIMATE FACTORIZATION:

$$\begin{aligned} \text{DEN} &\approx \left( L_1 C_1 s^2 + \frac{(1-D)^2 L_1}{R} s + 1 \right) \left( L_2 C_2 s^2 + \frac{L_2}{R} s + 1 \right) \\ &= L_1 C_1 L_2 C_2 s^4 + \left[ \frac{L_1 C_1 L_2}{R} + \frac{L_2 C_2 (1-D)^2 L_1}{R} \right] s^3 + \left[ L_1 C_1 + L_2 C_2 + \frac{(1-D)^2 L_1 L_2}{R^2} \right] s^2 + \left[ \frac{(1-D)^2 L_1}{R} + \frac{L_2}{R} \right] s + 1 \end{aligned}$$

TO BE ACCURATE  
REQUIRE:

$$1) \quad \frac{L_2 C_2 (1-D)^2 L_1}{R} \ll \frac{L_1 C_1 L_2}{R} \Rightarrow (1-D)^2 C_2 \ll C_1$$

$$2) \quad \frac{(1-D)^2 L_1 L_2}{R^2} \ll L_1 C_1 + L_2 C_2 \Rightarrow \text{if } L_2 \gg L_1 \Rightarrow \frac{(1-D)^2 L_1 L_2}{R^2} \ll L_2 C_1 \Rightarrow \frac{(1-D)^2 L_1}{R^2} \ll C_1 \checkmark$$

$$3) \quad (1-D)^2 C_2 L_1 \ll L_2 C_2 + L_1 C_1 \Rightarrow \text{if } L_2 \gg L_1 \Rightarrow (1-D)^2 C_2 L_1 \ll L_2 C_2 \Rightarrow (1-D)^2 L_1 \ll L_2 \checkmark$$

Adding losses:

$$G_{AR}(s) = \frac{V_g \left( L_1 C_1 s^2 + D(1-D) \frac{L_1}{R} s + 1 \right)}{\left( L_1 C_1 s^2 + \frac{(1-D)^2 L_1}{R} s + 1 \right) \left( L_2 C_2 s^2 + \frac{L_2}{R} s + 1 \right)}$$

$$sL_1 \rightarrow sL_1 + r_1 \quad ; \quad sL_2 \rightarrow sL_2 + r_2$$

$$sC_1 \rightarrow \frac{sC_1}{1 + s r_{c1} C_1} \quad ; \quad sC_2 \rightarrow \frac{sC_2}{1 + s r_{c2} C_2}$$

$$\Rightarrow = V_g \left[ \left( sL_1 + r_1 \right) \left( \frac{sC_1}{1 + s r_{c1} C_1} \right) + D(1-D) \left( \frac{sL_1 + r_1}{R} \right) + 1 \right]$$

$$\left[ \left( sL_1 + r_1 \right) \left( \frac{sC_1}{1 + s r_{c1} C_1} \right) + \frac{(1-D)^2 (sL_1 + r_1)}{R} + 1 \right] \left[ \left( sL_2 + r_2 \right) \left( \frac{sC_2}{1 + s r_{c2} C_2} \right) + \frac{sL_2 + r_2}{R} + 1 \right]$$

$$= V_g \left[ \frac{s^2 L_1 C_1}{1 + s r_{c1} C_1} + \frac{s r_1 C_1}{1 + s r_{c1} C_1} + \frac{(1-D) L_1 s}{R} + \frac{(1-D) r_1}{R} + 1 \right]$$

$$\left[ \frac{s^2 L_1 C_1}{1 + s r_{c1} C_1} + \frac{s r_1 C_1}{1 + s r_{c1} C_1} + \frac{(1-D) L_1 s}{R} + \frac{(1-D) r_1}{R} + 1 \right] \left[ \frac{s^2 L_2 C_2}{1 + s r_{c2} C_2} + \frac{s r_2 C_2}{1 + s r_{c2} C_2} + \frac{sL_2}{R} + \frac{r_2}{R} + 1 \right]$$

x Top and Bottom BT  $(1 + s r_{c1} C_1) (1 + s r_{c2} C_2) \Rightarrow$   
 Also  $r_1 \ll R$   $r_2 \ll R$

$$= V_g \left[ s^2 L_1 C_1 + s r_1 C_1 + \left[ \frac{(1-D) L_1 s}{R} + 1 \right] (1 + s r_{c1} C_1) \right] (1 + s r_{c2} C_2)$$

$$\left[ s^2 L_1 C_1 + s r_1 C_1 + \left[ \frac{(1-D) L_1 s}{R} + 1 \right] (1 + s r_{c1} C_1) \right] \left[ s^2 L_2 C_2 + s r_2 C_2 + \left[ \frac{sL_2}{R} + 1 \right] (1 + s r_{c2} C_2) \right]$$

$$\begin{aligned}
&= V_g \left\{ s^2 \left[ L_1 C_1 + \frac{D(1-D) r_{C1} L_1 C_1}{R} \right] + s \left[ r_{L1} C_1 + r_{C1} C_1 + \frac{2(1-D) L_1}{R} \right] + 1 \right\} (1 + s r_{C2} C_2) \\
&\frac{\left( s^2 \left[ L_1 C_1 + \frac{(1-D)^2 r_{C1} L_1 C_1}{R} \right] + s \left[ r_{L1} C_1 + r_{C1} C_1 + \frac{(1-D)^2 L_1}{R} \right] + 1 \right) \left( s^2 \left[ L_2 C_2 + \frac{r_{C2} L_2 C_2}{R} \right] + s \left( r_{L2} C_2 + r_{C2} C_2 + \frac{L_2}{R} \right) + 1 \right)}{\left[ s^2 L_1 C_1 + s \left[ (r_{L1} + r_{C1}) C_1 + \frac{2(1-D) L_1}{R} \right] + 1 \right] \left[ 1 + s r_{C2} C_2 \right]} \\
&\approx \frac{\left[ s^2 L_1 C_1 + s \left[ (r_{L1} + r_{C1}) C_1 + \frac{(1-D)^2 L_1}{R} \right] + 1 \right] \left[ s^2 L_2 C_2 + s \left[ (r_{L2} + r_{C2}) C_2 + \frac{L_2}{R} \right] + 1 \right]}{\left[ s^2 L_1 C_1 + s \left[ (r_{L1} + r_{C1}) C_1 + \frac{(1-D)^2 L_1}{R} \right] + 1 \right] \left[ s^2 L_2 C_2 + s \left[ (r_{L2} + r_{C2}) C_2 + \frac{L_2}{R} \right] + 1 \right]}
\end{aligned}$$

**Main result:** adds a zero to the transfer function due to the ESR of C2.


**Resonant frequencies are unchanged but the Q factors do change, as there is greater damping in the circuit.**

The output capacitor used: 47 micro Farad with 40 mOhm ESR :




Image shown is a representation only. Exact specifications should be obtained from the product data sheet.


## A750EK476M1EAAE040

Digi-Key Part Number	399-13665-ND
Manufacturer	<a href="#">KEMET</a>
Manufacturer Product Number	A750EK476M1EAAE040
Description	CAP ALUM POLY 47UF 20% 25V T/H
Manufacturer Standard Lead Time	20 Weeks
Detailed Description	47 $\mu$ F 25 V Aluminum - Polymer Capacitors Radial, Can 40mOhm 2000 Hrs @ 105°C
Customer Reference	<input type="text" value="Customer Reference"/>
Datasheet	 <a href="#">Datasheet</a>

## Product Attributes

TYPE	DESCRIPTION	SELECT
Category	<a href="#">Capacitors</a> <a href="#">Aluminum - Polymer Capacitors</a>	<input type="radio"/>
Mfr	KEMET	<input type="checkbox"/>
Series	<a href="#">A750</a>	<input type="checkbox"/>
Package	Bulk 	<input type="checkbox"/>
Product Status	Active	<input type="checkbox"/>
Type	Polymer	<input type="checkbox"/>
Capacitance	47 $\mu$ F	<input type="checkbox"/>
Tolerance	$\pm$ 20%	<input type="checkbox"/>
Voltage - Rated	25 V	<input type="checkbox"/>
ESR (Equivalent Series Resistance)	40mOhm	<input type="checkbox"/>

Compensator design:

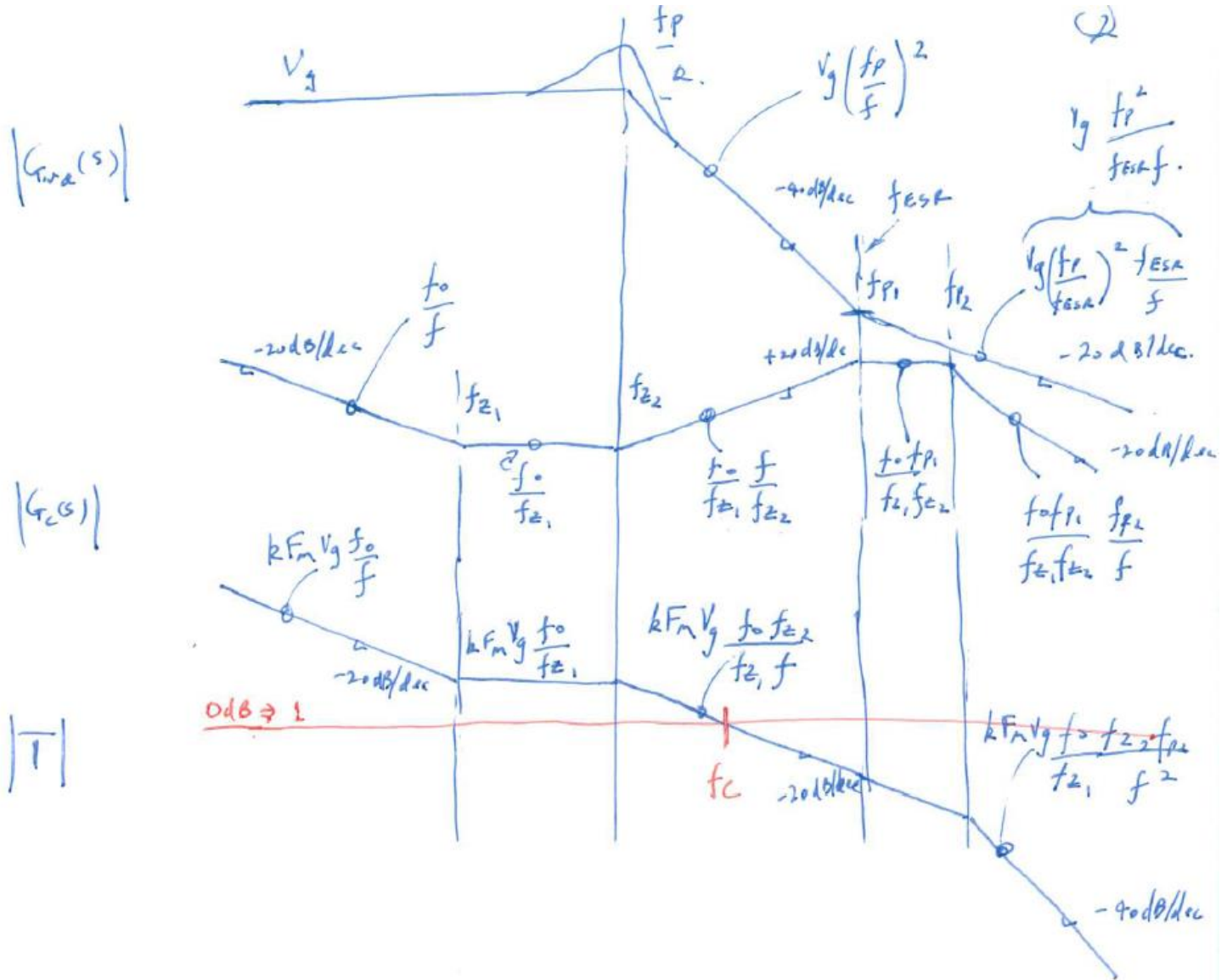

Compensator transfer function,  $G_c(s)$ , and resulting loop gain,  $T$ :


$$G_c(s) = \frac{\omega_0}{s} \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$T = k F_m G_c(s) G_{ud}(s)$$

$$\textcircled{a} \quad f = f_c \quad \Rightarrow \quad \frac{kF_m V_g f_0 t_{z2}}{t_{z1} f_c} = 1$$

$$\Rightarrow \quad f_0 = \frac{t_{z1} f_c}{kF_m V_g t_{z2}}$$

Compensator:

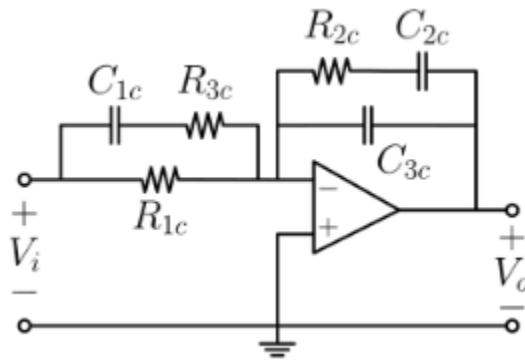

The transfer function  $G_c(s)$  of this compensator is given by:

$$G_c(s) = -\frac{\omega_0 \left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right)}{s \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

where

$$\omega_0 = \frac{1}{R_{1c} (C_{2c} + C_{3c})}$$

$$\omega_{z1} = \frac{1}{R_{2c} C_{2c}}$$

$$\omega_{z2} = \frac{1}{C_{1c} (R_{1c} + R_{3c})}$$

$$\omega_{p1} = \frac{1}{R_{3c} C_{1c}}$$

$$\omega_{p2} = \frac{1}{R_{2c} \frac{C_{2c} C_{3c}}{C_{2c} + C_{3c}}}$$



## Matlab code:

```
% D4_RPT_class.m
% undertakes the D4 regulator design using a classical control approach

clear
close all
format short e

L1=33e-6          % D4 converter component values
L2=180e-6
C1=100e-6
C2=47e-6

Vg=10            % The parameters for converter
Vo=5
D=0.5  % = Vo/Vg
R=5              % nominal load resistance

k=1/5            % voltage divider gain
Vm=0.6           % pk-to-pk amplitude of triangular waveform in TL5001 IC
Fm=1/Vm         % modulator gain

esr=40e-3        % output capacitor ESR (equivalent series resistance)
fx=12.5e3        % desired crossover frequency 12,500 Hz

fesr=1/(2*pi*esr*C2)
Wesr=2*pi*fesr
Wn=1/sqrt(L2*C2) % (dominant) corner frequency
fp=Wn/(2*pi)
fz2=fp
alpha=1          % alpha is between 0.3-1, choose alpha=1
fz1=alpha*fp
fp1=fesr
fp2=90e3        % Choose the fp2 at 90KHz
f0=(fz1*fx)/(k*Fm*Vg*fz2)

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

W0=2*pi*f0      % the parameters for the compensator
Wz1=2*pi*fz1
Wz2=2*pi*fz2
Wp1=2*pi*fp1
Wp2=2*pi*fp2

%Plot the phase margin and crossover frequency
s=tf('s');
% compensator TF
Gc=(W0/s)*((1+s/Wz1)*(1+s/Wz2))/((1+s/Wp1)*(1+s/Wp2))

% control to output TF of converter
Gvd_num = Vg*(C1*L1*s^2 + D*(1-D)*L1/R*s + 1);
Gvd_den = C1*C2*L1*L2*s^4 + C1*L1*L2/R*s^3 + ...
          ((1-D)^2*C2*L1+C2*L2+C1*L1)*s^2 + ((1-D)^2*L1+L2)/R*s + 1;
Gvd = Gvd_num/Gvd_den;

figure(1)
Gvd_zpk = zpk(Gvd)
Gvd_zpk_minreal = minreal(Gvd_zpk, 0.06) % cancellation
```

```

bode(Gvd,Gvd_zpk_minreal)
h = gcr; % Displayed the crossover frequency in Hz
h.AxesGrid.Xunits = 'Hz';

figure(2)
Loopgain=k*Gc*Fm*Gvd
margin(Loopgain)
h = gcr; % Displayed the crossover frequency in Hz
h.AxesGrid.Xunits = 'Hz';

Gc_zpk = zpk(Gc) % compensator TF

Gvd_den_approx = (L1*C1*s^2+(1-D)^2*L1/R*s+1) * (L2*C2*s^2+L2/R*s+1);
Gvd_approx = Gvd_num/Gvd_den_approx;
figure(3)
bode(Gvd,Gvd_approx)
h = gcr; % Displayed the crossover frequency in Hz
h.AxesGrid.Xunits = 'Hz';

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

% % with added damping (i.e. r and C3) to L1, C1
%
% C1=10e-6
% L1=33e-6
% C2=10e-6
% L2=180e-6
% r = 0.5
% C3 = 22e-6
%
% A1 = [0 0 1/L1 0 0
% 0 0 0 -1/L2 0
% -1/C1 0 -1/(r*C1) 0 1/(r*C1)
% 0 1/C2 0 -1/(R*C2) 0
% 0 0 1/(r*C3) 0 -1/(r*C3)];
%
% B1 = [-1/L1; 1/L2; 0; 0; 0];
%
% A2 = [0 0 1/L1 0 0
% 0 0 -1/L2 -1/L2 0
% -1/C1 1/C1 -1/(r*C1) 0 1/(r*C1)
% 0 1/C2 0 -1/(R*C2) 0
% 0 0 1/(r*C3) 0 -1/(r*C3)];
%
% B2 = [-1/L1; 1/L2; 0; 0; 0];
%
%
% A = D*A1+(1-D)*A2;
% B = D*B1+(1-D)*B2;
% C = [0, 0, 0, 1, 0];
%
% X = -A\B*Vg;
% Bd = (A1-A2)*X+(B1-B2)*Vg;
%
% sys_bd = ss(A,Bd,C,0);
% figure(4)
% bode(sys_bd, Gvd, {2*pi*100, 2*pi*1e5})
% h = gcr;

```

```

% h.AxesGrid.Xunits = 'Hz';
%
% sys_zpk = zpk(sys_bd)
% sys_zpk = minreal(zpk(sys_bd), 0.02)
% sys_zpk = minreal(zpk(sys_bd), 0.05)
%
% figure(5)
% margin(k*Gc*Fm*sys_bd)
% h = gcr;
% h.AxesGrid.Xunits = 'Hz';

% % sys_bd_zpk = zpk(sys_bd)
% % sys_bd_zpk_minreal = minreal(sys_bd_zpk, 0.05)
% % figure(4)
% % bode(sys_bd_zpk_minreal)
% % h = gcr;
% % h.AxesGrid.Xunits = 'Hz';

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

% calculate the compensator component values
% Gc=(W0/s)*(((1+s/Wz1)*(1+s/Wz2))/((1+s/Wp1)*(1+s/Wp2)))

C3 = 10e-12
R2 = 1/(Wp2*C3)
C2 = 1/(Wz1*R2)
R1 = 1/(W0*(C2+C3))
C1 = 1/R1 * (1/Wz2 - 1/Wp1)
R3 = 1/(Wp1*C1)
disp('*****')


% % results:
% C3 = 1.0000e-11    % 10 pF
% R2 = 1.7684e+05    % 180 kOhm
% C2 = 5.2012e-10    % 560 pF
% R1 = 8.0059e+04    % 82 kOhm
% C1 = 1.1254e-09    % 1.2 nF
% R3 = 1.6705e+03    % 1.8 kOhm

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%


% Or, swapping Wz1 and Wz2 (if they are different, depends on alpha above)
% C3a = 10e-12
% R2a = 1/(Wp2*C3a)
% C2a = 1/(Wz2*R2a)
% R1a = 1/(W0*(C2a+C3a))
% C1a = 1/R1a * (1/Wz1 - 1/Wp1)
% R3a = 1/(Wp1*C1a)

```


**Loop gain Bode plot:**

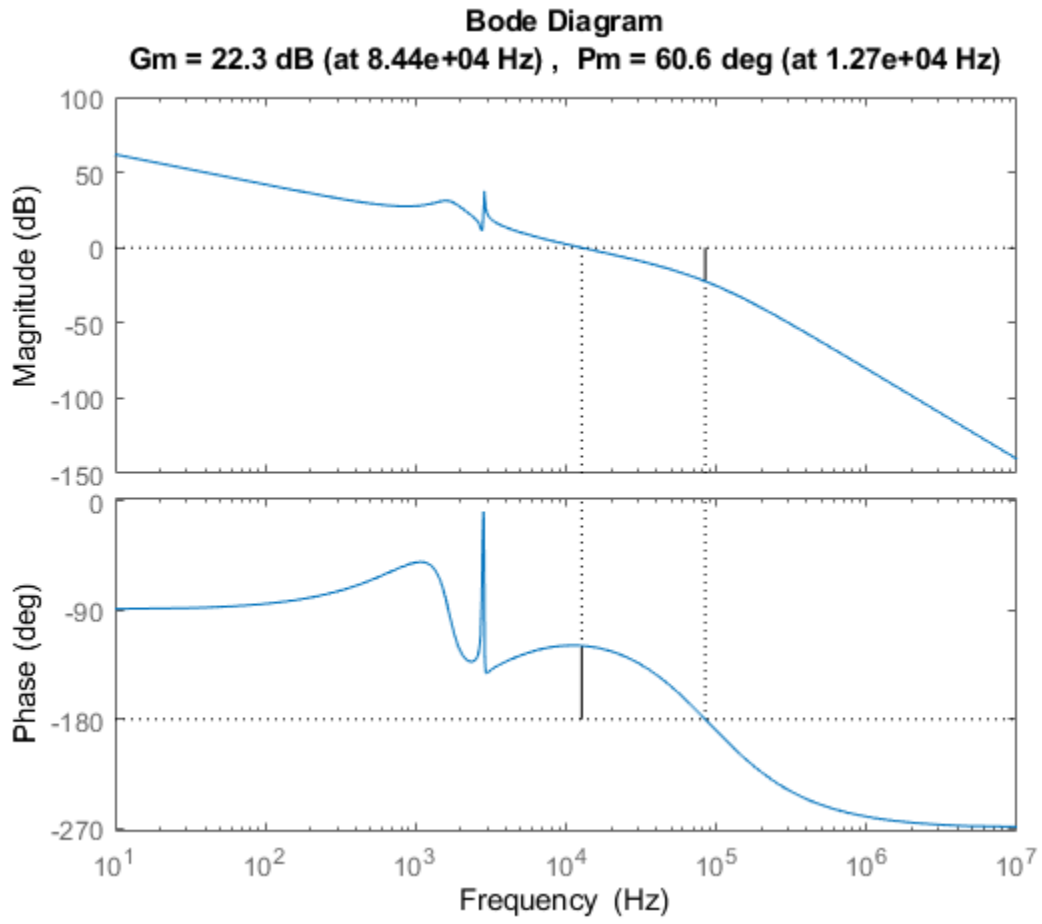

## PECS implementation:

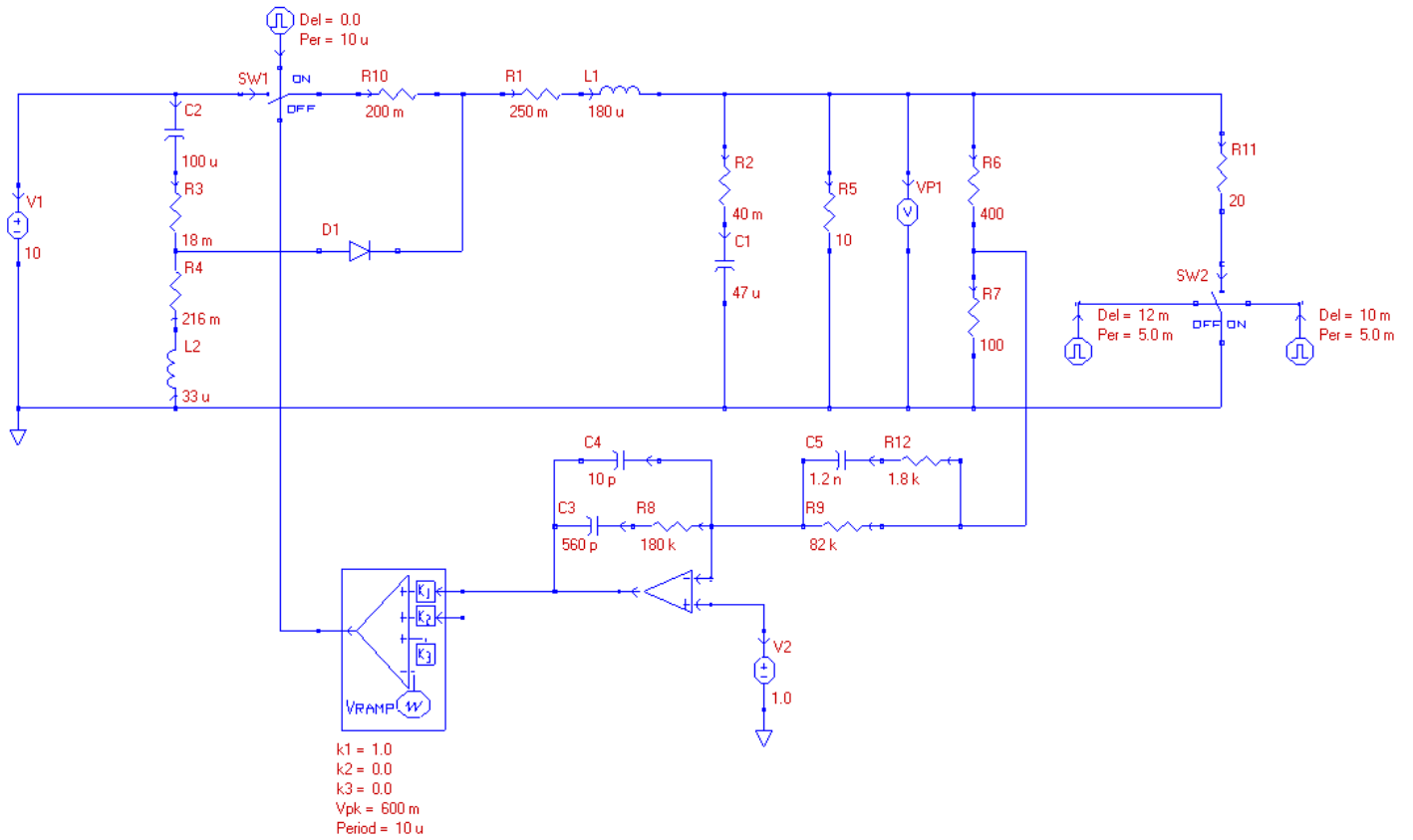

## Step load response:

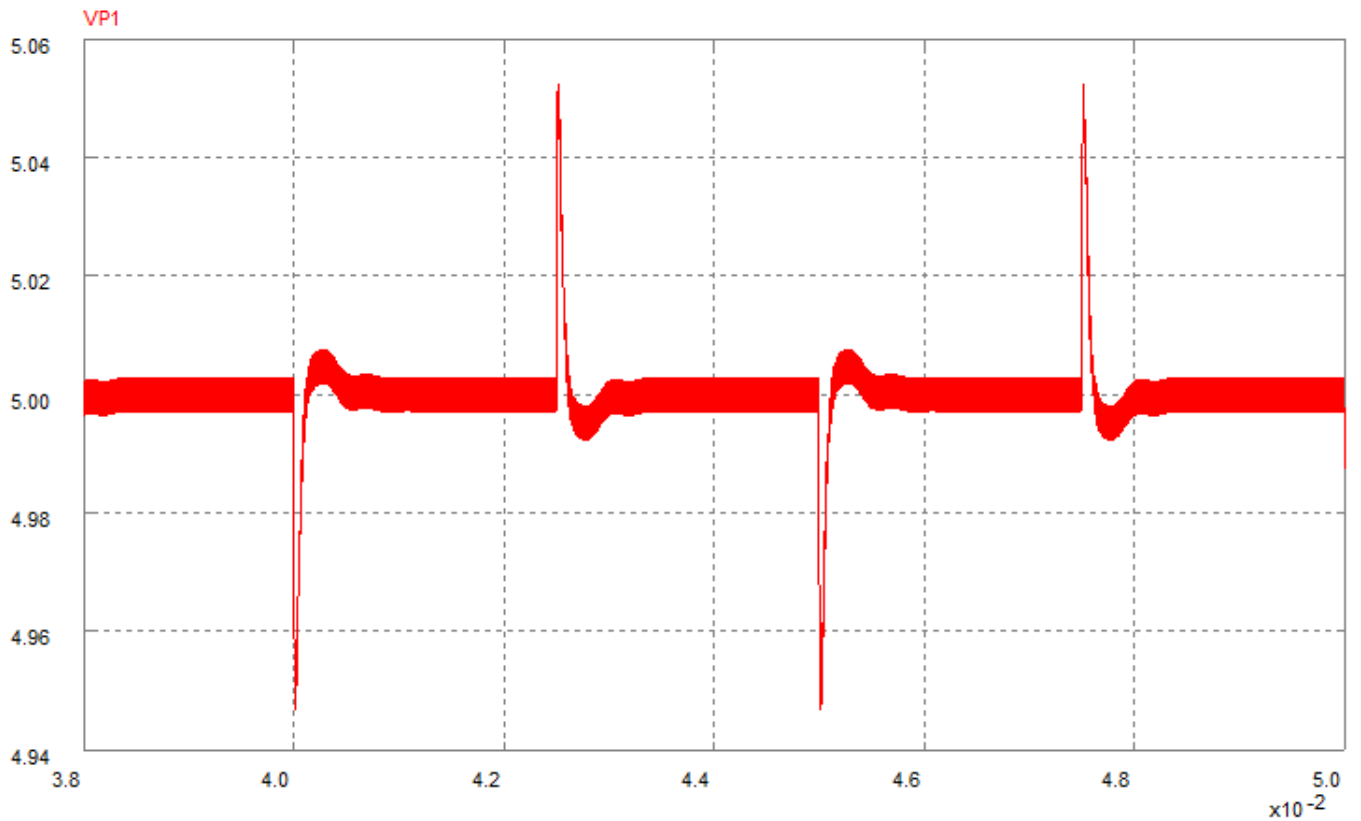

**Step input voltage response: 10 V -> 11 V -> 10 V**

